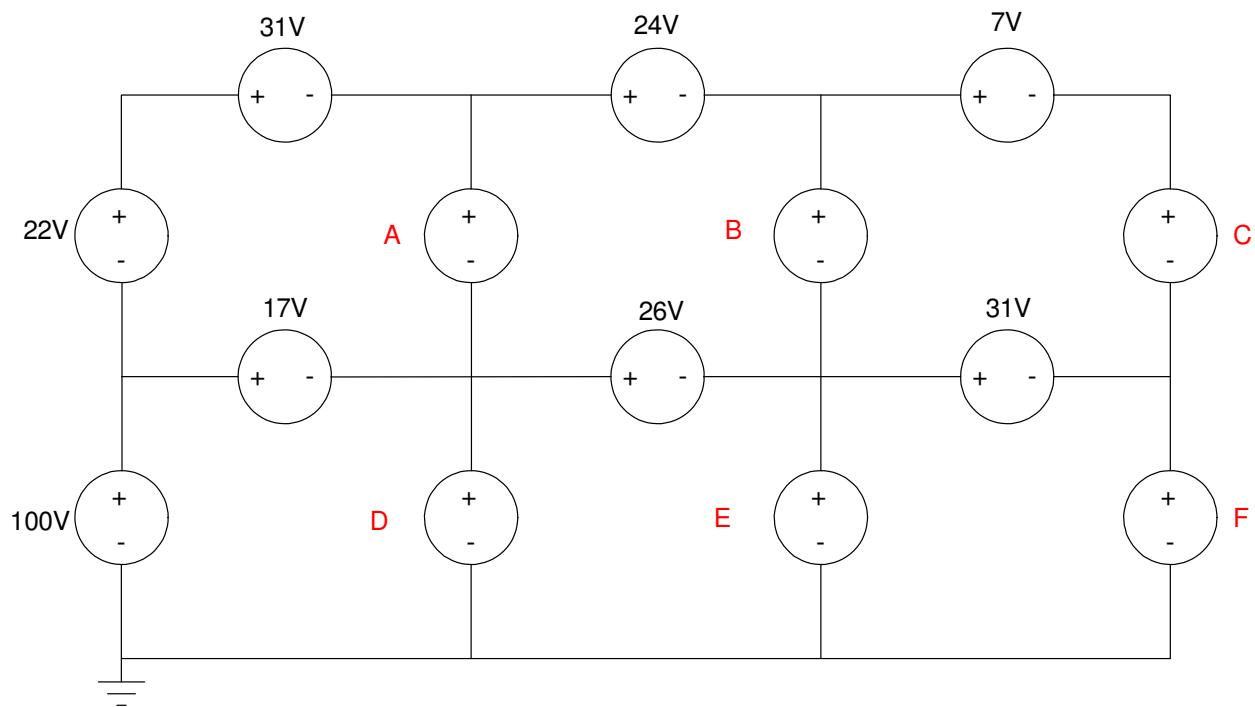



# ECE 111: Handout #8

Week #8: EE 206 Circuits I


- 1) Find the unknown voltages using conservation of voltage



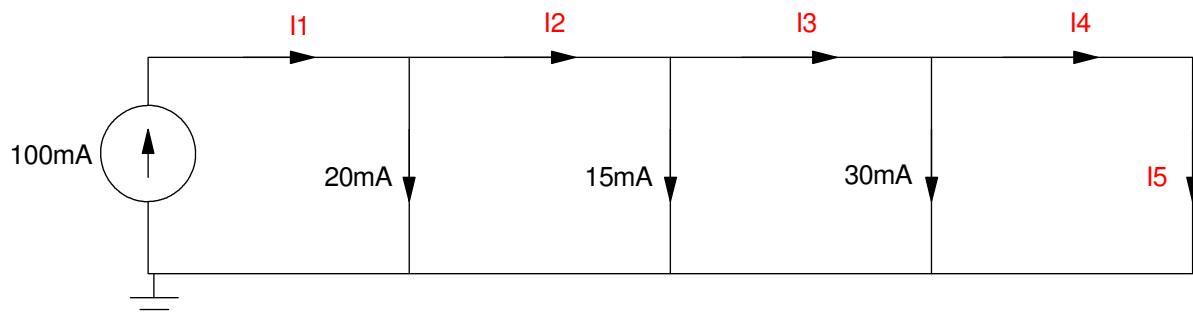
- 2) Find  $I_1..I_6$  using conservation of current



3) Determine the resistance  $R_{ab}$

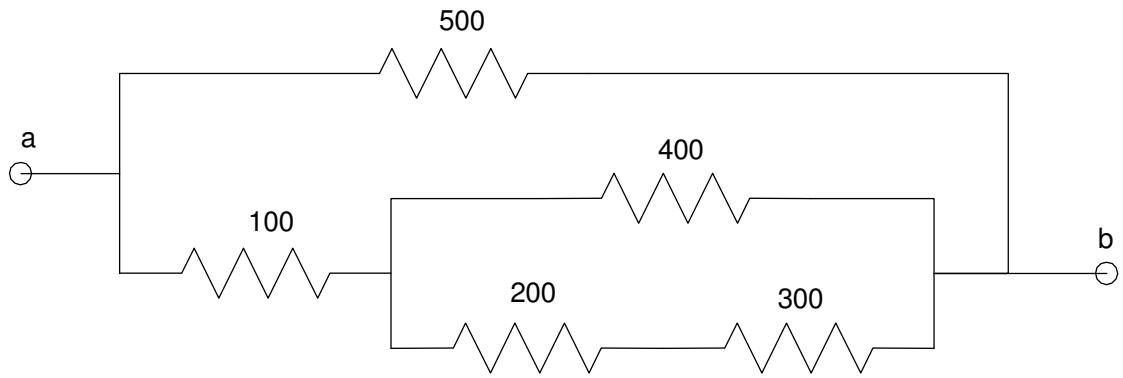

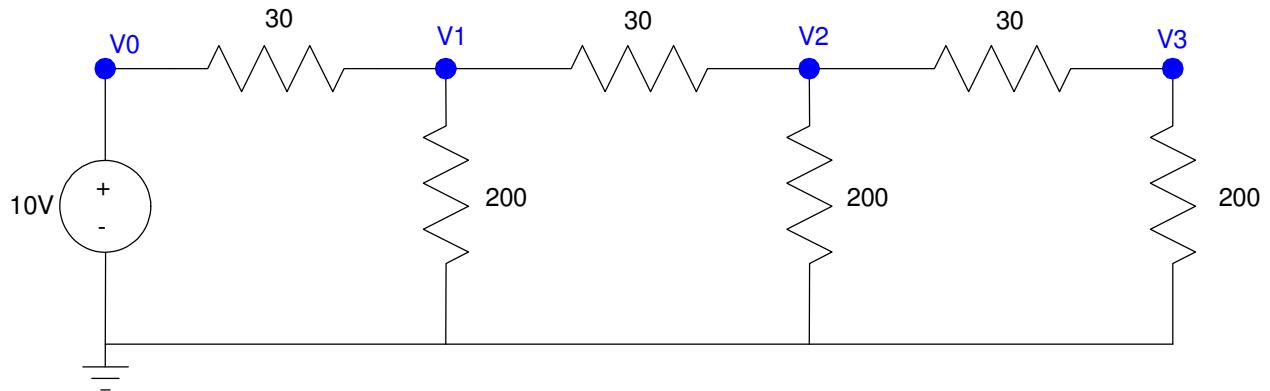
4) Use voltage division to determine  $V_1$ ,  $V_2$ , and  $V_3$




# Solutions

Week #5 Handouts for EE 206 Circuits I

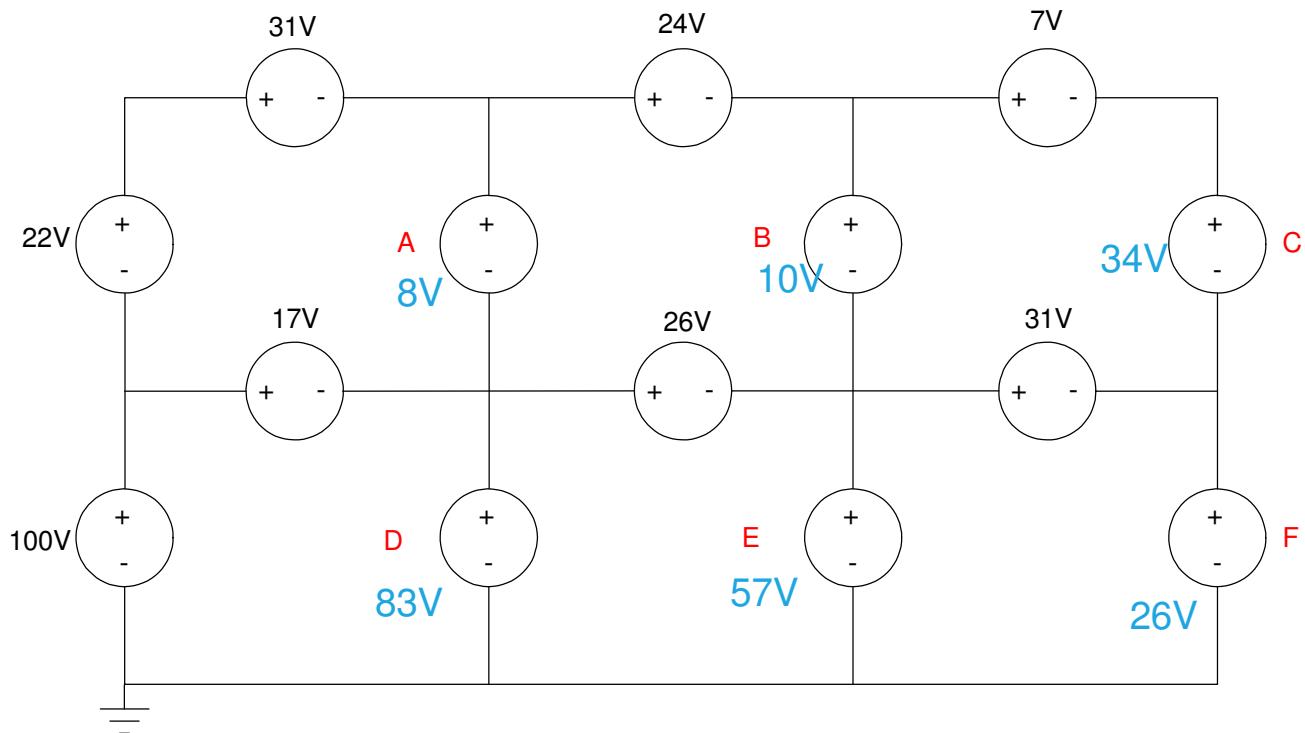
- 1) Find the unknown voltages using conservation of voltage



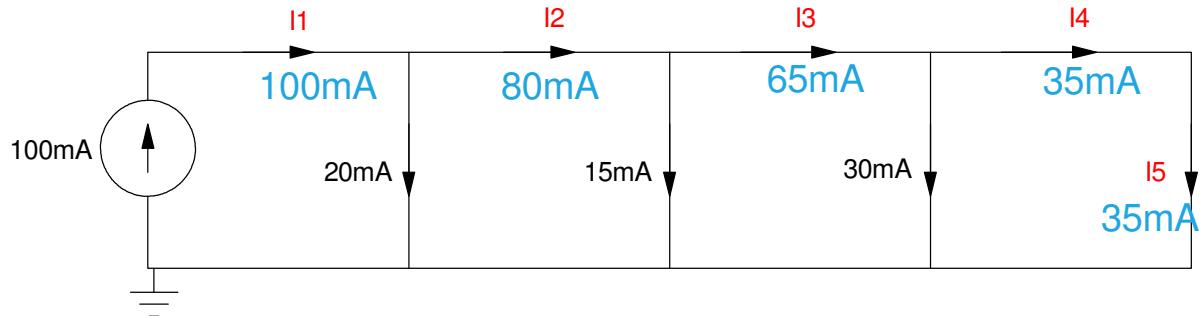- 2) Find  $I_1..I_6$  using conservation of current



3) Determine the resistance  $R_{ab}$

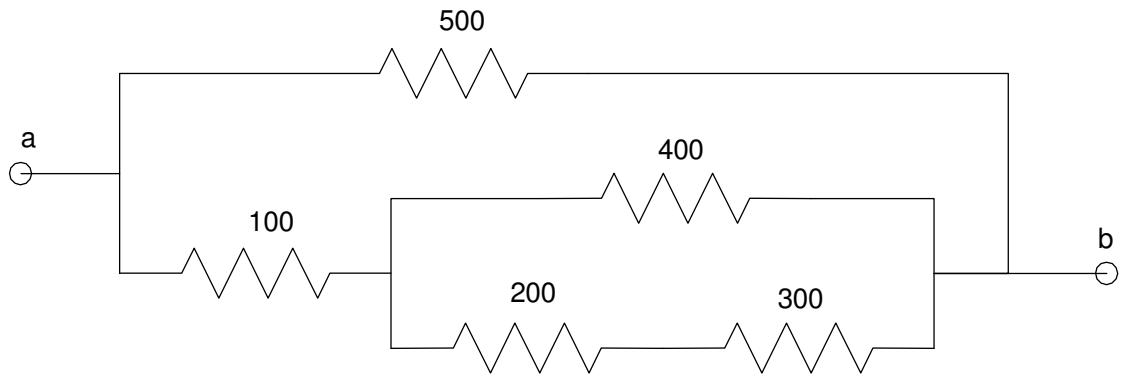

$$300 + 200 = 500$$


$$500 \parallel 400 = 222.222$$

$$222.222 + 100 = 322.222$$

$$322.222 \parallel 500 = 195.946$$

**ans:  $R_{ab} = 195.946$  Ohms**

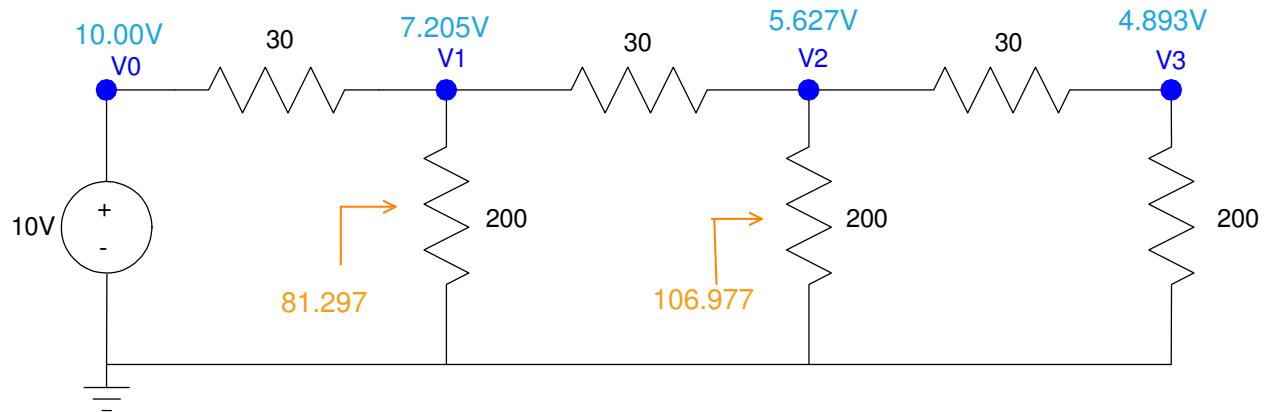4) Use voltage division to determine V1, V2, and V3



$$230 \parallel 200 = 106.977$$

$$106.977 + 30 = 136.977$$

$$136.977 \parallel 200 = 81.297$$

Now apply voltage division

$$V_1 = \left( \frac{81.297}{81.297+30} \right) 10V$$

$$V_1 = 7.205V$$

$$V_2 = \left( \frac{106.977}{106.977+30} \right) 7.205V$$

$$V_2 = 5.627V$$

$$V_3 = \left( \frac{200}{200+30} \right) 5.627V$$

$$V_3 = 4.893V$$