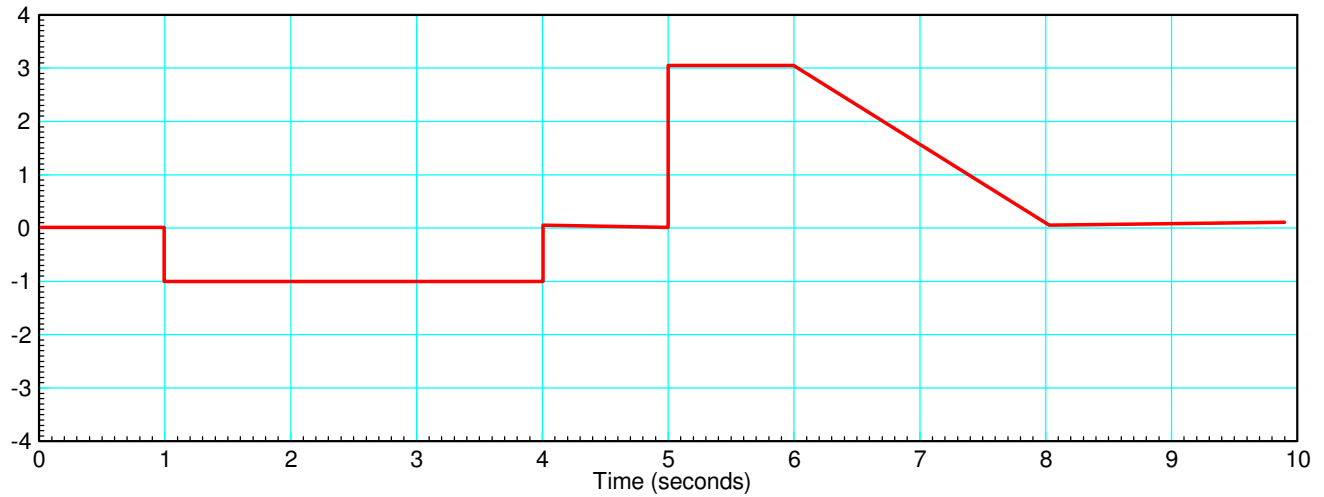


# ECE 111: Handout #10


Week #10: ECE 311 Circuits II

1) Assume the current flowing into a 1F capacitor is as shown below. Sketch the voltage.

- Assume  $V_c(0) = 0V$
- $V = \frac{1}{C} \int I(t) dt$



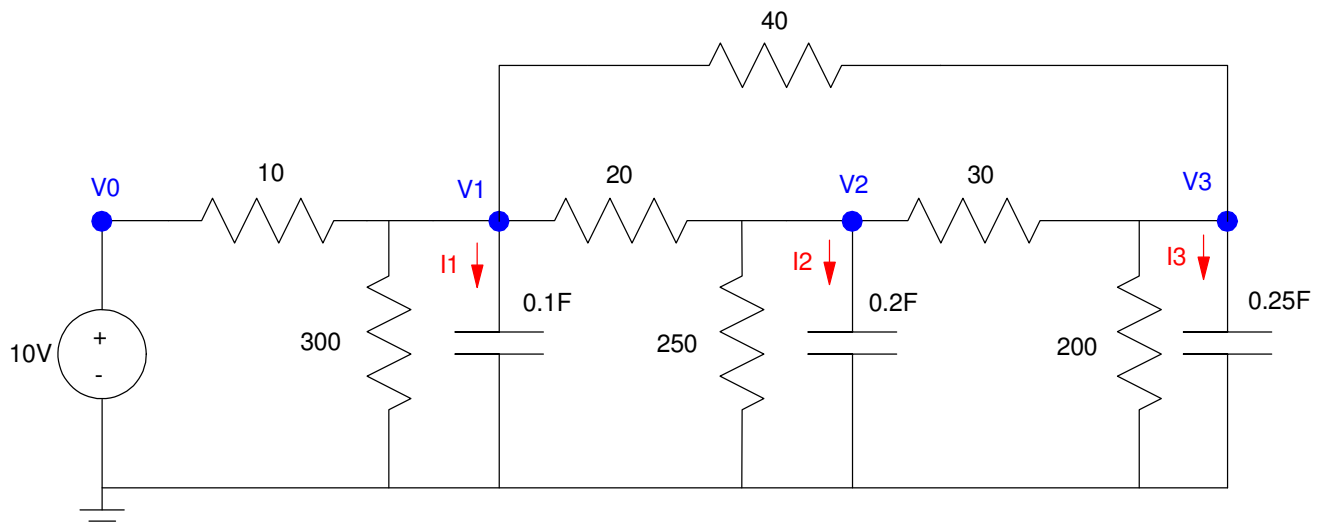
2) Write the differential equations which describe the following circuit


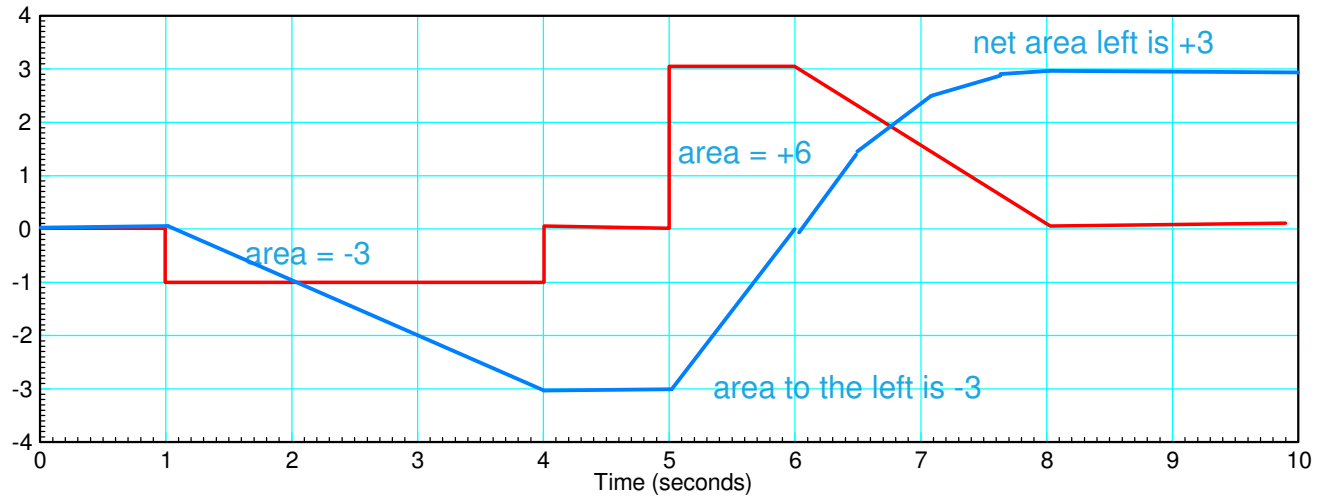
## Problem #1

Capacitors integrate. The voltage will be the integral of the current (shown in blue)

- note: integral is the area under the curve
- 



## Problem #2

The basic equations are

$$I = C \frac{dV}{dt} = C \dot{V}$$

$$I_1 = 0.1 \dot{V}_1 = \left( \frac{10 - V_1}{10} \right) + \left( \frac{V_2 - V_1}{20} \right) + \left( \frac{V_3 - V_1}{40} \right) - \left( \frac{V_1}{300} \right)$$

$$I_2 = 0.2 \dot{V}_2 = \left( \frac{V_1 - V_2}{20} \right) + \left( \frac{V_3 - V_2}{30} \right) - \left( \frac{V_2}{250} \right)$$

$$I_3 = 0.25 \dot{V}_3 = \left( \frac{V_1 - V_3}{40} \right) + \left( \frac{V_2 - V_3}{30} \right) - \left( \frac{V_3}{200} \right)$$

