

# ECE 111 - Homework #9

Week #9: ECE 311 Circuits II - Due 11am, Tuesday, October 25th

1) Solve for Y

$$Y = \left( \frac{(5+j2)(7-j3)}{(2-j6)} \right)$$

```
>> Y = (5 + j*2)*(7 - j*3) / (2 - j*6)
```


**Y = 2.2000 + 6.1000i**

$$Y = \left( \left( \frac{5+j2}{2-j6} \right) + \left( \frac{7-j3}{2+j5} \right) \right) \left( \frac{8+j3}{7+j9} \right)$$

```
>> A = (5 + j*2) / (2 - j*6);  
>> B = (7 - j*3) / (2 + j*5);  
>> C = (8 + j*3) / (7 + j*9);  
>> Y = (A + B) * C
```

**Y = -0.2751 - 0.3268i**

2) Determine the impedance Zab

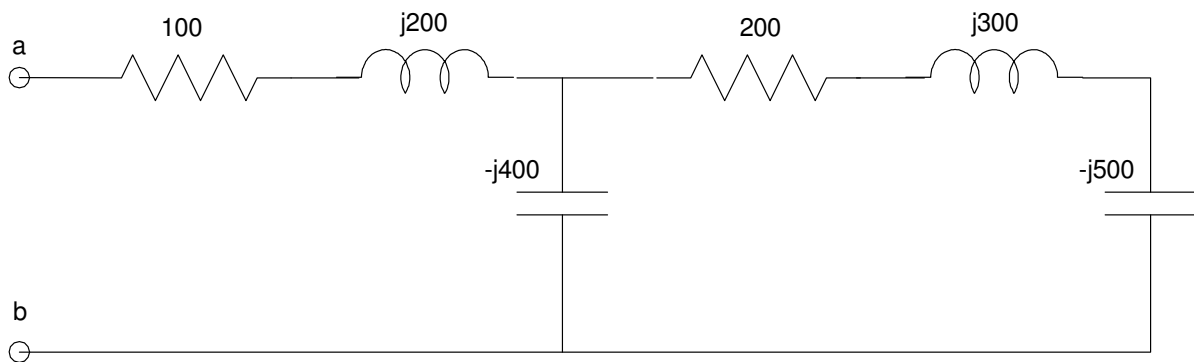

```
>> R1 = 200 + j*300 - j*500
```

R1 = 200.00 -200.00i

```
>> R2 = -j*400;
```


```
>> R3 = 1 / (1/R1 + 1/R2)
```

R3 = 80.000 -160.00i

```
>> Rab = R3 + 100 + j*200
```

**Rab = 180.00 + 40.000i**

3) Determine the impedance  $Z_{ab}$

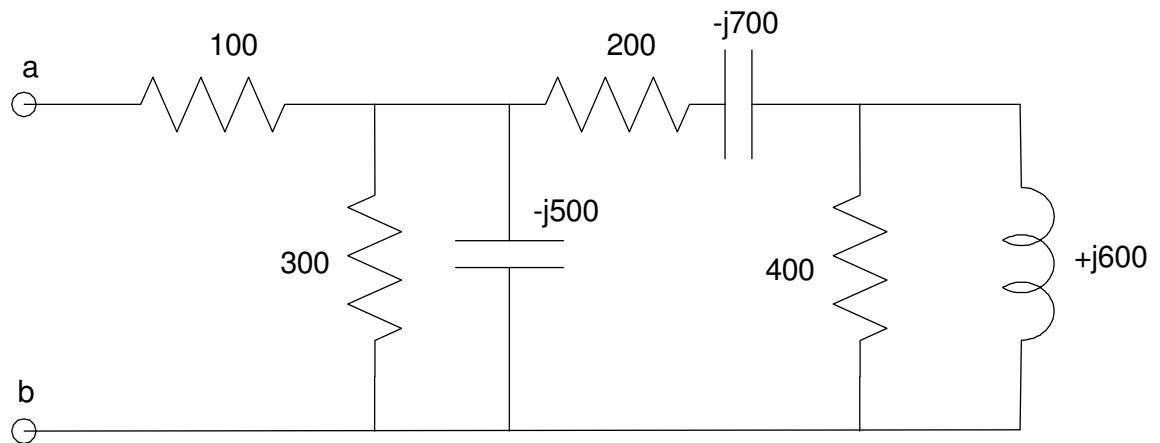

```
>> R1 = 400;
>> R2 = j*600;
>> R3 = 1/( 1/R1 + 1/R2 )

R3 = 276.92 + 184.62i

>> R4 = R3 + (200 - j*700)

R4 = 476.92 - 515.38i

>> R5 = 300;
>> R6 = -j*500;
>> R7 = 1/ (1/R4 + 1/R5 + 1/R6)


R7 = 154.87 - 109.67i

>> Rab = R7 + 100

Rab = 254.87 - 109.67i

>>
```

4) Assume  $V_0 = 10$

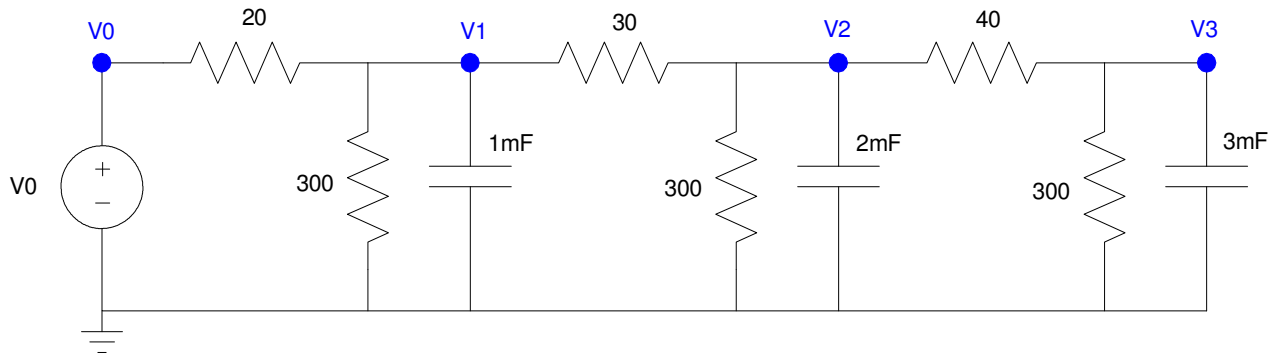

a) Determine the impedances of each element at 0 rad/sec

$$R \rightarrow R$$

$$C \rightarrow \frac{1}{j\omega C} = \infty$$

b) Write the voltage node equations

*The current is zero for the capacitors - meaning you could ignore them if you want*

$$V_0 = 10$$

$$\left( \frac{V_1 - V_0}{20} \right) + \left( \frac{V_1}{300} \right) + 0 + \left( \frac{V_1 - V_2}{30} \right) = 0$$

$$\left( \frac{V_2 - V_1}{30} \right) + \left( \frac{V_2}{300} \right) + 0 + \left( \frac{V_2 - V_3}{40} \right) = 0$$

$$\left( \frac{V_3 - V_2}{40} \right) + \left( \frac{V_3}{300} \right) + 0 = 0$$

c) Solve for  $V_1$ ,  $V_2$ , and  $V_3$ .

*Group terms*

$$V_0 = 10$$

$$-\left(\frac{1}{20}\right)V_0 + \left(\frac{1}{20} + \frac{1}{300} + \frac{1}{30}\right)V_1 - \left(\frac{1}{30}\right)V_2 = 0$$

$$-\left(\frac{1}{30}\right)V_1 + \left(\frac{1}{30} + \frac{1}{300} + \frac{1}{40}\right)V_2 - \left(\frac{1}{40}\right)V_3 = 0$$

$$-\left(\frac{1}{40}\right)V_2 + \left(\frac{1}{40} + \frac{1}{300}\right)V_3 = 0$$

*Place in matrix form*

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{300} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) & 0 \\ 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{300} + \frac{1}{40}\right) & \left(\frac{-1}{40}\right) \\ 0 & 0 & \left(\frac{-1}{40}\right) & \left(\frac{1}{40} + \frac{1}{300}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

*solve using matlab.*

```
a1 = [1,0,0,0];
a2 = [-1/20,1/20+1/300+1/30,-1/30,0];
a3 = [0,-1/30,1/30+1/300+1/40,-1/40];
a4 = [0,0,-1/40,1/40+1/300];
A = [a1;a2;a3;a4]
```

```
1.0000      0      0      0
-0.0500    0.0867   -0.0333      0
      0   -0.0333    0.0617   -0.0250
      0      0   -0.0250    0.0283
```

```
B = [10;0;0;0];
V = inv(A)*B
```



```
v0    10.0000
v1     8.5304
v2     7.1791
v3     6.3345
```

```
>>
```

5) Check your results in CircuitLab

The voltages match


▼ DC

V(V0)	10.00 V		
V(V1)	8.530 V		
V(V2)	7.179 V		
V(V3)	6.334 V		

[+ Add Expression](#)

 Export Results...

[Run DC Solver](#)

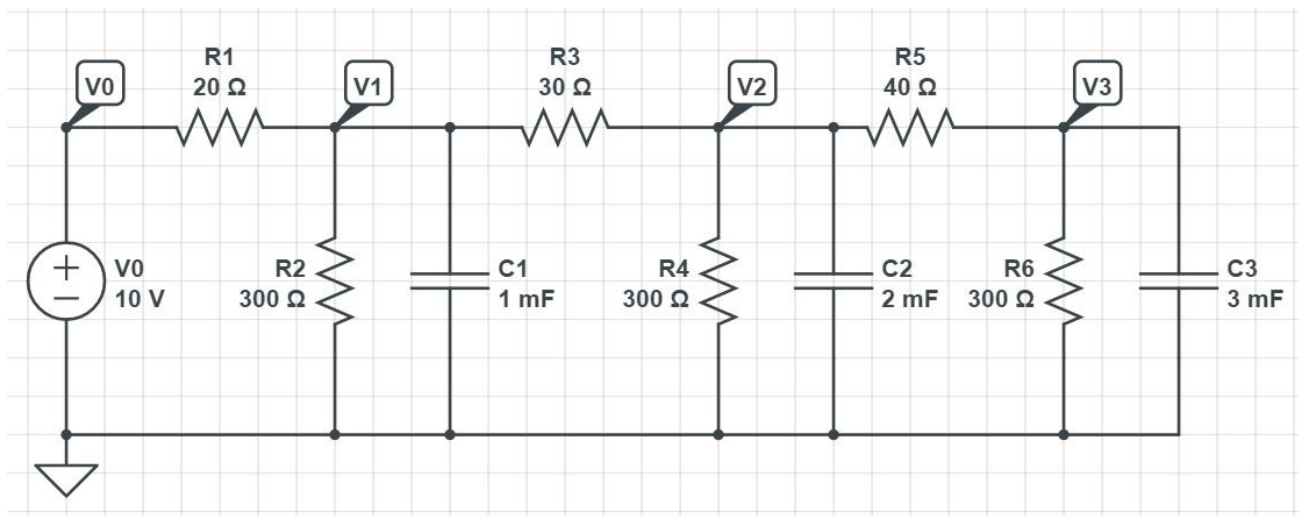

6) Assume  $V_0$  is a 10V, 5 rad/sec ( 0.796Hz )

$$V_0 = 10 \sin(5t)$$


a) Determine the impedances of each element at 5 rad/sec

$$\omega = 5$$

$$V_0 \rightarrow 0 - j10$$

$$R \rightarrow R$$

$$C \rightarrow \frac{1}{j\omega C}$$

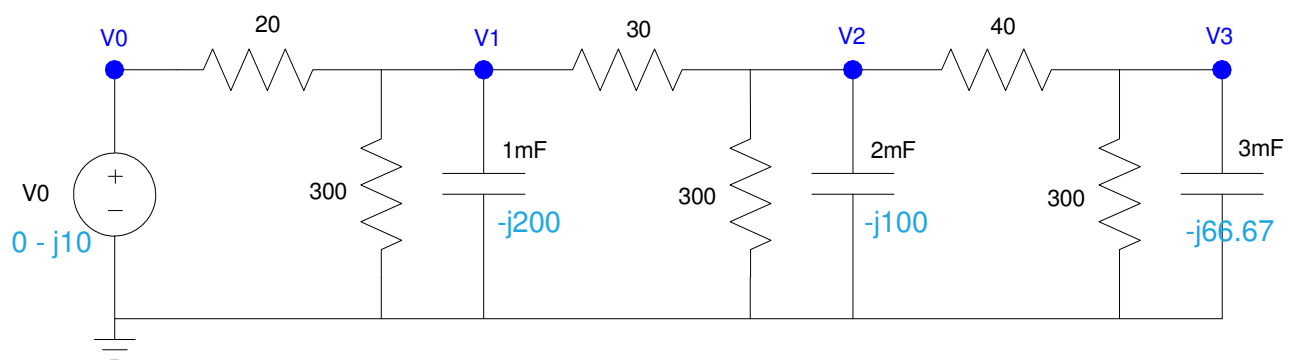

b) Write the voltage node equations

$$V_0 = -j10$$

$$\left( \frac{V_1 - V_0}{20} \right) + \left( \frac{V_1}{300} \right) + \left( \frac{V_1}{-j200} \right) + \left( \frac{V_1 - V_2}{30} \right) = 0$$

$$\left( \frac{V_2 - V_1}{30} \right) + \left( \frac{V_2}{300} \right) + \left( \frac{V_2}{-j100} \right) + \left( \frac{V_2 - V_3}{40} \right) = 0$$

$$\left( \frac{V_3 - V_2}{40} \right) + \left( \frac{V_3}{300} \right) + \left( \frac{V_3}{-j66.67} \right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

This will be the same as before but with one more term (the complex term from the capacitors)

Group terms

$$V_0 = -j10$$

$$-\left(\frac{1}{20}\right)V_0 + \left(\frac{1}{20} + \frac{1}{300} + \frac{1}{-j200} + \frac{1}{30}\right)V_1 - \left(\frac{1}{30}\right)V_2 = 0$$

$$-\left(\frac{1}{30}\right)V_1 + \left(\frac{1}{30} + \frac{1}{300} + \frac{1}{-j100} + \frac{1}{40}\right)V_2 - \left(\frac{1}{40}\right)V_3 = 0$$

$$-\left(\frac{1}{40}\right)V_2 + \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{-j66.67}\right)V_3 = 0$$

place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{20}\right) & \left(\frac{1}{20} + \frac{1}{300} + \frac{1}{-j200} + \frac{1}{30}\right) & \left(\frac{-1}{30}\right) & 0 \\ 0 & \left(\frac{-1}{30}\right) & \left(\frac{1}{30} + \frac{1}{300} + \frac{1}{-j200} + \frac{1}{40}\right) & \left(\frac{-1}{40}\right) \\ 0 & 0 & \left(\frac{-1}{40}\right) & \left(\frac{1}{40} + \frac{1}{300} + \frac{1}{-j66.67}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -j10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
a1 = [1,0,0,0];
a2 = [-1/20,1/20+1/300+1/30+1/(-j*200),-1/30,0];
a3 = [0,-1/30,1/30+1/300+1/40+1/(-j*100),-1/40];
a4 = [0,0,-1/40,1/40+1/300+1/(-j*66.67)];
A = [a1;a2;a3;a4]
B = [-j*10;0;0;0];
V = inv(A)*B
```

```
V0      0 -10.0000i
V1  -1.5652 - 7.2895i
V2  -2.9760 - 4.1875i
V3  -3.5789 - 1.8002i
```

d) Express V1, V2, and V3 in terms of sine and cosine function:

- hint:  $V_1 = a + jb$  (phasor representation) means  $V_1(t) = a \cos(5t) - b \sin(5t)$

```
V0 = 10 * sin(5t)
V1 = -1.5652 cos(5t) + 7.2895 sin(5t)
V2 = -2.9760 cos(5t) + 4.1875 sin(5t)
V3 = -3.5898 cos(5t) + 1.8002 sin(5t)
```

7) Check your results in CircuitLab using a transient simulation for 6 seconds

Note: polar form is easier to see in lab (or with CircuitLab)

```
>> abs(V)           CircuitLab
10.0000             10.000V
 7.4557             7.442V
 5.1373             5.113V
 4.0062             3.962V
```

```
>> angle(V)*180/pi
-90.0000           this is the delay to the peak in degrees
-102.1182
-125.4008
-153.2969
```

