


# ECE 111 - Homework #13

Week #13 - ECE 320 Electronics I. Due 11am, Tuesday November 22nd

Assume the VI characteristics for 1N4004 diodes are:

$$V_d = 0.038 \cdot \ln\left(\frac{I_d}{7.7 \cdot 10^{-11}} + 1\right) \quad I_d = 7.7 \cdot 10^{-11} \left(\exp\left(\frac{V_d}{0.038}\right) - 1\right)$$

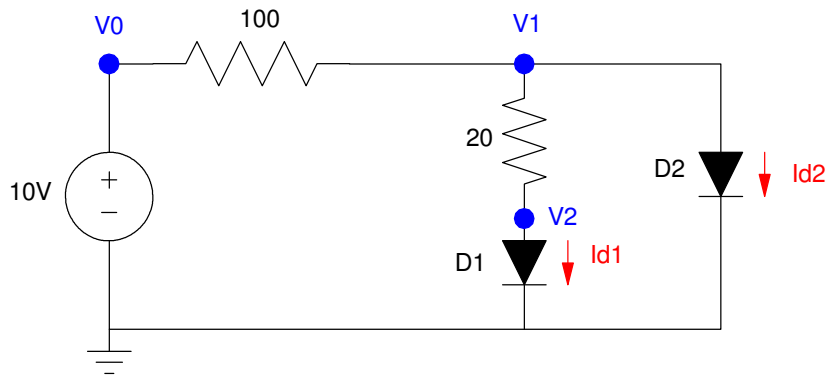1) Write the voltage node equations for the following circuit.



Start with the diode equations

$$I_{d1} = 7.7 \cdot 10^{-11} \left(\exp\left(\frac{V_2}{0.038}\right) - 1\right)$$

$$I_{d2} = 7.7 \cdot 10^{-11} \left(\exp\left(\frac{V_1}{0.038}\right) - 1\right)$$

Add in the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{100}\right) + \left(\frac{V_1 - V_2}{20}\right) + I_{d2} = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + I_{d1} = 0$$

## 2) Solve using fminsearch and MATLAB

First, write a Matlab function:

```
function [ J ] = diode2( X )

    V0 = 10;
    V1 = X(1);
    V2 = X(2);

    Id1 = 7.7e-11 * ( exp( V2 / 0.038 ) - 1 );
    Id2 = 7.7e-11 * ( exp( V1 / 0.038 ) - 1 );

    E1 = (V1 - V0)/100 + (V1 - V2)/20 + Id2;
    E2 = (V2 - V1)/20 + Id1;

    J = E1^2 + E2^2;

end
```

## Solve using fminsearch()


```
>> [V,e] = fminsearch('diode2',[1,2])

V =      V1      V2
    0.7920  0.6859


e = 1.6417e-011
```
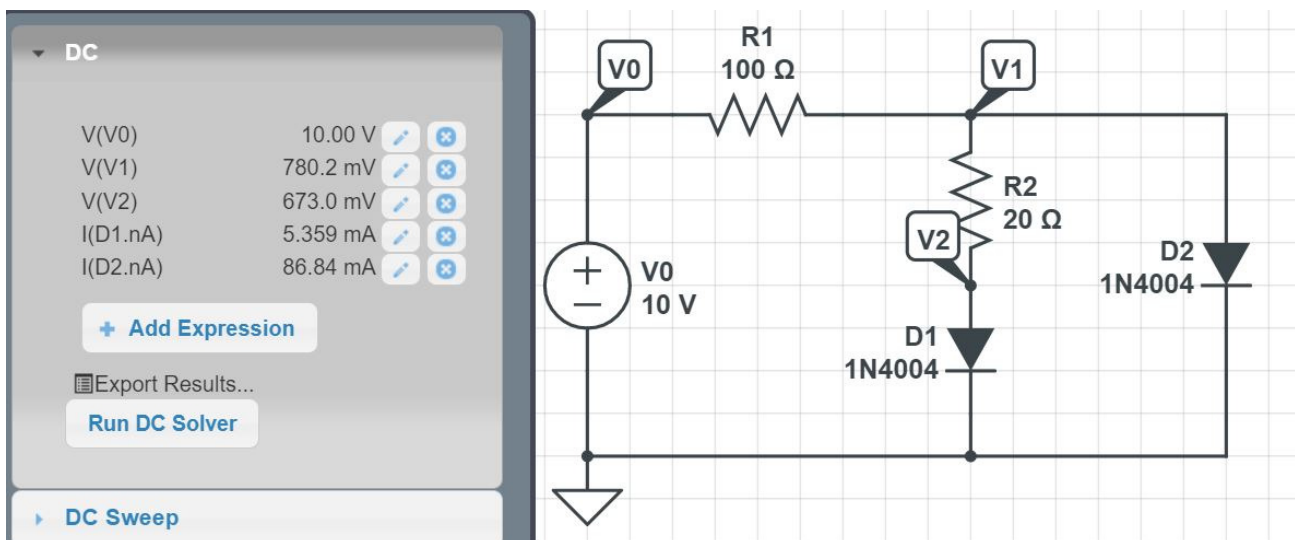
## 3) Check your results using CircuitLab and 1N4004 diodes

- The results are almost the same
- Diodes in parallel don't share: one takes the brunt of the current



4) Write the voltage node equations for the following circuit.

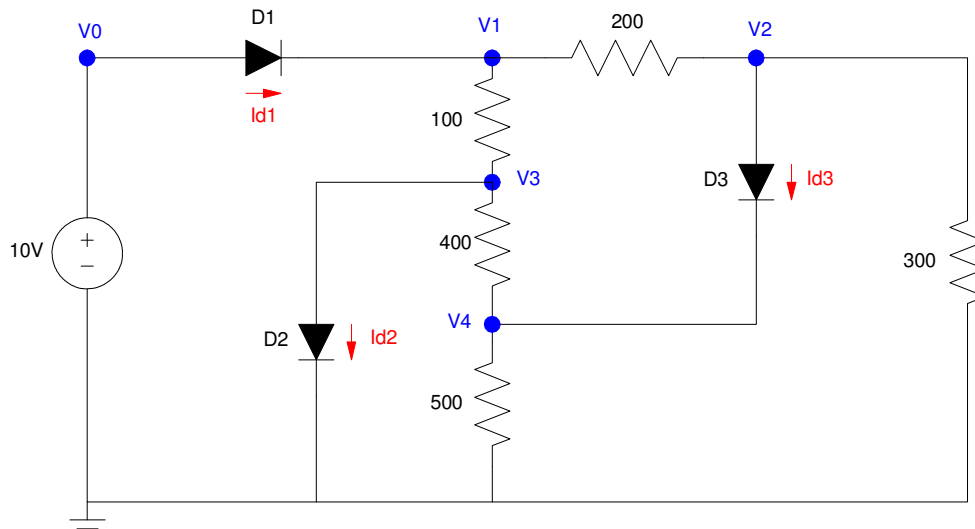

Problem 4-6

Start with the diode equations

$$I_{d1} = 7.7 \cdot 10^{-11} \left( \exp \left( \frac{V_0 - V_1}{0.038} \right) - 1 \right)$$

$$I_{d2} = 7.7 \cdot 10^{-11} \left( \exp \left( \frac{V_3 - 0}{0.038} \right) - 1 \right)$$

$$I_{d3} = 7.7 \cdot 10^{-11} \left( \exp \left( \frac{V_2 - V_4}{0.038} \right) - 1 \right)$$

Now write the voltage node equations

$$V_0 = 10$$

$$-I_{d1} + \left( \frac{V_1 - V_3}{100} \right) + \left( \frac{V_1 - V_2}{200} \right) = 0$$

$$\left( \frac{V_2 - V_1}{200} \right) + I_{d3} + \left( \frac{V_2}{300} \right) = 0$$

$$\left( \frac{V_3 - V_1}{100} \right) + I_{d2} + \left( \frac{V_3 - V_4}{400} \right) = 0$$

$$\left( \frac{V_4 - V_3}{400} \right) + \left( \frac{V_4}{500} \right) - I_{d3} = 0$$

## 5) Solve using fminsearch and MATLAB

Write a Matlab function

```
function [ J ] = diode3( X )

    V0 = 10;
    V1 = X(1);
    V2 = X(2);
    V3 = X(3);
    V4 = X(4);

    Id1 = 7.7e-11 * ( exp( (V0-V1) / 0.038 ) - 1 );
    Id2 = 7.7e-11 * ( exp( (V3-0) / 0.038 ) - 1 );
    Id3 = 7.7e-11 * ( exp( (V2-V4) / 0.038 ) - 1 );

    E1 = -Id1 + (V1 - V3)/100 + (V1 - V2)/200;
    E2 = (V2 - V1)/200 + Id3 + (V2/300);
    E3 = (V3-V1)/100 + Id2 + (V3-V4)/400;
    E4 = (V4-V3)/400 + (V4/500) - Id3;

    J = E1^2 + E2^2 + E3^2 + E4^2;

end
```

Solve using fminsearch...

It helps if you have a decent initial guess. A bad guess can wind up in la-la land

```
>> [V,e] = fminsearch('diode3',[1,2,3,4])
V =    9.1752  -15.0127    0.7654  -15.7831
e =    0.0297
```

(negative voltages are not possible with this circuit)

Try some better guesses

```
>> diode3([1,2,3,4])
ans =  3.1004e+185
>> diode3([9,8,7,6])
ans =  5.9733e+139
>> diode3([9,8,0.7,0.6])
ans =  1.6607e+149
>> diode3([9,0.8,0.7,0.6])
ans =  422.0521
```

Better, start from here

```
>> [V,e] = fminsearch('diode3',[9,0.8,0.7,0.6])
```

```
V = 9.1936 0.6789 0.7905 0.6243
```

```
e = 0.0016
```

e is still fairly large, so keep iterating

```
>> [V,e] = fminsearch('diode3',V)
```

```
V = V1 V2 V3 V4
     9.1989 3.9907 0.7935 3.2716
```

```
e = 4.8881e-013
```

Pretty close to zero. This is a valid answer

6) Check your results using CircuitLab and 1N4004 diodes

- The results are almost the same

