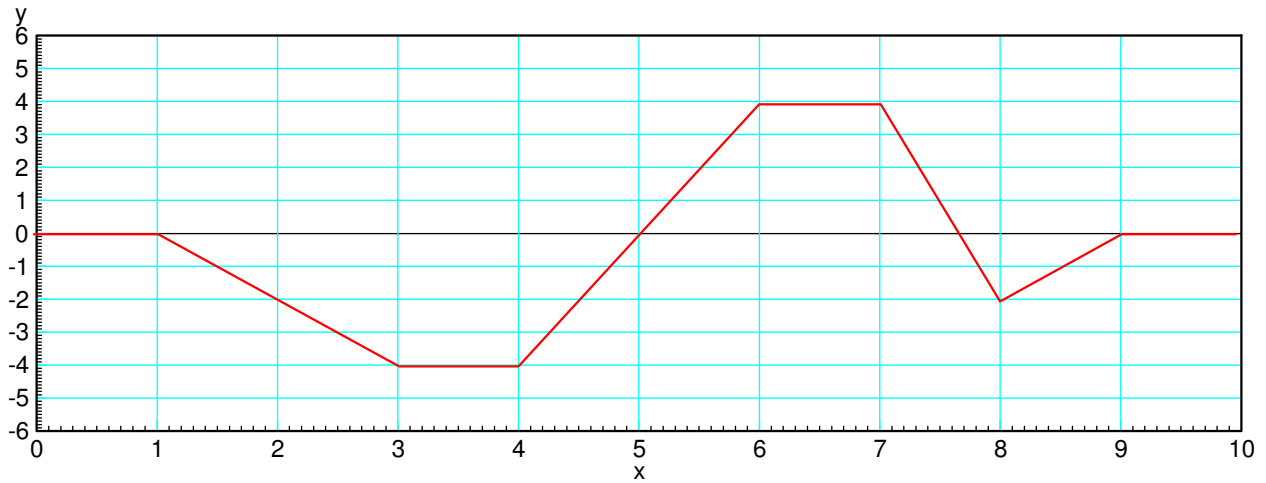


ECE 111 - Homework #11


ECE 351 Electromagnetics - Wave Equation
Due Tuesday, November 7th
Please submit BlackBoard

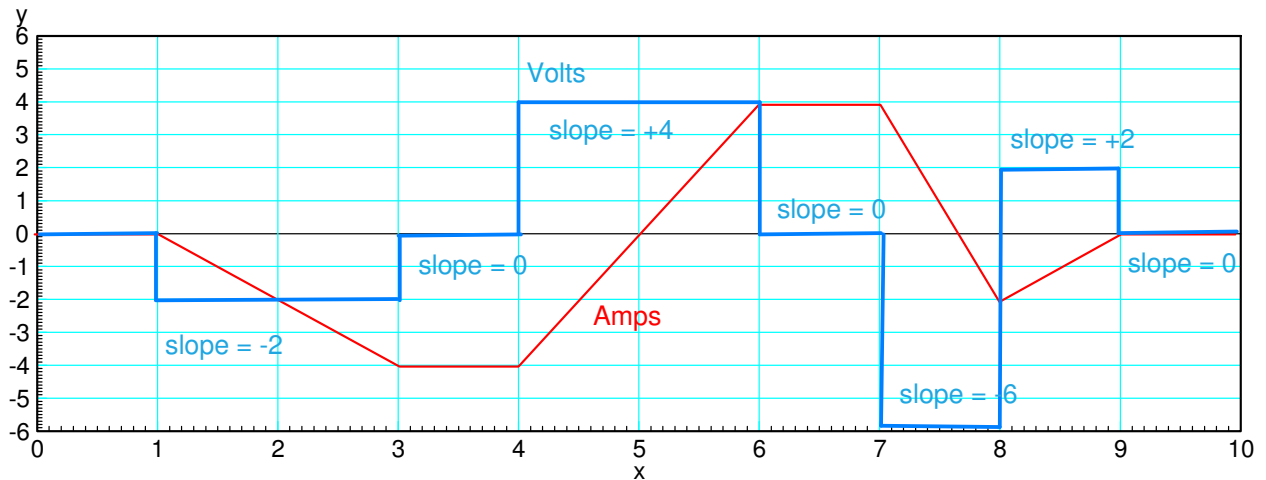1) Assume the current flowing through a one Henry inductor is shown below. Sketch the voltage.


$$V = L \frac{dI}{dt}$$



With $L = 1$, the voltage is the derivative of the current (the slope)



4-Node RLC Circuit

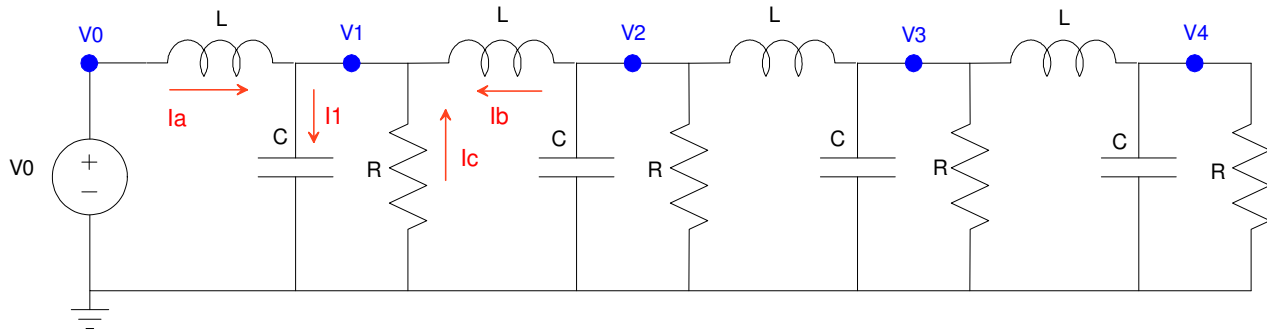

$R = 300\Omega$, $C = 0.2F$, $L = 0.2H$. Repeat for 30 nodes for problems 4-6

2) Write the dynamic equations for the following 4-stage RLC circuit. (i.e. write the node equations)

From before, the current to a capacitor is $C * dV/dt$

$$I_1 = CV'_1 = I_a + I_b + I_c$$

Take the derivative

$$CV''_1 = I'_a + I'_b + I'_c$$

For inductors, $V = L dI/dt$

$$V_0 - V_1 = LI'_a$$

$$V_2 - V_1 = LI'_b$$

Substitute

$$CV''_1 = \left(\frac{V_0 - V_1}{L}\right) + \left(\frac{V_2 - V_1}{L}\right) + \left(\frac{0 - V_1}{R}\right)'$$

Group terms and divide by C

$$V''_1 = \left(\frac{1}{LC}\right)V_0 - \left(\frac{2}{LC}\right)V_1 + \left(\frac{1}{LC}\right)V_2 - \left(\frac{1}{RC}\right)V'_1$$

Plug in numbers and you get the dynamics for nodes 1..3

$$V''_1 = 25V_0 - 50V_1 + 25V_2 - 0.0167V'_1$$

$$V''_2 = 25V_1 - 50V_2 + 25V_3 - 0.0167V'_2$$

$$V''_3 = 25V_2 - 50V_3 + 25V_4 - 0.0167V'_3$$

Node #4 is a little different since only inductor is connected

$$V''_4 = 25V_3 - 25V_4 - 0.0167V'_4$$

3) Assume $V_{in} = 10V$ and the initial conditions are zero ($V_1 = V_2 = V_3 = V_4 = 0$). Solve for the voltages at $t = 3$ seconds. *Hint: Solve numerically using Matlab*

Code:

- Compute the second derivative of each voltage
- Integrate once to get V'
- Integrate again to get V

```
V0 = 100;
V1 = 0;
V2 = 0;
V3 = 0;
V4 = 0;

dV1 = 0;
dV2 = 0;
dV3 = 0;
dV4 = 0;

V = [];

t = 0;
dt = 0.02;

while(t < 10)

    ddV1 = 25*V0 - 50*V1 + 25*V2 - 0.0167*dV1;
    ddV2 = 25*V1 - 50*V2 + 25*V3 - 0.0167*dV2;
    ddV3 = 25*V2 - 50*V3 + 25*V4 - 0.0167*dV3;
    ddV4 = 25*V3 - 25*V4 - 0.0167*dV4;

    dV1 = dV1 + ddV1*dt;
    dV2 = dV2 + ddV2*dt;
    dV3 = dV3 + ddV3*dt;
    dV4 = dV4 + ddV4*dt;

    V1 = V1 + dV1*dt;
    V2 = V2 + dV2*dt;
    V3 = V3 + dV3*dt;
    V4 = V4 + dV4*dt;

    t = t + dt;

    plot([0,1,2,3,4],[V0,V1,V2,V3,V4],'.-');
    ylim([-300,300]);
    clc
    disp(t)
    pause(0.01);


    V = [V; V1, V2, V3, V4];

end

t = [1:length(V)]' * dt;
plot(t,V);
```

Result:

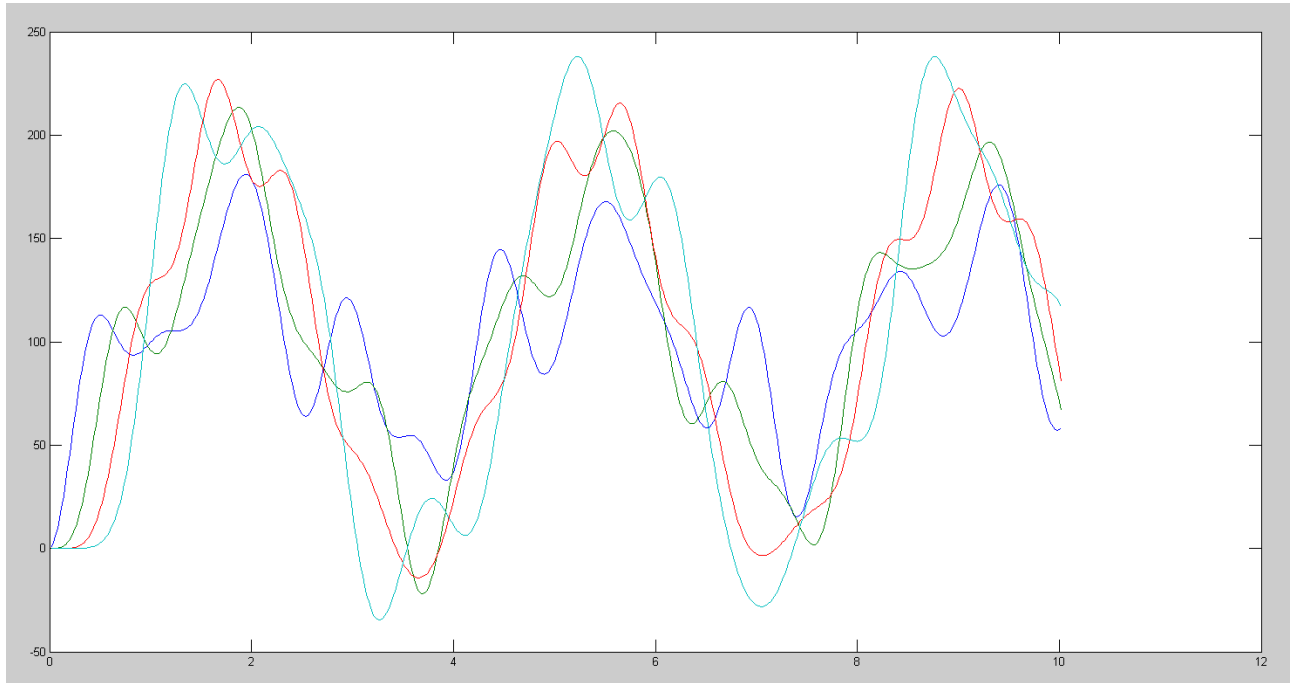- Note: The wave equation behaves very differently than the heat equation



30-Node RLC Circuit (hint: modify the program Wave.m)

4) Expand the RLC circuit from problem #2 to 30 nodes. Plot the voltage at $t = 12$ seconds (just after the reflection) for $1 / R_{30}C = 0.01$

Option 1: Make 30 copies of each section of code

Option 2: Use for-loops

Code:

```
N = 30;    % number of nodes

V = zeros(N,1);
dV = zeros(N,1);

t = 0;
dt = 0.02;

while(t < 8)

    if (t < 2) V0 = 100 * ( ( sin(0.5*pi*t) )^2 );
        else V0 = 0;
        end

    ddV(1) = 25*V0 - 50*V(1) + 25*V(2) - 0.0167*dV(1);


    for i=2:N-1
        ddV(i) = 25*V(i-1) - 50*V(i) + 25*V(i+1) - 0.0167*dV(i);
    end

    ddV(N) = 25*V(N-1) - 25*V(N) - 0.0167*dV(N);
    %
    %             ^^^
    %             change this term

    for i=1:N
        dV(i) = dV(i) + ddV(i)*dt;
        V(i) = V(i) + dV(i)*dt;
    end
    t = t + dt;


    plot([0:N],[V0;V],'.-');
    ylim([-150,250]);
    clc
    disp(t)
    pause(0.01);

end
```

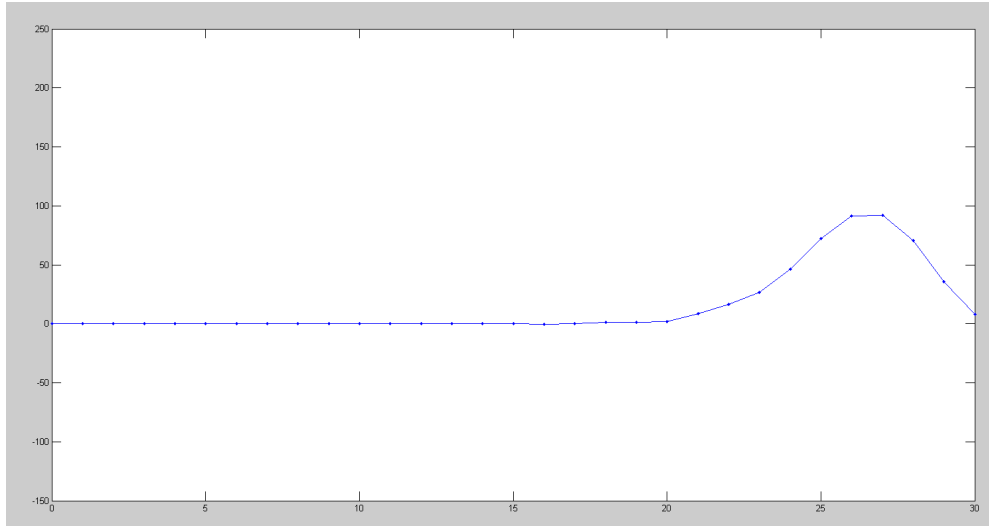


Result with $1/R_30C = 0.01$

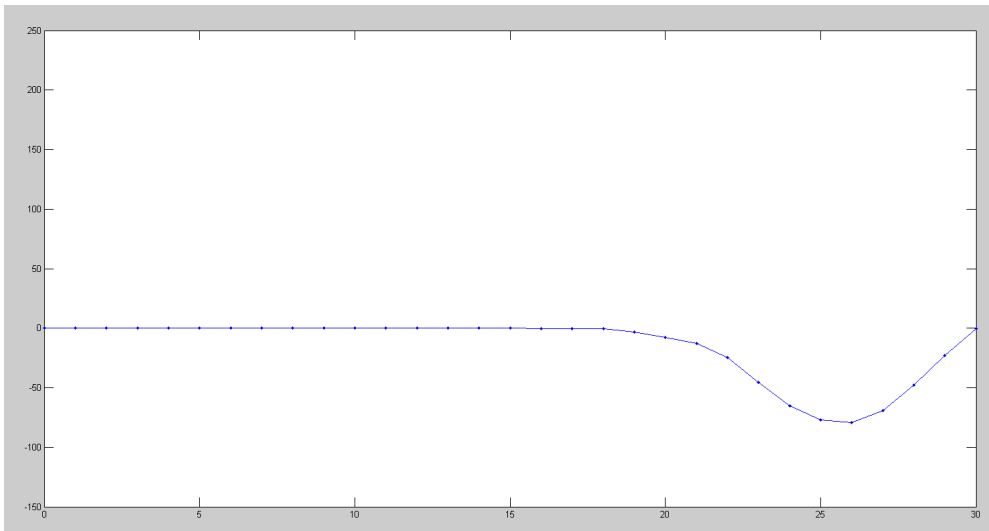5) Plot the voltage at $t = 8$ seconds for $1 / R_{30}C = 100$



Result with $1/R_30 C = 100$

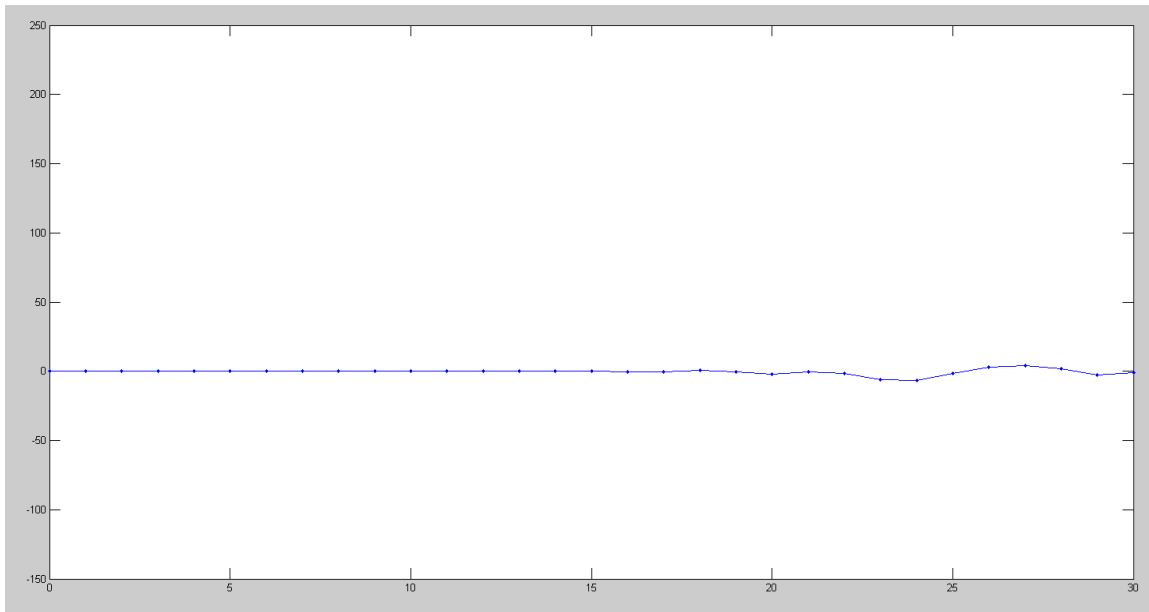6) Determine experimentally R_{30} so that the reflection is almost zero



Result with $1 / R_{30} C = 5$