


# ECE 111 - Homework #13

ECE 311 Circuits II - Phasors  
Due Monday, November 20th

## Phasor Voltages

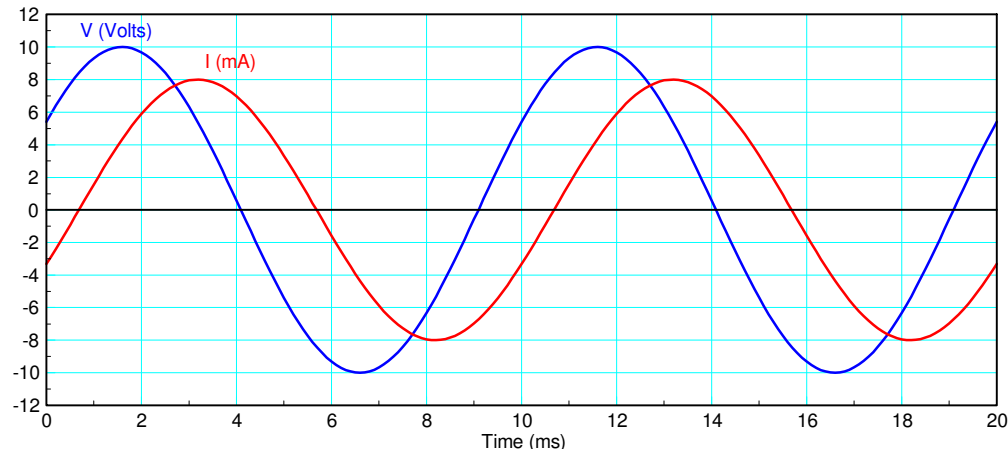1) Express  $V$  and  $I$  as phasors (i.e. as complex numbers)

- From this, determine the impedance,  $Z = V/I$



Voltage:

- Peak = 10V
- period = 10 ms
- delay = 1.5 ms

$$\theta = -\left(\frac{1.5s}{10s}\right) 360^\circ = -54.0^\circ$$

$$V = (10 \angle -54.0^\circ) V$$

Current

- Peak = 8mA
- delay = 3.2ms

$$\theta = -\left(\frac{3.2ms}{10ms}\right) 360^\circ = -115.2^\circ$$

$$I = (8 \angle -115.2^\circ) mA$$

Impedance


$$Z = \frac{V}{I} = \left( \frac{10 \angle -54.0^\circ}{0.008 \angle -115.2^\circ} \right)$$

$$Z = 1250 \angle 61.2^\circ \Omega \quad \text{polar form}$$

$$Z = (602.2 + j1095.4) \Omega \quad \text{rectangular form}$$

## Phasor Impedances

2) Determine the impedance,  $Z_{ab}$

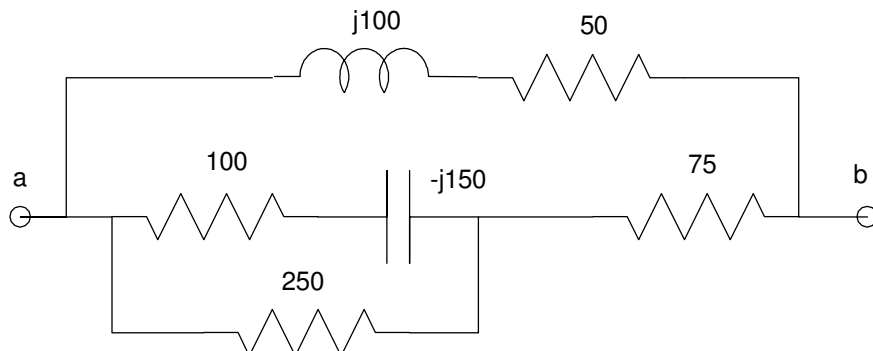


In Matlab

```
>> a = 100 - j*150;
>> b = 1/(1/a + 1/250)
b = 99.1379 -64.6552i
>> c = b + 75
c = 1.7414e+002 -6.4655e+001i
>> d = 1 / (1/c + 1/(50+j*100))
d = 75.7848 +51.3185i
```

With a HP42

```
100
enter
-150
complex
1/x
250
1/x
+
1/x
75
+
1/x
50
enter
100
complex
1/x
+
1/x
```

3) Determine the impedance,  $Z_{ab}$

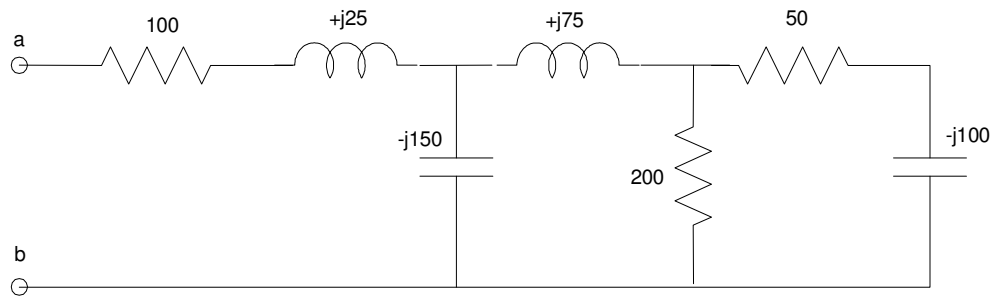


In Matlab

```
>> a = 50 - j*100;  
>> b = 1 / (1/a + 1/200)  
  
b = 62.0690 -55.1724i  
  
>> c = b + j*75  
  
c = 62.0690 +19.8276i  
  
>> d = 1 / ( 1/c + 1/(-j*150) )  
  
d = 67.1503 - 9.1710i  
  
>> e = d + 100 + j*25  
  
e = 1.6715e+002 +1.5829e+001i
```

With a HP42

```
50  
enter  
-100  
complex  
1/x  
200  
1/x  
+  
1/x  
0  
enter  
75  
complex  
+  
1/x  
0  
enter  
-150  
complex  
1/x  
+  
1/x  
100  
enter  
25  
complex  
+
```

## Voltage Nodes with Phasors

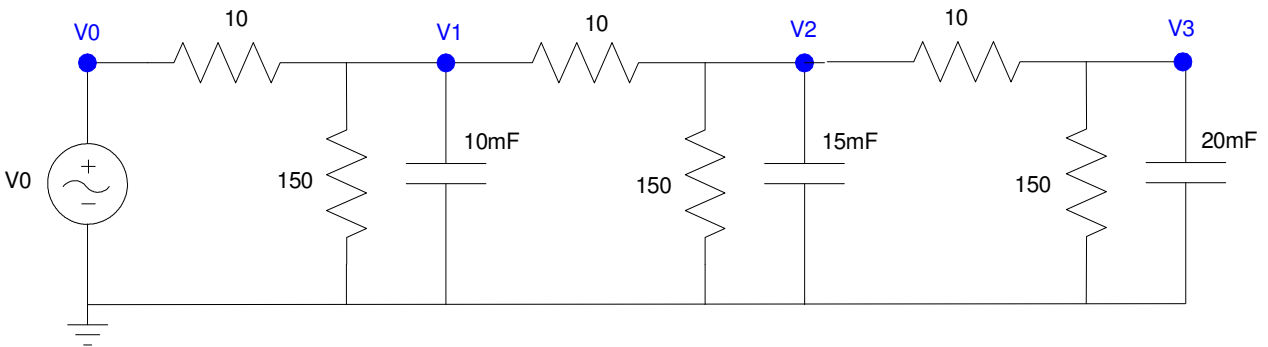

4) Assume  $V_0 = 10$ .

a) Determine the impedances of each element at 0 rad/sec

$$V_0 = 10$$

$$C \rightarrow \frac{1}{j\omega C} = \infty$$

Ignore capacitors at DC (the current is zero)

b) Write the voltage node equations

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{150}\right) + \left(\frac{V_1 - V_2}{10}\right) = 0$$

$$\left(\frac{V_2 - V_1}{10}\right) + \left(\frac{V_2}{150}\right) + \left(\frac{V_2 - V_3}{10}\right) = 0$$

$$\left(\frac{V_3 - V_2}{10}\right) + \left(\frac{V_3}{150}\right) = 0$$

c) Solve for  $V_1$ ,  $V_2$ , and  $V_3$ .

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{10}\right)V_0 + \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{10}\right)V_1 - \left(\frac{1}{10}\right)V_2 = 0$$

$$-\left(\frac{1}{10}\right)V_1 + \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{10}\right)V_2 - \left(\frac{1}{10}\right)V_3 = 0$$

$$-\left(\frac{1}{10}\right)V_2 + \left(\frac{1}{10} + \frac{1}{150}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{10}\right) & \left(\frac{-1}{10}\right) & 0 \\ 0 & \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{10}\right) & \left(\frac{-1}{10}\right) \\ 0 & 0 & \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> a1 = [1,0,0,0];  
>> a2 = [-1/10,1/10+1/150+1/10,-1/10,0];  
>> a3 = [0,-1/10,1/10+1/150+1/10,-1/10];  
>> a4 = [0,0,-1/10,1/10+1/150];  
>> A = [a1;a2;a3;a4]
```

```
    1.0000         0         0         0  
   -0.1000    0.2067   -0.1000         0  
         0   -0.1000    0.2067   -0.1000  
         0         0   -0.1000    0.1067
```

```
>> B = [10;0;0;0]
```

```
    10  
     0  
     0  
     0
```


```
>> V = inv(A)*B
```

```
V0    10.0000  
V1     8.4670  
V2     7.4984  
V3     7.0298
```

```
>>
```

5) Check your results in CircuitLab

Input the circuit in CircuitLab

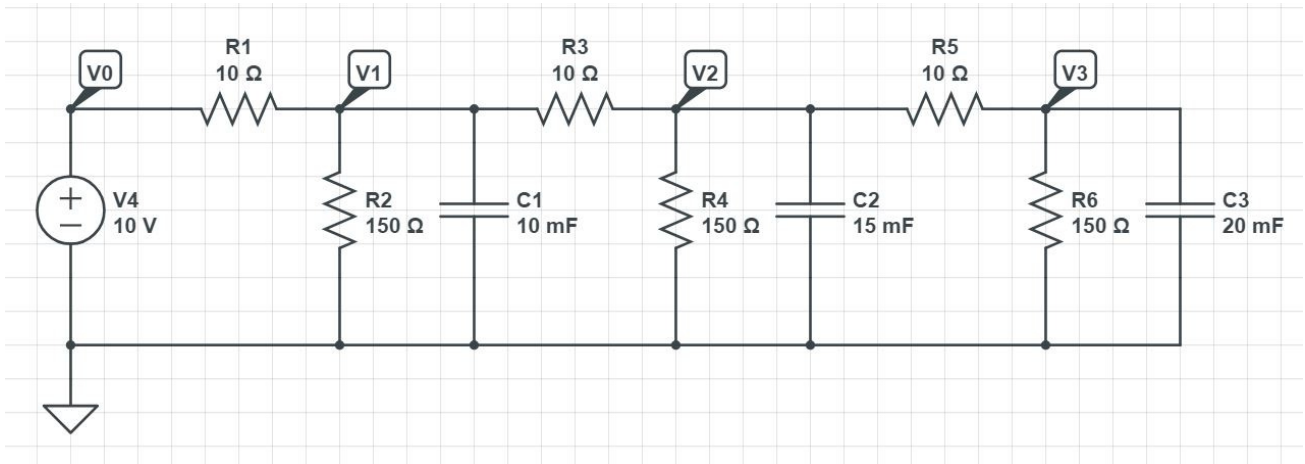

Run a DC simulation


The screenshot shows the DC simulation results in CircuitLab. On the left, a panel displays the following data:

Component	Value
V(V0)	10.00 V
V(V1)	8.467 V
V(V2)	7.498 V
V(V3)	7.030 V

Below the table are buttons for '+ Add Expression', 'Export Results...', and 'Run DC Solver'. At the bottom of the panel are tabs for 'DC Sweep', 'Time Domain', and 'Frequency Domain'. On the right, a partial circuit diagram is visible, showing the source V4, resistor R1, and resistor R2, with voltmeters V0 and V1 connected across them.

The answers are the same as Matlab

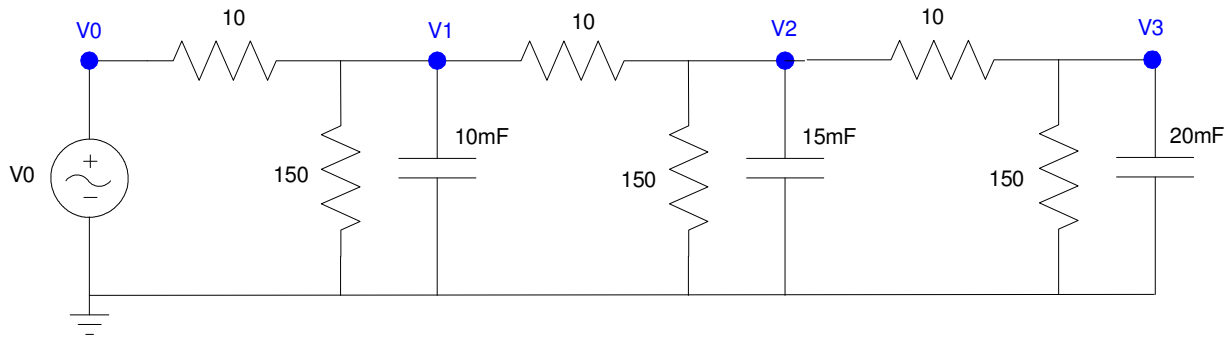6) Assume  $V_0 = 10 \sin(2t)$   $10V, 2 \text{ rad/sec sine wave } (0.318\text{Hz})$



a) Determine the impedances of each element at 2 rad/sec


$$V_0 = 0 - j10, \quad \omega = 2$$

$$C_1 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(0.01)} = -j50$$

$$C_2 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(0.015)} = -j33.3$$

$$C_3 \rightarrow \frac{1}{j\omega C} = \frac{1}{j(2)(0.02)} = -j25$$

Redraw the circuit

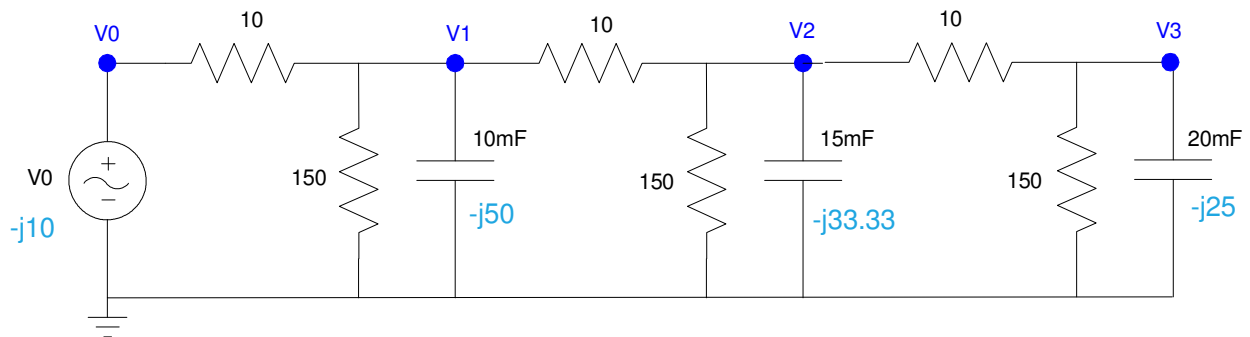

b) Write the voltage node equations

$$V_0 = -j10$$

$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{150}\right) + \left(\frac{V_1}{-j50}\right) + \left(\frac{V_1 - V_2}{10}\right) = 0$$

$$\left(\frac{V_2 - V_1}{10}\right) + \left(\frac{V_2}{150}\right) + \left(\frac{V_2}{-j33.33}\right) + \left(\frac{V_2 - V_3}{10}\right) = 0$$

$$\left(\frac{V_3 - V_2}{10}\right) + \left(\frac{V_3}{150}\right) + \left(\frac{V_3}{-j25}\right) = 0$$

c) Solve for V1, V2, and V3 as complex numbers

Group terms

$$V_0 = -j10$$

$$-\left(\frac{1}{10}\right)V_0 + \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{10}\right)V_1 - \left(\frac{1}{10}\right)V_2 = 0$$

$$-\left(\frac{1}{10}\right)V_1 + \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j33.33} + \frac{1}{10}\right)V_2 - \left(\frac{1}{10}\right)V_3 = 0$$

$$-\left(\frac{1}{10}\right)V_2 + \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j25}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{10}\right) & \left(\frac{-1}{10}\right) & 0 \\ 0 & \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j33.3} + \frac{1}{10}\right) & \left(\frac{-1}{10}\right) \\ 0 & 0 & \left(\frac{-1}{10}\right) & \left(\frac{1}{10} + \frac{1}{150} + \frac{1}{-j25}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -j10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve using Matlab

```
>> a1 = [1,0,0,0];
>> a2 = [-1/10,1/10+1/150+1/10+1/(-j*50),-1/10,0];
>> a3 = [0,-1/10,1/10+1/150+1/10+1/(-j*33.33),-1/10];
>> a4 = [0,0,-1/10,1/10+1/150+1/(-j*25)];
>> A = [a1;a2;a3;a4]
```

```
    1.0000         0         0         0
   -0.1000         0.2067 + 0.0200i   -0.1000         0
         0        -0.1000         0.2067 + 0.0300i   -0.1000
         0         0         -0.1000         0.1067 + 0.0400i
```

```
>> B = [-j*10;0;0;0]
```

```
    0 -10.0000i
    0
    0
    0
```

```
>> V = inv(A)*B
```

```
V0         0 -10.0000i
V1  -2.2688 - 6.2245i
V2  -3.4439 - 3.3177i
V3  -3.8532 - 1.6654i
```



d) Express  $V_1$ ,  $V_2$ , and  $V_3$  in terms of sine and cosine function:

$$\mathbf{v}_0 \quad 0 - 10.0000i$$

$$\mathbf{v}_1 \quad -2.2688 - 6.2245i$$

$$\mathbf{v}_2 \quad -3.4439 - 3.3177i$$

$$\mathbf{v}_3 \quad -3.8532 - 1.6654i$$

meaning

$$V_0 = 10 \sin(2t)$$

$$V_1 = -2.2688 \cos(2t) + 6.2245 \sin(2t)$$

$$V_2 = -3.4439 \cos(2t) + 3.3177 \sin(2t)$$

$$V_3 = -3.8532 \cos(2t) + 1.6654 \sin(2t)$$

7) Check your results in CircuitLab using a transient simulation for 15 seconds (time step = 15ms).

Note: polar form works better for graphs. This tells you the magnitude of each voltage and its delay

```
>> abs(V)

10.0000
 6.6251
 4.7820
 4.1977


>> angle(V)*180/pi

-90.0000
-110.0263
-136.0689
-156.6249

>>
```


Input the system into CircuitLab. Note
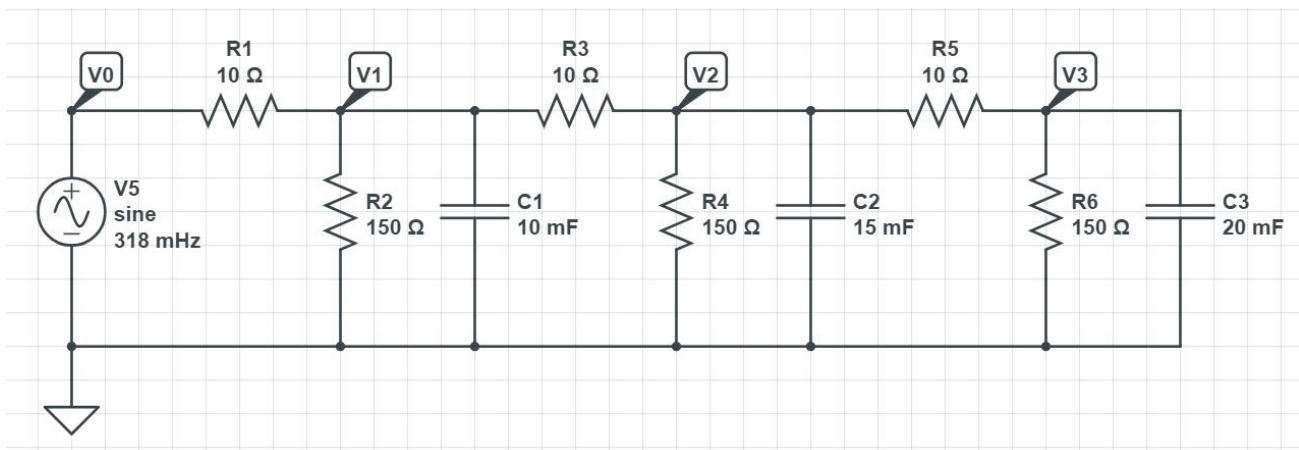
$$2 \frac{\text{rad}}{\text{sec}} = \left( \frac{2}{2\pi} \right) \text{Hz} = 0.318 \text{Hz}$$




One cycle is  $1/0.318 = 3$  seconds. Simulate for two cycles (7 seconds)

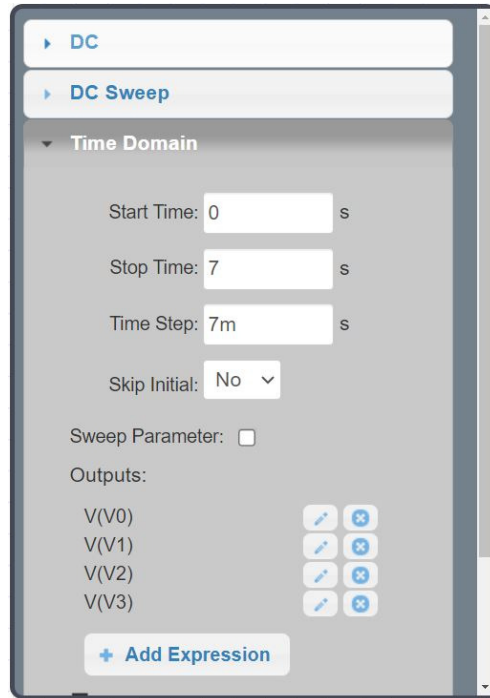- Make the step size 1000x smaller to get 1000 points on the plot



This results in

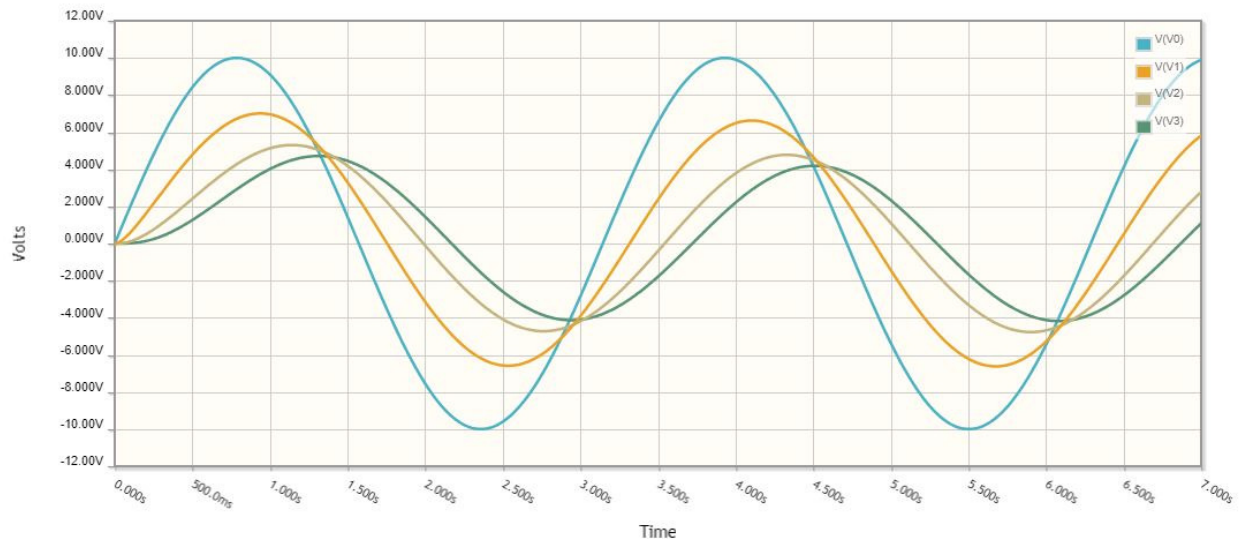

Note: This matches Matlab's numbers. The magnitude of the voltages should be

V0 = 10.0000V  
V1 = 6.6251V  
V2 = 4.7820V  
V3 = 4.1977V