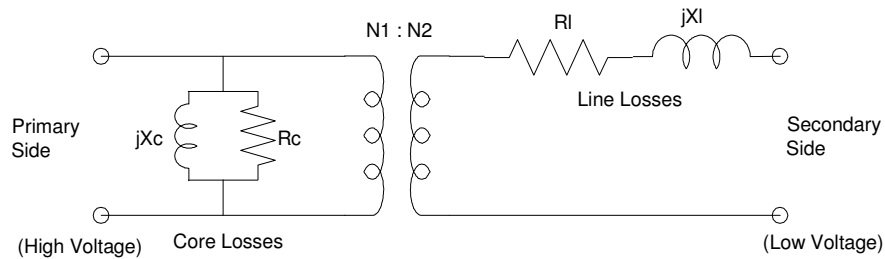


ECE 111: Homework 16

ECE 331 Energy Conversion
Due Monday, December 11th

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	$V_1 = 13.2\text{kV}$	40 W	0.015
Short-Circuit Test	$V_2 = 40\text{V}$	12 W	0.985

Open Circuit Test

$$P = V \cdot I \cdot pf$$

```
>> V = 13.2e3;
>> P = 40;
>> pf = 0.015;
>> I = P / ( V * pf )
```

$$I = 0.2020$$

$$Z = \left(\frac{V}{I} \right) \angle \theta$$

$$\cos \theta = pf$$

```
>> q = acos(pf)
```

$$q = 1.5558 \text{ radians}$$

The series model for the core is then:

```
>> Z = V/I * (cos(q) + j*sin(q))
```

$$Z = 9.8010e+002 + 6.5333e+004i$$

The parallel model for the core is then:

```
>> Rc = 1/real(1/Z)
```

```
Rc = 4.3560e+006
```

```
>> Xc = - 1/imag(1/Z)
```

```
Xc = 6.5347e+004
```

Line Model:

```
>> V = 40;
```

```
>> P = 12;
```

```
>> pf = 0.985;
```

```
>> I = P / ( V * pf )
```

```
I = 0.3046
```

```
>> q = acos(pf)
```

```
q = 0.1734 radians
```

```
>> Z = V/I * (cos(q) + j*sin(q))
```


```
Z = 1.2936e+002 +2.2662e+001i
```

```
>> RL = real(Z)
```


```
RL = 129.3633
```

```
>> XL = imag(Z)
```

```
XL = 22.6621
```

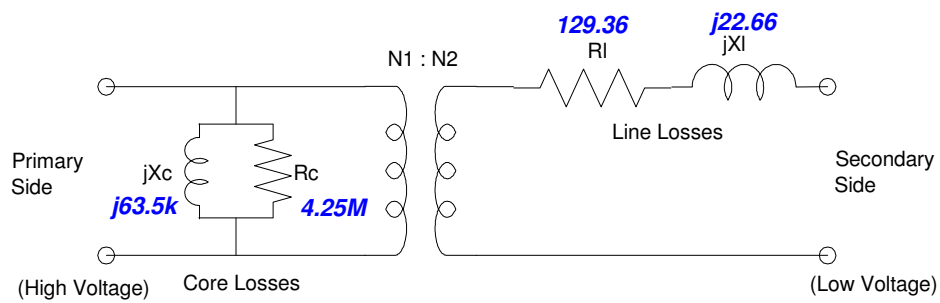


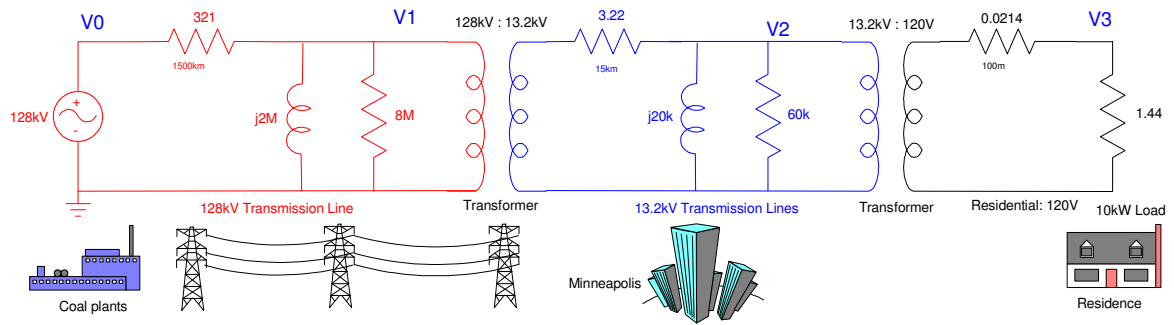2) Convert the voltages and impedances to the 120V node (right side)



```
>> V0 = 128000 * (120/128000)
V0      120
>> R01 = 321 * (120/128000)^2
R01 = 2.8213e-004
>> R1 = 2e6 * (120/128000)^2
R1 = 1.7578
>> X1 = j*8e6 * (120/128000)^2
X1 = 0 + 7.0313i
>> R12 = 3.22 * (120/13200)^2
R12 = 2.6612e-004
>> R2 = 60e3 * (120/13200)^2
R2 = 4.9587
>> X2 = j*20e3 * (120/13200)^2
X2 = 0 + 1.6529i
>> R23 = 0.0214;
>> R3 = 1.44;
```

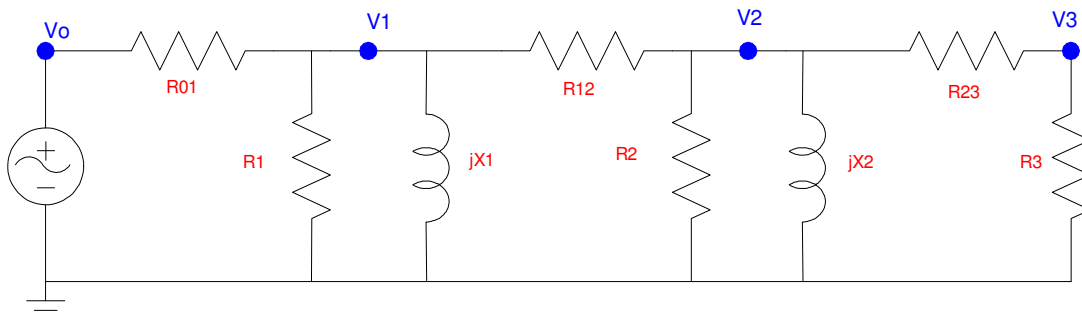3) Write the voltage node equations for this circuit (with transformers removed)



$$V_0 = 120$$

$$\left(\frac{V_1 - V_0}{R_{01}}\right) + \left(\frac{V_1}{R_1}\right) + \left(\frac{V_1}{jX_1}\right) + \left(\frac{V_1 - V_2}{R_{12}}\right) = 0$$

$$\left(\frac{V_2 - V_1}{R_{12}}\right) + \left(\frac{V_2}{R_2}\right) + \left(\frac{V_2}{jX_2}\right) + \left(\frac{V_2 - V_3}{R_{23}}\right) = 0$$

$$\left(\frac{V_3 - V_2}{R_{23}}\right) + \left(\frac{V_3}{R_3}\right) = 0$$

4) Determine the voltages at each node

Group terms

$$V_0 = 120$$

$$-\left(\frac{1}{R_{01}}\right)V_0 + \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right)V_1 - \left(\frac{1}{R_{12}}\right)V_2 = 0$$

$$-\left(\frac{1}{R_{12}}\right)V_1 + \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right)V_2 - \left(\frac{1}{R_{23}}\right)V_3 = 0$$

$$-\left(\frac{1}{R_{23}}\right)V_2 + \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ \left(\frac{-1}{R_{01}}\right) & \left(\frac{1}{R_{01}} + \frac{1}{R_1} + \frac{1}{jX_1} + \frac{1}{R_{12}}\right) & \left(\frac{-1}{R_{12}}\right) & 0 \\ 0 & \left(\frac{-1}{R_{12}}\right) & \left(\frac{1}{R_{12}} + \frac{1}{R_2} + \frac{1}{jX_2} + \frac{1}{R_{23}}\right) & \left(\frac{-1}{R_{23}}\right) \\ 0 & 0 & \left(\frac{-1}{R_{23}}\right) & \left(\frac{1}{R_{23}} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
>> a1 = [1,0,0,0];
>> a2 = [-1/R01,1/R01+1/R1+1/X1+1/R12,-1/R12,0];
>> a3 = [0,-1/R12,1/R12+1/R2+1/X2+1/R23,-1/R23];
>> a4 = [0,0,-1/R23,1/R23+1/R3];
>> A = [a1;a2;a3;a4]
```

```
0.0010          0          0          0
-3.5445         7.3028 - 0.0001i  -3.7578          0
0              -3.7578         3.8047 - 0.0006i  -0.0467
0              0              -0.0467         0.0474
```

```
>> B = [120;0;0;0]
```

```
120
0
0
0
```

```
>> V = inv(A)*B
```

```
V0 120.00  
V1 119.95 + 0.03i  
V2 119.92 + 0.04i  
V3 118.17 + 0.04i
```

If you prefer polar form:

```
>> abs(V)  
  
120.0000  
119.9508  
119.9225  
118.1664
```

The voltage at the customer has dropped to 118.16 Volts.

5) Determine the efficiency of this system

- Ignoring the core losses
 - Assumes a large number of customers share these losses
- Including the core losses
 - Assumes a single customer

Compute the power dissipated in each resistor

```
>> V0 = V(1);  
>> V1 = V(2);  
>> V2 = V(3);  
>> V3 = V(4);  
>> P01 = (abs(V0-V1))^2 / R01
```

```
P01 = 10.8551
```

```
>> P1 = (abs(V1))^2 / R1
```

```
P1 = 8.1853e+003
```

```
>> P12 = (abs(V1-V2))^2 / R12
```

```
P12 = 4.4047
```

```
>> P2 = (abs(V2))^2 / R2
```

```
P2 = 2.9002e+003
```

```
>> P23 = (abs(V2-V3))^2 / R23
```

```
P23 = 144.1043
```

```
>> P3 = (abs(V3))^2 / R3
```

```
P3 = 9.6967e+003
```

a) The efficiency including everything (single customer)

```
>> eff = P3 / (P01 + P12 + P23 + P1 + P2 + P3)
```

```
eff = 0.4630
```

b) Efficiency ignoring the core losses (many customers)

```
>> eff = P3 / (P01 + P12 + P23 + P3)
```

```
eff = 0.9838
```

```
>>
```

