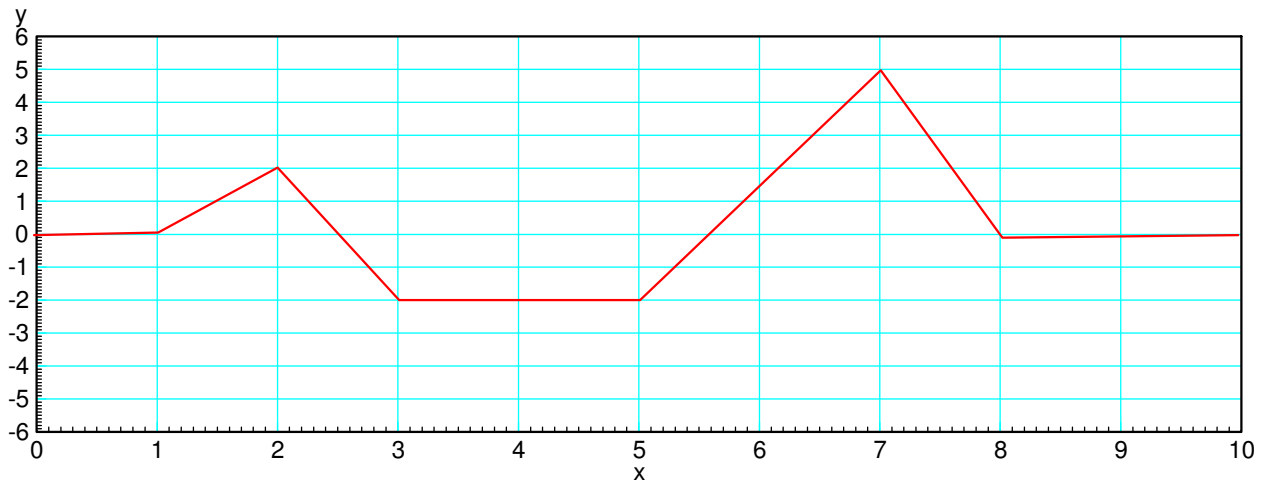


ECE 111 - Homework #7


Week #7: ECE 311 Circuits II - Due Tuesday, February 28th

1) Assume the current flowing through a one Farad capacitor is shown below. Sketch the voltage. Assume $V(0) = 0$. The voltage is the integral of the current (capacitors are integrators)

$$V = \frac{1}{C} \int I \cdot dt$$




Since $C = 1\text{F}$, the voltage is simply the integral of the current (same as homework #4)

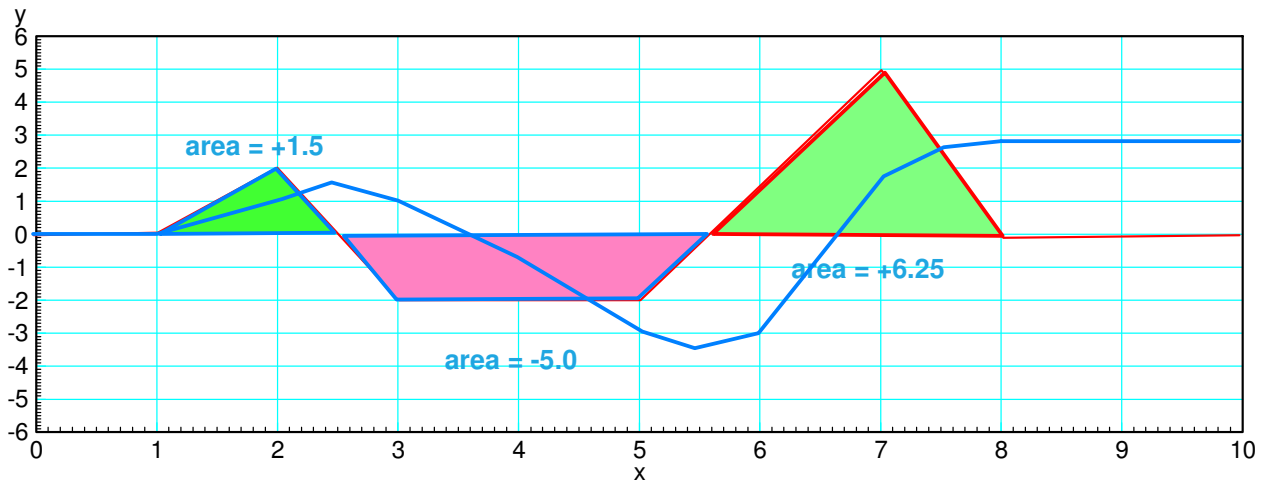

Problem 2-5: Assume a 10-stage RC filter (V0 .. V10)

10snip

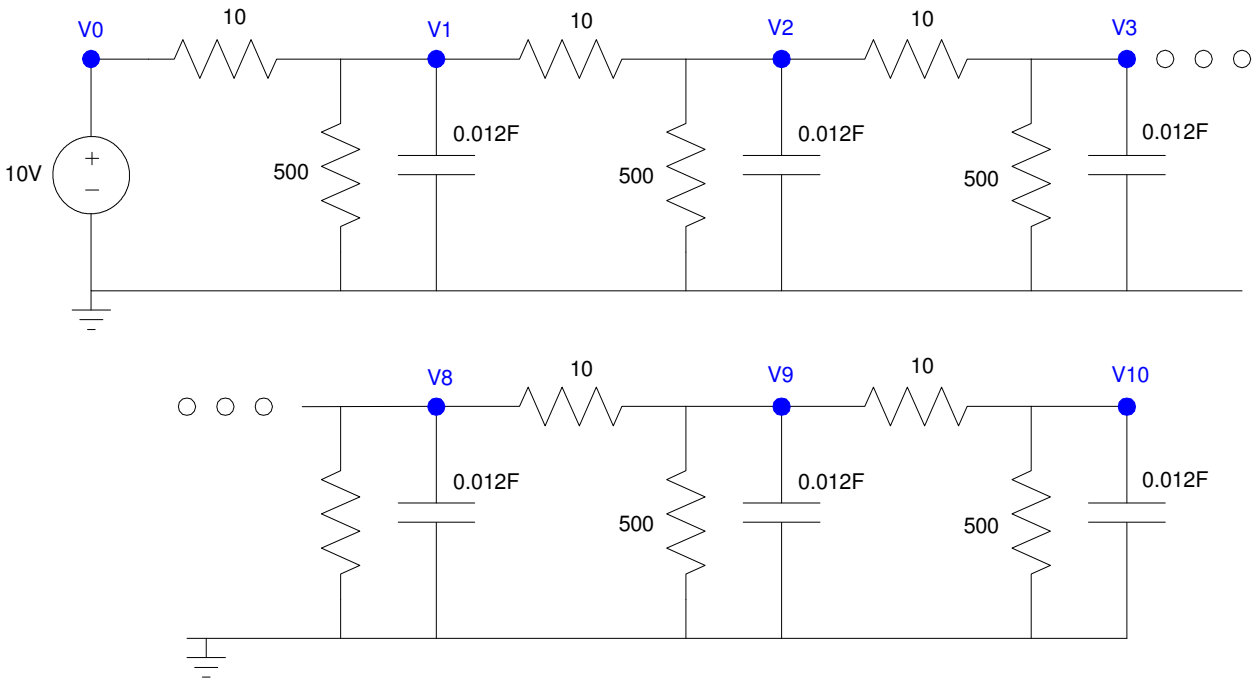

Problem 2) Write the dynamics for this system as a set of ten coupled differential equations:

$$I_1 = C \frac{dV_1}{dt} = \sum(\text{current to node } V_1)$$

$$I_1 = 0.012 \frac{dV_1}{dt} = \left(\frac{V_0 - V_1}{10} \right) + \left(\frac{V_2 - V_1}{10} \right) + \left(\frac{0 - V_1}{500} \right)$$

$$0.012 \frac{dV_1}{dt} = \left(\frac{1}{10} \right) V_0 - \left(\frac{1}{10} + \frac{1}{500} + \frac{1}{10} \right) V_1 + \left(\frac{1}{10} \right) V_2$$

$$\frac{dV_1}{dt} = 8.333V_0 - 16.833V_1 + 8.333V_2$$

The same pattern holds for nodes 2..9

$$\frac{dV_2}{dt} = 8.333V_1 - 16.833V_2 + 8.333V_3$$

$$\frac{dV_3}{dt} = 8.333V_2 - 16.833V_3 + 8.333V_4$$

⋮

Node #10 is a little different since there is only one 10-Ohm resistor connected to it

$$I_{10} = 0.012 \frac{dV_{10}}{dt} = \left(\frac{V_9 - V_{10}}{10} \right) + \left(\frac{0 - V_{10}}{500} \right)$$

$$\frac{dV_{10}}{dt} = 8.333V_9 - 8.50V_{10}$$

Forced Response for a 10-Node RC Filter (heat.m):

Problem 3) Using Matlab, solve these ten differential equations for $0 < t < 5$ s assuming


- The initial voltages are zero, and
- $V_0 = 10$ V.

Matlab Code:


```
% ECE 111 Homework #7
V = zeros(10,1);
dV = zeros(10,1);
V0 = 10;
dt = 0.01;
t = 0;
y = [];
while(t < 10)
    dV(1) = 8.333*V0 - 16.833*V(1) + 8.333*V(2);
    dV(2) = 8.333*V(1) - 16.833*V(2) + 8.333*V(3);
    dV(3) = 8.333*V(2) - 16.833*V(3) + 8.333*V(4);
    dV(4) = 8.333*V(3) - 16.833*V(4) + 8.333*V(5);
    dV(5) = 8.333*V(4) - 16.833*V(5) + 8.333*V(6);
    dV(6) = 8.333*V(5) - 16.833*V(6) + 8.333*V(7);
    dV(7) = 8.333*V(6) - 16.833*V(7) + 8.333*V(8);
    dV(8) = 8.333*V(7) - 16.833*V(8) + 8.333*V(9);
    dV(9) = 8.333*V(8) - 16.833*V(9) + 8.333*V(10);
    dV(10) = 8.333*V(9) - 8.5*V(10);
    V = V + dV*dt;
    t = t + dt;
    plot([0:10], [V0;V], '.-');
    ylim([0,10]);
    pause(0.01);
    y = [y ; V'];
end
pause(3)

t = [1:length(y)]' * dt;
plot(t,y);
xlabel('Time (seconds)');
ylabel('Volts');
```

Resulting Graph (for 0..10 seconds)


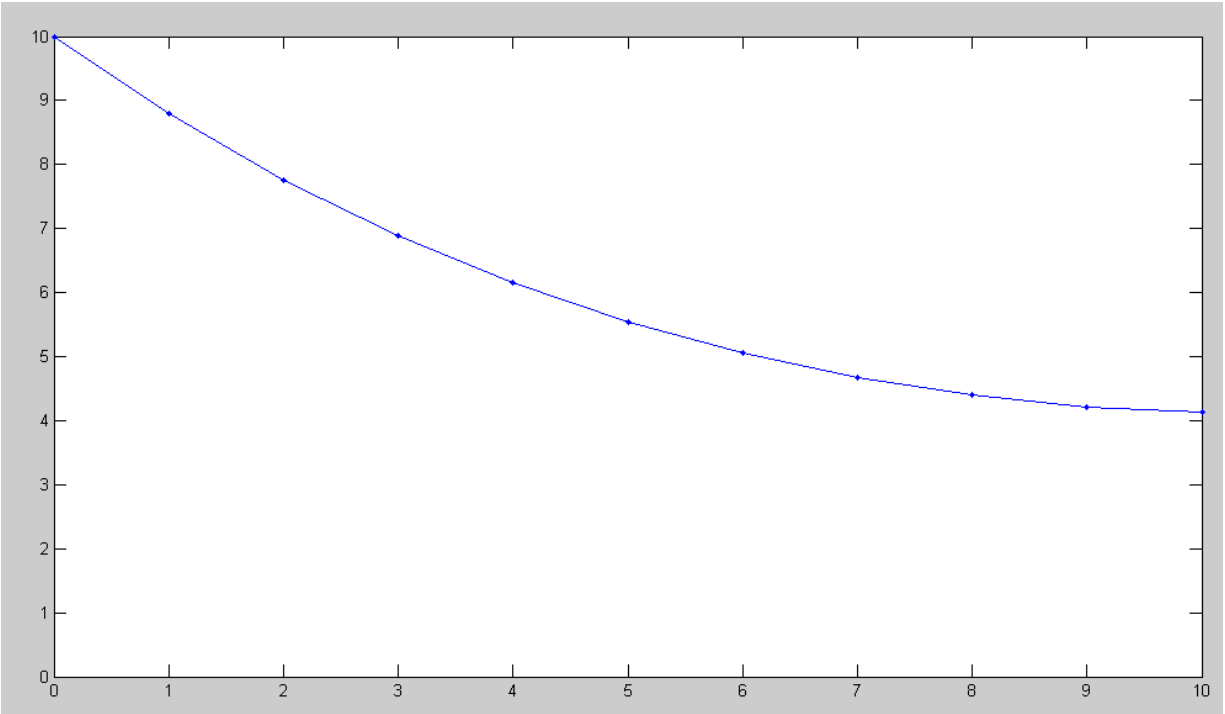


Voltage at Eac Node at t = 10 second

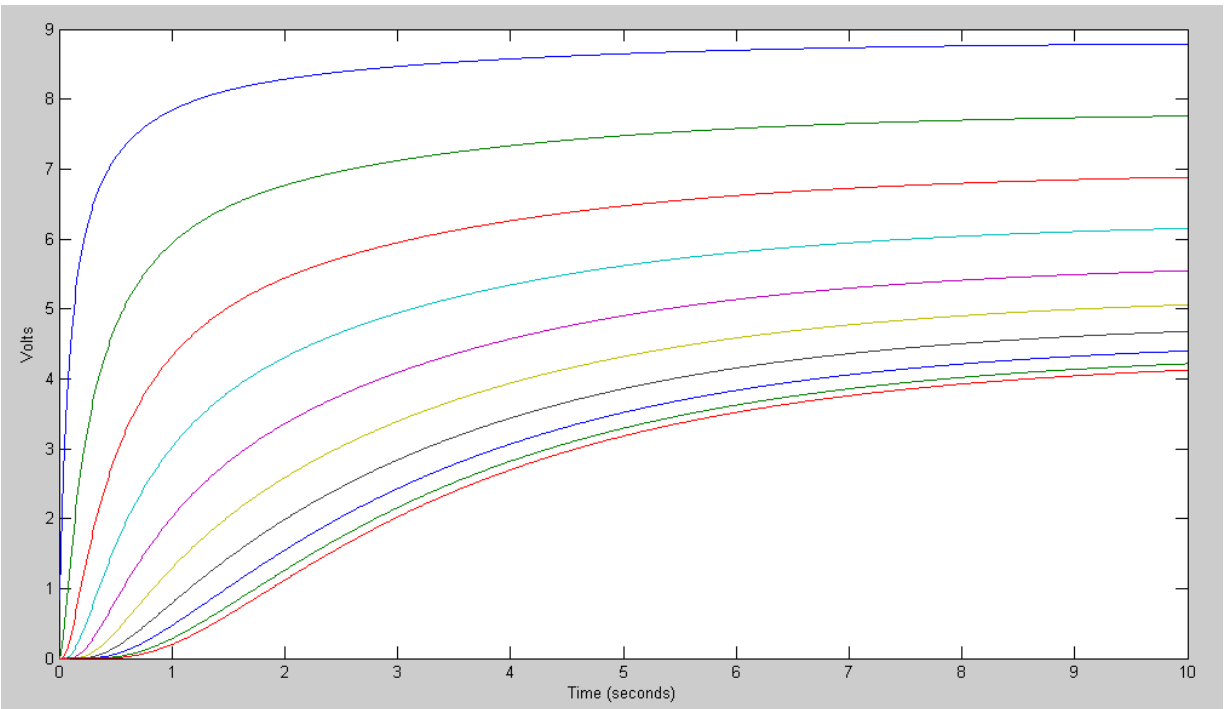

Voltage of each node vs. Time

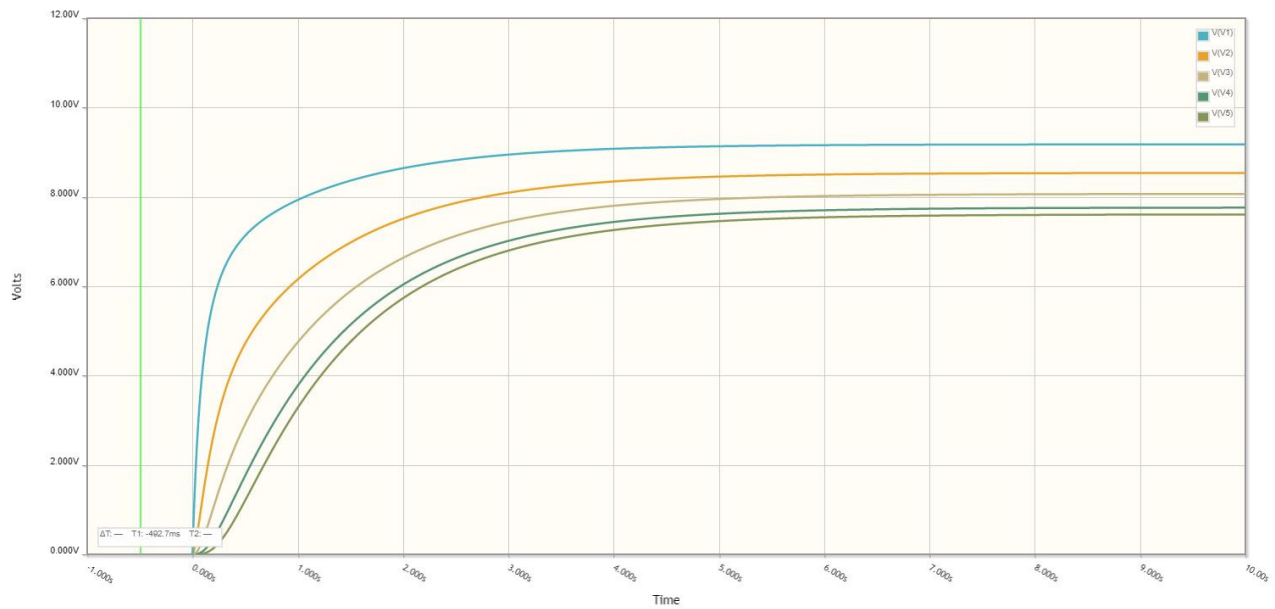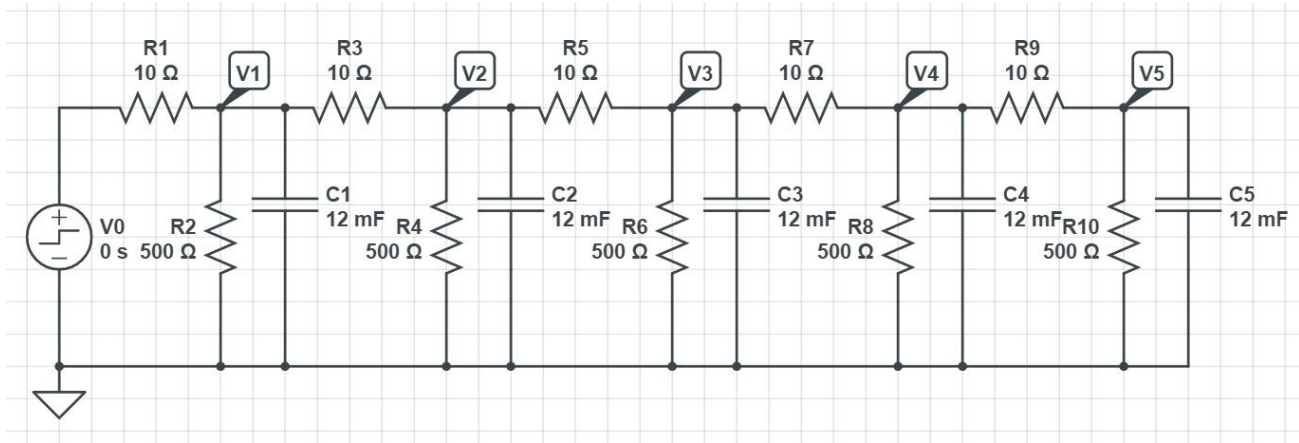Problem 4) Using CircuitLab, find the response of this circuit to a 10V step input. *note: It's OK if you only build this circuit to 3 nodes...*



This is almost the same result as Matlab (a little different since there are only four capacitors rather than ten)

Natural Response

Problem 5) Assume $V_0 = 0V$. Determine the initial conditions of $V_1..V_{10}$ so that

- The maximum voltage is 10V and
- 5a) The voltages go to zero as slow as possible
- 5b) The voltages go to zero as fast as possible.

Simulate the response for these initial conditions in Matlab.

This is an eigenvector problem

- A is a 10x10 matrix
- A has ten eigenvalues (how the system behaves)
- A has ten eigenvectors (what behaves that way)

The slow eigenvector decays as per its eigenvector (red)

The fast eigenvector decays as per its eigenvector (blue)

```
>> A = zeros(10,10);
>> for i=1:9
A(i,i) = -16.833;
A(i+1,i) = 8.333;
A(i,i+1) = 8.333;
end
>> A(10,10) = -8.5;
>> A

-16.8330    8.3330     0         0         0         0         0         0         0         0
 8.3330   -16.8330    8.3330     0         0         0         0         0         0         0
 0         8.3330   -16.8330    8.3330     0         0         0         0         0         0
 0         0         8.3330   -16.8330    8.3330     0         0         0         0         0
 0         0         0         8.3330   -16.8330    8.3330     0         0         0         0
 0         0         0         0         8.3330   -16.8330    8.3330     0         0         0
 0         0         0         0         0         8.3330   -16.8330    8.3330     0         0
 0         0         0         0         0         0         8.3330   -16.8330    8.3330     0
 0         0         0         0         0         0         0         8.3330   -16.8330    8.3330
 0         0         0         0         0         0         0         0         8.3330   -8.5000

>> [M,V] = eig(A)

M =

    fast
-0.1286   -0.2459    0.3412    0.4063    0.4352    0.4255    0.3780    0.2969   -0.1894    0.0650
 0.2459    0.4063   -0.4255   -0.2969   -0.0650    0.1894    0.3780    0.4352   -0.3412    0.1286
-0.3412   -0.4255    0.1894   -0.1894   -0.4255   -0.3412   -0.0000    0.3412   -0.4255    0.1894
 0.4063    0.2969    0.1894    0.4352    0.1286   -0.3412   -0.3780    0.0650   -0.4255    0.2459
-0.4352   -0.0650   -0.4255   -0.1286    0.4063    0.1894   -0.3780   -0.2459   -0.3412    0.2969
 0.4255   -0.1894    0.3412   -0.3412   -0.1894    0.4255   -0.0000   -0.4255   -0.1894    0.3412
-0.3780    0.3780    0.0000    0.3780   -0.3780   -0.0000    0.3780   -0.3780    0.0000    0.3780
 0.2969   -0.4352   -0.3412    0.0650    0.2459   -0.4255    0.3780   -0.1286    0.1894    0.4063
-0.1894    0.3412    0.4255   -0.4255    0.3412   -0.1894    0.0000    0.1894    0.3412    0.4255
 0.0650   -0.1286   -0.1894    0.2459   -0.2969    0.3412   -0.3780    0.4063    0.4255    0.4352


    slow
-0.0650
 0.1286
 0.1894
 0.2459
 0.2969
 0.3412
 0.3780
 0.4063
 0.4255
 0.4352

V =

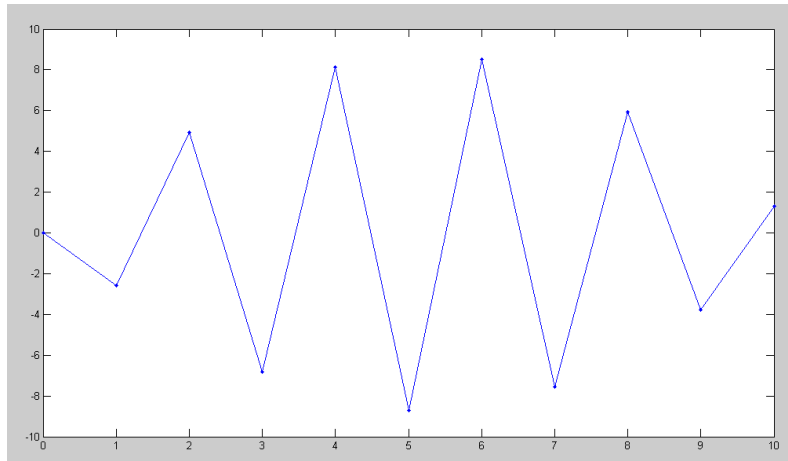
-32.7586  -30.6031  -27.2241  -22.9218  -18.0785  -13.1245  -8.5000  -4.6160  -1.8175  -0.3531
```

Change the Matlab code for the fast eigenvector


```
% ECE 111 Homework #7
V = M(:,1) * 20;
dV = zeros(10,1);
V0 = 0;
dt = 0.001;
t = 0;
y = [];
while(t < 1)
    dV(1) = 8.333*V0 - 16.833*V(1) + 8.333*V(2);
    etc
```




Fast Eigenvector

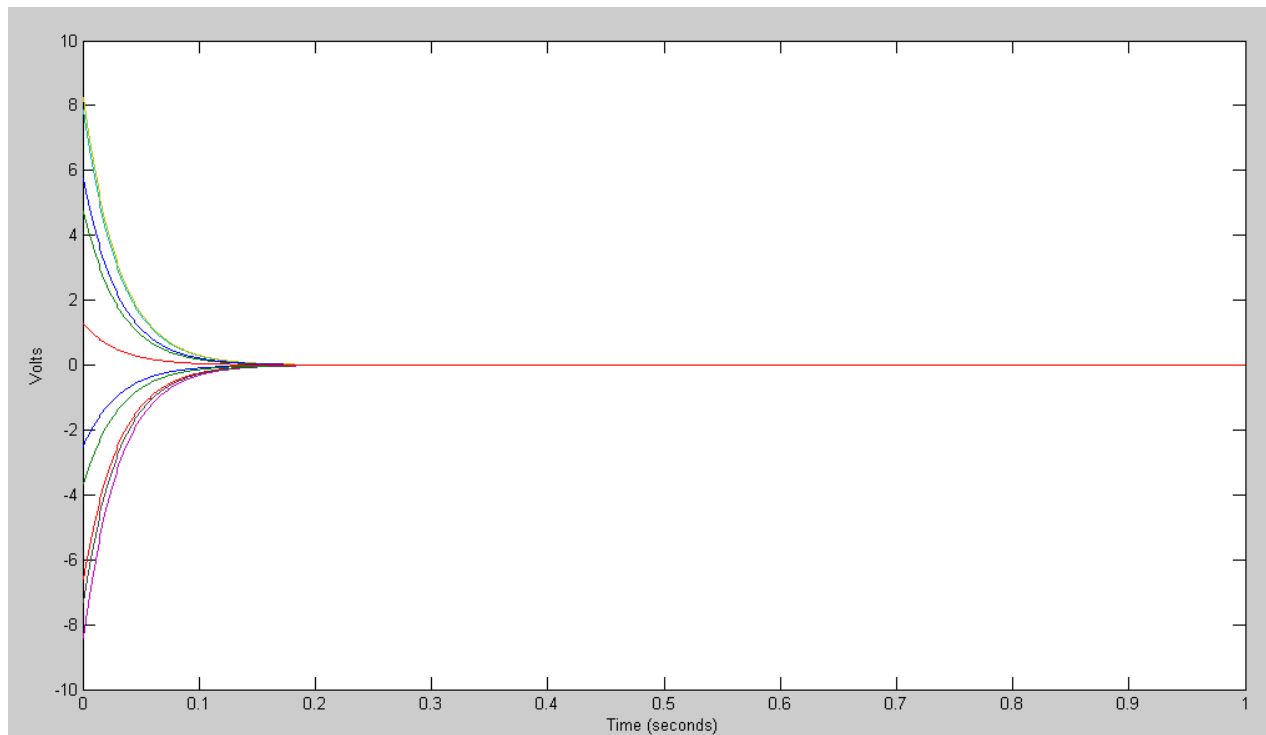

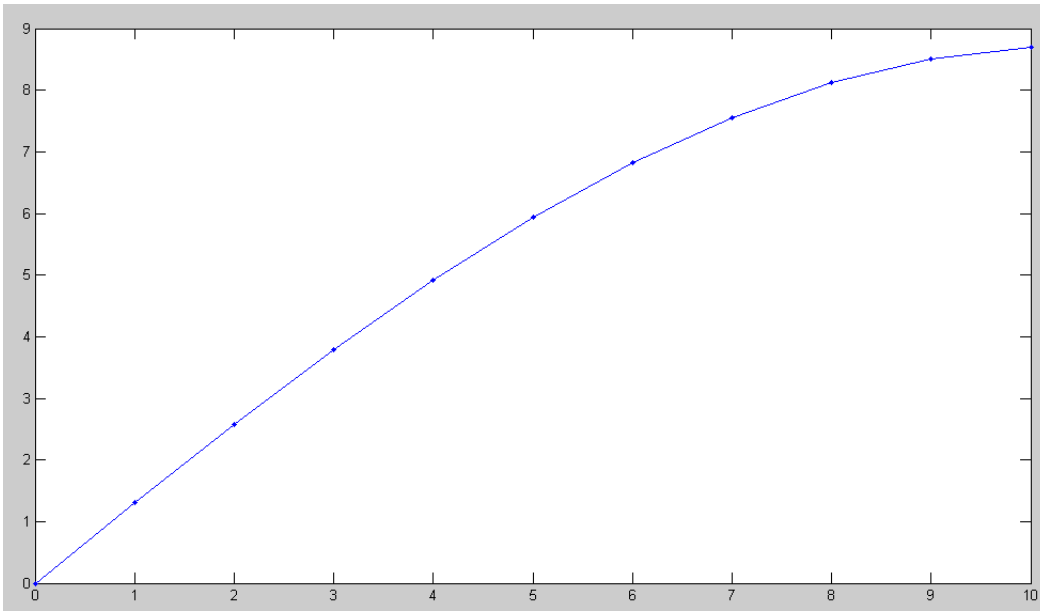The fast eigenvector decays quickly (as $\exp(-32.75t)$)



Slow Eigenvector

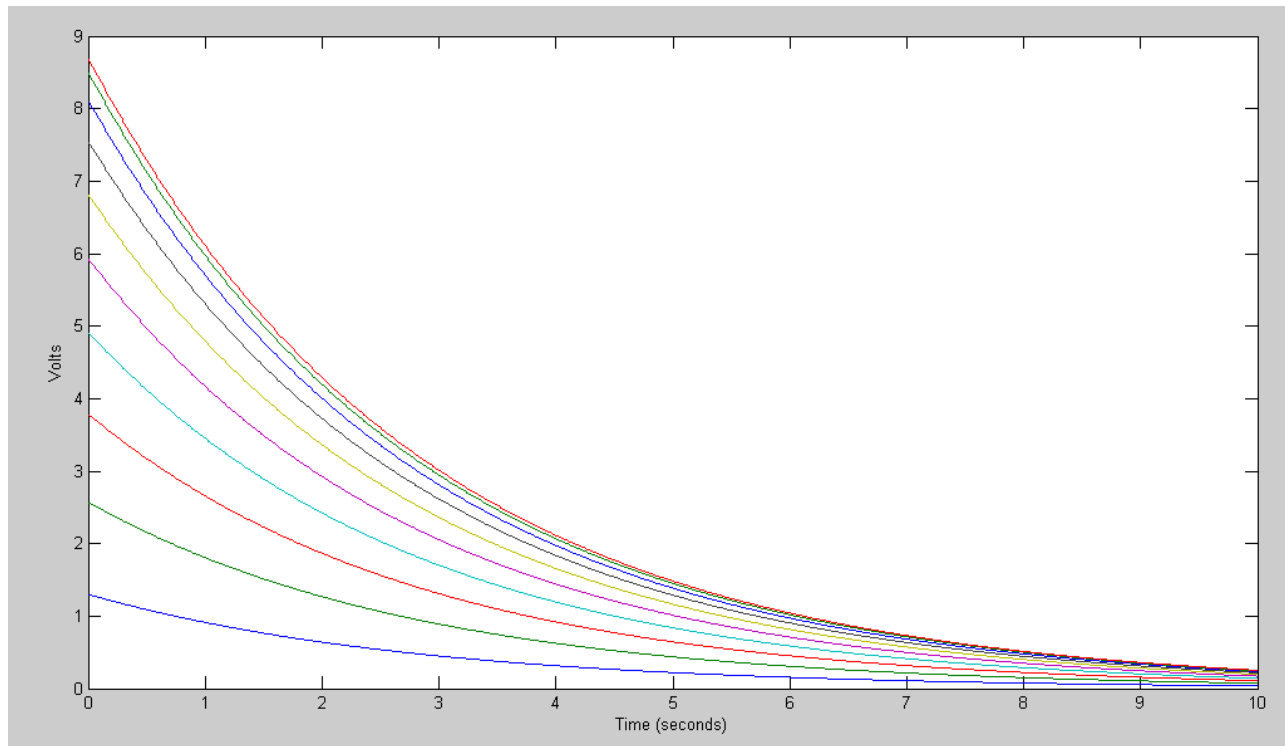


The slow eigenvector decays slowly

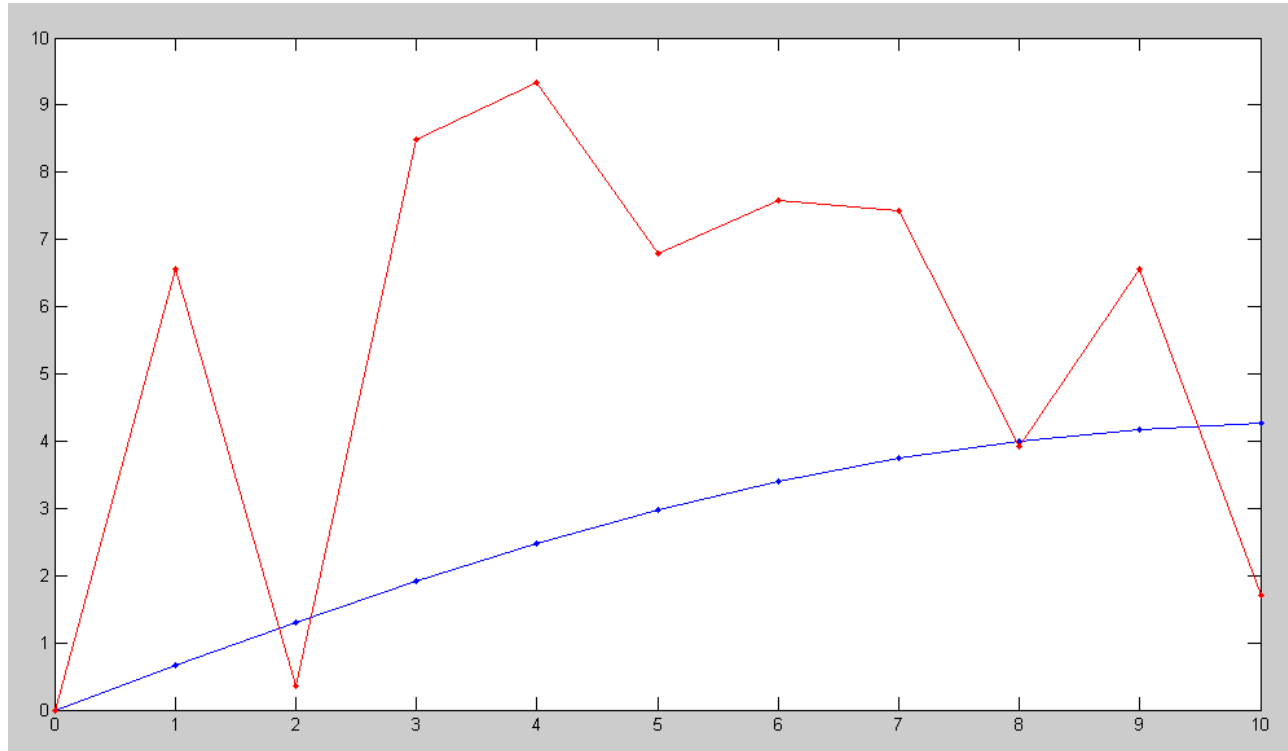Problem 6) Assume $V_{in} = 0V$. Pick random voltages for $V_1 .. V_{10}$ in the range of $(0V, 10V)$:

$$V = 10 * \text{rand}(10,1)$$

Plot the voltages at $t = 2$. Which eigenvector does it look like?



Initial Voltage (red) and voltage after 2 seconds (blue)

After two seconds, the voltage looks like the slow eigenvector