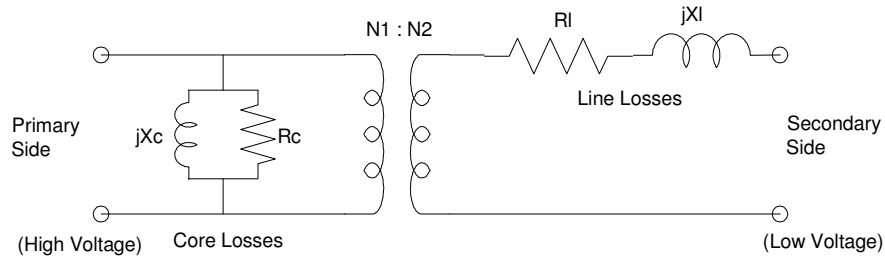


ECE 111: Homework 15

Week #15 - ECE 331 Energy Conversion. Due Tuesday, May 2nd

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	V1 = 13.2kV	56 W	0.025
Short-Circuit Test	V2 = 40V	9 W	0.975

Open-Circuit Test:

$$P = V \cdot I \cdot pf$$

$$56W = 13.2kV \cdot I \cdot 0.025$$

$$I = 0.1697A$$

$$Z = \left(\frac{V}{I}\right) \angle \arccos(pf)$$

$$Z = 77,785 \angle 88.5675^\circ$$

Convert to rectangular coordinates

$$Z = 1944.64 + j77,761.40$$

To find Rc and Xc, take the inverse

$$\frac{1}{Z} = \frac{1}{R_c} + \frac{1}{jX_c} = (3.2140e-7) - (j1.2852e-5)$$

$$R_c = \frac{1}{3.2140e-7} = 3.111M\Omega$$

$$jX_c = \frac{1}{-j1.2852e-5} = j77.81k\Omega$$

V	Power	pf
---	-------	----

Open-Circuit Test	V1 = 13.2kV	56 W	0.025
Short-Circuit Test	V2 = 40V	9 W	0.975

Short-Circuit Test

$$P = V \cdot I \cdot pf$$

$$9W = 40V \cdot I \cdot 0.975$$

$$I = 0.2308A$$

$$Z = \left(\frac{V}{I} \right) \angle \arccos(pf)$$

$$Z = 173.333 \angle 12.83^\circ$$

Convert to rectangular form

$$Z = 169.00 + j38.5155$$

This is the line model

$$R_L = 169.00\Omega$$

$$jX_L = j38.5155\Omega$$

For the utility grid on the back of the page....

2) Convert the voltages and impedances to the 120V node (right side)


Matlab Code

```
V0 = 138000 * (120/138000)
R01 = 342 * (120/138000)^2
R1 = 3e6 * (120/138000)^2
X1 = j*600e3 * (120/138000)^2
R12 = 2.14 * (120/9600)^2
X2 = j*6e3 * (120/9600)^2
R2 = 20e3 * (120/9600)^2
R23 = 0.01704
R3 = 0.36
```

Results

```
V0 = 120
R01 = 2.5860e-004
R1 = 2.2684
X1 = 0 + 0.4537i
R12 = 3.3438e-004
X2 = 0 + 0.9375i
R2 = 3.1250
R23 = 0.0170
R3 = 0.3600
```

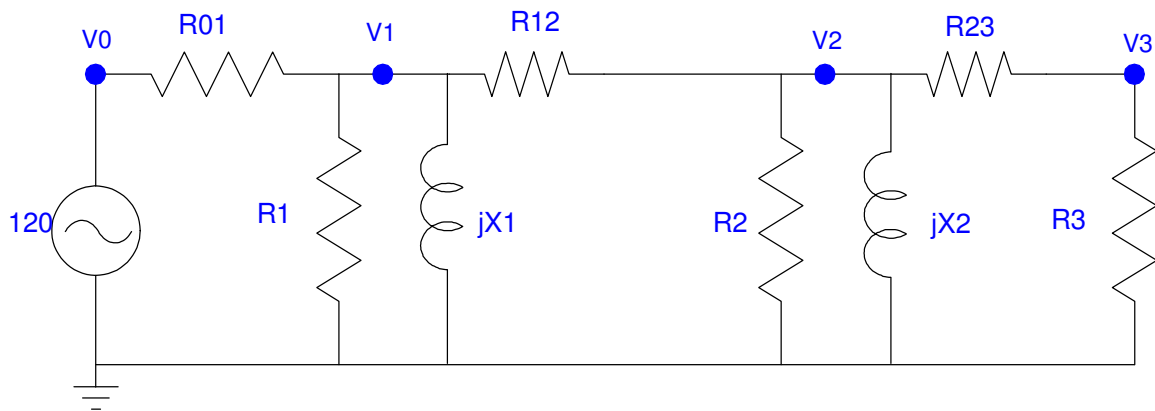3) Write the voltage node equations for this circuit (with transformers removed)



4) Determine the voltages at each node

Matlab Code

```
a0 = [1,0,0,0];  
a1 = [-1/R01,1/R01 + 1/R1 + 1/X1 + 1/R12, -1/R12, 0];  
a2 = [0,-1/R12, 1/R12 + 1/R2 + 1/X2 + 1/R23, -1/R23];  
a3 = [0,0,-1/R23, 1/R23 + 1/R3];  
A = [a0;a1;a2;a3]  
B = [120 ; 0 ; 0 ; 0]  
  
V = inv(A)*B
```

Result:

```
V0 120.00  
V1 119.89 + 0.10i  
V2 119.78 + 0.14i  
V3 114.36 + 0.14i
```

5) Determine the efficiency of this system

- Ignoring the core losses
 - Assumes a large number of customers share these losses
- Including the core losses
 - Assumes a single customer

Matlab Code

```
P01 = ( abs(V0 - V1) )^2 / R01  
P1 = abs(V1)^2 / R1  
P12 = ( abs(V1 - V2) )^2 / R12  
P2 = abs(V2)^2 / R2  
P23 = ( abs(V2 - V3) )^2 / R23  
P3 = abs(V3)^2 / R3  
  
eff1 = P3 / (P3 + P1 + P2 + P01 + P12 + P23)  
  
eff2 = P3 / (P3 + P01 + P12 + P23)
```

Result:

```
P01 = 3.1237e-024  
P1 = 6348.0  
P12 = 64.1564  
P2 = 4599.9  
P23 = 0.9387  
P3 = 39850
```

Total Efficiency (including everything)

```
eff1 = 0.7835
```

Efficiency ignoring core losses

```
eff2 = 0.9984
```

P01 = 3.1237e-024
P1 = 6348.0
P12 = 64.1564
P2 = 4599.9
P23 = 0.9387
P3 = 39850

