

# Current Loops

Write the current loop equations for the following circuits



