

Thevenin Equivalents & Max Power Transfer

Find the Thevenin equivalent for the following circuit.

Determine the maximum power this circuit can output to a load

