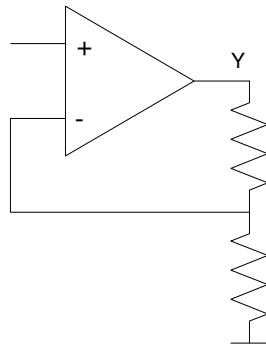


# Op-Amp Amplifiers


Design a circuit to implement

$$Y = +7 X$$



Design a circuit to implement

$$Y = -7 X$$

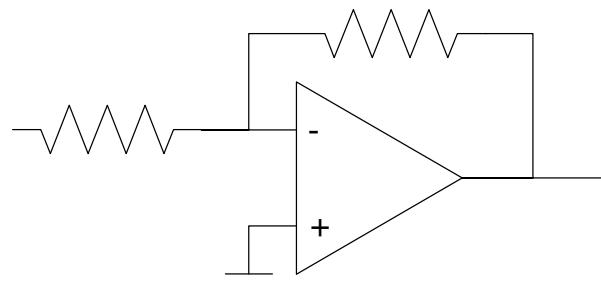

Design a circuit to implement

$$Y = 7X - 14$$

