

Capacitors

Determine the differential equations which describe the following RC circuit

