

# EE 206: Lab #9

## Phasors and RC Circuits

Note: The phasor impedance of resistors, inductors, and capacitors are


$$R \rightarrow R \quad L \rightarrow j\omega L \quad C \rightarrow \frac{1}{j\omega C}$$

1) Pick a resistor, inductor, and capacitor from the bin. Record it's value and compute its impedance at 100Hz (628 rad/sec). Note that the inductor has a resistance (due to the length of wire used) as well as an inductance.

	R	L		C
		R (DC resistance)	L	
Value				
Impedance at 100Hz				

2a) Using phasor analysis, compute the voltage at Y

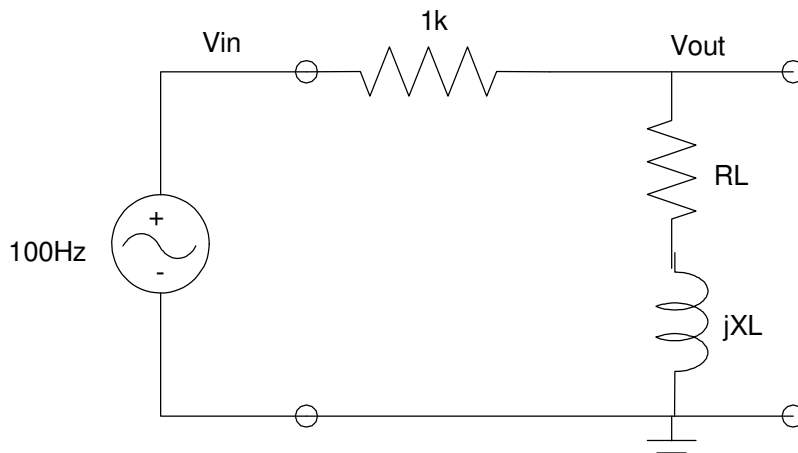2b) Build this circuit and compute the gain and phase shift from  $V_{in}$  to  $V_{out}$




Circuit for part 2. Note: the inductor produces  $R_L$  and  $jX_L$   
( you don't have to add a resistor in series with the inductor: it has a resistance  $R_L$  built in. )

	Calculated	Measured
Gain $V_{out} / V_{in}$		
Phase Shift $V_{out} / V_{in}$		

3a) Using phasor analysis, compute the voltage at Y

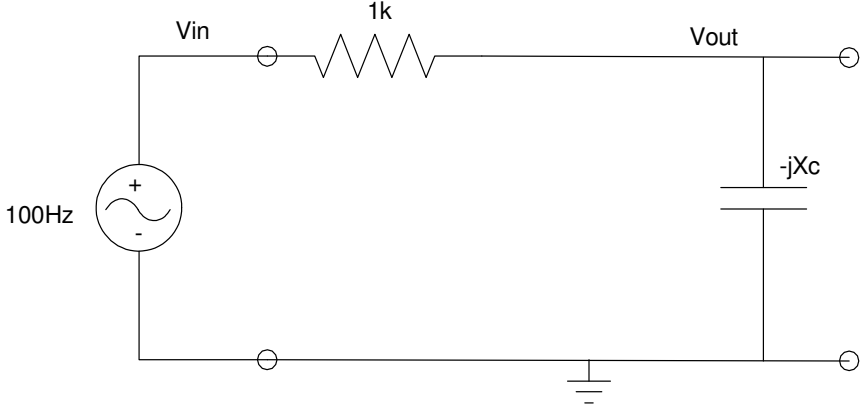
3b) Build this circuit and compute the gain and phase shift from  $V_{in}$  to  $V_{out}$



	Calculated	Measured
Gain $V_{out} / V_{in}$		
Phase Shift $V_{out} / V_{in}$		


4a) Using phasor analysis, compute the voltage at Y

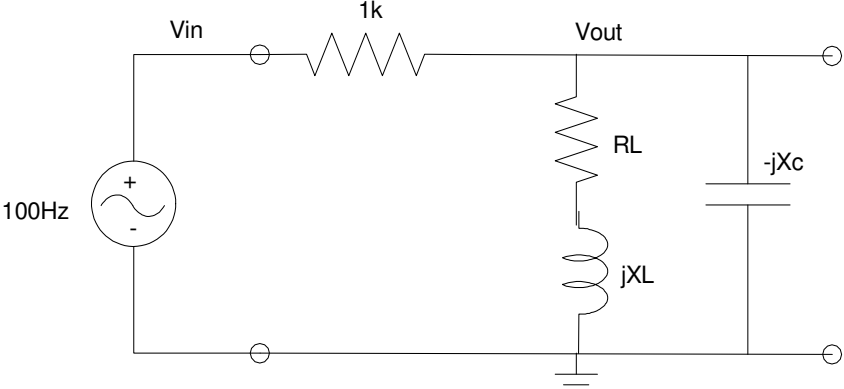4b) Build this circuit and compute the gain and phase shift from  $V_{in}$  to  $V_{out}$



	Calculated	Measured
Gain $V_{out} / V_{in}$		
Phase Shift $V_{out} / V_{in}$		

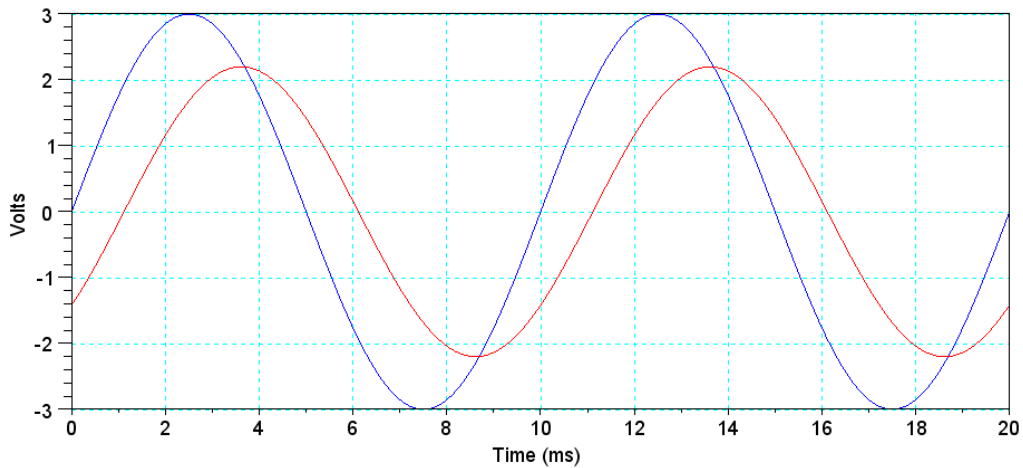Sample Calculations: To measure the gain and phase shift at 100Hz, display both  $V_{in}$  and  $V_{out}$  on the oscilloscope. For example, if the traces look like the following:



Sample Voltages:  $V_{in}$  (blue) and  $V_{out}$  (red)

Gain Calculations:

$$\text{Output} = \text{Gain} * \text{Input}$$

If you use the peak voltages

$$\text{gain} = \left( \frac{3V}{2.2V} \right) = 1.36$$

Phase Calculations:

One cycle is 360 degrees. The output (red line) is delayed from the input by

$$\theta = \left( \frac{1\text{ms delay}}{10\text{ms period}} \right) \cdot 360^\circ = -36^\circ$$

( negative phase is a delay, positive phase is a time advance )

The gain at 100Hz for this graph is thus

$$V_{out} = (1.36 \angle -36^\circ) \cdot V_{in}$$