



# Thevenin Equivalent and Load Lines

Sofar we have used two methods to solve a circuit: current loops and voltage nodes. You can solve any circuit using these techniques.

Another option, Thevenin Equivalents, is a little more tricky but it can make some circuits a lot easier to analyze if you understand the relationship for a linear circuit.

The idea behind Thevenin equivalents is that the voltage-current relationship for a linear circuit follows a straight line. This relationship will be exactly the same for any circuit which has the same voltage-current relationship.

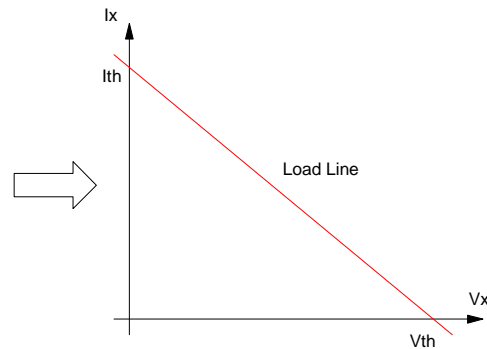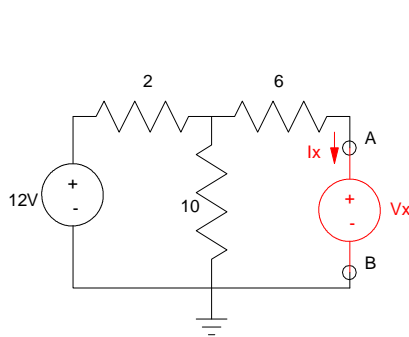For example, consider the following circuit:



Since it's a linear circuit, the  $V-I$  relationship at the load (V as the load is connected) in any circuit with the same load line is indistinguishable.

$I_x$  vs  $V_x$  will follow a straight line as shown on the right. A far simpler circuit will have the same  $V-I$  relationship.


Since all circuits with the same load line are indistinguishable, let's use the simplest one possible.

- A voltage source and resistance in series (called Thevenin equivalent)
- A current source and resistance in parallel (called Norton equivalent)


Let's use the simplest one possible.

$V_{th}$ ,  $R_{th}$ , or  $I_{th}$

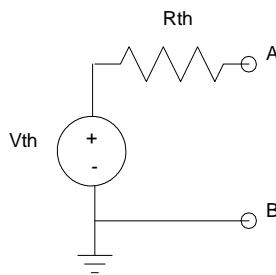The trick is to find the values of  $V_{th}$ ,  $R_{th}$ , or  $I_{th}$ .



Thevenin Equivalent

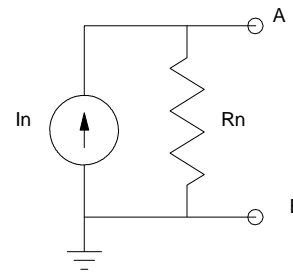

Norton Equivalent

Note that these circuits are equivalent to the circuit you're analyzing. This leads to the following procedure to find the Thevenin and Norton equivalents.


Following this procedure will find the Thevenin and Norton equivalents for any circuit.

- $V_{th}$  Measure the open-circuit voltage of your circuit.
- $R_{th} = R_n$  Turn off all sources ( $V=0$ ,  $I=0$ ). Measure the resulting resistance.
- $I_n$  Measure the short-circuit current.

Measure the resulting resistance.

It's probably easiest to illustrate this through examples.

Example 1: Determine the Thevenin and Norton equivalent for the following circuit:

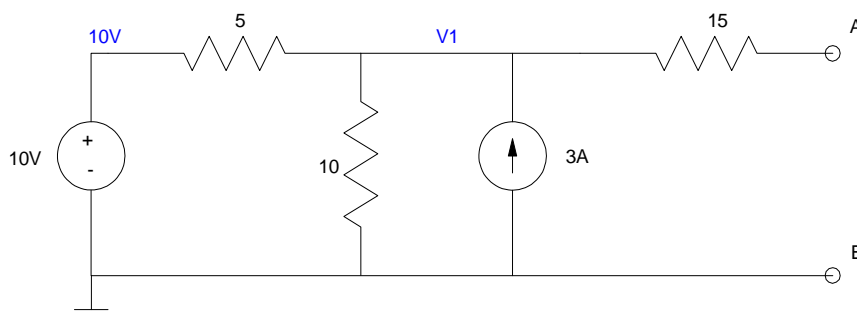

Example 1: To find  $V_{th}$ , compute the open-circuit voltage

$V_{th}$ : Measure the open-circuit voltage.


This isn't obvious so let's write the voltage node equation

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} - 3 = 0$$

$$V_{th} = V_1 = 16.67V$$

This is  $V_{th}$

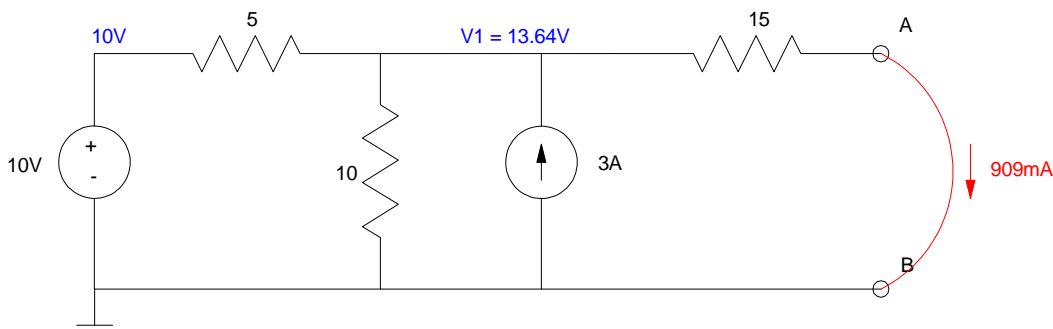$I_N$ : Short AB and measure the current. Again, this isn't obvious so write the node equation at  $V_1$




To find  $I_N$ , short the output and compute the short-circuit current

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} - 3 + \frac{V_1}{15} = 0$$

$$V_1 = 13.64V$$

$$I_{short} = I_N = \frac{13.64V}{15\Omega} = 909.1mA$$

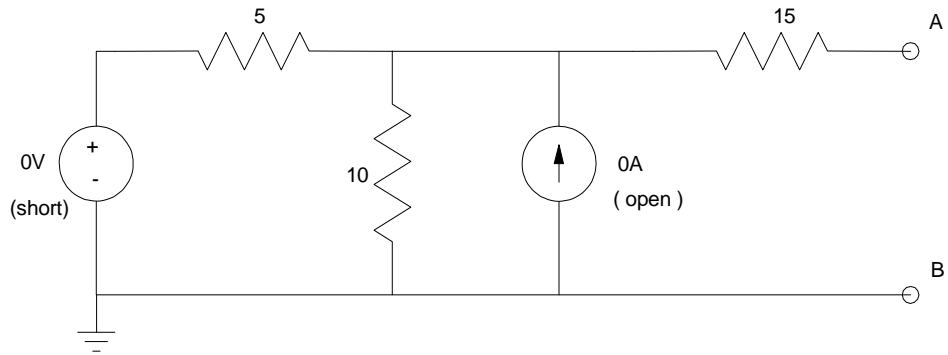Rth: Turn off the sources ( $V = 0$ ,  $I = 0$ ). Measure the resistance between A and B



To measure the Thevenin resistance, turn off all sources and compute the resistance between A and B



The resistance is

$$R_{AB} = 15 + 5 || 10$$

$$R_{AB} = 18.33\Omega$$

Note that you only need to compute two of these: the redundant.
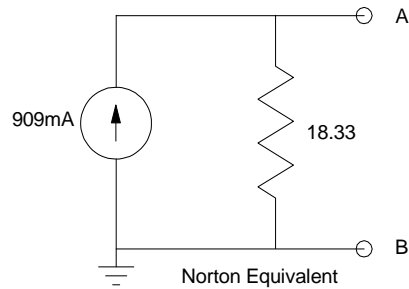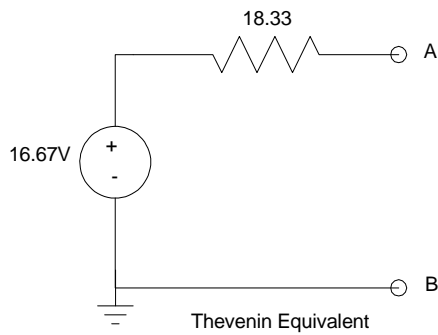
$$R_{AB} = \frac{V_{tn}}{I_n} = \frac{16.67V}{909mA} = 18.33\Omega$$



Resulting Thevenin and Norton equivalents of Example 1

Circuit Simplification using Thevenin and Norton Equivalent

Given a circuit, you can find the Thevenin and Norton equivalent


using the relationship

$$R_{Thevenin} = R_{Norton}$$

$$V_{Thevenin} = I_{Norton} \cdot R$$

$$I_{Norton} = \frac{V_{Thevenin}}{R}$$

For example, determine the Thevenin equivalent seen at terminal AB

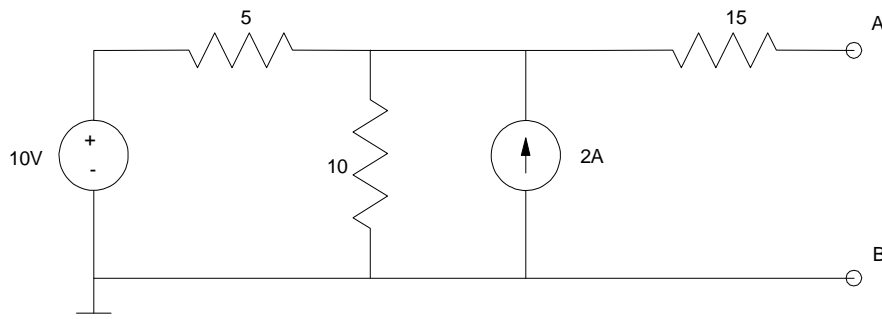


Example 2: Find the Thevenin equivalent at AB

Step 1: Convert the 10V : 5Ω resistor to its Norton equivalent

equivalent

$$I_N = \frac{10V}{5\Omega} = 2A$$

$$R_N = R_{Th} = 5\Omega$$

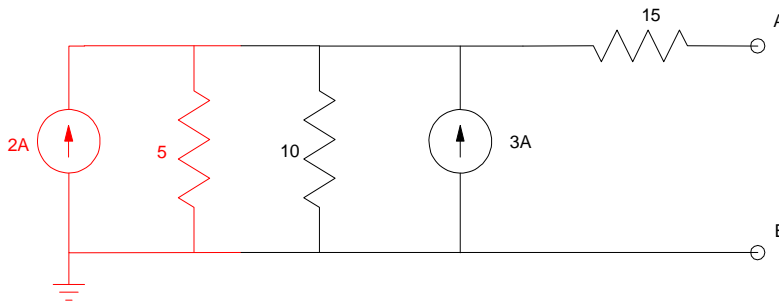


Convert the 10V : 5 Ohm source to its Norton equivalent (shown in red)

All the resistors in parallel

$$R_{net} = 5 || 10 = \left( \frac{1}{5} + \frac{1}{10} \right)^{-1} = 3.33 \Omega$$

All the current sources


$$I_{net} = 2 + 3 = 5$$

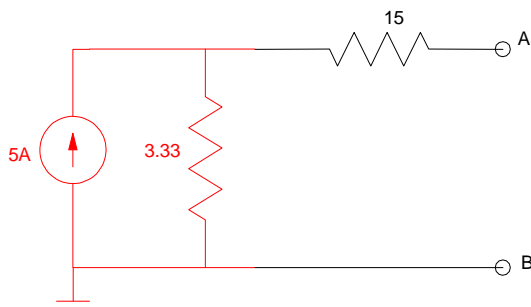

Add the resistors and current sources in parallel:

Convert back to Thevenin equivalent

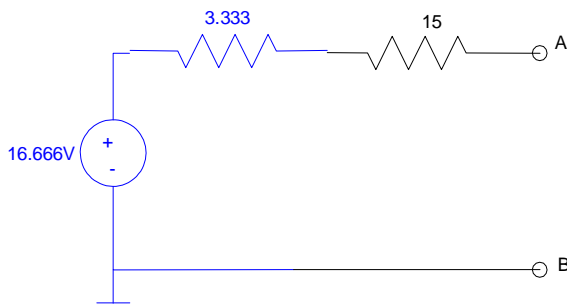
$$V_{th} = 5A \times 3.333 \quad W = 16.666 \quad V$$



Convert to a Thevenin equivalent (shown in blue)


All the resistors in series and you have the Thevenin equivalent

looking in from terminals A B

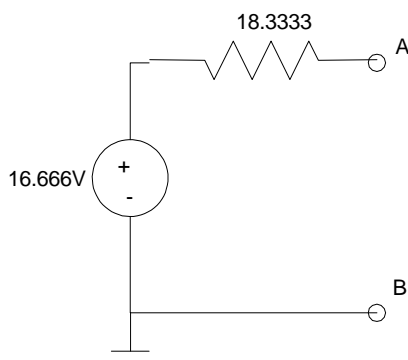

Thevenin Equivalent of Example 2

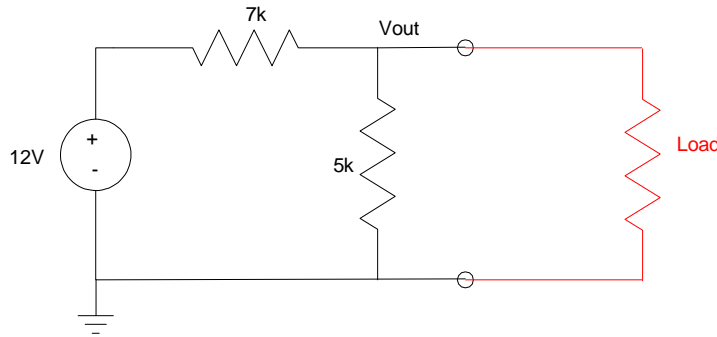Example 3: Thevenin equivalents can sometimes provide insight as to why something doesn't work. For example, the following circuit will convert 12VDC to 5VDC:



Voltage divider used to convert 12V to 5V

If you build this circuit and test it without a load, it works:  $V_{out} = 5V$ . If you then connect it to your iPhone, the output disappears. Why?

To explain that, think Thevenin equivalents. If you convert the circuit to its Thevenin equivalent, you get


$$V_{th} = V_{open} = \frac{5k}{5k+7k} 12V = 5V$$

$$R_{th} = 7k || 5k = 2916\Omega$$

If your load draws 100mA @ 5V, it looks like a 50 Ohm resistor

$$R_{load} = \frac{5V}{100mA} = 50\Omega$$

The circuit then becomes

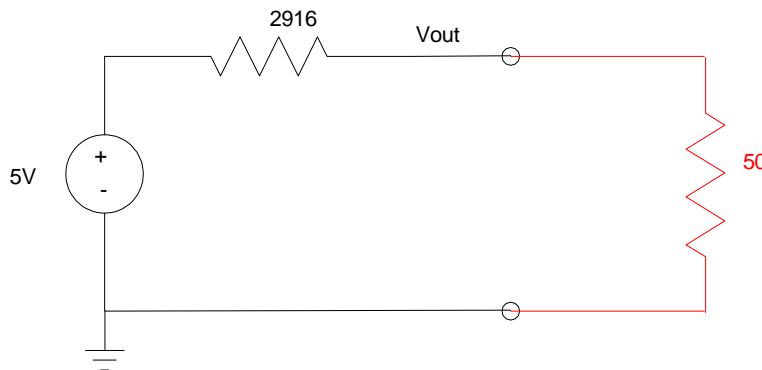

Thevenin equivalent of the voltage divider driving a load which draws 100mA @ 5V (i.e. a 50 Ohm resistor)

By voltage division,  $V_{out}$  is now

$$V_{out} = \frac{50}{50+2916} \times 5V$$

$$V_{out} = 0.0843V$$

This circuit works as a 5V source as long as you don't use Electronics, we'll cover other circuits which do work.

