

Capacitors & The Heat Equation


Capacitors

A capacitor is a set of parallel plates¹ with the capacitance equal to

$$C = \epsilon \frac{A}{d} \text{ (Farads)}$$

where

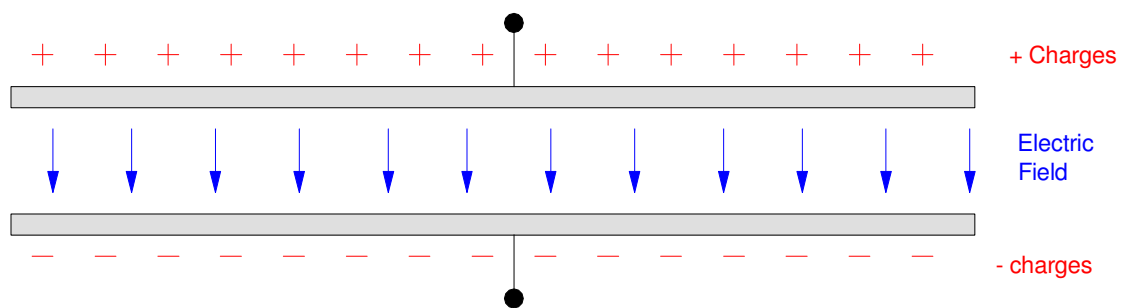- ϵ is the dielectric constant of the material between plates (air = $8.84 \cdot 10^{-12}$)
- A is the area of the capacitor, and
- d is the distance between plates.



A capacitor is two parallel plates. They store energy in the electric field between the plates

The area you need for 1 Farad with plates 1mm apart is

$$1 = (8.84 \cdot 10^{-12}) \frac{A}{0.001m}$$

$$A = 113,122,171m^2$$

The capacitor would need to have dimensions of 10.6km x 10.6km for a capacitance of 1 Farad. Typically, capacitors are in the order of micro-farads.

The charge stored in a capacitor is proportional to the voltage as

$$Q = C \cdot V$$

where Q is the charge in Coulombs (one Coulomb is equal to $6.242 \cdot 10^{18}$ electrons). When the voltage across a capacitor drops, the charge stored drops proportionally. This gives the fundamental equation for a capacitor:

$$I = \frac{dQ}{dt} = C \frac{dV}{dt} + V \frac{dC}{dt}$$

Assuming the capacitance is constant

¹ <http://www.electronics-tutorials.ws/>

$$I = C \frac{dV}{dt}$$

This means that capacitors are integrators:

$$V = \frac{1}{C} \int I \cdot dt$$

In Calculus, you will be covering integration and differentiation and how to come up with a closed-form solution to various problems. With MATLAB (i.e. in this class) you can solve using numerical methods.

Capacitors and Energy Storage

Capacitors store energy when charged. The energy stored is

$$P = VI = V \cdot C \frac{dV}{dt}$$

$$E = \int P dt = \int \left(VC \frac{dV}{dt} \right) dt = \int (VC) dV$$

$$E = \frac{1}{2} CV^2$$

The energy stored in a capacitor isn't large - but it is there. To put this in perspective, the energy stored in a 1F capacitor compared to other common items are as follows:

Item	Energy	Cost	\$ / MJ
1 pound Wyoming Coal	3,600,000 Joules	\$0.028	\$0.0078
1 pound ND Lignite	1,565,217 Joules	\$0.017	\$0.0108
1 pint of gasoline	15,000,000 Joules	\$0.37	\$0.0247
Lithium battery (D cell)	246,240 Joules	\$22	\$89.43
1F Capacitor (5V)	12.5 Joules	\$2.87	\$229,600


In theory, you *could* build an electric car using capacitors to store the energy. This would have advantages:

-

Example 2: 3-Stage RC Filter

Next, find the voltages for the following 3-stage RC filter when

$$V_0(t) = 10u(t)$$

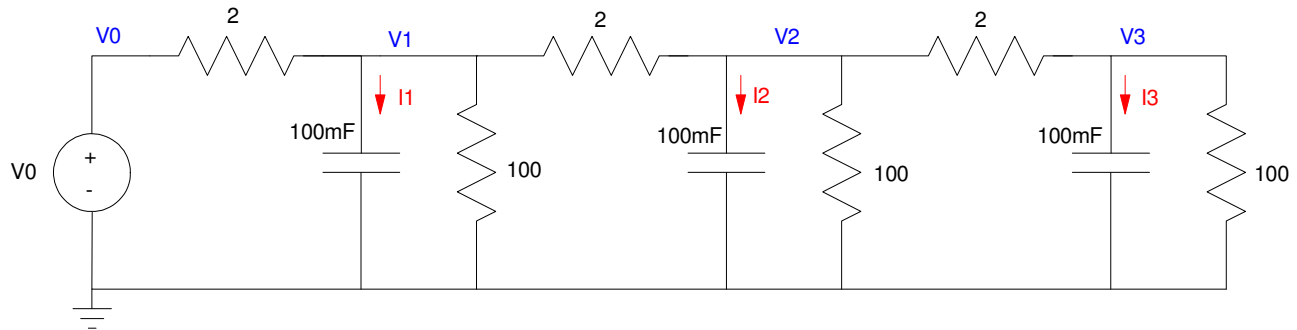

3-Stage RC Filter

To solve for V_1 , V_2 , and V_3

- Determine the currents to each capacitor: I_1 , I_2 , and I_3
- From this find dV/dt ,
- From this, integrate to find $V(t)$

Step 1: Determine I_1 , I_2 , and I_3 . From *current in = current out*

$$C_1 \frac{dV_1}{dt} = I_1 = \left(\frac{V_0 - V_1}{2} \right) + \left(\frac{0 - V_1}{100} \right) + \left(\frac{V_2 - V_1}{2} \right)$$

$$C_2 \frac{dV_2}{dt} = I_2 = \left(\frac{V_1 - V_2}{2} \right) + \left(\frac{0 - V_2}{100} \right) + \left(\frac{V_3 - V_2}{2} \right)$$

$$C_3 \frac{dV_3}{dt} = I_3 = \left(\frac{V_2 - V_3}{2} \right) + \left(\frac{0 - V_3}{100} \right)$$

Next, determine dV/dt

$$\frac{dV_1}{dt} = 5V_0 - 10.1V_1 + 5V_2$$

$$\frac{dV_2}{dt} = 5V_1 - 10.1V_2 + 5V_3$$

$$\frac{dV_3}{dt} = 5V_2 - 5.1V_3$$

Now integrate using Euler integration and Matlab.

- Note: You will get the same results if you run a Time Domain simulation in CircuitLab

In Matlab:

```
% 3-stage RC Filter

V0 = 10;
V1 = 0;
V2 = 0;
V3 = 0;
dt = 0.01;
t = 0;
Y = [];

while(t < 4)
    dV1 = 5*V0 -10.1*V1 + 5*V2;
    dV2 = 5*V1 -10.1*V2 + 5*V3;
    dV3 = 5*V2 -5.1*V3;


    V1 = V1 + dV1 * dt;
    V2 = V2 + dV2 * dt;
    V3 = V3 + dV3 * dt;

    t = t + dt;

    Y = [Y ; [V1, V2, V3] ];
end

t = [1:length(Y)]' * dt;


plot(t, Y);
```

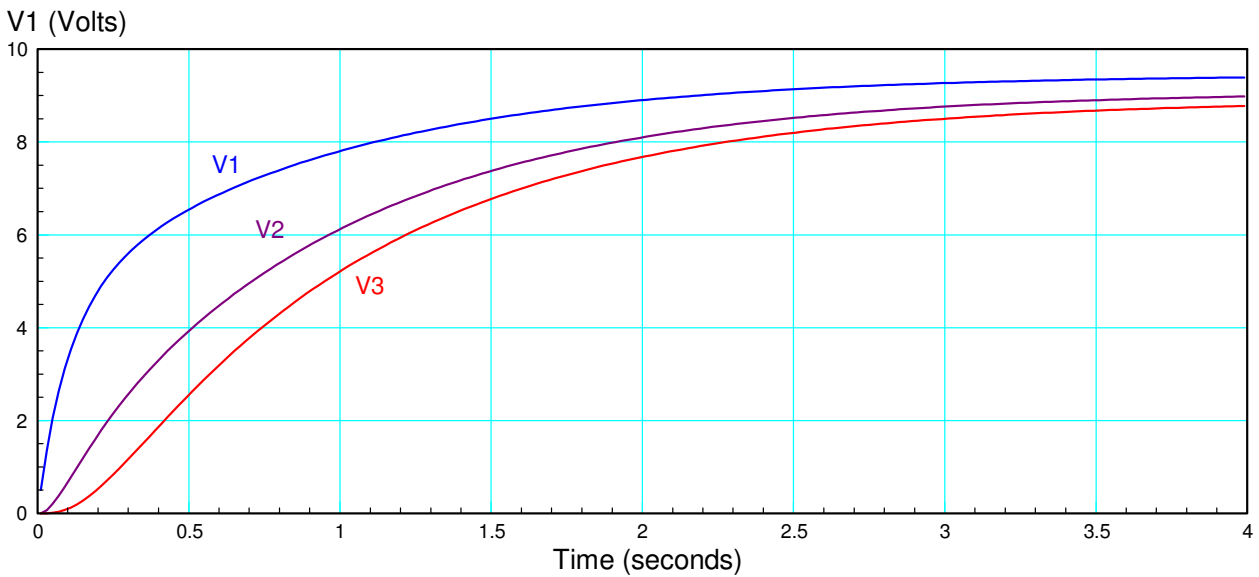

Votlages for a 3-stage RC filter

Case 3: 10-Stage RC Filter: Heat Equation

Now repeat for 10 stages

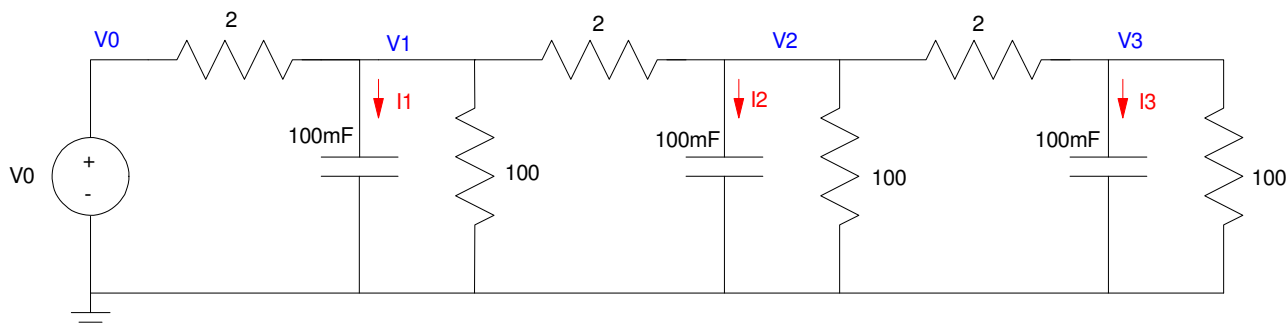

Note that stage 1 .. 9 all have the same differential equation except for the last stage

$$\frac{dV_2}{dt} = 5V_1 - 10.1V_2 + 5V_3$$

The only different one will be the last stage (which only has a single 2-Ohm resistor attached to it)

$$\frac{dV_{10}}{dt} = 5V_9 - 5.1V_{10}$$

In Matlab:

```
% 10-stage RC Filter

V0 = 10;
V = zeros(10,1);
dV = 0*V;
dt = 0.01;
t = 0;
Y = [];

while(t < 10)
    dV(1) = 5*V0 - 10.1*V(1) + 5*V(2);
    for i=2:9
        dV(i) = 5*V(i-1) - 10.1*V(i) + 5*V(i+1);
    end
    dV(10) = 5*V(9) - 5.1*V(10);


    V = V + dV * dt;
    t = t + dt;

    N = [0:10];
    plot(N, [V0; V], 'b.-');
    ylim([0,10]);
    pause(0.01);

    Y = [Y ; [V'] ];
end


pause(5);
t = [1:length(Y)]' * dt;
plot(t, Y);
```

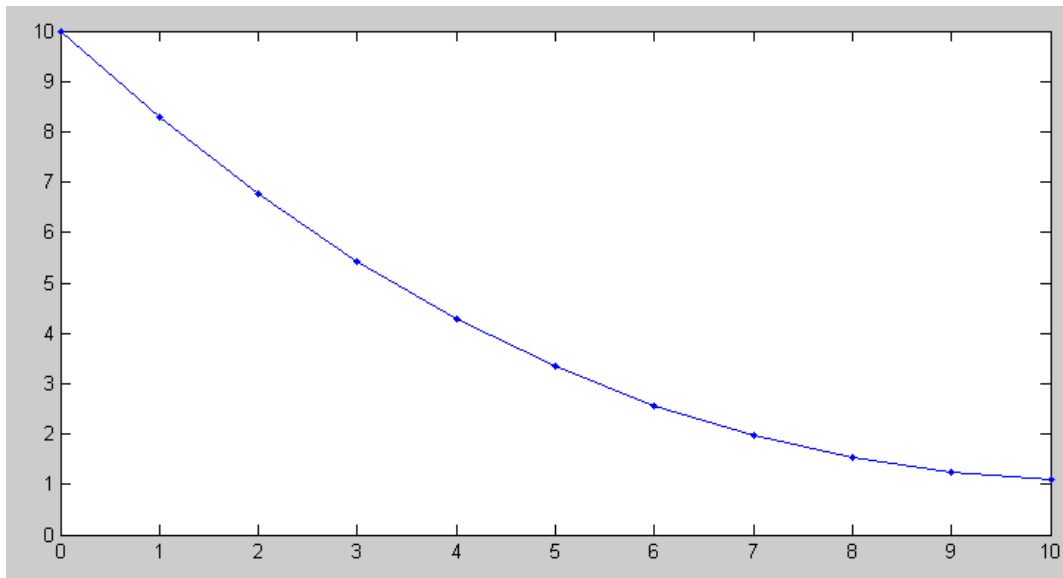For the first 10 seconds, this program shows the voltages along the circuit



Voltages V1, V2, ... V10 at each time point

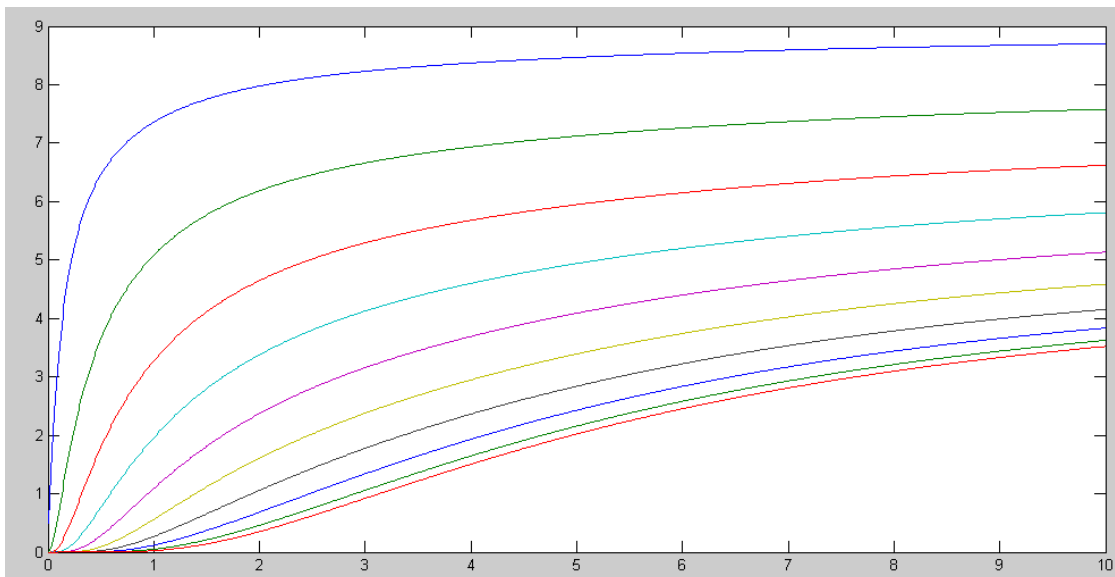Then, the final voltages vs. time are displayed



Votlages V1.. V10 vs. Time

Note that this program simulates

- The charging of 10 capacitors in an RC circuit,
- The temperature along a metal rod as it heats up when the base is connected to 10 degrees

Coupled first-order differential equations like this also describe heat flow - hence differential equations of this form are called *the heat equation*

Eigenvalues and Eigenvectors

The dynamics for the 10-stage RC filter are:

$$\frac{dV_1}{dt} = \dot{V}_1 = 5V_0 - 10.1V_1 + 5V_2$$

$$\frac{dV_2}{dt} = \dot{V}_2 = 5V_1 - 10.1V_2 + 5V_3$$

$$\vdots$$

$$\frac{dV_9}{dt} = \dot{V}_9 = 5V_8 - 10.1V_9 + 5V_{10}$$

$$\frac{dV_{10}}{dt} = \dot{V}_{10} = 5V_9 - 5.1V_{10}$$

In matrix form, this can be written as

$$\dot{V} = AV + BV_0$$

or

$$\begin{bmatrix} \dot{V}_1 \\ \dot{V}_2 \\ \dot{V}_3 \\ \dot{V}_4 \\ \dot{V}_5 \\ \dot{V}_6 \\ \dot{V}_7 \\ \dot{V}_8 \\ \dot{V}_9 \\ \dot{V}_{10} \end{bmatrix} = \begin{bmatrix} -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 5 & -5.1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \\ V_{10} \end{bmatrix} + \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_0$$

The *eigenvalues* of matrix A tell you *how* the system behaves. Matrix A is a 10x10 matrix:

```
A = zeros(10,10);
for i=1:9
    A(i,i) = -10.1;
    A(i,i+1) = 5;
    A(i+1,i) = 5;
end
```

```
A(10,10) = -5.1;
```

```
A
```

A =

```

-10.1000    5.0000         0         0         0         0         0         0         0         0
  5.0000   -10.1000    5.0000         0         0         0         0         0         0         0
         0    5.0000   -10.1000    5.0000         0         0         0         0         0         0
         0         0    5.0000   -10.1000    5.0000         0         0         0         0         0
         0         0         0    5.0000   -10.1000    5.0000    5.0000         0         0         0
         0         0         0         0    5.0000   -10.1000    5.0000   -10.1000         0         0
         0         0         0         0         0    5.0000   -10.1000    5.0000    5.0000         0
         0         0         0         0         0         0    5.0000   -10.1000    5.0000   -10.1000
         0         0         0         0         0         0         0    5.0000   -10.1000    5.0000
         0         0         0         0         0         0         0         0    5.0000   -5.1000

```

A has 10 eigenvalues and 10 eigenvectors:

[M,V] = eig(A)

M = Eigenvectors:

```

-0.1286   -0.2459    0.3412    0.4063    0.4352    0.4255    0.3780    0.2969   -0.1894    0.0650
 0.2459    0.4063   -0.4255   -0.2969   -0.0650    0.1894    0.3780    0.4352   -0.3412    0.1286
-0.3412   -0.4255    0.1894   -0.1894   -0.4255   -0.3412   -0.0000    0.3412   -0.4255   -0.1894
 0.4063    0.2969    0.1894    0.4352    0.1286   -0.3412   -0.3780    0.0650   -0.4255   -0.2459
-0.4352   -0.0650   -0.4255   -0.1286    0.4063    0.1894   -0.3780   -0.2459   -0.3412   -0.2969
 0.4255   -0.1894    0.3412   -0.3412   -0.1894    0.4255    0.0000   -0.4255   -0.1894   -0.3412
-0.3780    0.3780   -0.0000    0.3780   -0.3780    0.0000    0.3780   -0.3780   -0.0000   -0.3780
 0.2969   -0.4352   -0.3412    0.0650    0.2459   -0.4255    0.3780   -0.1286    0.1894   -0.4063
-0.1894    0.3412    0.4255   -0.4255    0.3412   -0.1894    0.0000    0.1894    0.3412   -0.4255
 0.0650   -0.1286   -0.1894    0.2459   -0.2969    0.3412   -0.3780    0.4063    0.4255   -0.4352

```

V = Eigenvalues:

```

-19.6557  -18.3624  -16.3349  -13.7534  -10.8473  -7.8748  -5.1000  -2.7695  -1.0903  -0.2117

```

The eigenvalues tell you *how* the mode behaves

The eigenvector tells you *what* behaves that way.

For example, assume

- $V_0 = 0$, and
- $V(0)$ = the last column (show in red: the eigenvector associated with the slow eigenvalue)

Then, $V(t)$ will be

$$V(t) = V_0 e^{-0.2117t}$$

In Matlab, you can see this by

- Setting $V_0 = 0$, and
- Changing the initial conditions


```
V0 = M(:,10) * 10 / max(M(:,10))
```

```
% 10-stage RC Filter
V0 = 0;
V = [ 1.4946
      2.9558
      4.3510
      5.6490
      6.8208
      7.8402
      8.6845
      9.3348
      9.7766
      10.0000];
dV = 0*V;
dt = 0.01;
t = 0;
Y = [];

while(t < 10)
    % rest of code stays the same
```

The result is as follows:

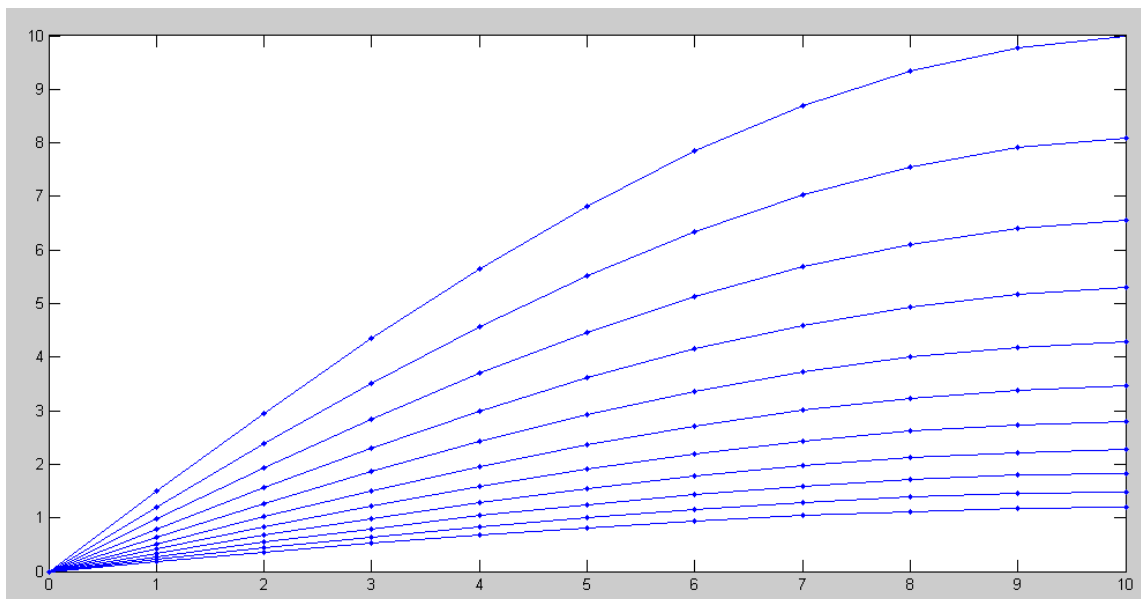- The shape of the curve stays the same: the shape is the slow eigenvector (what behaves this way)
- The amplitude decays slowly, as $\exp(-0.2117t)$ (the slow eigenvalue, how it behaves)



Voltages plotted every 1.00 second when the initial condition is the slow eigenvector

If you make the initial condition the fast eigenvector (shown in blue)

$$V_0 = M(:,1) * 10 / \max(\text{abs}(M(:,1)))$$

% 10-stage RC Filter

V0 = 0;

V = [-2.9558

5.6490

-7.8402

9.3348

-10.0000

9.7766

-8.6845

6.8208

-4.3510

1.4946];


dV = 0*V;

dt = 0.01;

etc...

the response is as shown below. Note

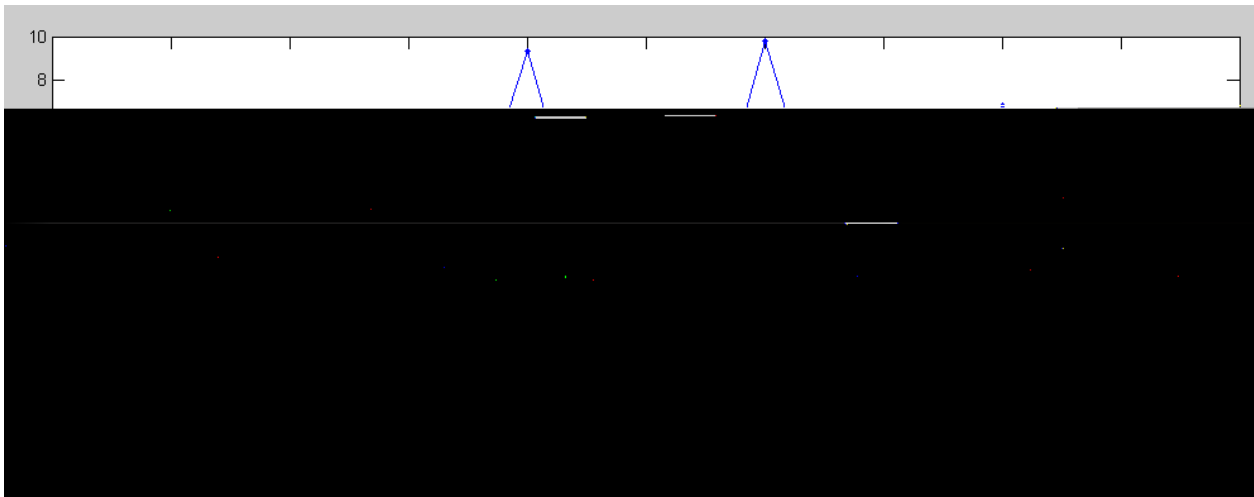- The shape of the curve is the same for all time: only one eigenvector is present
- The amplitude drops quickly: as $\exp(-19.65t)$ (the fast eigenvalue)



Voltages plotted every 0.05 seconds when the initial condition is the fast eigenvector

If you make the initial condition a set of random voltages,

- All eigenvectors will be excited
- The fast ones quickly decay,
- Leaving the slow eigenvector

```
% 10-stage RC Filter

V0 = 0;
V = 10*rand(10,1);
dV = 0*V;
dt = 0.001;
t = 0;
Y = [];

N = [0:10];
plot(N, [V0; V], 'r.-');
hold on
t1 = 0;
while(t < 2)
    dV(1) = 5*V0 - 10.1*V(1) + 5*V(2);
    for i=2:9
        dV(i) = 5*V(i-1) - 10.1*V(i) + 5*V(i+1);
    end
    dV(10) = 5*V(9) - 5.1*V(10);

    V = V + dV * dt;
    t = t + dt;
    t1 = t1 + dt;
    N = [0:10];

    if(t1 >= 0.15)
        plot(N, [V0; V], 'b.-');
        t1 = 0;
    end
    pause(0.01);

    Y = [Y ; [V'] ];
end
```

