

Phasor Impedances

Objective:

- Represent the impedance of a resistor, inductor, and capacitor as a complex number (termed its phasor impedance)
- Determine the impedance of RLC networks.

Resistors

From before, a current (or voltage)

$$i(t) = a \cos(\omega t) + b \sin(\omega t)$$

can be written in phasor form as

$$I = a - jb$$

The voltage produced by a current flowing through a resistor is


$$v(t) = i(t) \cdot R$$

or in phasor form

$$V = IR$$

The complex impedance of a resistor is R

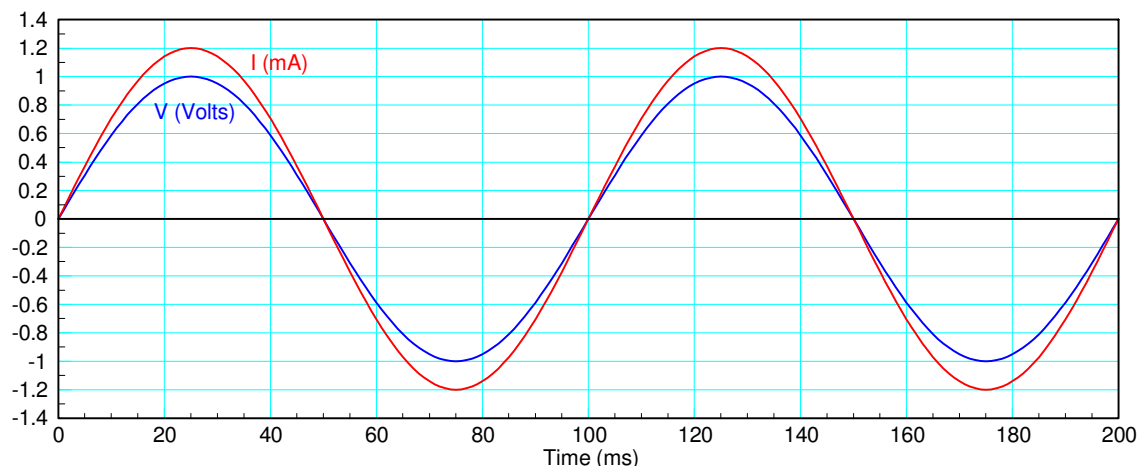For example: The current flowing through an 833 Ohm resistor is shown below: current is in phase with voltage for resistors.



Voltage and current are in phase for resistors

Capacitors

The current through a capacitor is

$$i(t) = C \frac{dv(t)}{dt}$$

If $v(t)$ is a sinusoid:

$$v(t) = a \cos(\omega t) + b \sin(\omega t)$$

$$V = a - jb$$

then the current will be

$$\begin{aligned} i(t) &= C \cdot \frac{d}{dt}(a \cos(\omega t) + b \sin(\omega t)) \\ &= C \cdot (-a\omega \sin(\omega t) + b\omega \cos(\omega t)) \end{aligned}$$

$$I = C \cdot (ja\omega + b\omega) = j\omega C \cdot (a - jb)$$

The impedance is then the ratio:


$$\begin{aligned} Z &= \frac{V}{I} \\ Z &= \left(\frac{a - jb}{j\omega C \cdot (a - jb)} \right) \end{aligned}$$

Doing some algebra

$$Z = \left(\frac{1}{j\omega C} \right)$$

The complex impedance of a capacitor is $\frac{1}{j\omega C}$

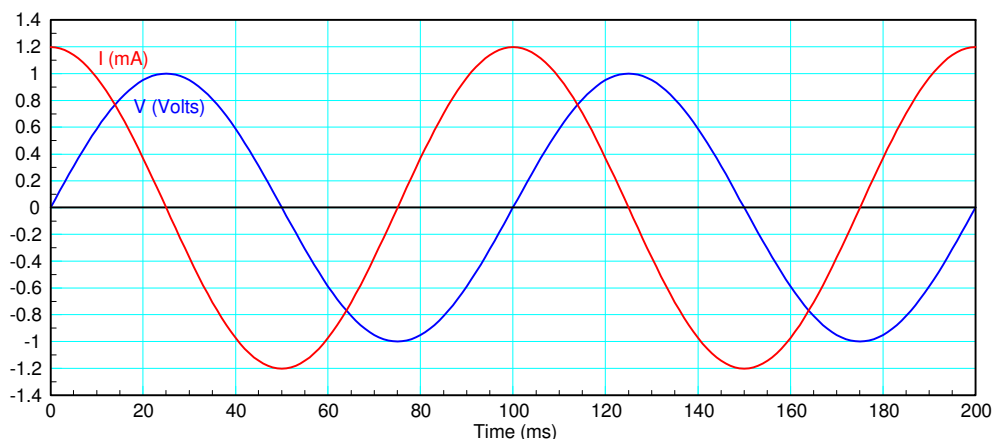For example, the current flowing through a capacitor with an impedance of $-j833$ Ohms is shown below: note that there is a 90 degree phase shift ($1/j$) and the current leads voltage for capacitors



Current leads voltage for capacitors

Inductors:

The VI relationship of an inductor is

$$v(t) = L \frac{di(t)}{dt}$$

Assume current is

$$i(t) = a \cos(\omega t) + b \sin(\omega t)$$

$$I = a - jb$$

The voltage is then

$$v(t) = L \cdot \frac{d}{dt}(a \cos(\omega t) + b \sin(\omega t))$$

$$v(t) = L \cdot (-a\omega \sin(\omega t) + b\omega \cos(\omega t))$$

$$V = L\omega \cdot (ja + b) = j\omega L \cdot (a - jb)$$

The impedance of an inductor is then


$$Z = \frac{V}{I}$$

$$Z = \left(\frac{j\omega L \cdot (a - jb)}{a - jb} \right)$$

$$Z = j\omega L$$

The complex impedance of an inductor is $j\omega L$

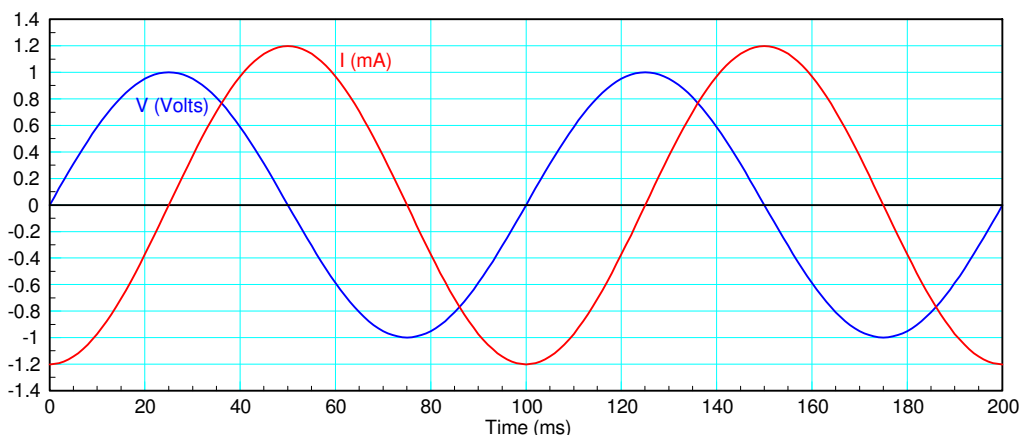For example, the voltage and currents through an inductor with an impedance of $j833$ Ohms is shown below. Note that there is a 90 degree phase shift (j) and that voltage leads current for inductors.



Voltage leads current for inductors

ELI the ICE man: One way to remember the current - voltage relationship for capacitors and inductors is the phrase

ELI the ICE man

ELI: Voltage (E) leads current for inductors (L)

ICE: Current (I) leads voltage (E) for capacitors

Example: Determine the impedance of a

- 100 Ohm resistor, a
- 100mH inductor, and a
- 1uF capacitor

at { 0, 100 Hz, and 10kHz }

Solution: Note that

$$\omega = 2\pi f$$


| | | | |
|--------------|--------------|------------|-------------|
| f (Hz) | 0 Hz | 100 Hz | 10 kHz |
| w (rad/sec) | 0 | 628.3 | 62,831 |
| R = 100 Ohms | Z = 100 | Z = 100 | Z = 100 |
| L = 100mH | Z = 0 | Z = j62.83 | Z = j6283.1 |
| C = 1uF | Z = infinity | Z = -j1591 | Z = -j15.91 |

- Resistors don't change with frequency:
- Inductors are short circuits at DC (0 Ohms) and have a +j impedance
- Capacitors are open circuits at DC (infinity Ohms) and have a -j impedance.

RLC Networks:

If you have a circuit with resistors, inductors, and capacitors, the impedance will be a complex number. The same rules that apply to resistors (parallel, series) apply when using complex impedances.

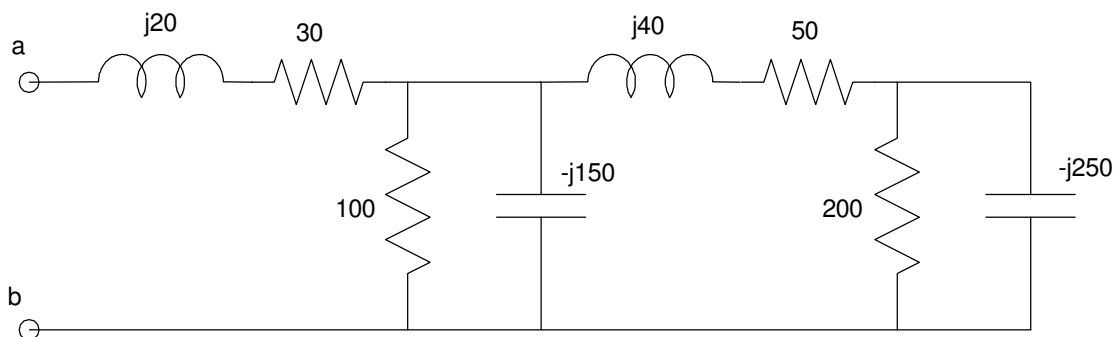Example 1: Determine the complex impedance Z_{ab}



Solution: Going right to left:

200 and $-j250$ are in parallel:

$$200 \parallel -j250 = \left(\frac{1}{200} + \frac{1}{-j250} \right)^{-1} = 121.95 - j97.56$$

This is in series with $(50 + j40)$ Ohms

$$(121.95 - j97.56) + (50 + j40) = 171.95 - j57.56$$

which is in parallel with $-j150$ and 100 Ohms

$$(171.95 - j57.56) \parallel (-j150) \parallel (100) = 50.30 - j27.80$$

which is in series with $20 + j30$ Ohms


$$(50.30 - j27.80) + (20 + j30) = 70.30 + j2.20$$

answer:

$$Z_{ab} = 70.30 + j2.20 \text{ Ohms}$$

note: it really helps to have a calculator that does complex numbers. I recommend an HP35s or the Free42 app on a cell phone

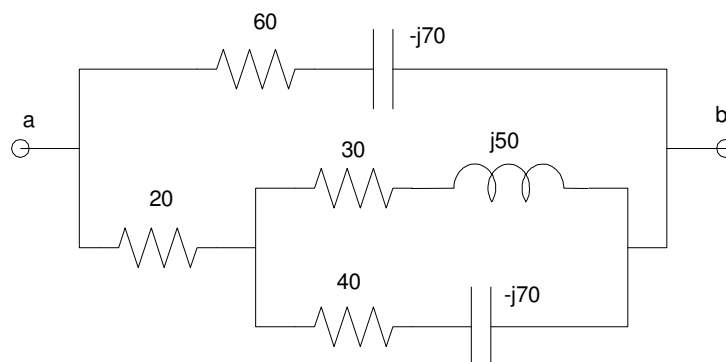Example 2: Determine the complex impedance Z_{ab}



Solution: Go inside out

$$(40 - j70) \parallel (30 + j50) = 62.45 + j16.42$$

$$(62.45 + j16.42) + 20 = 82.45 + j16.42$$

$$(82.45 + j16.42) \parallel (60 - j70) = 48.56 - j15.34$$

answer:

$$Z_{ab} = 48.56 - j15.34 \text{ Ohms}$$