
Circuit Elements and Kirchoff's Laws



EE 206 Circuits I

Jake Glower - Lecture #2



Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions






Circuit Elements: Voltage Sources

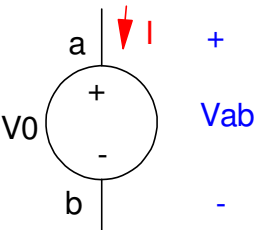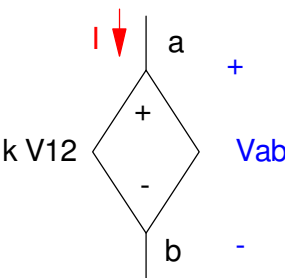Element	Symbol	VI Relationship
Voltage Source (battery)		$V_{ab} = V_0$ $I = \text{any}$
Voltage Controlled Voltage Source (amplifier)		$V_{ab} = kV_{12}$ $I = \text{any}$

Circuit Elements: Current Sources

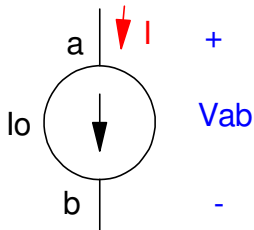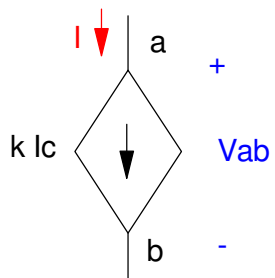Element	Symbol	VI Relationship
Current Source (LED driver)		$I = I_0$ $V_{ab} = \text{any}$
Current Controlled Current Source (transistor)		$I = kI_c$ $V_{ab} = \text{any}$


Passive Circuit Elements

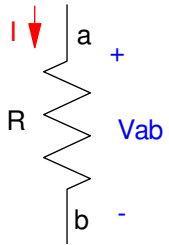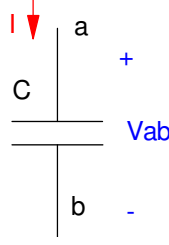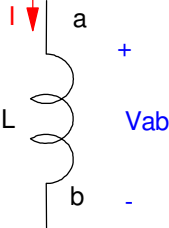Element	Symbol	VI Relationship
Resistor (basic circuit element)		$V_{ab} = IR$
Capacitor (basic circuit element)		$I = C \frac{dV_{ab}}{dt}$
Inductor (basic circuit element)		$V_{ab} = L \frac{dI}{dt}$


Independent Sources

Voltage Source: Like a battery: the voltage is fixed

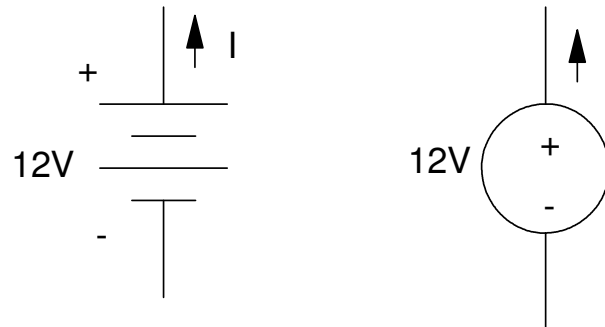- Current depends upon the load (can be anything, positive or negative)





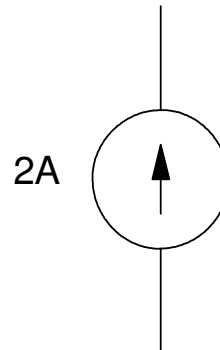Current Source: LED driver: the current is fixed



Dependent Sources

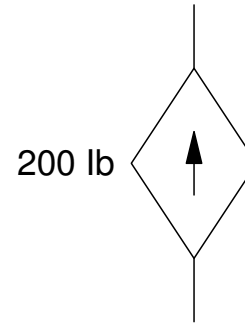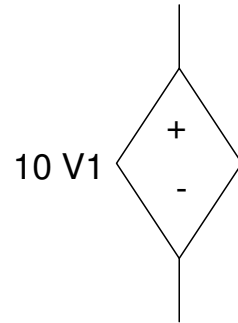Controlled Current and Voltage Sources: A diamond indicates a controlled voltage source or a controlled current source.



Controlled sources arise from various components covered in ECE 320 Electronics

- Operational Amplifiers (voltage controlled voltage source)
- Transistors (current controlled current source)
- MOSFET (voltage controlled current source)

For this class, just treat them as a device.

Ohm's Law

- $V = IR$
- Current goes into the + terminal

Other Forms:

$$I = \frac{V}{R}$$



$$R = \frac{V}{I}$$

Power:

$$P = VI$$

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

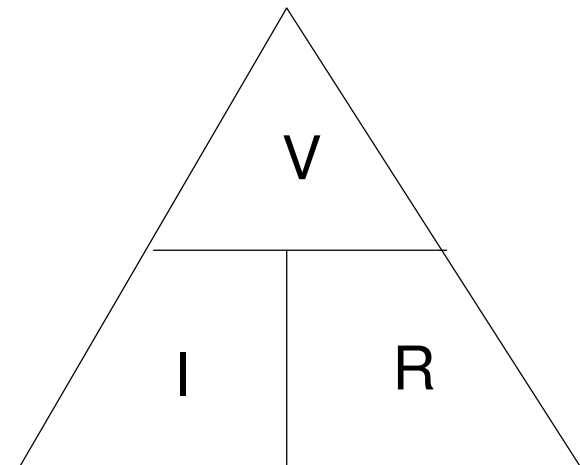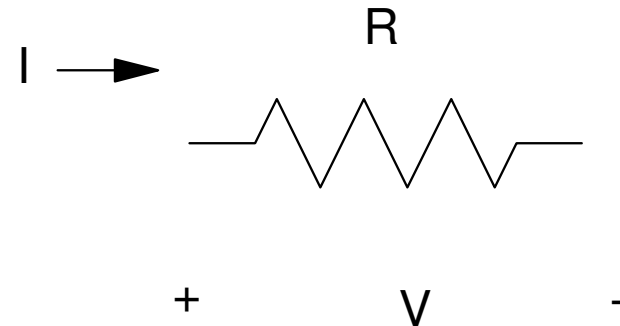

Kirchoff's Laws

Kirchoff's laws simply restate the conservation of voltage and current:

- If you sum the voltages around any closed path, the sum must be zero.
- If you sum the current flowing away from a point, the sum must be zero.




Conservation of Voltage:

Around any closed path, the voltages must add to zero.

- You can use this to find unknown voltages.

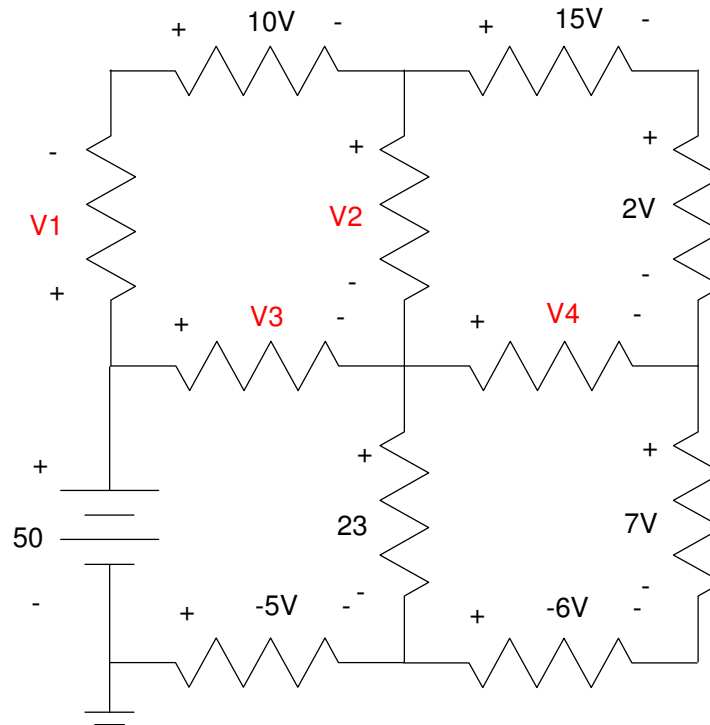Example: determine the voltages $V1..V4$ for the following circuit:



Solution:

- Around any closed-path, the voltages must sum to zero.
- Add if you hit the + sign first
- Subtract if you hit the - sign first

Path 1: (Blue)


$$-50 + V_3 + 23 - (-5) = 0$$

$$V_3 = 22V$$

Path 2: (Red)

$$-23 + V_4 + 7 - (-6) = 0$$

$$V_4 = 10V$$

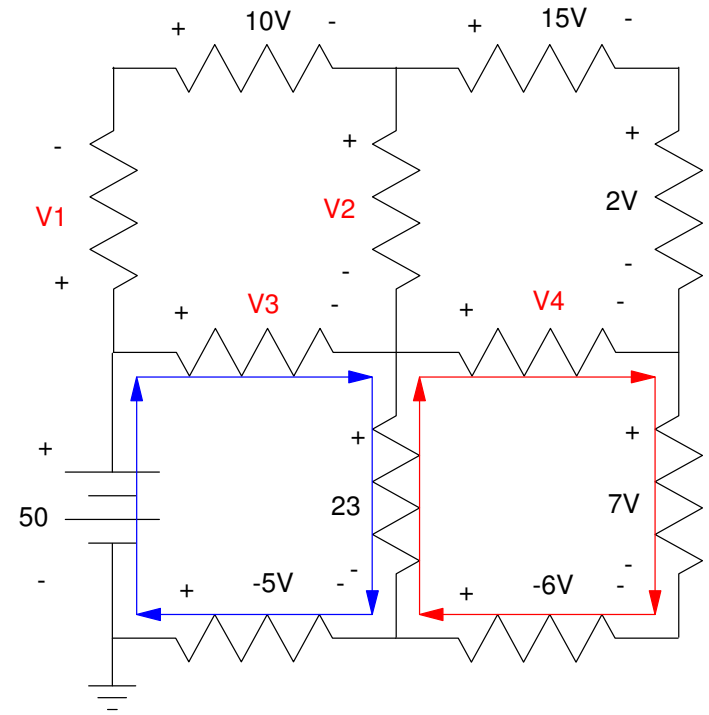

Path 3: (Red)

$$-50 + V_1 + 10 + 15 + 2 - 8 - (-6) - (-5) = 0$$


$$V_1 = 5V$$

Path 4 (Cyan)

$$-23 - V_2 + 15 + 2 + 7 - (-6) = 0$$

$$V_2 = 10V$$


Other paths are also valid

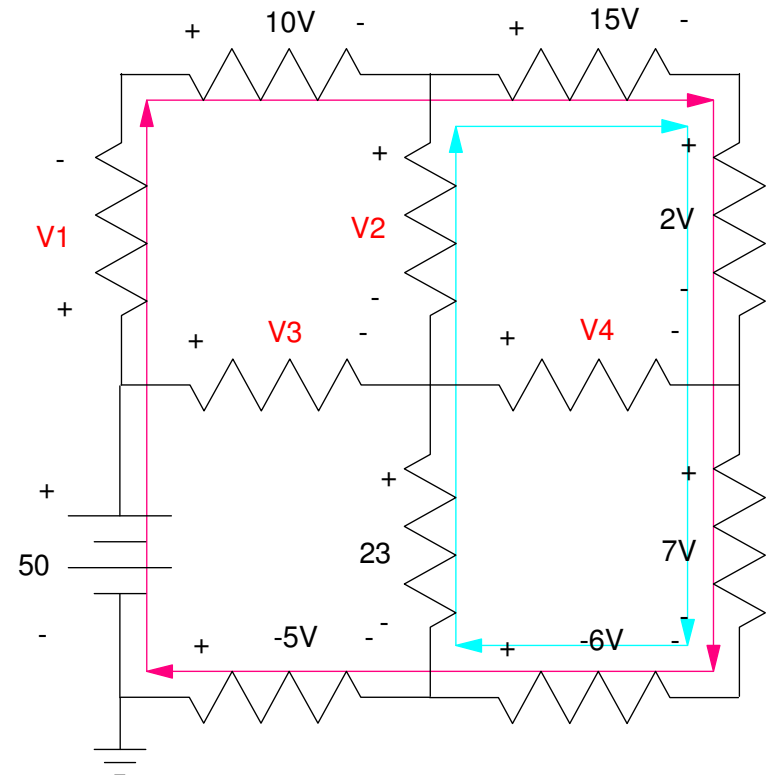

Conservation of Current

- *Electrons cannot be created or destroyed: they can only be pushed around (Uncle Wally)*
- The current into a node must equal the current out of that node
- The sum of the current from a node must add to zero

Example: Determine $I_1..I_7$

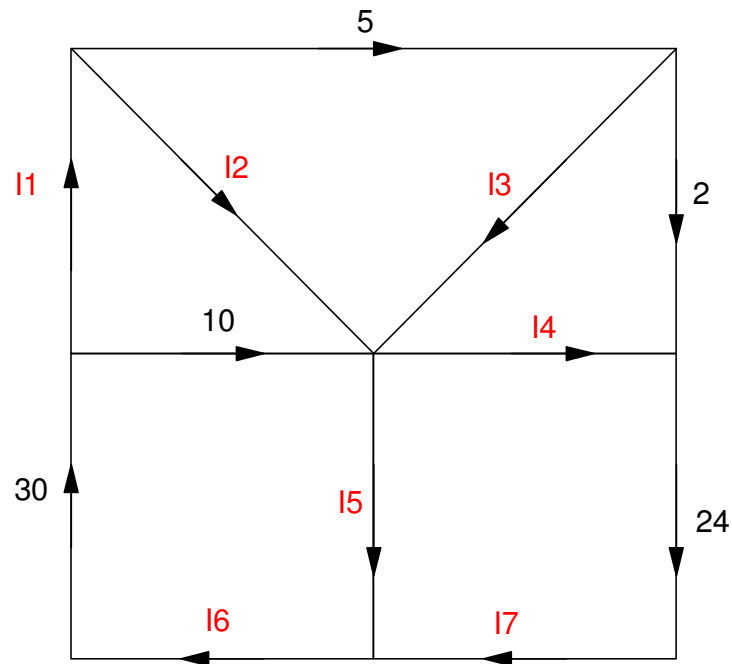

A: $30 = 10 + I_1$

$I_1 = 20$

B: $I_6 = 30$


C: $24 = I_7$

D: $5 = I_3 + 2$

$I_3 = 3$

E: $2 + I_4 = 24$

$I_4 = 22$

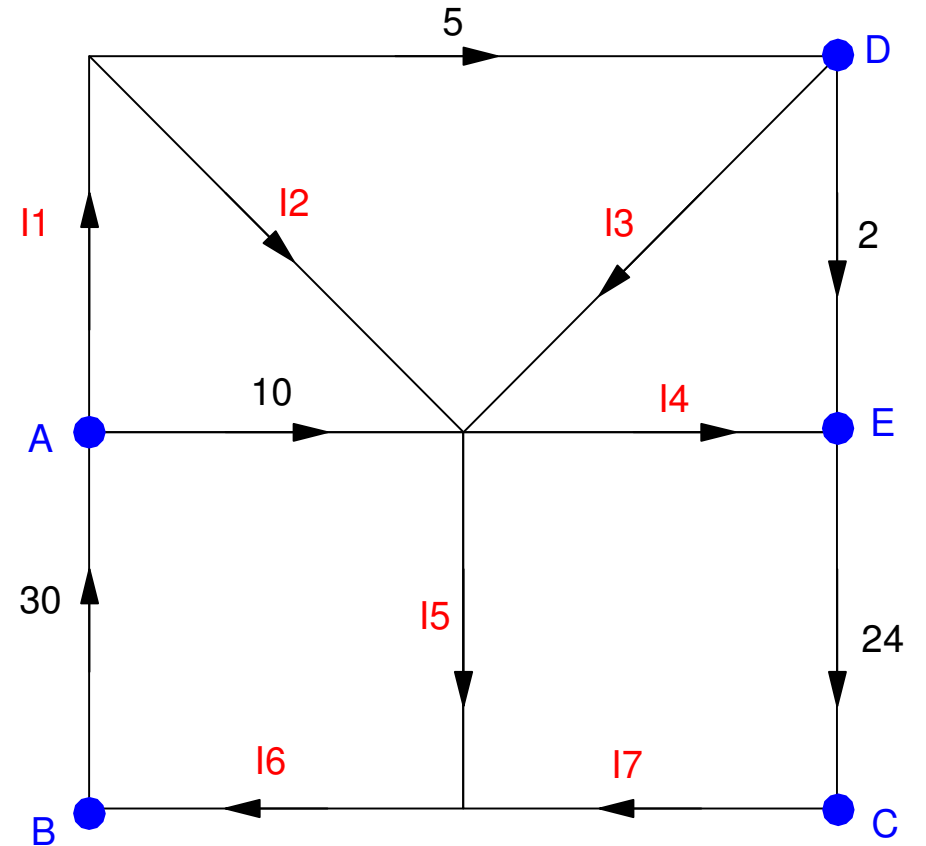

This lets you solve for I2 and I5:

F: $20 = I_2 + 5$

$I_2 = 15$

G: $I_5 + 24 = 30$

$I_5 = 6$

