

---

# **SuperNodes:**

## **EE 206 Circuits I**

### **Jake Glower - Lecture #6**

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions


---

## SuperNodes:

- A closed path that encloses 2+ nodes
- The current coming out of any closed path must sum to zero
 
## Why?

- Sometimes you can't sum the current to zero at each node
  - A voltage source is connected to the node
  - It supplies whatever current is needed to maintain the voltage
- In that case, use a SuperNode



## SuperNode Example:

Find  $V_1$ ,  $V_2$ , and  $V_3$


- Need 3 equations for 3 unknowns

Voltage Source

$$V_1 - V_3 = 5 \quad (1)$$

Node  $V_2$
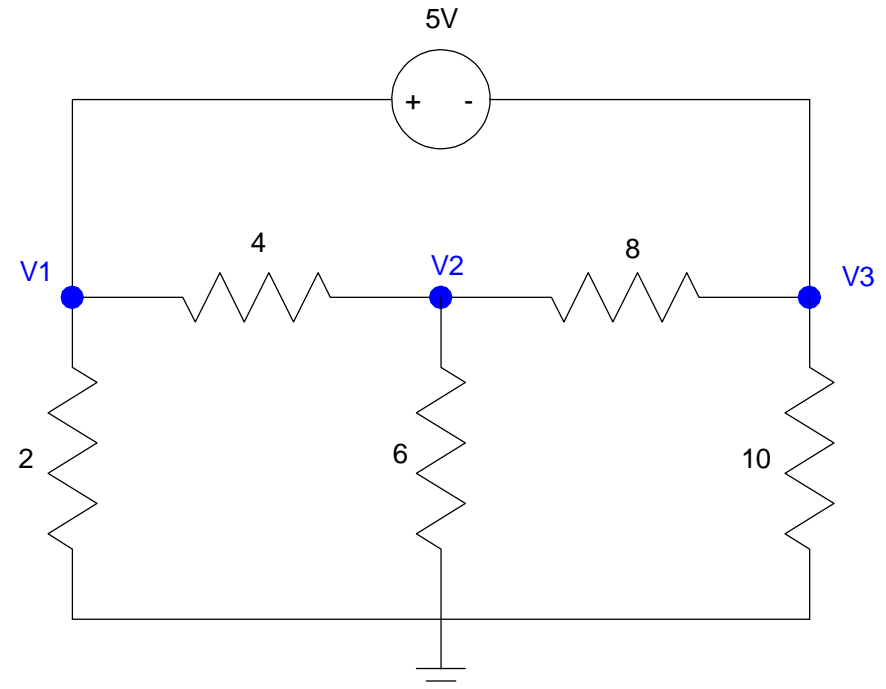
$$\frac{V_2 - V_1}{4} + \frac{V_2}{6} + \frac{V_2 - V_3}{8} = 0 \quad (2)$$




Now we're stuck.

- We can't sum the current to zero at node  $V_1$  since we don't know the current into the 5V source
- We can't sum the current to zero at node  $V_3$  since we don't know the current into the - terminal of the 5V source

SuperNode:

- Draw a path that encloses the 5V source and only has resistors attached to it
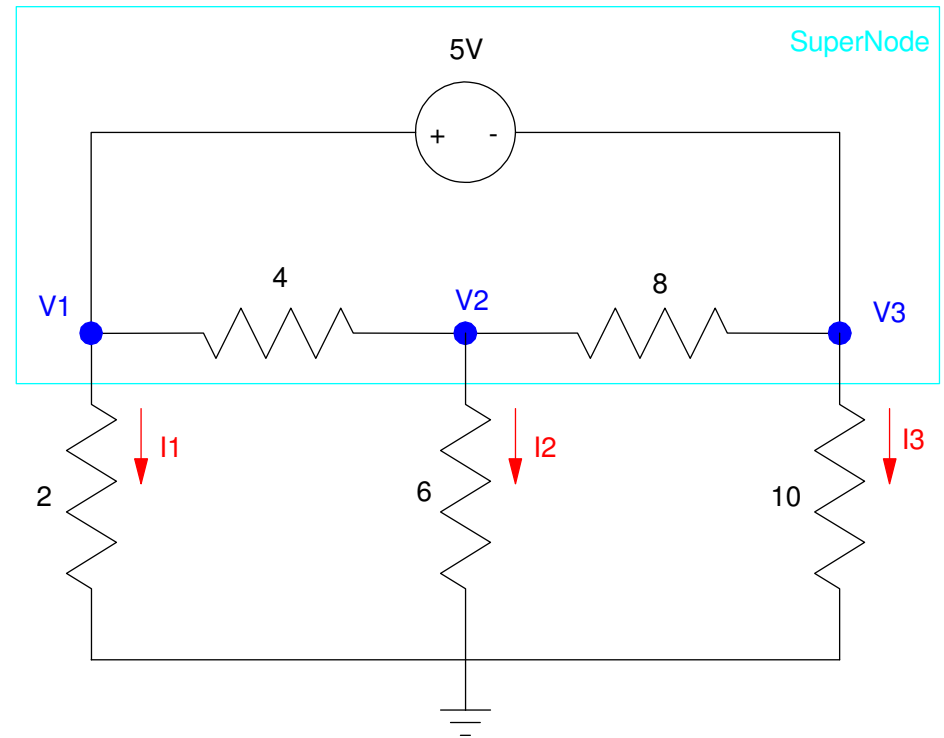
$$\frac{V_1}{2} + \frac{V_2}{6} + \frac{V_3}{10} = 0 \quad (3)$$



---

## SuperNode

- Another perfectly valid 3rd equation

$$\left(\frac{V_1}{2}\right) + \left(\frac{V_1 - V_2}{4}\right) + \left(\frac{V_3}{10}\right) + \left(\frac{V_3 - V_2}{8}\right) = 0$$

Solve:

- Group terms:

$$V_1 - V_3 = 5$$

$$-\left(\frac{1}{4}\right)V_1 + \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{8}\right)V_2 - \left(\frac{1}{8}\right)V_3 = 0$$

$$\left(\frac{V_1}{2}\right) + \left(\frac{V_2}{6}\right) + \left(\frac{V_3}{10}\right) = 0$$

---

---

Place in matrix form:

$$\begin{array}{ccc|c|c} 1 & 0 & -1 & V_1 & 5 \\ -0.25 & 0.5417 & -0.125 & V_2 & = 0 \\ 0.5 & 0.1666 & 0.1 & V_3 & 0 \end{array}$$

Solve in Matlab

```
A = [1,0,-1 ; -0.25,0.5417,-0.125 ; 0.5,0.16666,0.1]
```

```
1.0000    0 -1.0000
-0.2500    0.5417 -0.1250
0.5000    0.1667    0.1000
```

```
B = [5;0;0]
```

```
5
0
0
```

```
V = inv(A)*B
```

---

---

V1	0.9677
V2	-0.4838
V3	-4.0323

Same as CircuitLab

---

---

# Voltage Nodes with Dependent Sources

- Same as voltage nodes
- Plus one equation for each dependent source

Example: Find  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_x$

- 4 equations for 4 unknowns

Easy ones:

$$V_x = V_3 - V_2$$

$$V_1 = 12$$

$$V_3 = 4V_x$$

Node equation at  $V_2$

$$\left(\frac{V_2 - V_1}{2}\right) + \left(\frac{V_2}{4}\right) + \left(\frac{V_2 - V_3}{6}\right) = 0$$

---



---

Solve: Group terms

$$V_x - V_3 + V_2 = 0$$

$$V_1 = 12$$

$$V_3 - 4V_x = 0$$

$$\left(\frac{-1}{2}\right)V_1 + \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{6}\right)V_2 + \left(\frac{-1}{6}\right)V_3 = 0$$

Placing in matrix form

$$\begin{bmatrix} 0 & 1 & -1 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -4 \\ -0.5 & 0.9167 & -0.1666 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 0 \end{bmatrix}$$



---

## Solve in Matlab

```
A = [0,1,-1,1 ; 1,0,0,0 ; 0,0,1,-4 ; -0.5,0.9167,-0.1666,0]
```

```
      0      1.0000     -1.0000      1.0000
    1.0000         0         0         0
      0         0      1.0000     -4.0000
   -0.5000     0.9167    -0.1666         0
```

```
B = [0;12;0;0]
```


```
  0
 12
  0
  0
```

```
V = inv(A)*B
```

```
V1    12.0000
V2     8.6385
V3    11.5180
Vx     2.8795
```

---
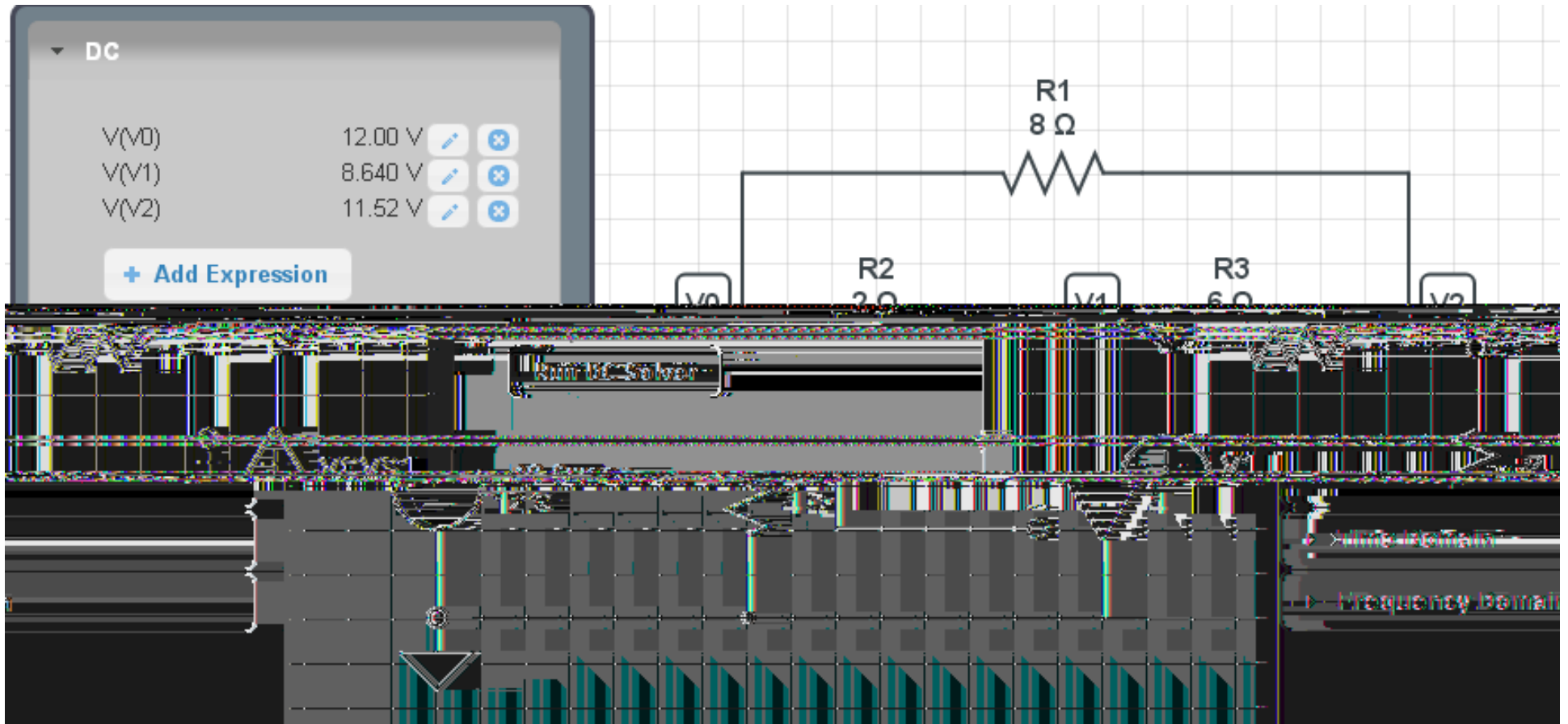
## Checking in Circuitlab - the voltages match



# SuperNodes and Dependent Sources

- If needed, define a closed-path (i.e. a SuperNode) to give the rest of the N equations needed

Example: Find {  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_x$  }

Easy Equations:

$$I_x = \left( \frac{V_1 - V_2}{2} \right)$$


$$V_1 = 12$$

$$V_2 - V_3 = 5I_x$$

Define a SuperNode

- Current out of the SuperNode = 0
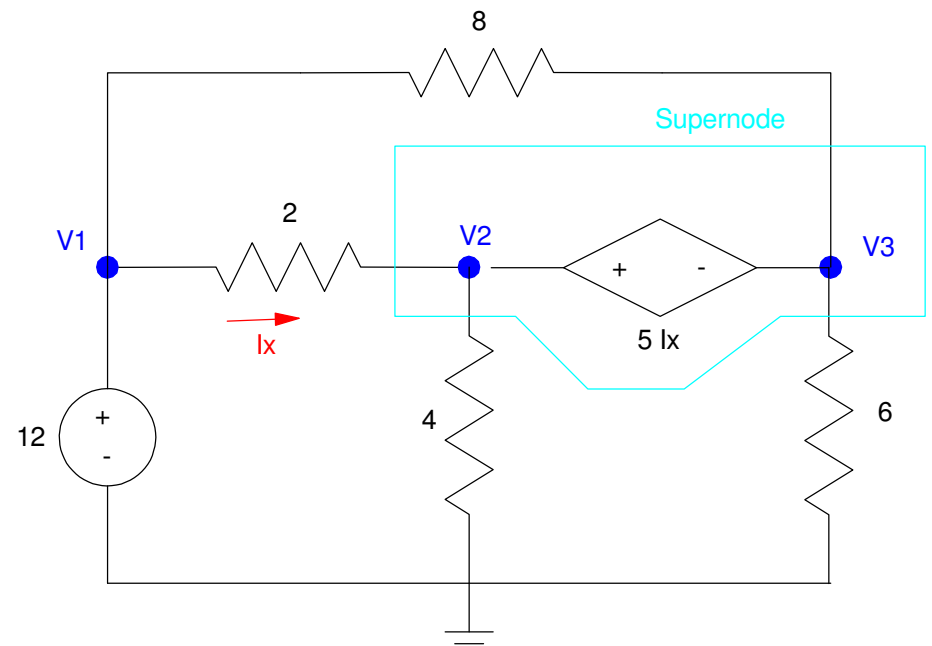
$$\left( \frac{V_2 - V_1}{2} \right) + \left( \frac{V_2}{4} \right) + \left( \frac{V_3}{6} \right) + \left( \frac{V_3 - V_1}{8} \right) = 0$$



---

## Group Terms

$$V_1 - V_2 - 2I_x = 0$$


$$V_1 = 12$$

$$V_2 - V_3 - 5I_x = 0$$

$$\left(\frac{-1}{2} + \frac{-1}{8}\right)V_1 + \left(\frac{1}{2} + \frac{1}{4}\right)V_2 + \left(\frac{1}{6} + \frac{1}{8}\right)V_3 = 0$$

Place in matrix form
 
$$\begin{bmatrix} 1 & -1 & 0 & -2 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & -1 & -5 \\ -0.625 & 0.75 & 0.2917 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_x \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 0 \end{bmatrix}$$



---

## Solve in Matlab

```
A = [1,-1,0,-2 ; 1,0,0,0 ; 0,1,-1,-5 ; -0.625,0.75,0.2917,0]
```

```
    1.0000    -1.0000         0    -2.0000
    1.0000         0         0         0
         0     1.0000    -1.0000    -5.0000
   -0.6250     0.7500     0.2917         0
```

```
B = [0;12;0;0]
```

```
    0
   12
    0
    0
```

```
V = inv(A)*B
```

```
V1    12.0000
V2     9.1764
V3     2.1175
Ix     1.4118
```

---

# Verify using Circuitlab

▼ DC

V(V0)	12.00 V		
V(V1)	9.176 V		
V(V2)	2.118 V		
I(R2.nA)	1.412 A		

+ Add Expression

Export Results...

Run DC Solver

▶ DC Sweep

▶ Time Domain

▶ Frequency Domain

