
Thevenin Equivalent and Load Lines

EE 206 Circuits I

Jake Glower - Lecture #10

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions

Thevenin Equivalent

So far, we have two tools:

- Voltage Nodes: Find the voltages so that the currents balance (sum to zero)
- Current Loops: Find the currents so that the voltages balance (sum to zero)


Thevenin Equivalent is tool #3

- Harder to find
 - More difficult to comprehend
 - Not necessary: you can solve any circuit using current loops or voltage nodes
 - But, Thevenin equivalents can make some circuits much easier to analyze
-

Load Lines:

Idea:

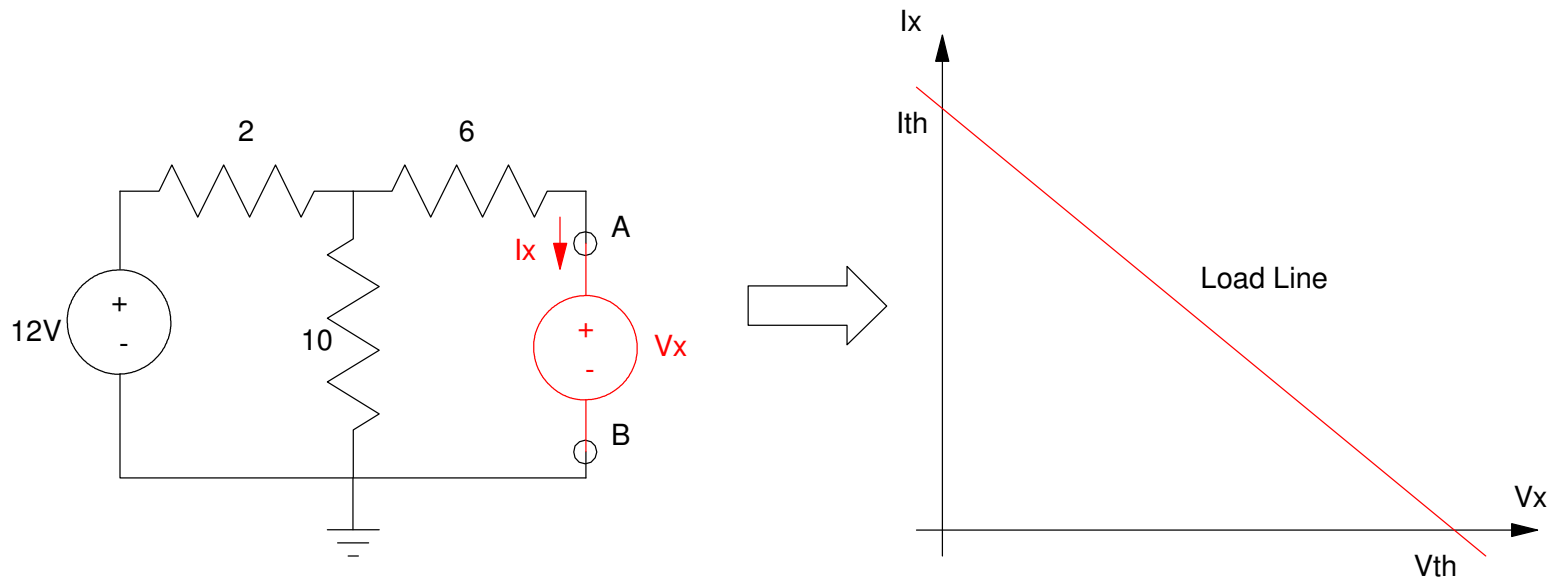- The voltage-current relationship for a linear circuit follows a straight line.
- Any circuit which produces the same load line behaves the same
- The simplest circuit which does this is
 - A voltage source & resistor (Thevenin equivalent)
 - A current source & a resistor (Norton equivalent)




Thevenin and Norton Equivalent


Simplest circuit to produce a load line

- A voltage source and resistance in series (termed a Thevenin equivalent)
- A current source and resistance in parallel (termed a Norton equivalent)

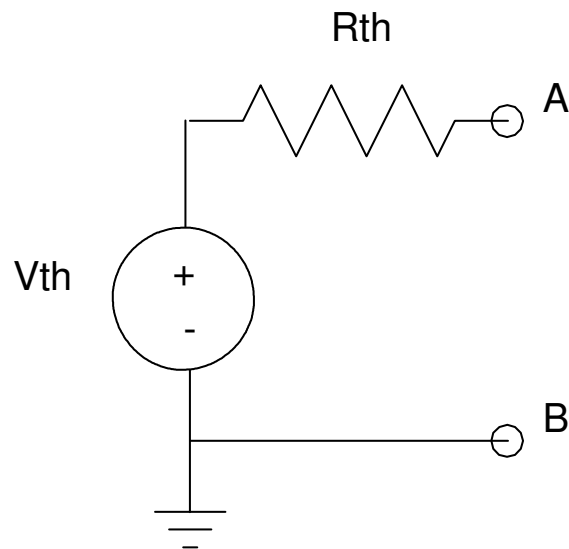The trick is to find the values of V_{th} , R_{th} , or I_{th}



Thevenin Equivalent

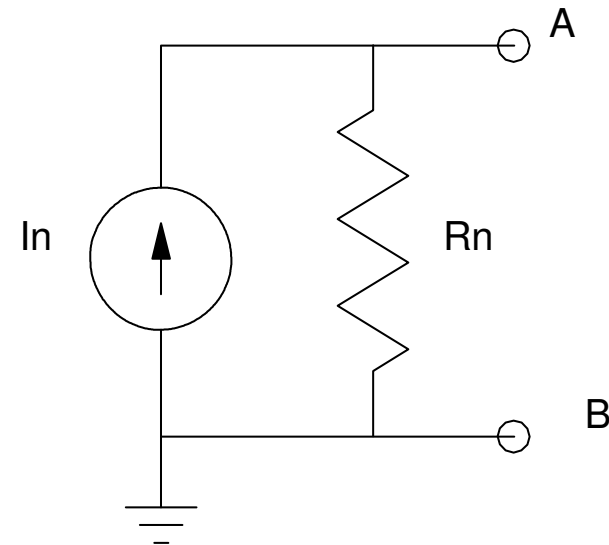

Norton Equivalent


Finding V_{th} , R_{th} , I_n , R_n

Circuits are equivalent


- Whatever works for your original circuit works for the Thevenin / Norton equivalent

Procedure:

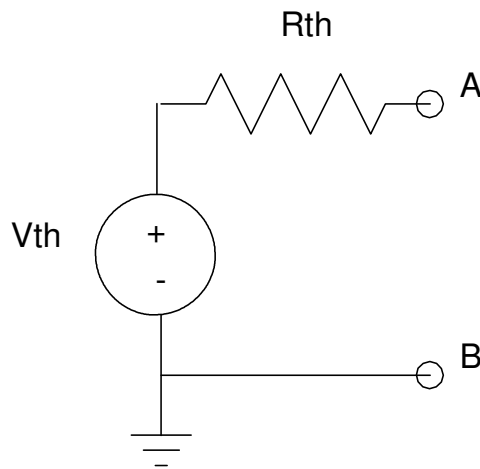- V_{th} : Measure the open-circuit voltage of your circuit.
- $R_{th} = R_n$: Turn off all sources ($V = 0$, $I = 0$). Measure the resulting resistance.
- I_n : Measure the short-circuit current



Thevenin Equivalent

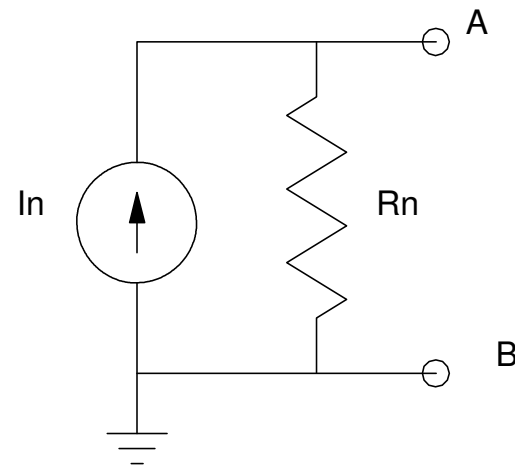

Norton Equivalent

Example
circuit:


Determine the Thevenin and Norton equivalent for the following

1. Measure the open-circuit voltage.

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} - 3 = 0$$

$$V_{th} = V_1 = 16.67V$$

This is V_{th}

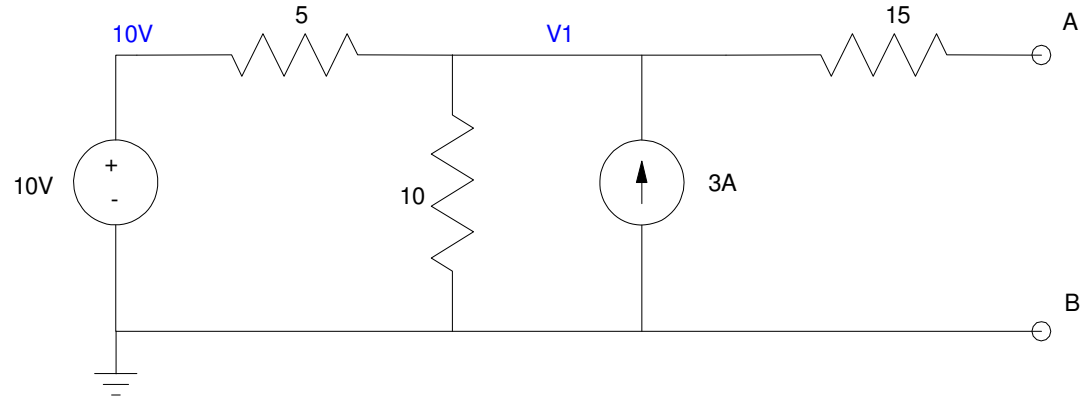


In: Short AB and measure the current. Again, this is obvious so write the node equation at V1

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} - 3 + \frac{V_1}{15} = 0$$

$$V_1 = 13.64V$$
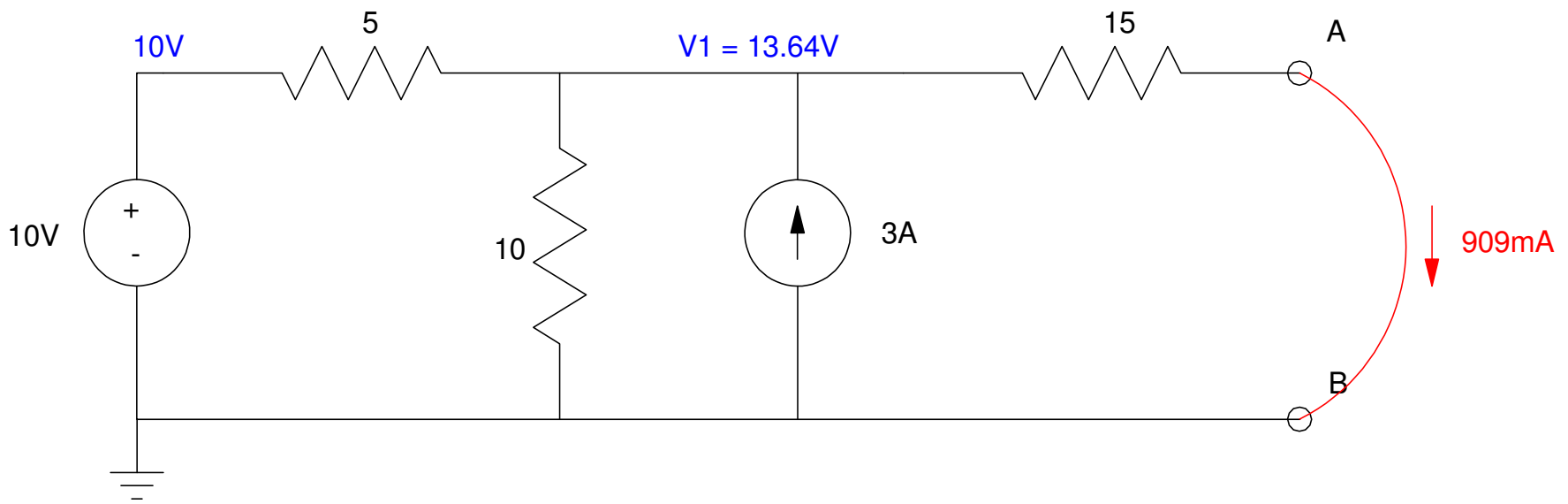
$$I_{\text{short}} = I_N = \frac{13.64V}{15\Omega} = 909.1\text{mA}$$




Rth: Turn off the sources ($V = 0$, $I = 0$). Measure the resistance between A and B

$$R_{AB} = 15 + 5 \parallel 10$$



$$R_{AB} = 18.33\Omega$$

Note that you only need to compute two of these; the third is redundant.
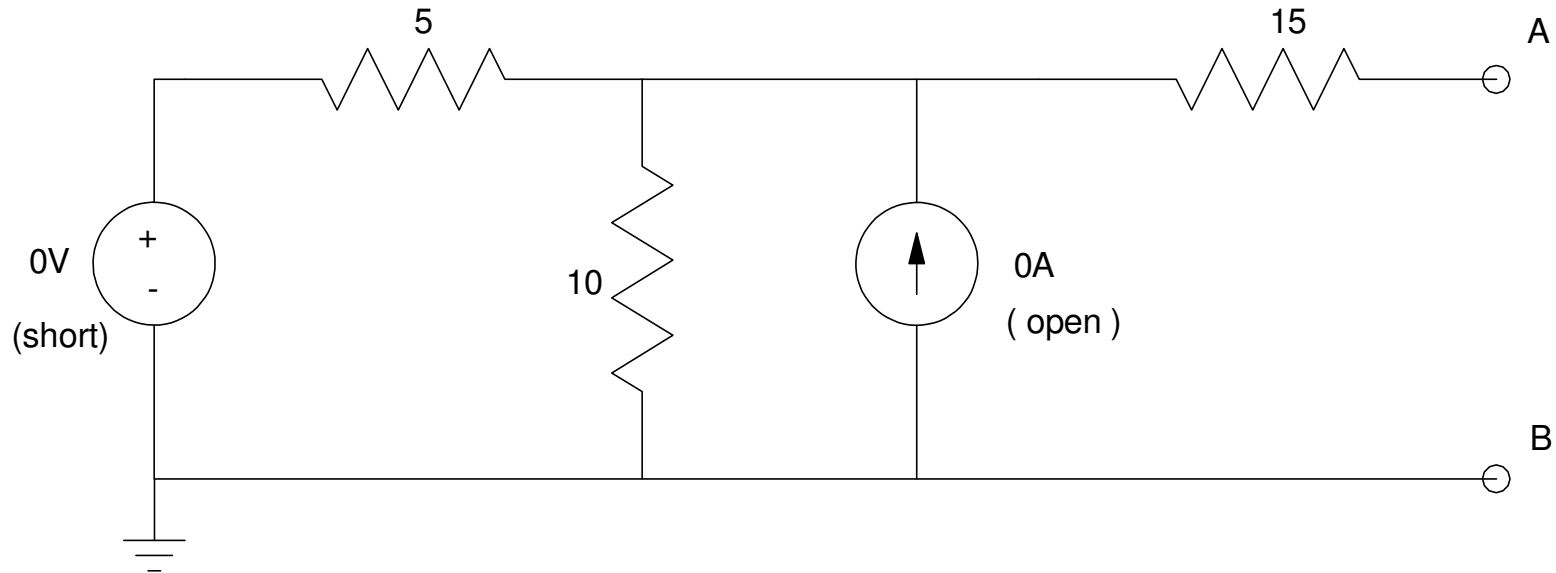
$$R_{AB} = \frac{V_{tn}}{I_n} = \frac{16.67V}{909mA} = 18.33\Omega$$



Result:

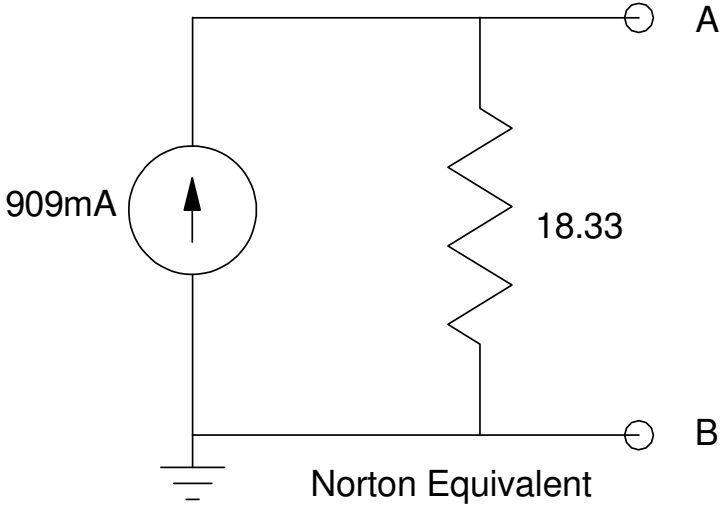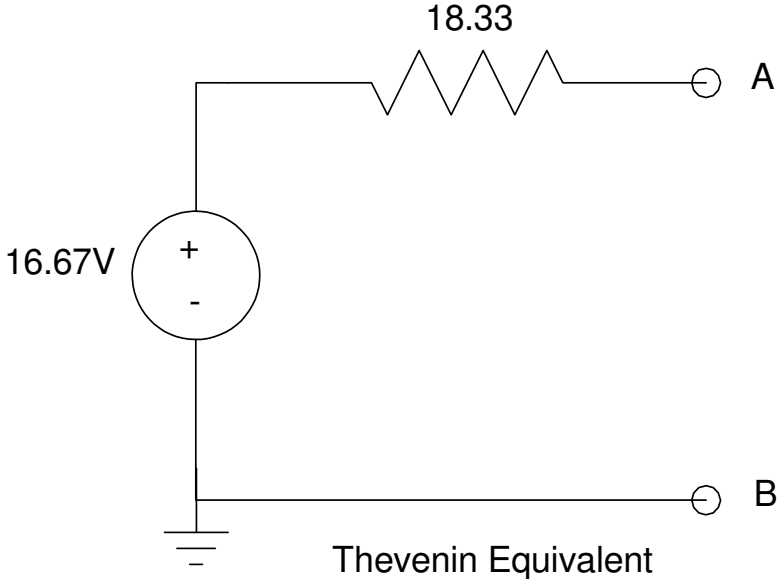

Resulting Thevenin and Norton equivalents of Example 1

Circuit Simplification using Thevenin and Norton Equivalent


Sometimes you can simplify a circuit by flipping between Thevenin and Norton equivalents

$$R_{\text{Thevenin}} = R_{\text{Norton}}$$

$$V_{\text{Thevenin}} = I_{\text{Norton}} \cdot R$$

$$I_{\text{Norton}} = \frac{V_{\text{Thevenin}}}{R}$$


Example: Find the Thevenin equivalent

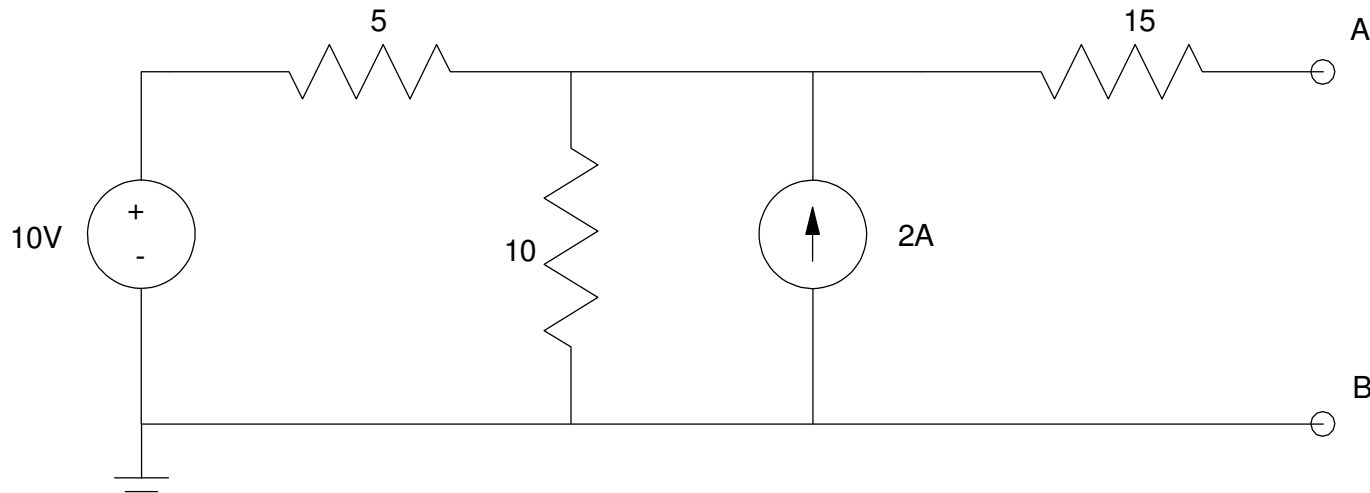

Step 1: Convert the 10V / 5 Ohm resistor to its Norton equivalent

$$I_N = \frac{10V}{5\Omega} = 2A$$

$$R_N = R_{Th} = 5\Omega$$

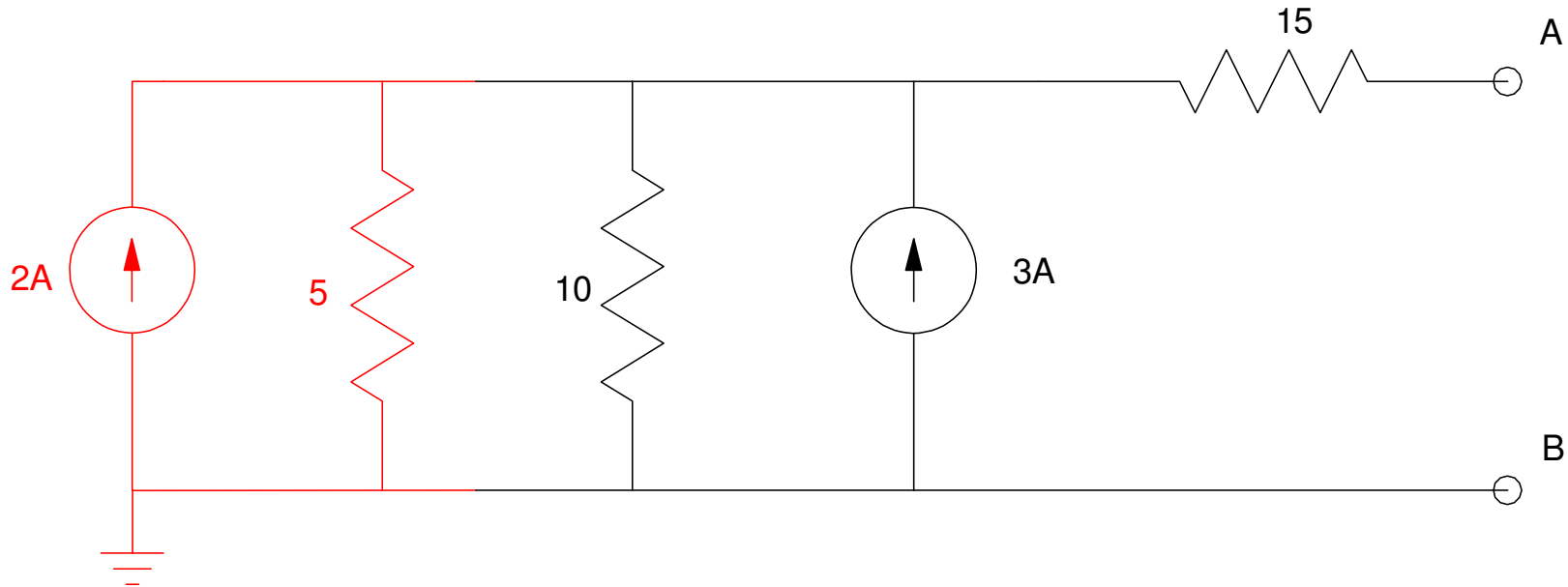


Convert the 10V : 5 Ohm source to its Norton equivalent (shown in red)

Add the resistors in parallel

$$R_{\text{net}} = 5 \parallel 10 = \frac{1}{\frac{1}{5} + \frac{1}{10}}^{-1} = 3.333\Omega$$

Add the current sources


$$I_{\text{net}} = 2 + 3 = 5$$

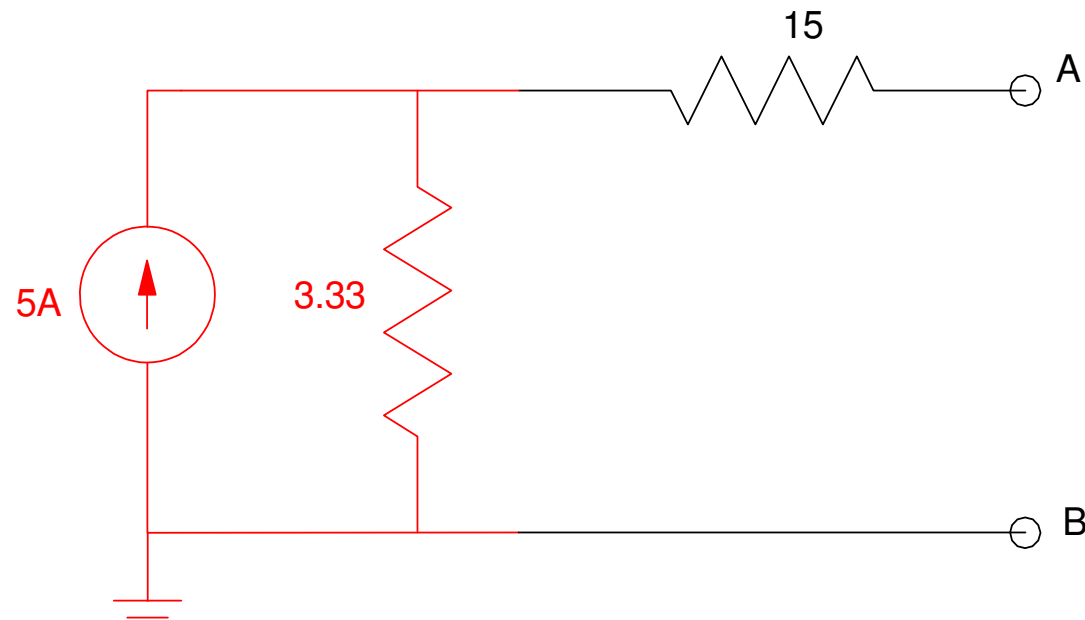

Add the resistors and current sources in parallel:


Convert back to a Thevenin equivalent
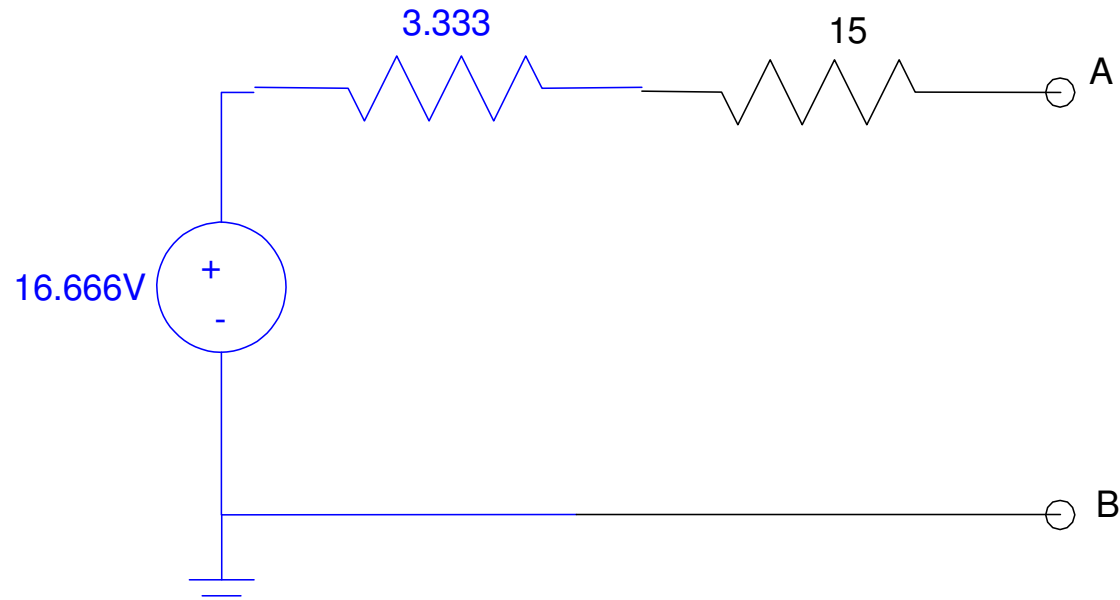
$$V_{th} = 5A \cdot 3.333\Omega = 16.666V$$



Convert to a Thevenin equivalent (shown in blue)

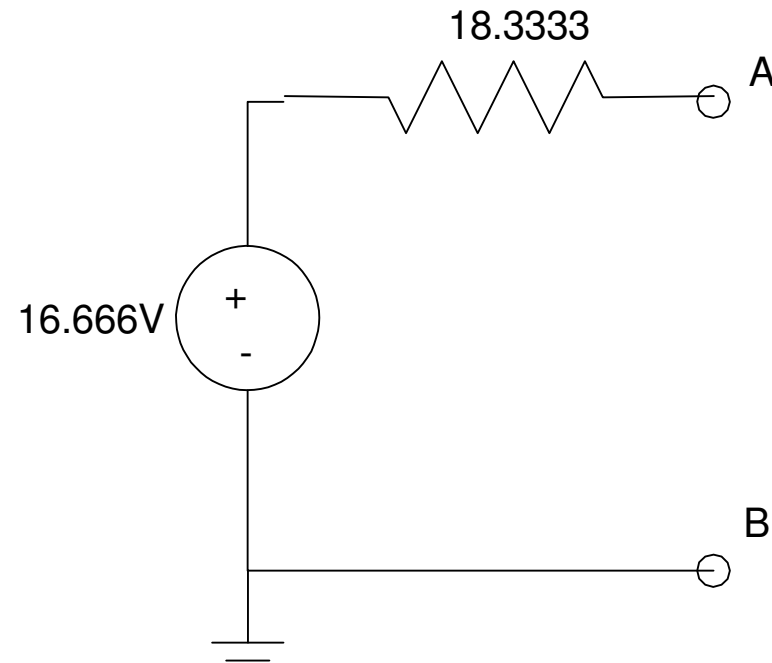Add the resistors in series and you have the Thevenin equivalent looking in from terminals AB




Thevenin Equivalet of Example 2

Example Thevenin equivalents can provide insight.

- The following voltage divider works ($V_{out} = 5V$) if there is no load
- When you add a load (100mA @ 5V) the output voltage goes to zero

Why?

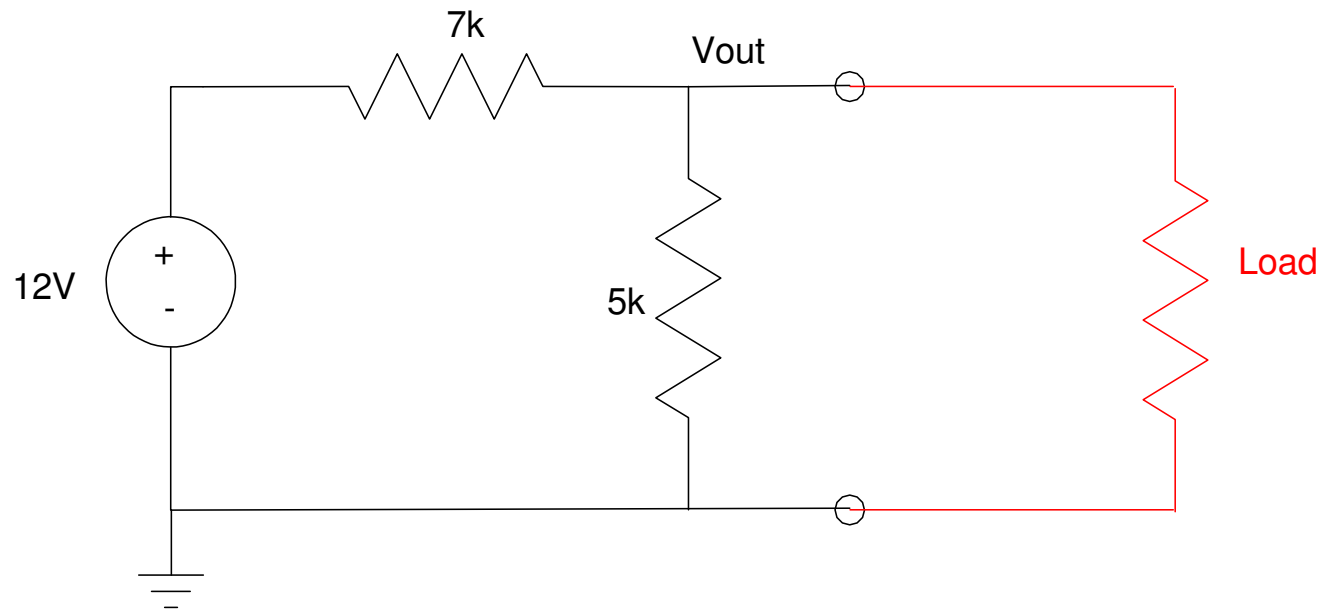

Voltage divider used to convert 12V to 5V


Convert to a Thevenin equivalent

$$V_{th} = V_{open} = \frac{5k}{5k+7k} 12V = 5V$$

$$R_{th} = 7k || 5k = 2916\Omega$$

If your load draws 100mA @ 5V, it looks like a 50 Ω resistor
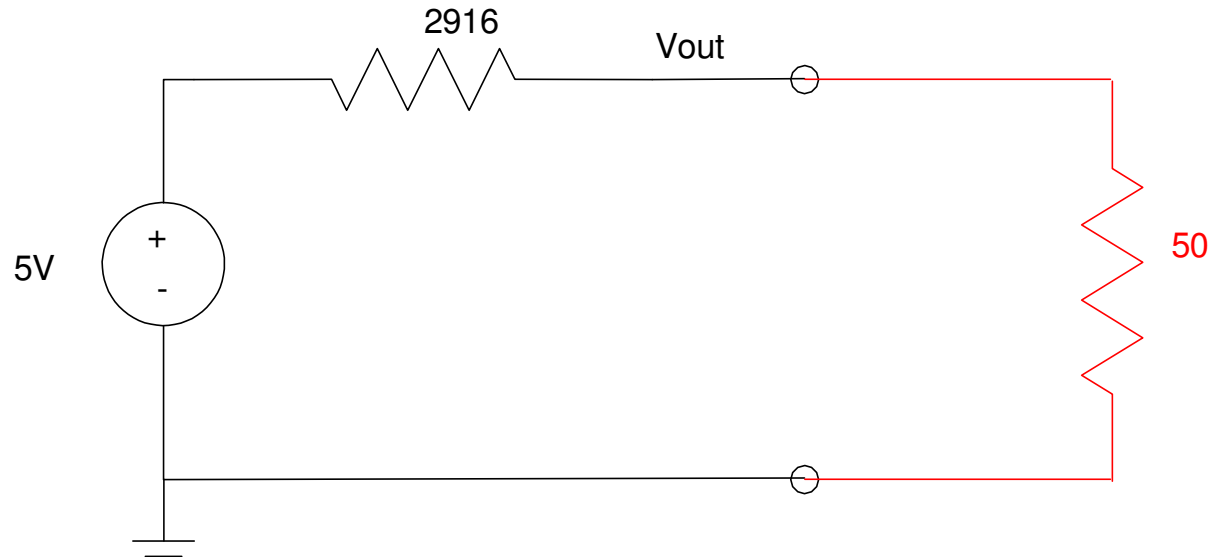
$$R_{load} = \frac{5V}{100mA} = 50\Omega$$



By voltage division, V_{out} is now

$$V_{out} = \frac{50}{50+2916} \cdot 5V$$

$$V_{out} = 0.0843V$$

This circuit works as a 5V source as long as you use it. In Electronics, we'll cover other circuits which do work.

