
Operational Amplifiers

EE 206 Circuits I

Jake Glower - Lecture #13


Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

Operational Amplifiers

An operational amplifier is a 2-input device with


$$V_o \approx k(V^+ - V^-)$$

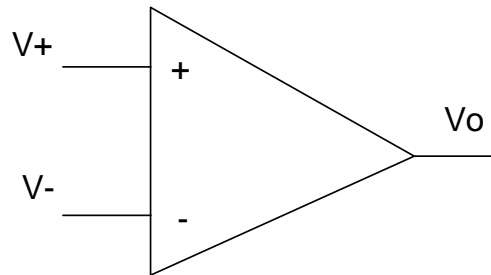where k is a large number. For short, the following symbol is used for an differential amplifier:



Symbol for an operational amplifier (op-amp)

Operational Amplifier Characteristics

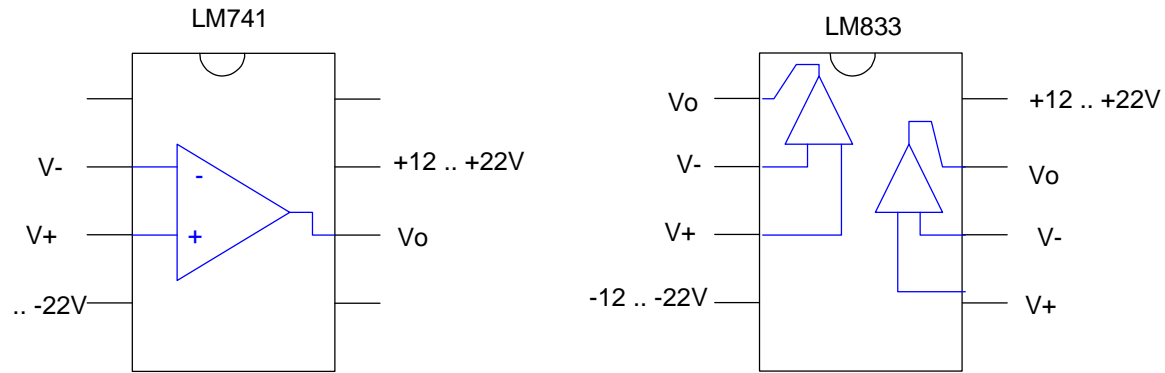

| | LM741 | LM833 | Ideal |
|-------------------------------|--------------------|---------------------|----------------------|
| Input Resistance | 2M Ohms | 4G Ohms | infinite |
| Output Resistance | 75 Ohms | 20 Ohms | 0 |
| Output Short Circuit Current: | 25mA | 50 mA | infinite |
| Operating Voltage | +/- 12V .. +/- 22V | +/- 2.5V .. +/- 15V | any |
| Differential Mode Gain | 200,000 | 100,000 | infinite |
| Common Mode Rejection Ratio | 90dB | 100dB | common mode gain = 0 |
| Slew Rate | 0.5V/us | 7V/us | infinite |
| Gain Bandwidth Product | 1.5MHz | 15MHz | infinite |
| Price (qty 100) | \$0.35 | \$0.52 | - |

Translation

Input Resistance: The Thevenin equivalent of the op-amp at V_+ and V_-

Short Circuit Current: The maximum current you can get

Operating Voltage: What you need to make it work

Differential Mode Gain: The gain from $(V_+ - V_-)$ to the output

Slew Rate: How fast the output can change.

Gain Bandwidth Product = 1.5MHz:

- If you want a gain of one, the bandwidth is 1.5MHz
 - If you want a gain of 10, the bandwidth is 150kHz.
 - etc.
-

Operational Amplifier Circuit Analysis

Problem: Write the voltage node equations for the following circuit. Assume (a) a LM741 op amp. (b) an ideal op-amp.

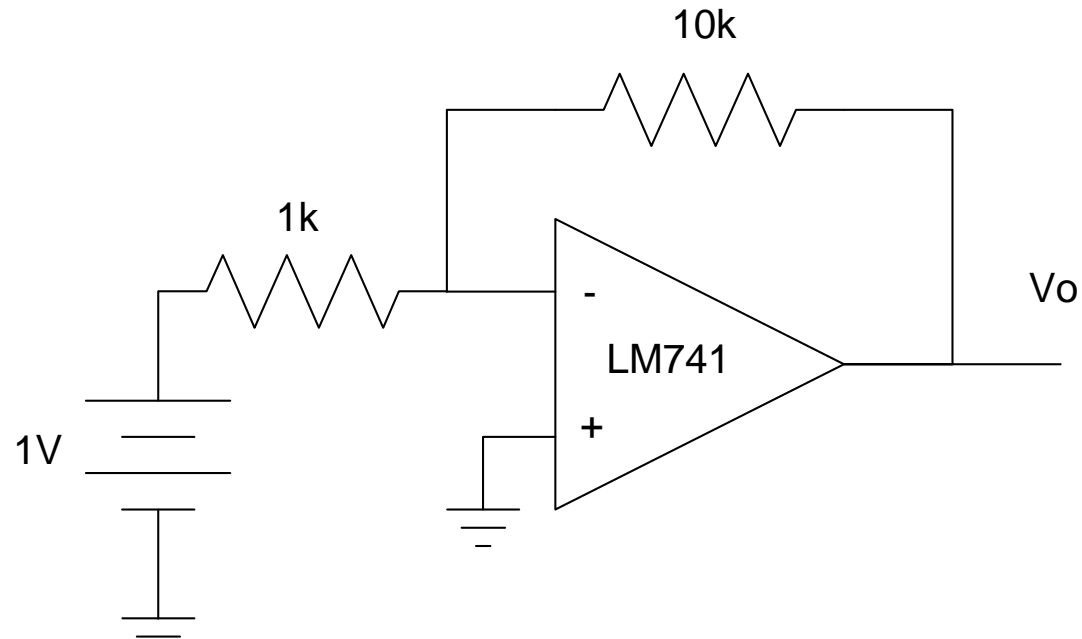


Figure 2: Find V_o for this op-amp circuit

741 Op Amp Analysis:

First, replace the op-amp with a model taking into account the input, output resistance and gains:


$$V_p = 0$$

$$\frac{V_m - 1V}{1k} + \frac{V_m}{2M} + \frac{V_m - V_x}{10k + 75} = 0$$

$$V_x = -199,994V_m$$

Solving

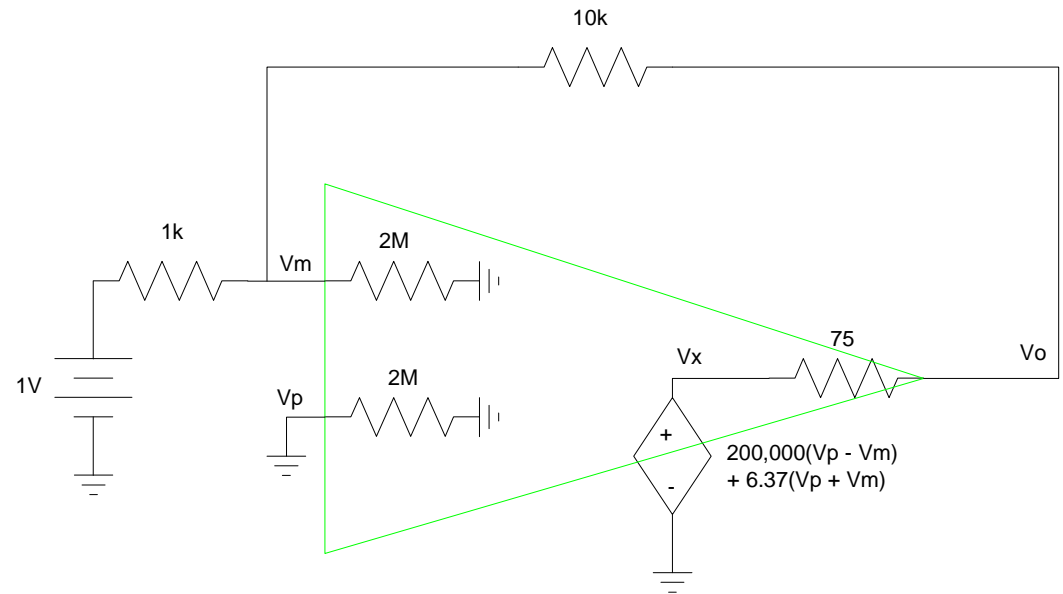
- $V_p = 0.000\ 0000\ V$
- $V_m = 0.000\ 050\ V$
- $V_o = -9.999\ 940\ V$



Ideal Op Amp:

Note that many of the terms don't affect the output all that much:

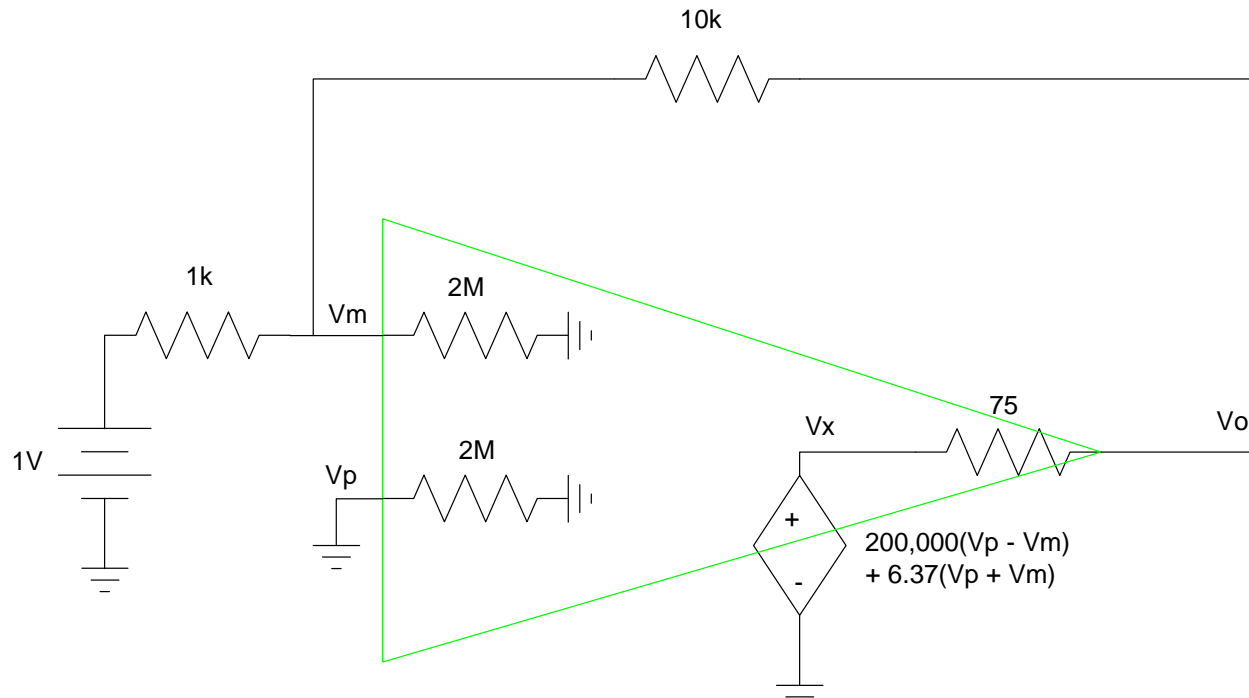- $2M\Omega \parallel 1k\Omega \approx 1k\Omega$
- $0.0000504V \approx 0V$



If you approximate these terms, you're essentially using an ideal-op amp.

This is *much* easier to analyze


$$V_p = 0$$

$$V_p = V_m$$

$$\frac{V_m - 1V}{1k} + \frac{V_m - V_o}{10k} = 0$$

which gives

$$V_o = -10.000V$$

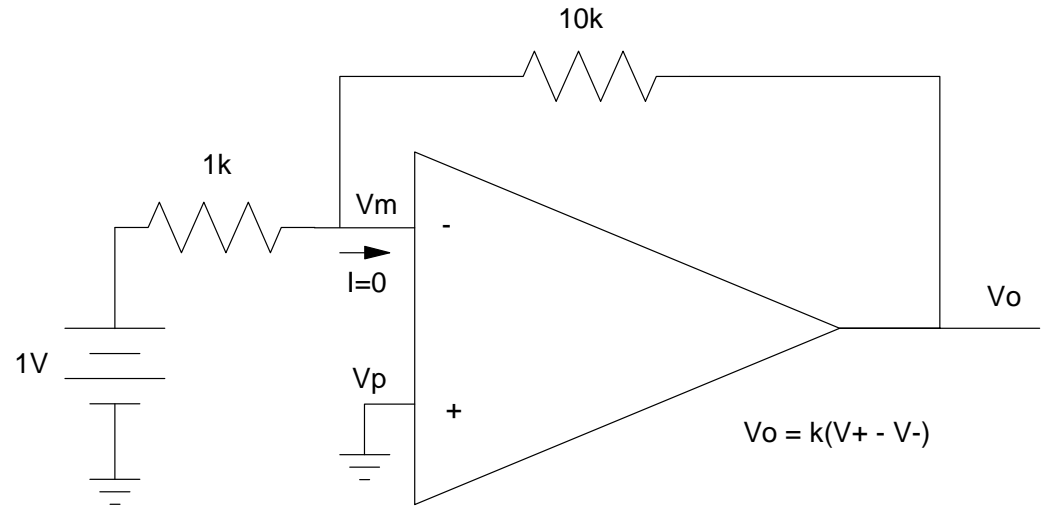

Note:

- When analyzing an op-amp circuit, you almost have to use voltage nodes.
- If assuming an ideal op-amp, the voltage node equation at V_o is

$$V_p = V_m$$

Example 2: Find $V_1..V_4$

- Assume ideal op-amps

$$V_p = V_m$$


meaning

$$V_1 = 2V$$

$$V_3 = 2V$$


$$\frac{V_1 - 3}{100k} + \frac{V_1 - V_2}{100k} = 0$$
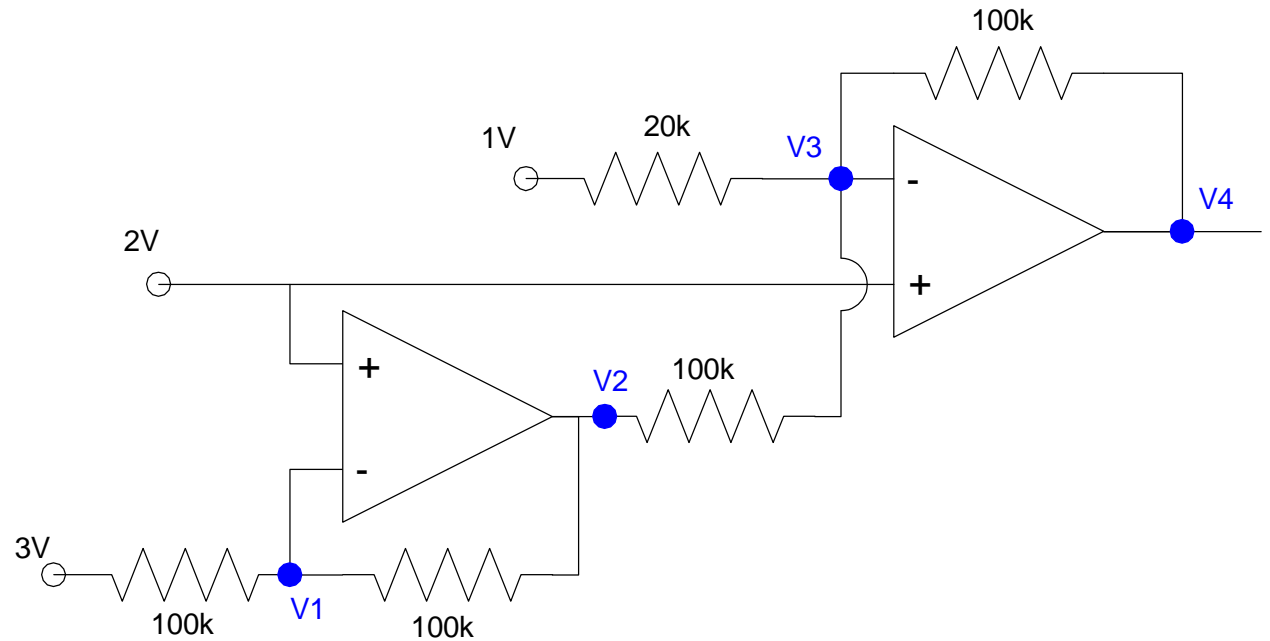
$$\frac{V_3 - V_2}{100k} + \frac{V_3 - 1}{20k} + \frac{V_3 - V_4}{100k} = 0$$



Solving gives $V1 = 2.00\text{V}$, $V2 = 1.00\text{V}$, $V3 = 2.00\text{V}$, $V4 = 8.00\text{V}$

- Same as CircuitLab

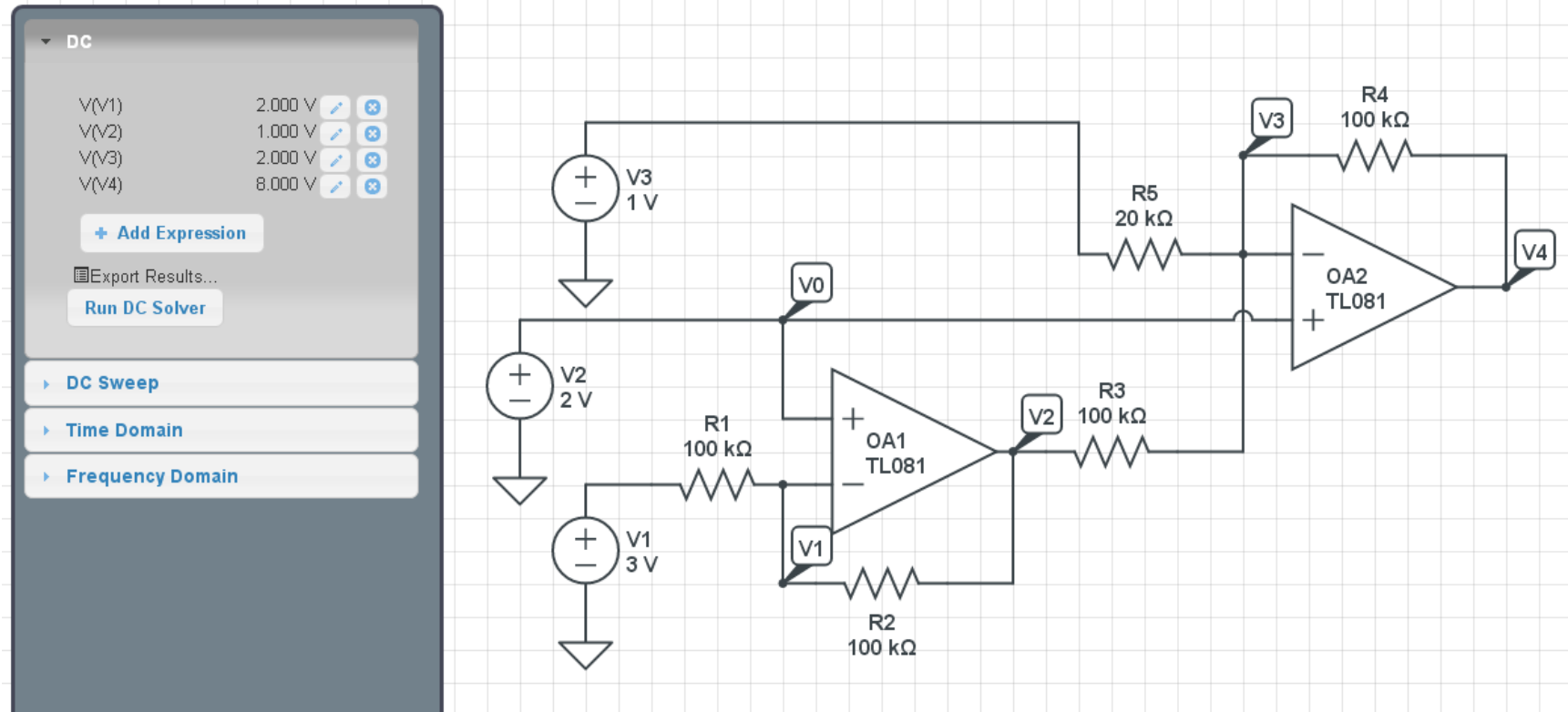

Example 3: Assume ideal op-amps. Find the node voltages.

$$V_1 = 2$$

$$V_3 = 2$$

$$\frac{V_1}{1k} + \frac{V_1 - V_2}{2k} = 0$$

$$\frac{V_3 - V_2}{3k} + \frac{V_3 - V_4}{4k} = 0$$

