
Voltage Nodes with Phasors

EE 206 Circuits I

Jake Glower

03/18/20

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions


Voltage Nodes:

- .

Example 2: 3-Stage RC Circuit

Find the voltages for the following circuit when the input is

$$x(t) = 100 \cos(2t)$$

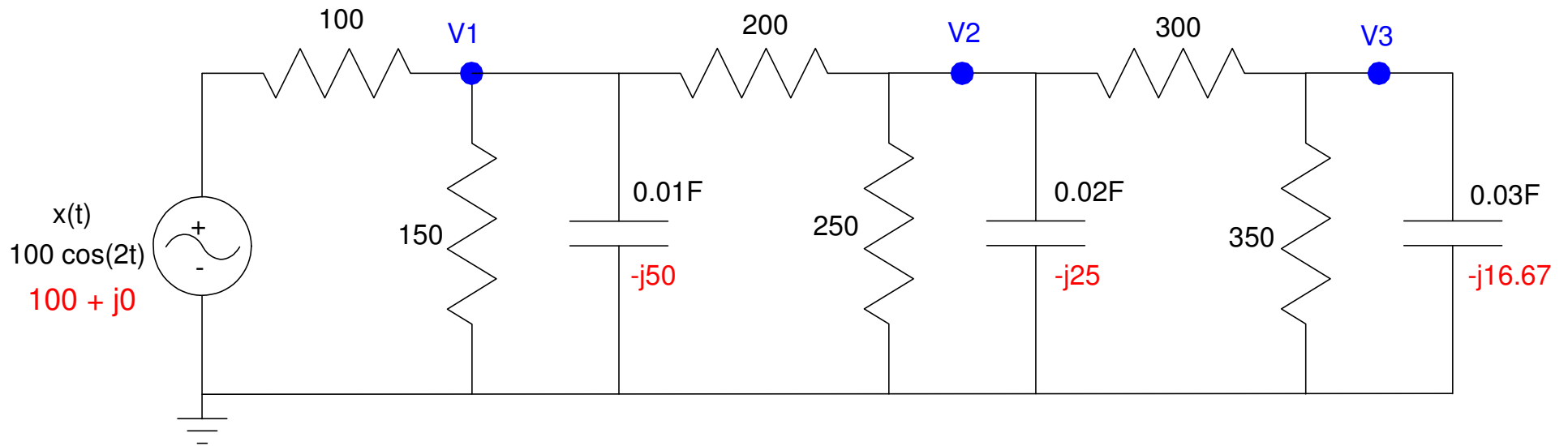

Step 1: Express in Phasor form


- (shown in red)
-

Step 2: Write N equations for N unknowns

$$\left(\frac{V_1 - X}{100}\right) + \left(\frac{V_1}{150}\right) + \left(\frac{V_1}{-j50}\right) + \left(\frac{V_1 - V_2}{200}\right) = 0$$

$$\left(\frac{V_2 - V_1}{200}\right) + \left(\frac{V_2}{250}\right) + \left(\frac{V_2}{-j25}\right) + \left(\frac{V_2 - V_3}{300}\right) = 0$$
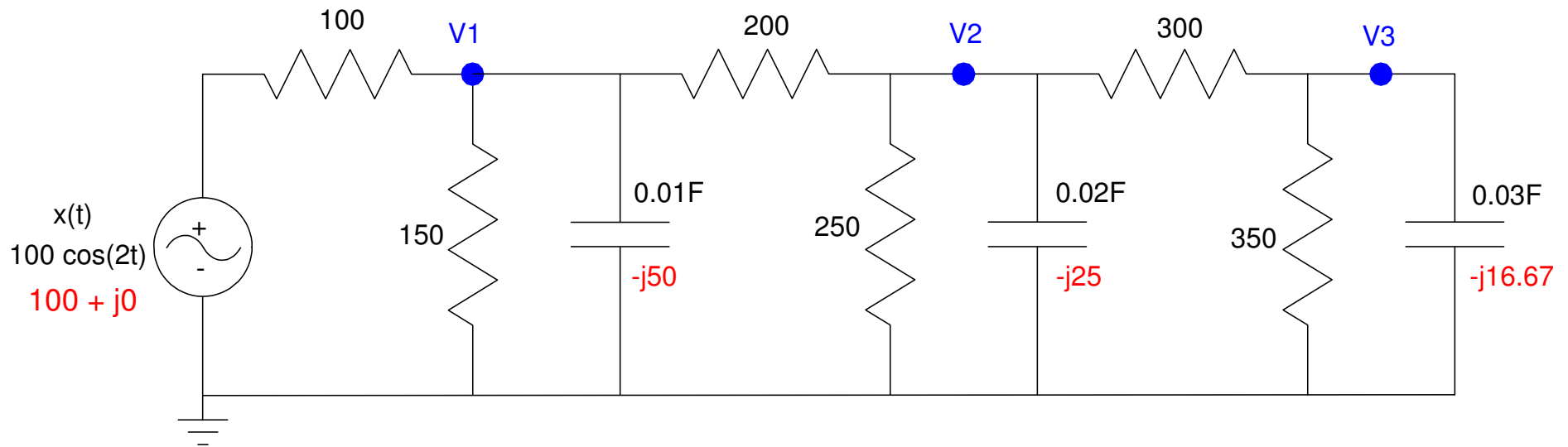
$$\left(\frac{V_3 - V_2}{300}\right) + \left(\frac{V_3}{350}\right) + \left(\frac{V_3}{-j16.67}\right) = 0$$



Step 3: Solve.

First, group terms

$$\left(\frac{1}{100} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{200}\right) V_1 + \left(\frac{-1}{200}\right) V_2 = \left(\frac{1}{100}\right) X$$

$$\left(\frac{-1}{200}\right) V_1 + \left(\frac{1}{200} + \frac{1}{250} + \frac{1}{-j25} + \frac{1}{300}\right) V_2 + \left(\frac{-1}{300}\right) V_3 = 0$$

$$\left(\frac{-1}{300}\right) V_2 + \left(\frac{1}{300} + \frac{1}{350} + \frac{1}{-j16.67}\right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} \left(\frac{1}{100} + \frac{1}{150} + \frac{1}{-j50} + \frac{1}{200}\right) & \left(\frac{-1}{200}\right) & 0 \\ \left(\frac{-1}{200}\right) & \left(\frac{1}{200} + \frac{1}{250} + \frac{1}{-j25} + \frac{1}{300}\right) & \left(\frac{-1}{300}\right) \\ 0 & \left(\frac{-1}{300}\right) & \left(\frac{1}{300} + \frac{1}{350} + \frac{1}{-j16.67}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} \left(\frac{1}{100}\right) \\ 0 \\ 0 \end{bmatrix} X$$

Solve in Matlab

$$V = \text{inv}(A) * B * X$$

$$\begin{array}{l} 24.2853 - 23.2416i \\ -1.7971 - 3.5726i \\ -0.2066 + 0.0785i \end{array}$$

$$v_1(t) = 24.28 \cos(2t) + 23.24 \sin(2t)$$

$$v_2(t) = -1.79 \cos(2t) + 3.57 \sin(2t)$$

$$v_3(t) = 0.21 \cos(2t) + 0.08 \sin(2t)$$

$$v_1(t) = 33.61 \cos(2t - 43.7^\circ)$$


$$v_2(t) = 3.999 \cos(2t - 116.7^\circ)$$

$$v_3(t) = 0.22 \cos(2t + 159.2^\circ)$$

CircuitLab Simulation


Build the circuit

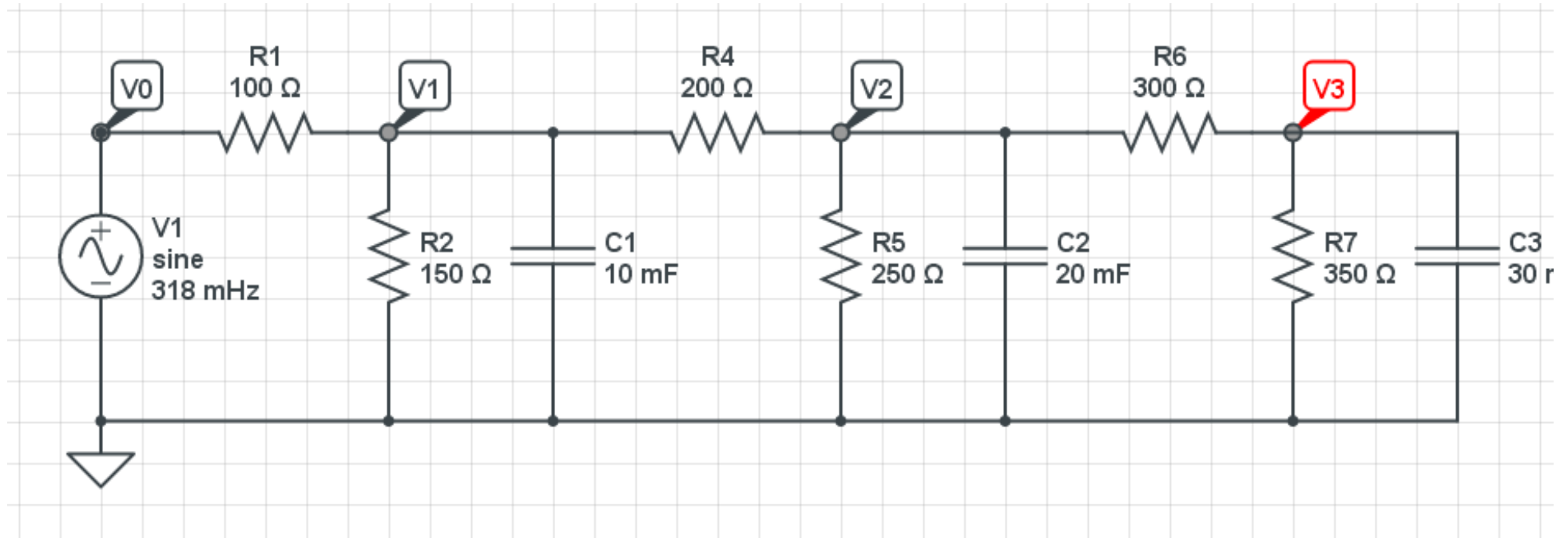- Note: $2 \text{ rad/sec} = 0.318 \text{ Hz}$



Run a transient simulation

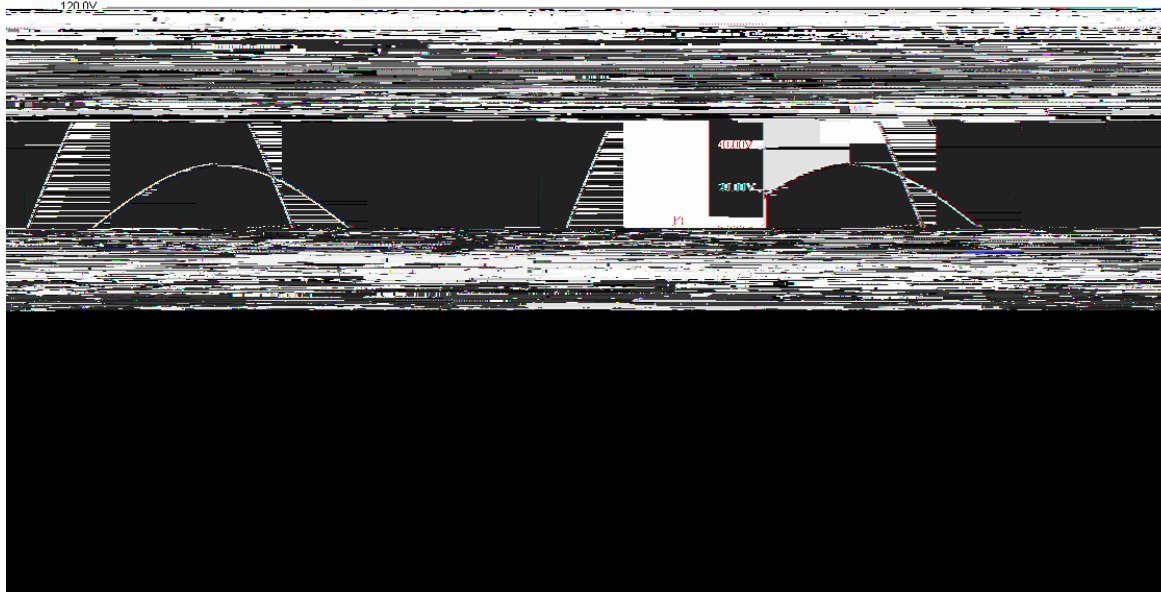- max time = 20 seconds (6 cycles)
- time step = 20ms (1000 points on the plot)



This matches our calculations:

$$v_1(t) = 33.61 \cos(2t - 43.7^\circ)$$

$$v_2(t) = 3.999 \cos(2t - 116.7^\circ)$$
