

ECE 320: Handout #7

LEDs


The specifications for an RGB LED are

Color	$V_f @ 20\text{mA}$	$\text{mcd} @ 20\text{mA}$
Red	1.9V	10,000
Green	3.0V	10,000
Blue	3.0V	10,000

1) Assume $R_r = 1\text{k}$. Determine how bright the red LED is.

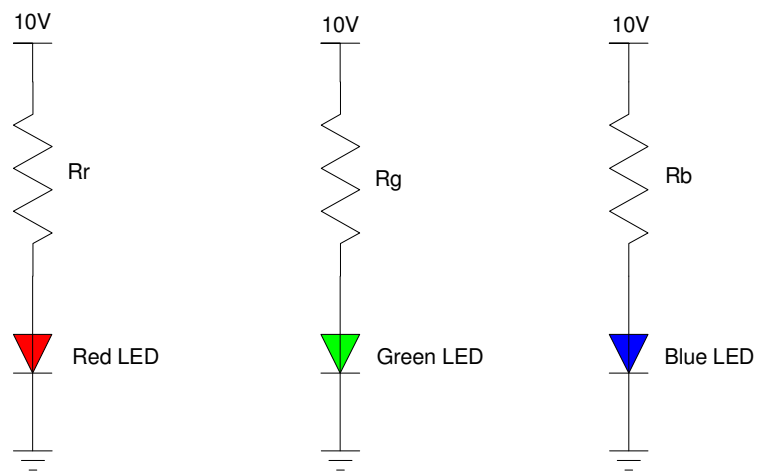2) Find $\{R_r, R_g, R_b\}$ so that the RGB LED outputs orange

- Red = 8000 mcd
- Green = 3000 mcd
- Blue = 750 mcd



The specifications for an RGB LED are

Color	Vf @ 20mA	mcd @ 20mA
Red	1.9V	10,000
Green	3.0V	10,000
Blue	3.0V	10,000


1) Assume $R_r = 1k$. Determine how bright the red LED is.

$$I_r = \left(\frac{10V - 1.9V}{1000} \right) = 8.1mA$$

$$mcd = \left(\frac{8.1mA}{20mA} \right) 10,000mcd$$

$$mcd = 4050mcd$$

.

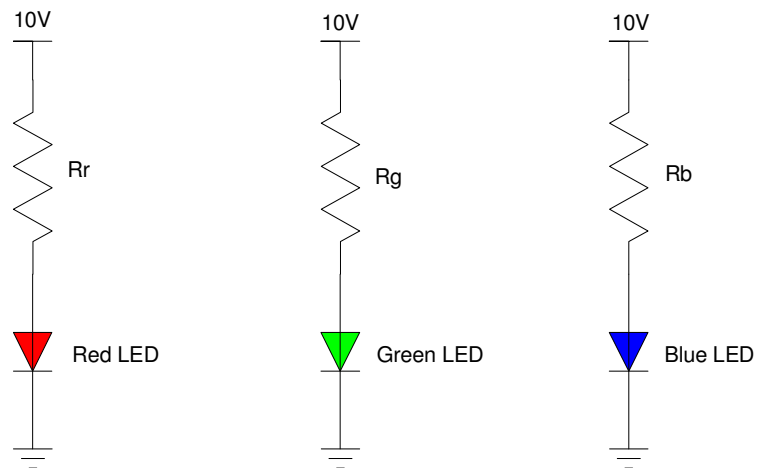

2) Find $\{R_r, R_g, R_b\}$ so that the RGB LED outputs orange

- Red = 8000 mcd
- Green = 3000 mcd
- Blue = 750 mcd

$$I_r = \left(\frac{8000\text{mcd}}{10000\text{mcd}} \right) 20\text{mA} = 16.0\text{mA}$$

$$R_r = \left(\frac{10\text{V} - 1.9\text{V}}{16\text{mA}} \right) = 506.25\Omega$$

$$I_g = \left(\frac{3000\text{mcd}}{10000\text{mcd}} \right) 20\text{mA} = 6.0\text{mA}$$

$$R_g = \left(\frac{10\text{V} - 3.2\text{V}}{6\text{mA}} \right) = 1133\Omega$$

$$I_b = \left(\frac{750\text{mcd}}{10000\text{mcd}} \right) 20\text{mA} = 1.50\text{mA}$$

$$R_b = \left(\frac{10\text{V} - 3.2\text{V}}{1.5\text{mA}} \right) = 4533\Omega$$

