
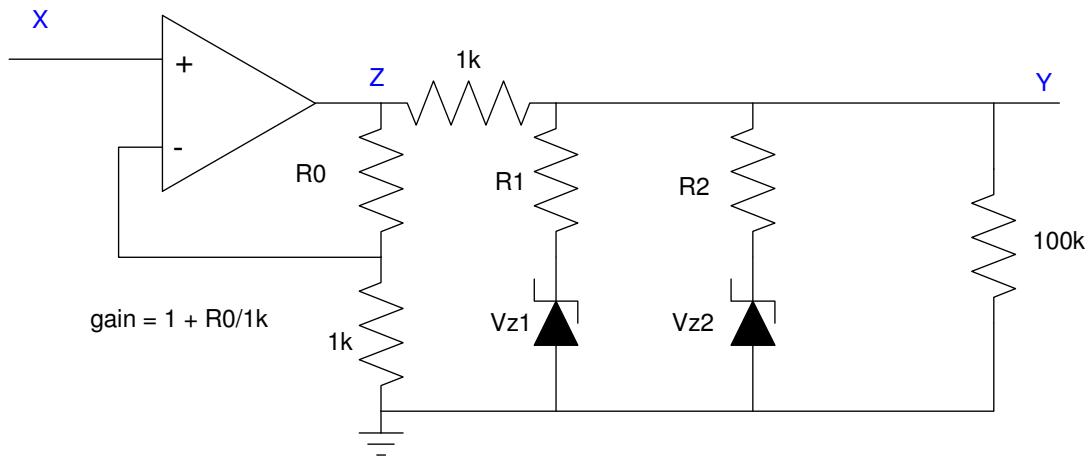


ECE 320: Handout #10

Clipper Circuits

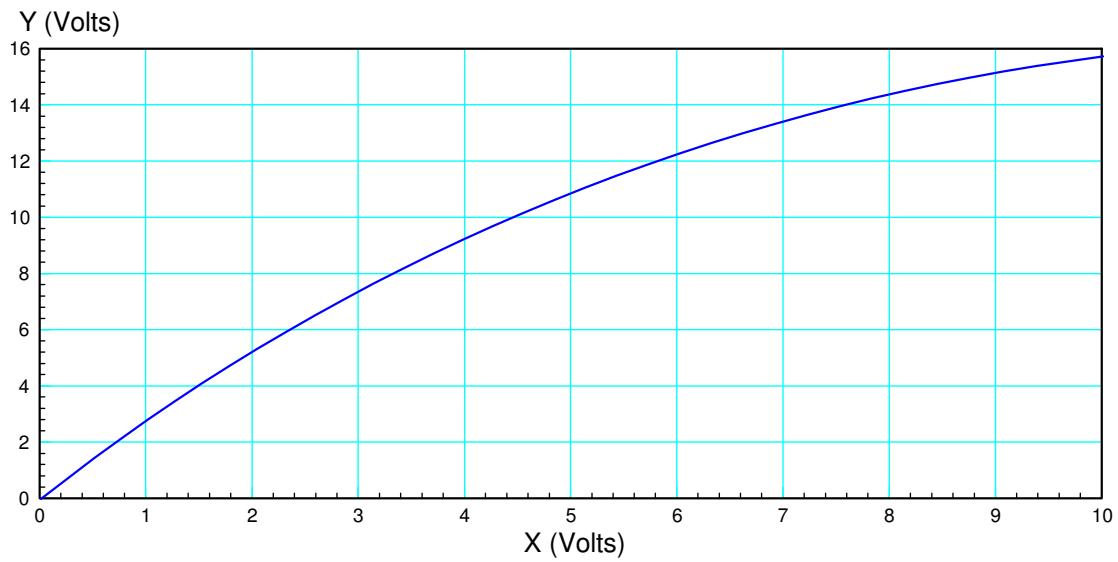Design a circuit to implement the following function



Solution

First, draw in a straight-line approximation for the function with two corners (two zener diodes)

- The voltage at the corner is the zener voltage
- The slope determines R_0 , R_1 , R_2

R_0 : Initial slope = 3.0

$$1 + \frac{R_0}{1k} = 3 \Rightarrow R_0 = 2k$$

R_1 : Slope = 1.71

$$\left(\frac{R_1}{R_1+1k} \right) \cdot 3 = 1.71 \Rightarrow R_1 = 1325\Omega$$

R_2 : Slope = 0.89. Let $R_{12} = R_1 \parallel R_2$

$$\left(\frac{R_{12}}{R_{12}+1k} \right) \cdot 3 = 0.89 \Rightarrow R_{12} = 422\Omega = R_1 \parallel R_2$$

