


ECE 320: Handout #13

H Bridges

Determine the voltages and currents. Assume 3904 and 3906 transistors


- $|V_{be}| = 0.7V$
- $|V_{ce(sat)}| = 0.2V$
- $\beta = 100$

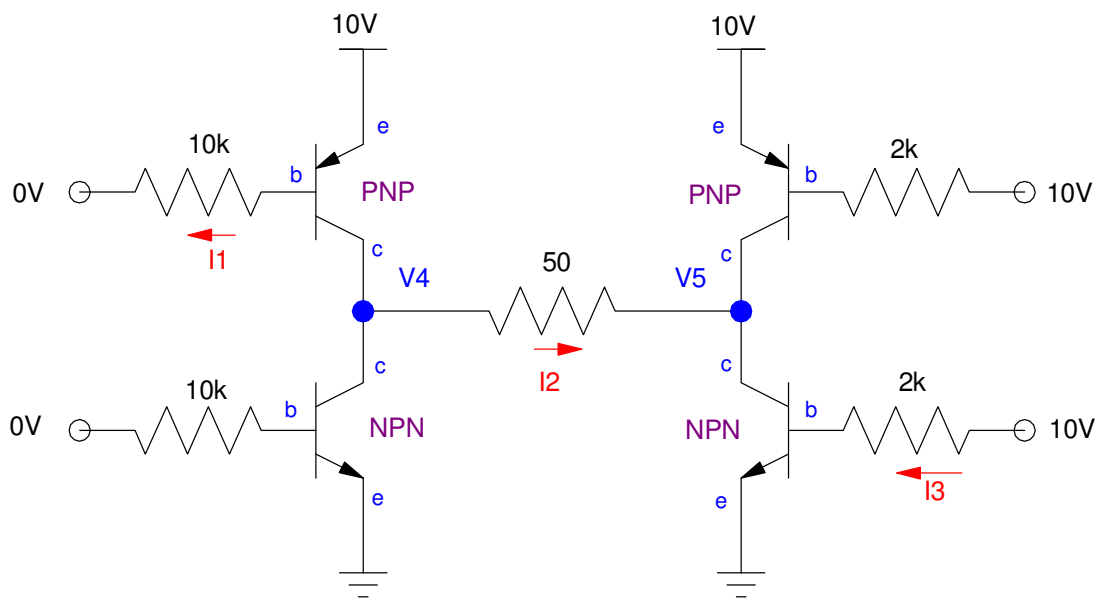Modify the circuit so that the transistors are saturated when on



Solution:

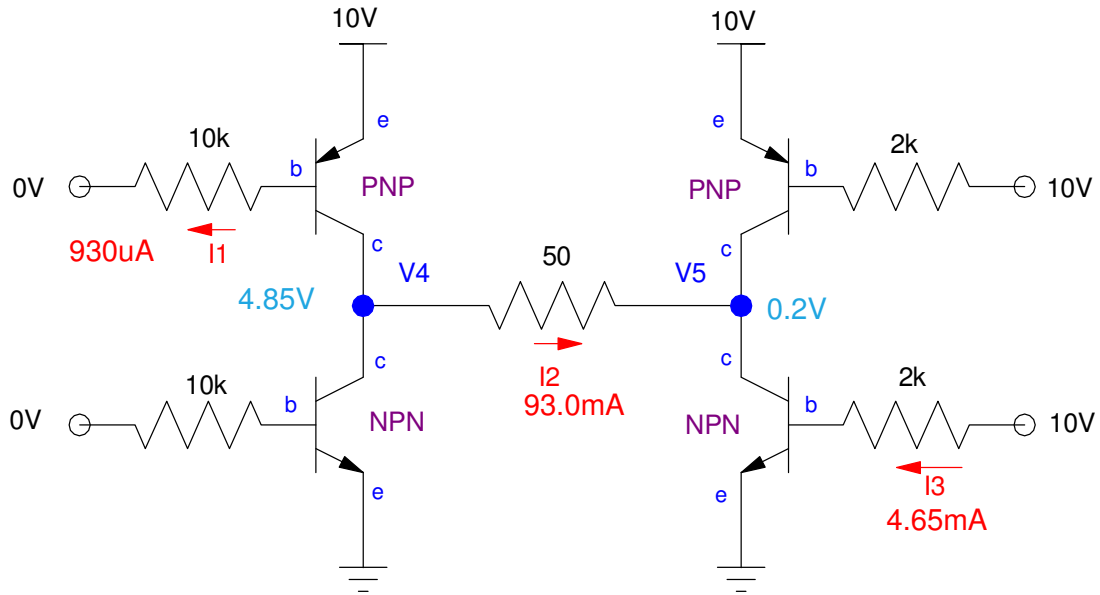Determine the voltages and currents. Assume 3904 and 3906 transistors



Current

$$I_1 = \left(\frac{10 - 0.7}{10k} \right) = 930\mu A$$

allows....

$$\beta I_1 = 93.0mA$$

$$\max(I_2) = \left(\frac{10V - 0.2V - 0.2V}{50} \right) = 192mA$$

$$I_3 = \left(\frac{10V - 0.7V}{2k} \right) = 4.65mA$$

$$\beta I_3 = 465mA$$

The smallest current wins...

$$I_2 = 93.0mA$$

Transistor #1 is active mode ($I_c = 100 I_b$)

Transistor #4 is saturated ($100 I_b = 465mA > 93mA$)

$$V_5 = 0.2V \quad \text{transistor \#4 is saturated}$$

$$V_4 = 0.2V + 50\Omega \cdot 93.0mA$$

$$V_4 = 4.85V$$