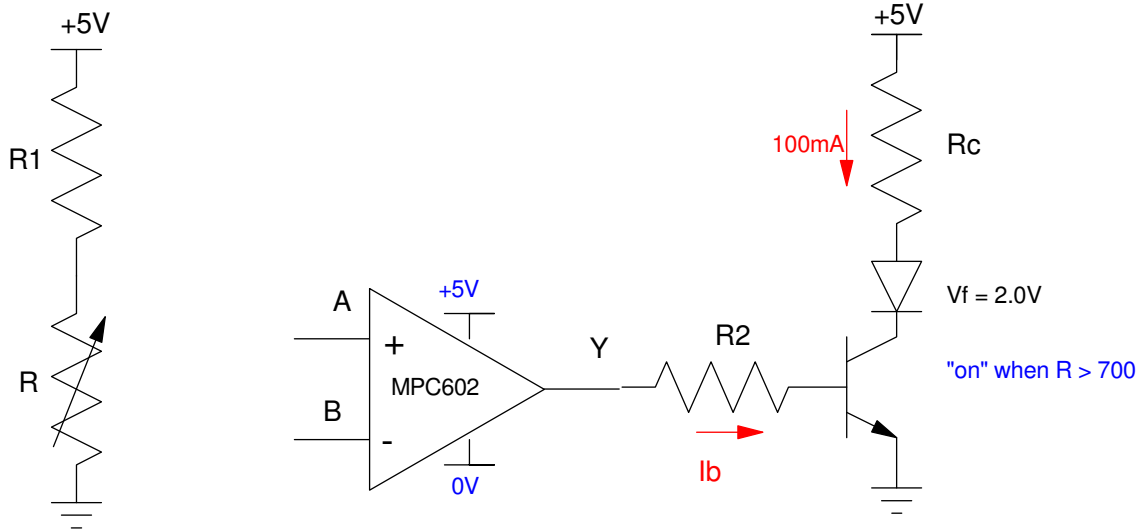


ECE 320: Handout #14


Comparitors & Schmitt Triggers

Comparator: Design a circuit which turns on a yellow LED when $R > 700$ Ohms. Assume

- $\beta = 100$
- "on" means 100mA
- The op-amp can output 25mA (max)



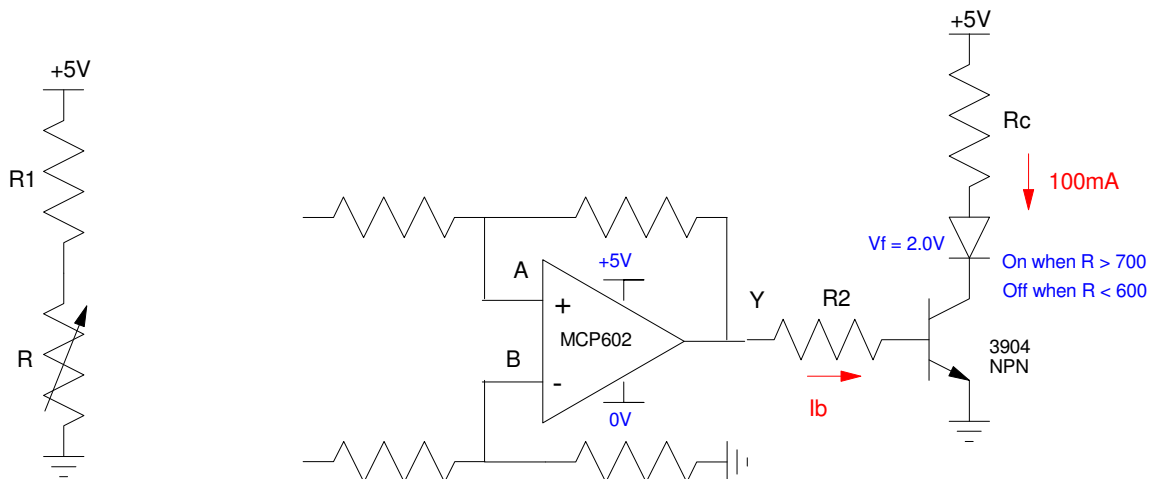Schmitt Trigger: Design a circuit which turns on a yellow LED when $R > 700$ and off when $R < 600$



Comparator

Assume $R_1 = 1k$ (somewhat arbitrary). The voltage corresponding to 700 Ohms is

$$V_x = \left(\frac{700}{700+1000} \right) 5V = 2.059V$$

When R goes up, V_x goes up and Y goes up. Connect to the + input (A)

Connect the - input to 2.059V (B)

Pick R_c so that $I_c = 100mA$

$$R_c = \left(\frac{5V-2.0V-0.2V}{100mA} \right) = 28\Omega$$


Pick R_b so that the transistor is saturated

$$\beta I_b > I_c$$

$$I_b > 1mA$$

Let $I_b = 2mA$
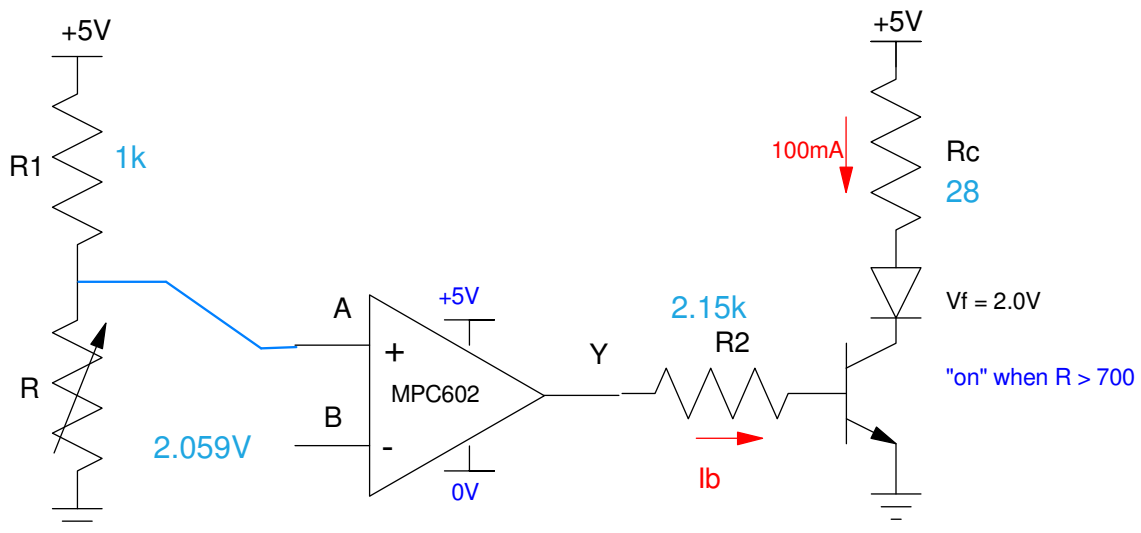
$$R_b = \frac{5V-0.7V}{2mA} = 2.15k\Omega$$



Schmitt Trigger

R2 and Rc are unchanged. Let R1 = 1000

R = 700: Y = 5V (on)

$$\bullet V_x = \left(\frac{700}{700+1000} \right) 5V = 2.059V$$

R = 600: Y = 0V (off)

$$\bullet V_x = \left(\frac{600}{600+1000} \right) 5V = 1.875V$$

As Vx goes up, Y goes up. Connect to the + input

When Y = 0V, you switch when Vx = 2.059V. Make the offset 2.059V

The gain needed is

$$gain = \left(\frac{\text{change in output}}{\text{change in input}} \right) = \left(\frac{5V-0V}{2.059V-1.875V} \right) = 27.20$$

Pick the resistors in a 27.2 : 1 ratio. Make them large so that the loading on R is small

