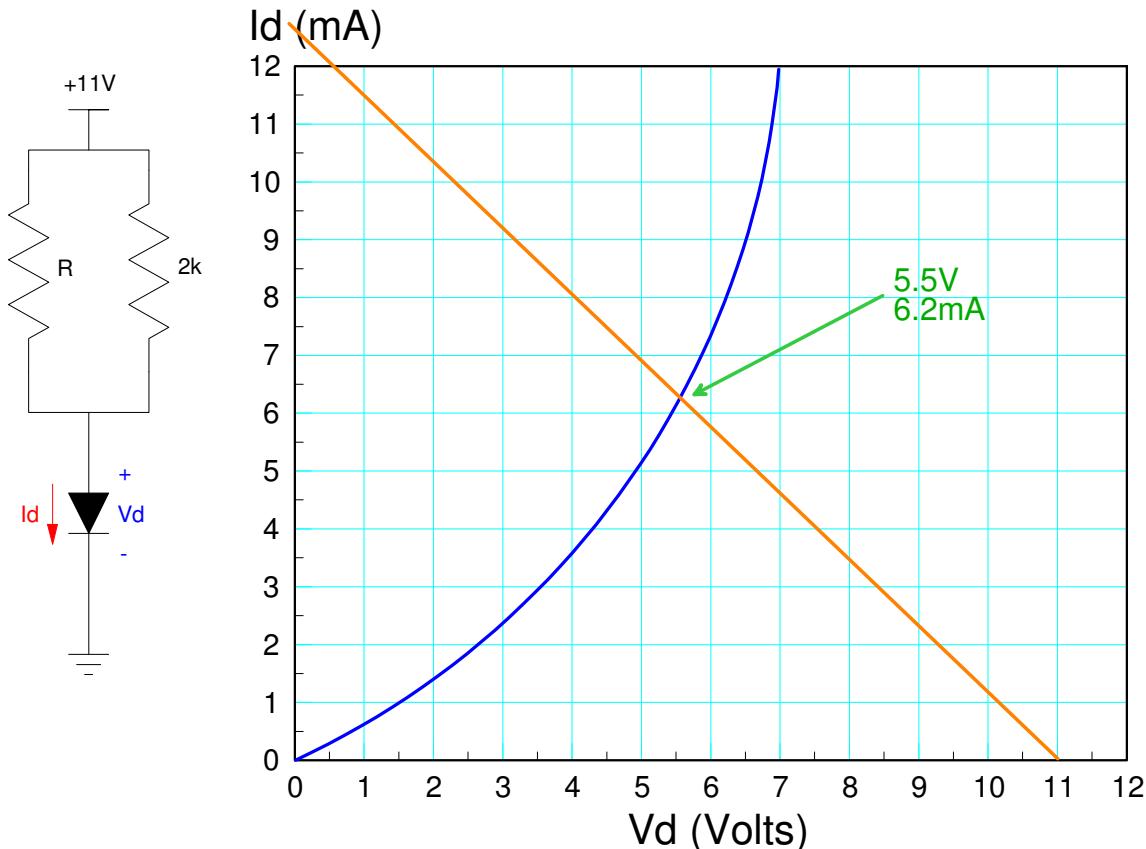


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

- 1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

R $1000 + 100 \cdot \text{mo} + \text{day}$	Load Line x-intercept (volts)	Load Line y-intercept (mA)	V_d Volts	I_d mA
1514	11V	12.77mA	5.5V	6.2mA




2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.052 \ln(10^8 \cdot I_d + 1) \quad I_d = 10^{-8} \cdot \left(\exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

Write N equations to solve for N unknonws: {V1, V2, V3, V4, Id1, Id2, Id3}.

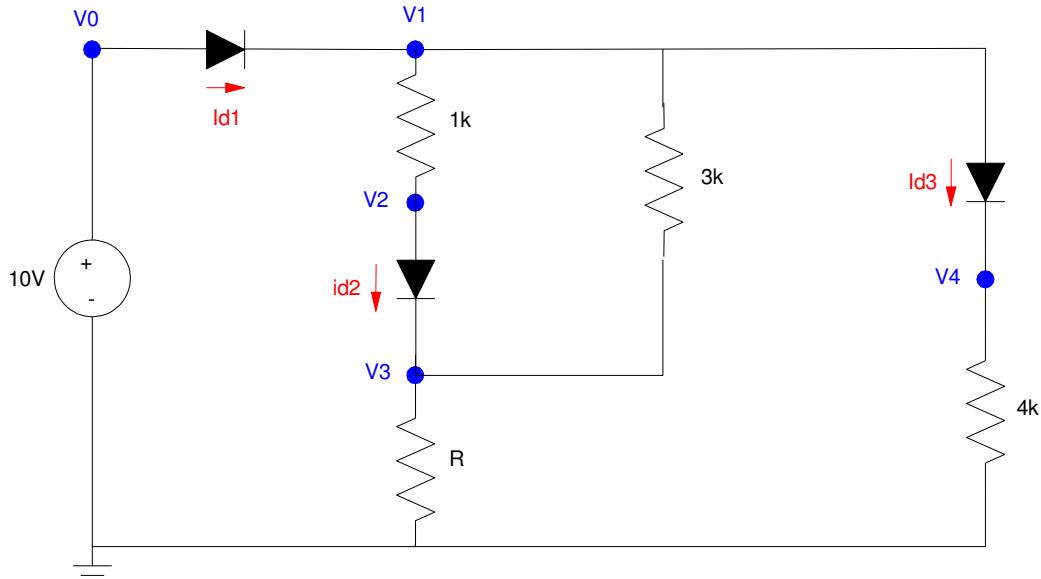- Note: you do not need to solve.
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.



$$I_{d1} = 10^{-8} \cdot \left(\exp\left(\frac{V_0 - V_1}{0.052}\right) - 1 \right)$$

$$I_{d2} = 10^{-8} \cdot \left(\exp\left(\frac{V_2 - V_3}{0.052}\right) - 1 \right)$$

$$I_d = 10^{-8} \cdot \left(\exp\left(\frac{V_1 - V_4}{0.052}\right) - 1 \right)$$

$$-I_{d1} + \left(\frac{V_1 - V_2}{1k}\right) + \left(\frac{V_1 - V_3}{3k}\right) + I_{d3} = 0$$

$$\left(\frac{V_2 - V_1}{1k}\right) + I_{d2} = 0$$


$$-I_{d2} + \left(\frac{V_3 - V_1}{3k}\right) + \left(\frac{V_3}{1514}\right) = 0$$

$$-I_{d3} + \left(\frac{V_4}{4k}\right) = 0$$

3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V \quad Id > 0$
- $Id = 0 \quad V_d < 0.7V$
- $R = 1000 + 100*(\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.

R	Id1	V1	V2	V3	V4
1514	6.026mA	9.3V	6.568V	5.868V	8.6V

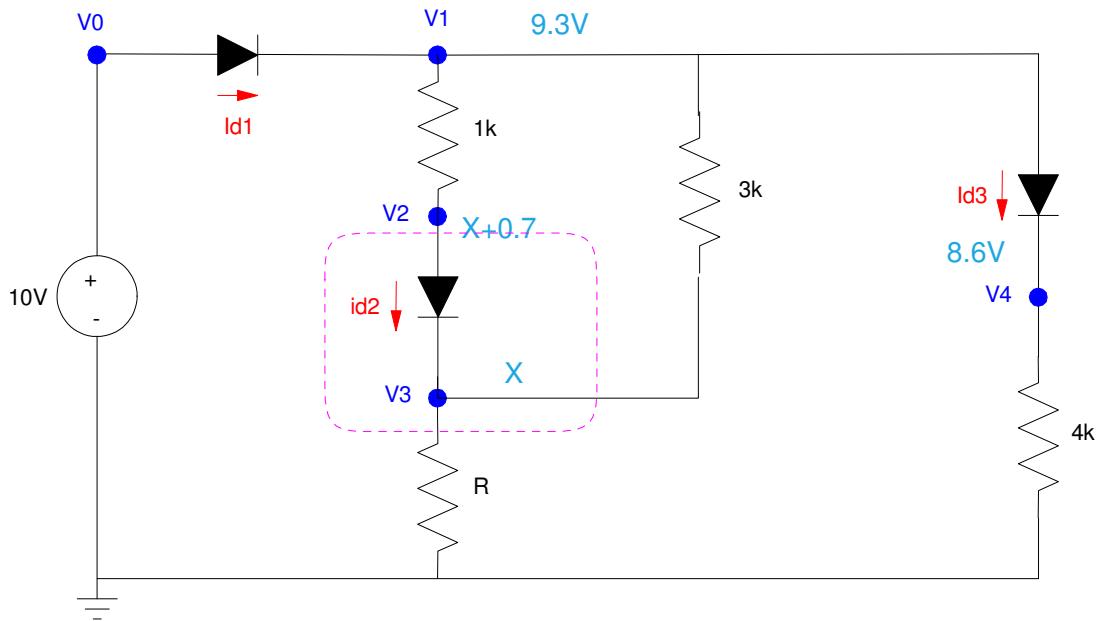

There is one unknown (V_3). Writing the supernode equation

$$\left(\frac{V_3}{1514}\right) + \left(\frac{V_3 - 9.3}{3k}\right) + \left(\frac{(V_3 + 0.7) - 9.3}{1k}\right) = 0$$

$$V_3 = 5.868V$$

$$V_2 = V_3 + 0.7 = 6.568V$$


To find Id_1

$$I_{d1} = \left(\frac{V_1 - V_2}{1k}\right) + \left(\frac{V_1 - V_3}{3k}\right) + \left(\frac{V_4}{4k}\right)$$

$$I_{d1} = 6.026mA$$

4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter

R	V1		V2	
	DC	AC	DC	AC
1514	18.48V	1.640Vpp	17.12V	0.372Vpp

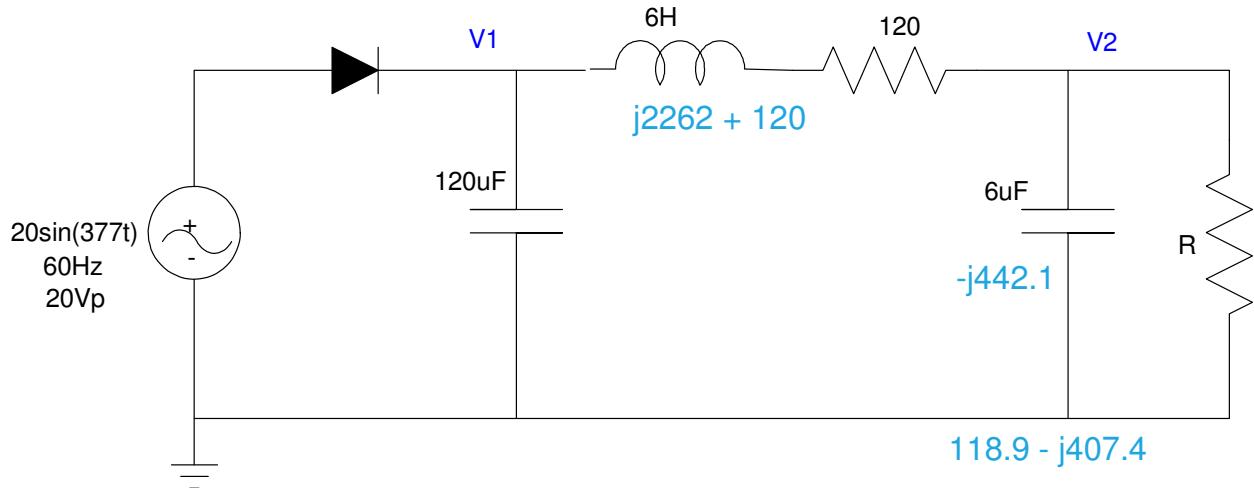

$$\max(V1) = 19.3V$$

$$I \approx \left(\frac{19.3V}{120+1514} \right) = 11.81mA \quad \text{worst case}$$

$$I = C \frac{dV}{dt}$$

$$11.81mA = 120\mu F \cdot \left(\frac{dV}{1/60s} \right)$$

$$dV = 1.640V_{pp} \quad VI(AC)$$

$$V_1(DC) = 19.3V - \frac{1}{2} \cdot 1.640V = 18.48V$$

$$V_2(DC) = \left(\frac{1514}{1514+120} \right) V_1(DC) = 17.12V$$



$$V_2(AC) = \left(\frac{(118.9-j407.4)}{(118.9-j407.4)+(120+j2262)} \right) V_1(AC)$$

$$V_2(AC) = 0.372V_{pp}$$

5) Clipper Circuit: Determine the resistors and zener voltages to implement the following function: $Y = f(X)$.
 Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$

R $1000 + 100 \cdot \text{mo day}$	R_0	R_1	V_{z1}	R_2	V_{z2}
1514	1.86k	974	4.0V	320	6.8V

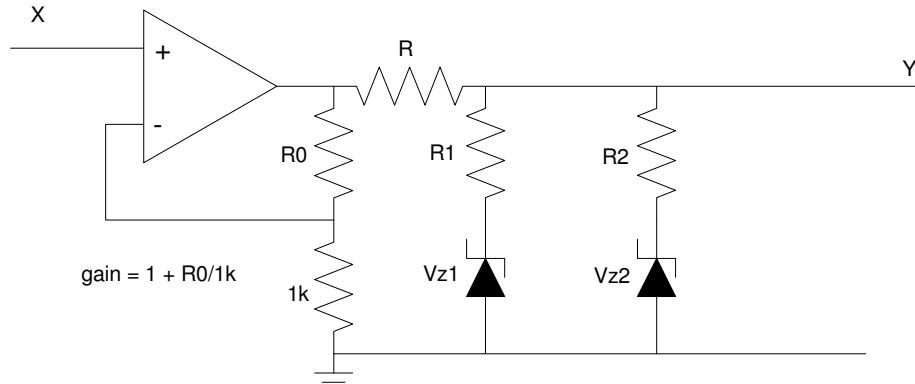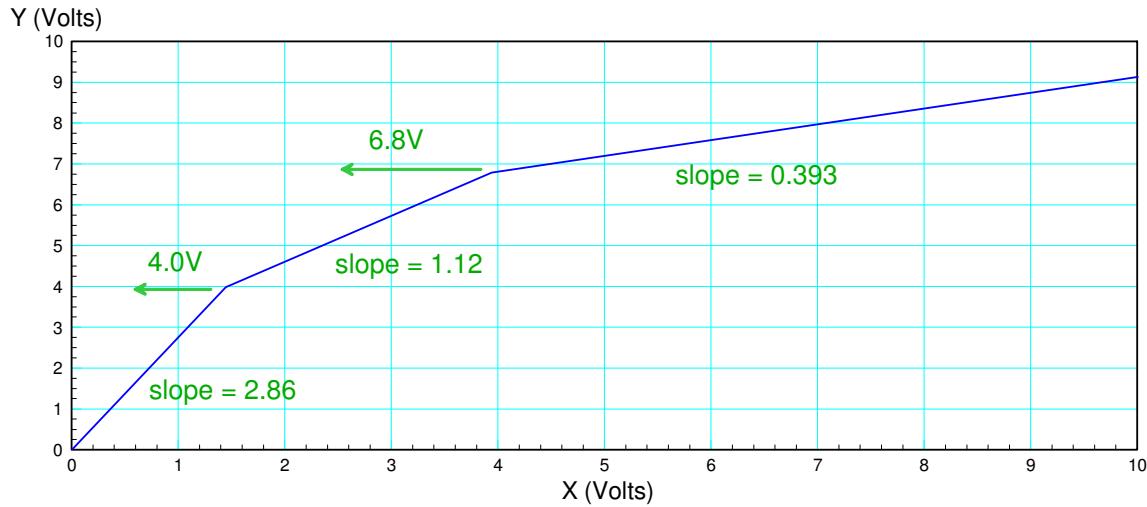

R_1 :

$$\left(\frac{R_1}{R_1 + 1514} \right) (2.86) = 1.12$$

$$R_1 = \left(\frac{1.12}{2.86 - 1.12} \right) 1514 = 974\Omega$$

R_2 :

$$\left(\frac{R_{12}}{R_{12} + 1514} \right) (2.86) = 0.393$$


$$R_{12} = \left(\frac{0.393}{2.86 - 0.393} \right) 1514 = 241.2\Omega$$

$$R_2 = 320.5\Omega$$

- 6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 5V$

R $1000 + 100\Omega \text{ Mo + Day}$	Current Gain $hfe = \beta$	Load Line x-intercept (Volts)	Load Line y-intercept (mA)	V_{ce} $V_{in} = 5V$	I_c $V_{in} = 5V$
1514	20	11V	110mA	5.3V	56mA
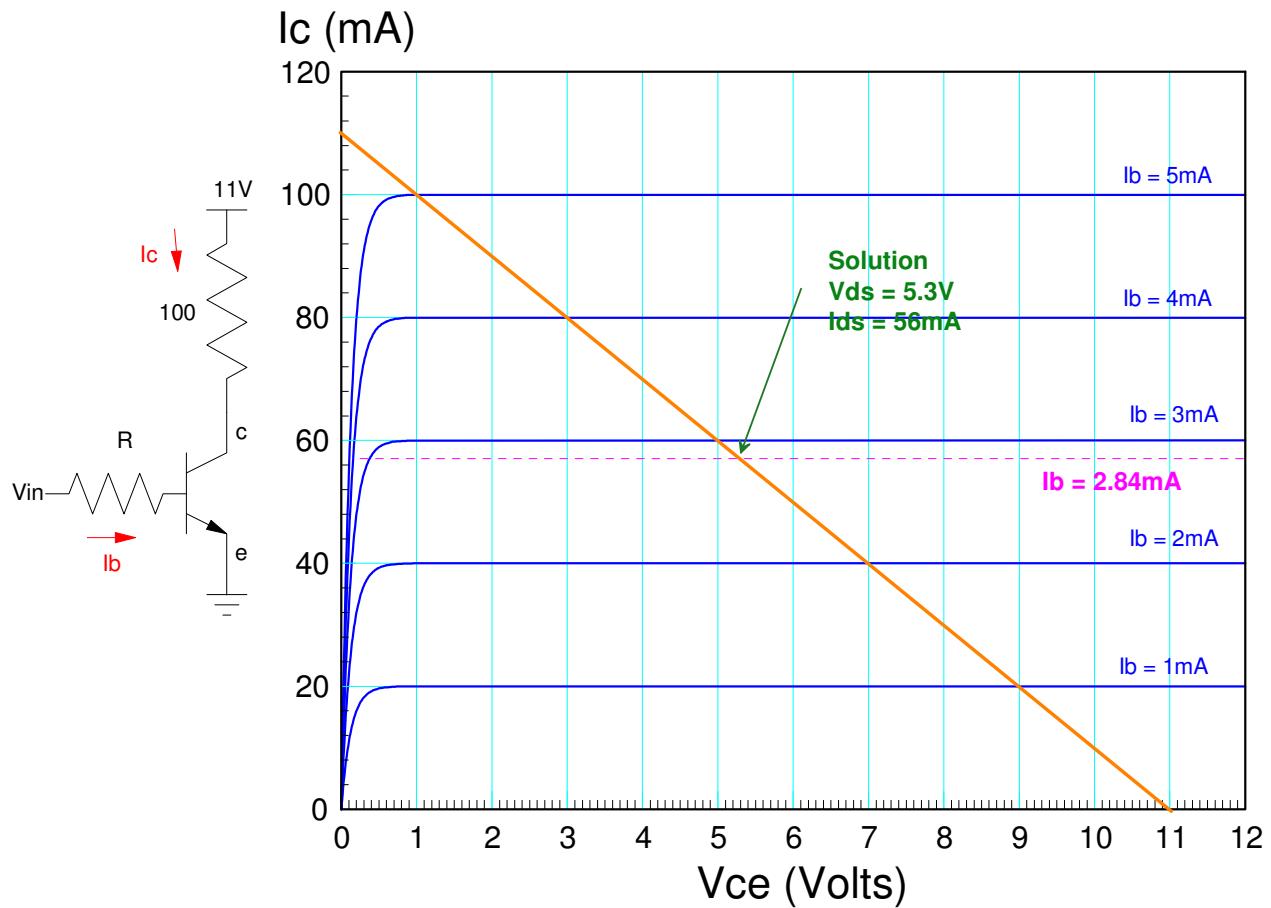
$$I_b = \left(\frac{5V - 0.7V}{1514\Omega} \right) = 2.84mA$$




7) Design a Schmitt Trigger & transistor switch so that

- Turns on the LED at $RT > 1500$ Ohms
- Turns off the LED when $RT < 1200$ Ohms

Assume

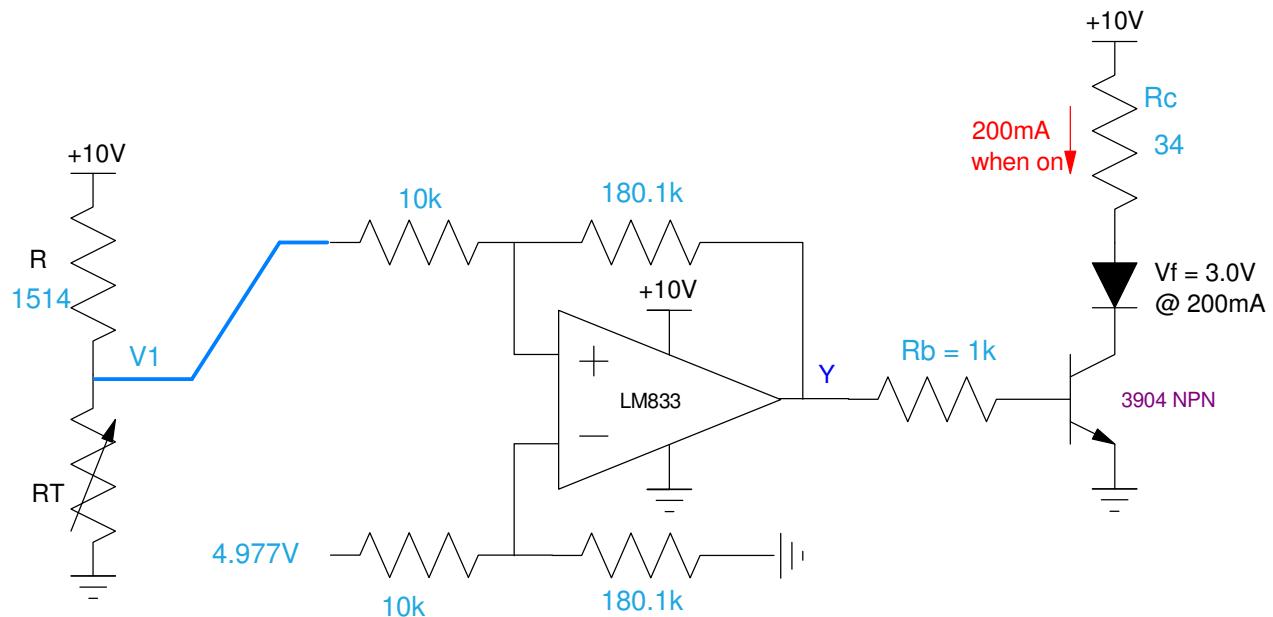- $R = 1000 + 100 \times (\text{your birth month}) + (\text{your birth date})$
- $V_{ce(\text{sat})} = 0.2V$
- Current gain (β) = 100



$$RT = 1500 \text{ Ohms}$$

$$I_b > \frac{200mA}{\beta} = 2mA$$

- $V_1 = \left(\frac{1500}{1500+1514} \right) 10V = 4.977V$
- $Y = 10$

Let $I_b = 9.3mA$

$$R_b = \left(\frac{10V - 0.7V}{9.3mA} \right) = 1k$$

$$RT = 1200 \text{ Ohms}$$

- $V_1 = \left(\frac{1200}{1200+1514} \right) 10V = 4.422V$
- $Y = 0V$

$$R_c = \left(\frac{10V - 3V - 0.2V}{200mA} \right) = 34\Omega$$

Y goes down as V1 goes down (positive correlation). Connect to the + input.


Gain is

$$\text{gain} = \left(\frac{10V - 0V}{4.977V - 4.422V} \right) = 18.01$$

8) DTL Logic: Determine the voltages and currents for the following DTL logic gage. Assume

- $R = 1000 + 100*(\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(\text{sat})} = 0.2V$, $\beta=100$)


R $1000 + 100*\text{mo} + \text{day}$	I1	I2	I3	V4	V5
1514	2.38 mA	0	2.38mA	0.2V	0.2V

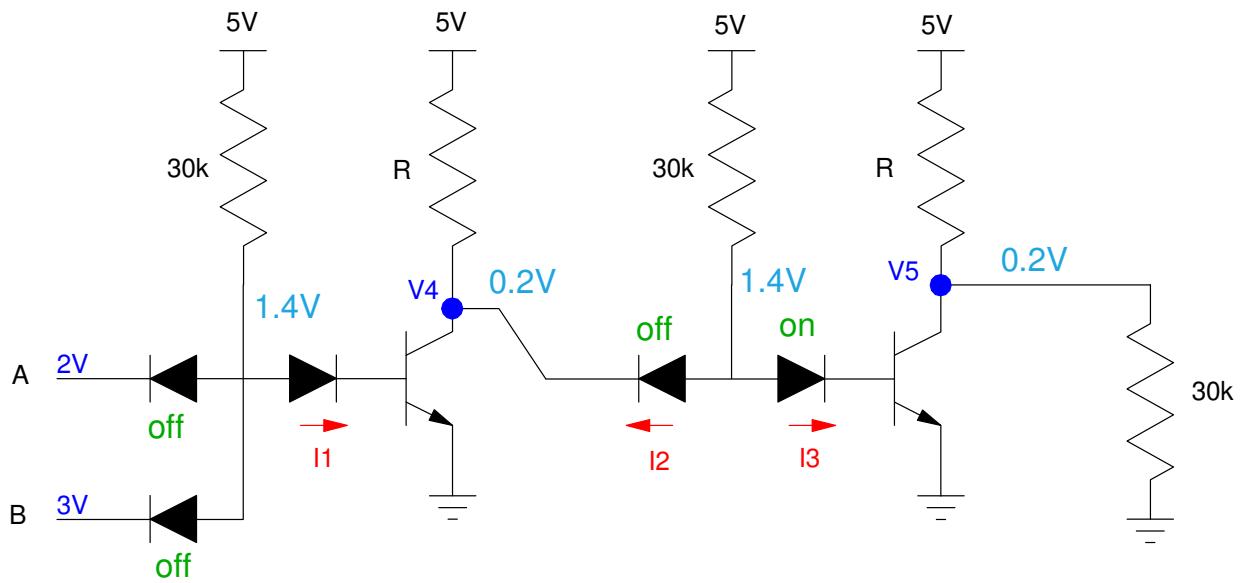

9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine { V_{ds} , I_{ds} } when $V_g = 7V$

R 1000 + 100*mo + day	k_n transconductance gain	Load Line x=intercept	Load Line y intercept	V_{ds} $V_g = 7V$	I_{ds} $V_g = 7V$	Operating Region off / active / ohmic
1514	298 $\mu A/V^2$	8V	5.28mA	2.4V	3.6mA	ohmic

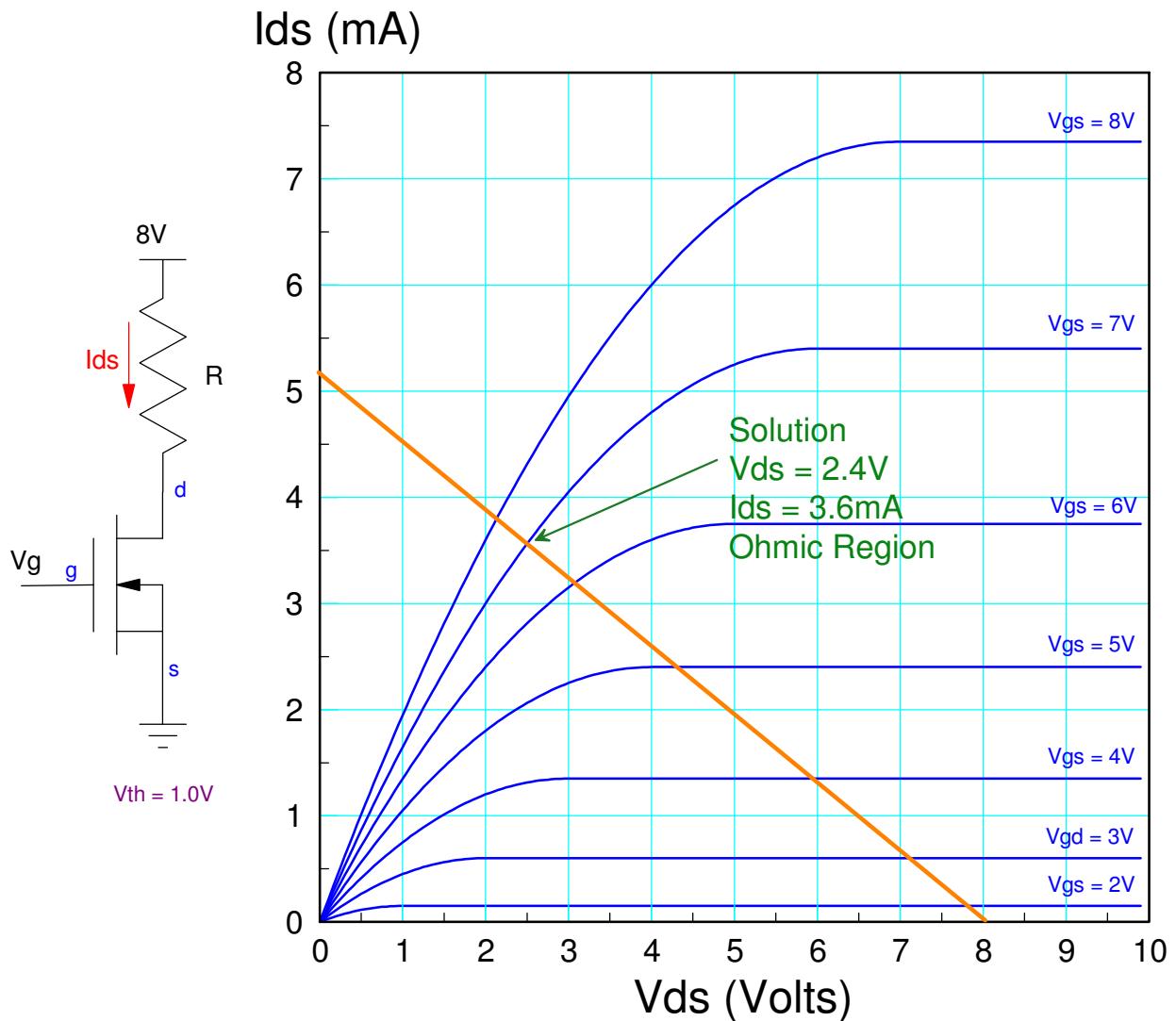

k_n calculations: Pick a point ($V_s = 10V$, $V_{gs} = 8V$, $I_{ds} = 7.3mA$) . Region = saturated

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$7.3mA = \frac{k_n}{2} (8 - 1)^2$$

$$k_n = 298 \frac{\mu A}{V^2}$$

10) CMOS Logic

a) Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD	
		00	01
AB	00	1	1
	01	1	x
11	0	x	x
10	0	0	1

$$\bar{Y} = \bar{A}C + A\bar{C}$$

This is the logic on the low-side (n-channel MOSFETs)

from DeMorgan's law

$$Y = (A + \bar{C})(\bar{A} + C)$$

This is the logic for the high-side (p-channel MOSFETs)

