
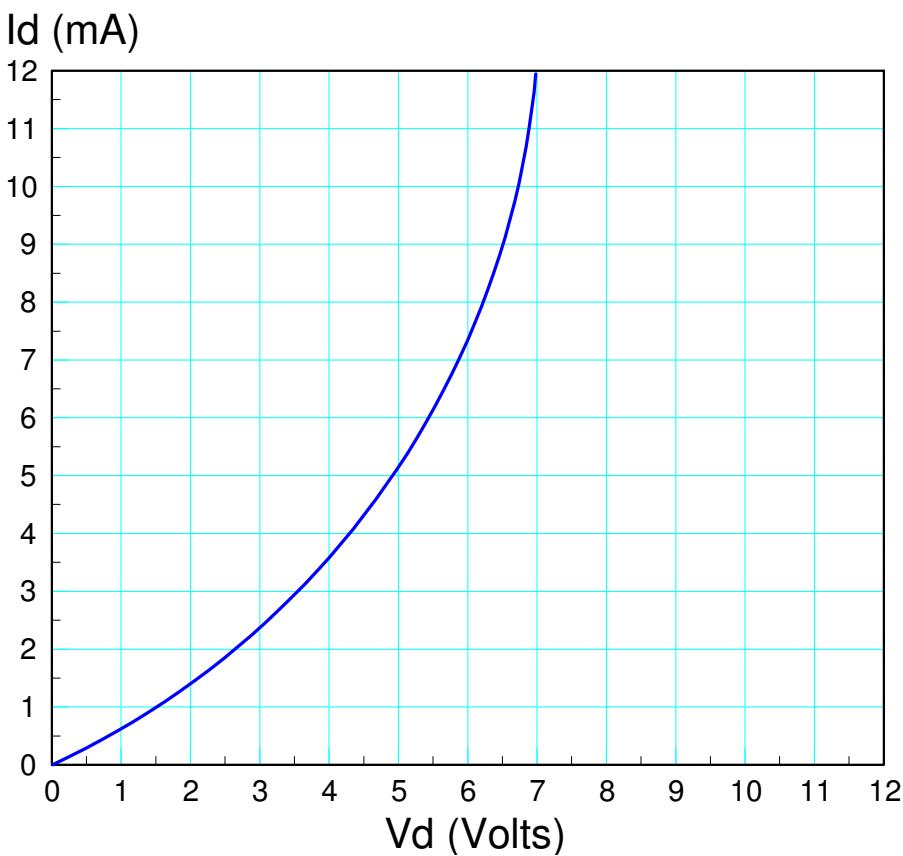


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

- 1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.


R $1000 + 100 \cdot \text{mo} + \text{day}$	Load Line x-intercept (volts)	Load Line y-intercept (mA)	V_d Volts	I_d mA

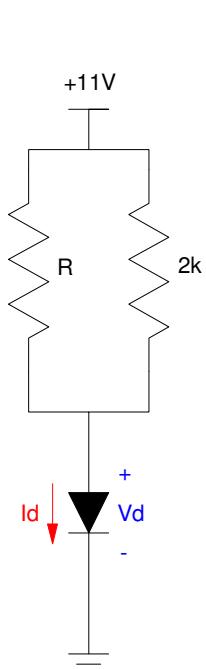

3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:


- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 1000 + 100*(\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.

R	Id1	V1	V2	V3	V4

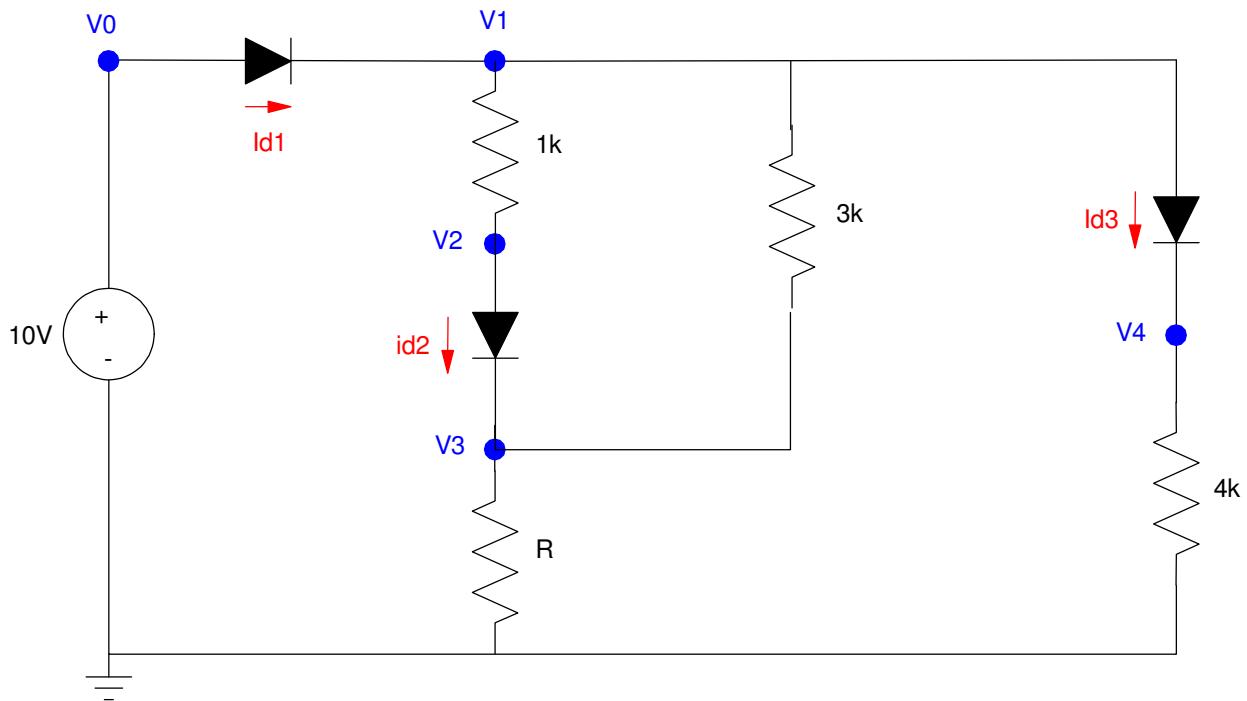

4) AC to DC: Analysis: Determine V₁ and V₂ (both DC and AC) for the following AC to DC converter

R	V ₁		V ₂	
	DC	AC	DC	AC


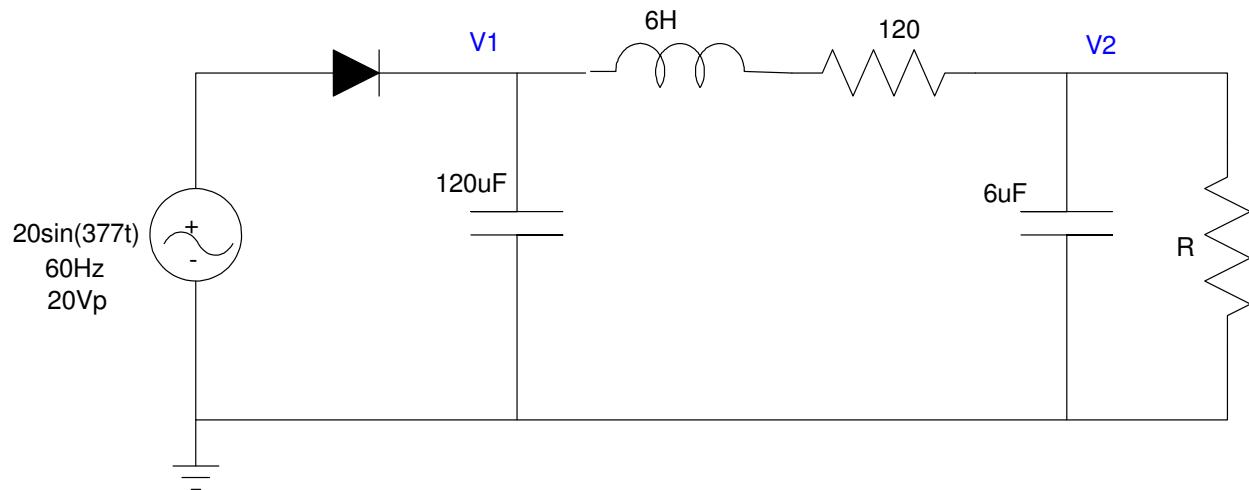


5) Clipper Circuit: Determine the resistors and zener voltages to implement the following function: $Y = f(X)$.
 Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$

R $1000 + 100 \cdot \text{mo day}$	R_0	R_1	V_{z1}	R_2	V_{z2}

Y (Volts)

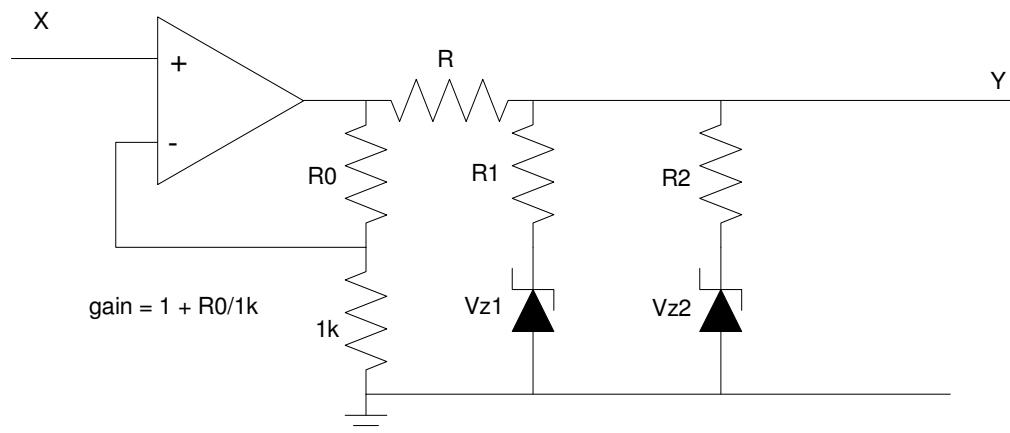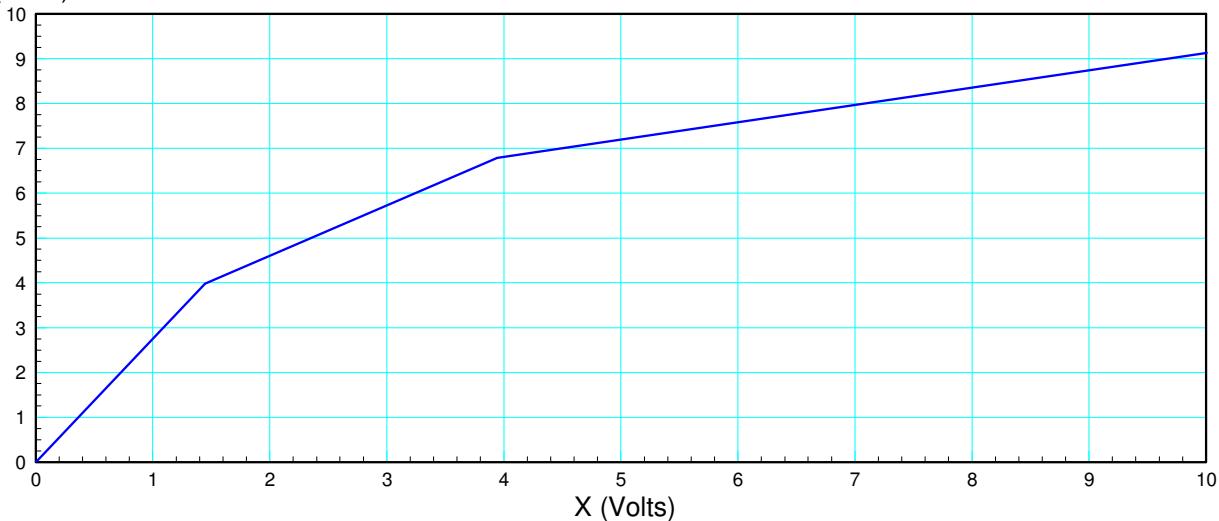


ECE 320 - Final (pt 2) - Name _____

Transistors and Mosfets

- 6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 5V$

R $1000 + 100 \cdot Mo + Day$	Current Gain $hfe = \beta$	Load Line x-intercept (Volts)	Load Line y-intercept (mA)	V_{ce} $V_{in} = 5V$	I_c $V_{in} = 5V$

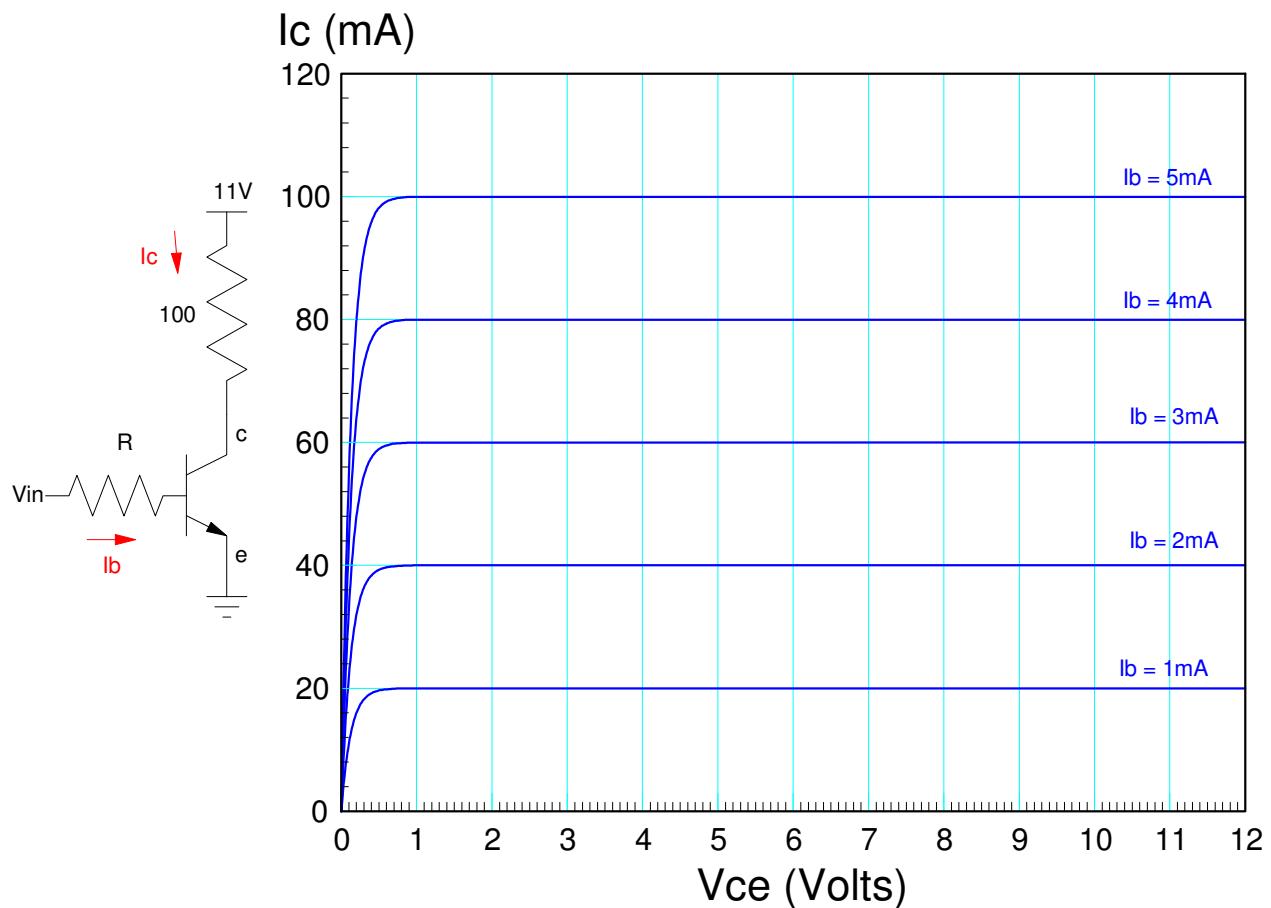


7) Design a Schmitt Trigger & transistor switch so that

- Turns on the LED at 200mA when $RT > 1500 \text{ Ohms}$
- Turns off the LED when $RT < 1200 \text{ Ohms}$

Assume

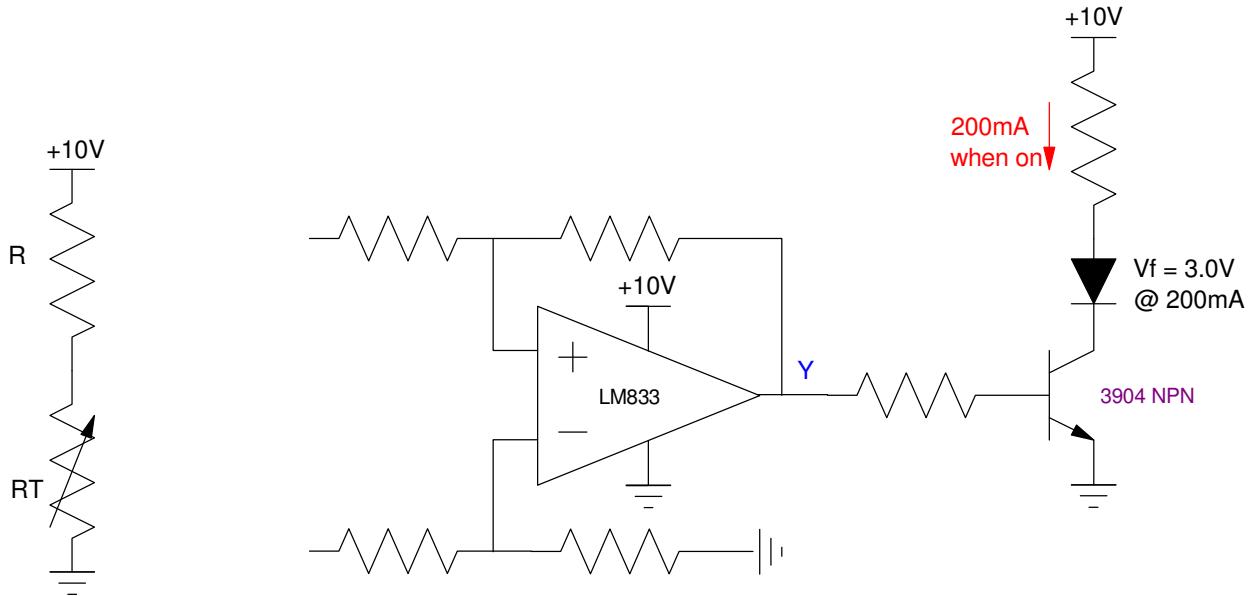
- $R = 1000 + 100*(\text{your birth month}) + (\text{your birth date})$
- $V_{ce(\text{sat})} = 0.2\text{V}$
- Current gain (β) = 100



8) DTL Logic: Determine the voltages and currents for the following DTL logic gate. Assume

- $R = 1000 + 100*(\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(\text{sat})} = 0.2V$, $\beta=100$)


R $1000 + 100*\text{mo} + \text{day}$	I1	I2	I3	V4	V5

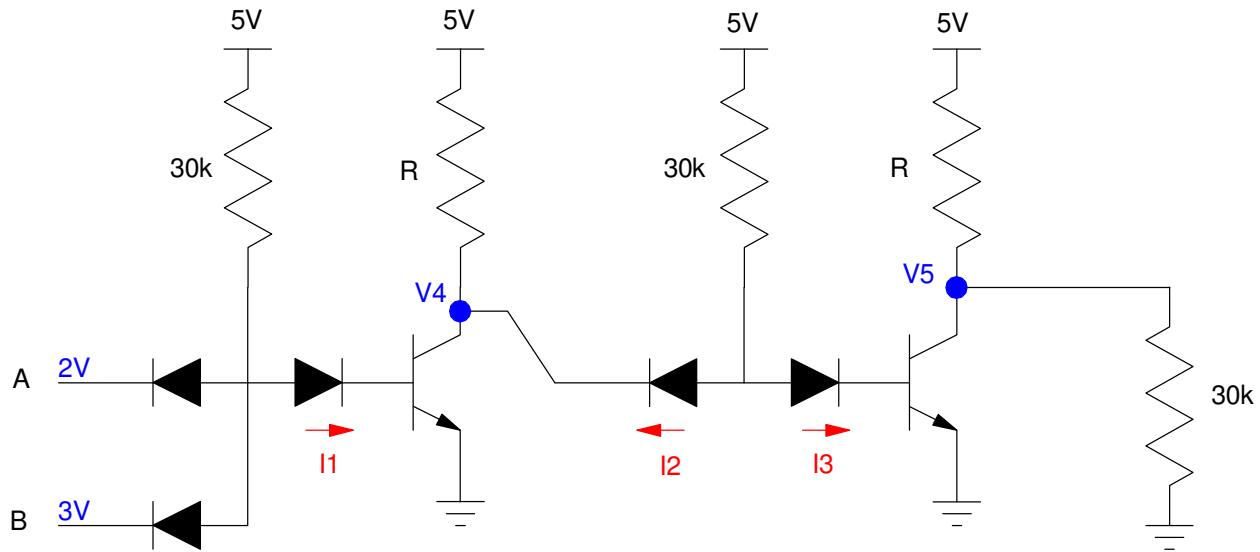

9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine $\{V_{ds}, I_{ds}\}$ when $V_g = 7V$

R $1000 + 100 \cdot m_o + d_a y$	k_n transconductance gain	Load Line $x=$ intercept	Load Line y intercept	V_{ds} $V_g = 7V$	I_{ds} $V_g = 7V$	Operating Region off / active / ohmic

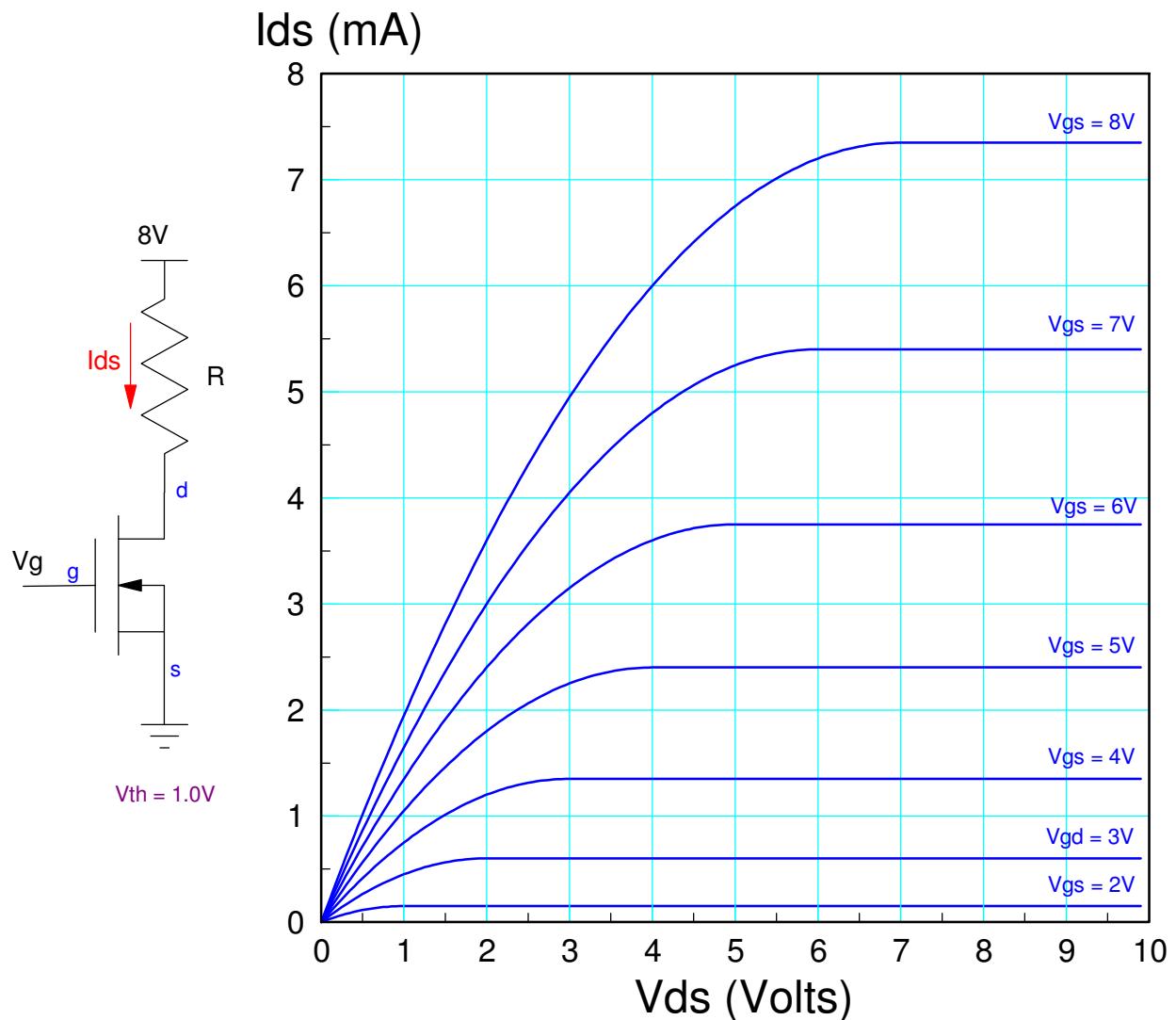

10) CMOS Logic

a) Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD				
		00	01	11	10	
AB		00	1	1	0	0
		01	1	x	x	0
11		11	0	x	x	1
10		10	0	0	1	1