

# ECE 320 - Homework #3

LEDs, AC to DC Converters. Due Monday, September 13th

Please make the subject "ECE 320 HW#3" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## LEDs

The specifications for a Piranah RGB LED are

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

1) Design a circuit to drive these LEDs with a 5V source to produce Kelly Green:

- Red = 2784 mcd (71/255)
- Green = 6156 mcd (157/255)
- Blue = 2039 mcd (52/255)

2) Design a circuit to drive these LEDs with a 5V source producing Cobalt Blue:

- Red = 352 mcd (9/255)
- Green = 3450 mcd (88/255)
- Blue = 9254 mcd (236/255)

Other colors can be obtained from


<https://www.rapidtables.com/web/color/color-wheel.html>

## AC to DC Converters

For the circuit below:

- 5) Determine the voltages at V1 and V2 (DC and AC)
- 6) Build the circuit in CircuitLab (or similar program) and verify your calculations for problem #5

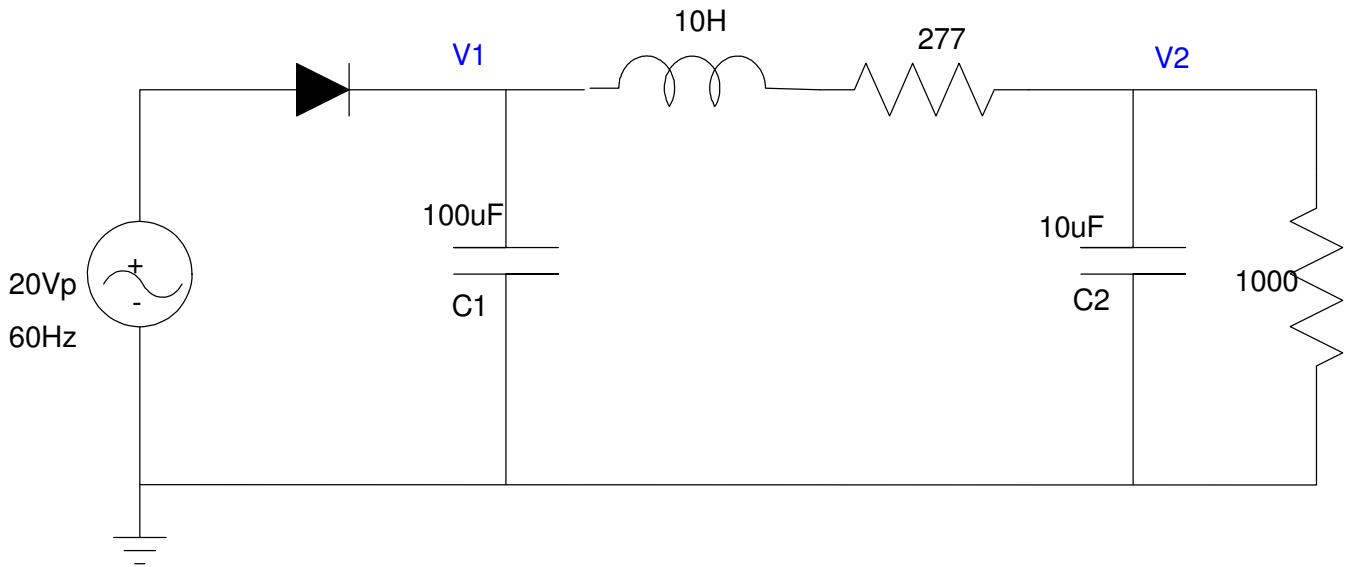- 
- 7) Determine C1 and C2 so that AC voltages are:  $V1 = 2V_{pp}$  and  $V2 = 250mV_{pp}$ .
  - 8) Build this circuit in CircuitLab (or similar program) and verify your calculations for problem #7



Circuit for problems 5 - 9