

ECE 320 - Homework #5

555 Timers, Transistors used as a Switch, Schmitt Triggers. Due Monday, Sept 27th

Assume a 3904 transistor (NPN) and 3906 (PNP) (\$0.04 each)

$$\beta = 100 \quad \min(|V_{ce}|) = 0.2V \quad \max(I_c) = 200mA$$

Assume a thermistor with

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

Transistor Switch

1) For the circuit shown below

- Assume $V_1 = 5V$. Determine I_b , I_c , V_b , and V_c .
- Assume $V_1 = 0V$. Determine I_b , I_c , V_b , and V_c .

2) Using CircuitLab, determine $\{I_b, I_c, V_b, \text{ and } V_c\}$ for

- $V_1 = 0V$
- $V_1 = 5V$


Is the transistor turning on ($V_c = 0.2V$) and off ($I_c = 0$)?

3) Simulate the circuit with the 555 timer in CircuitLab.

- What frequency should you hear at the speaker?

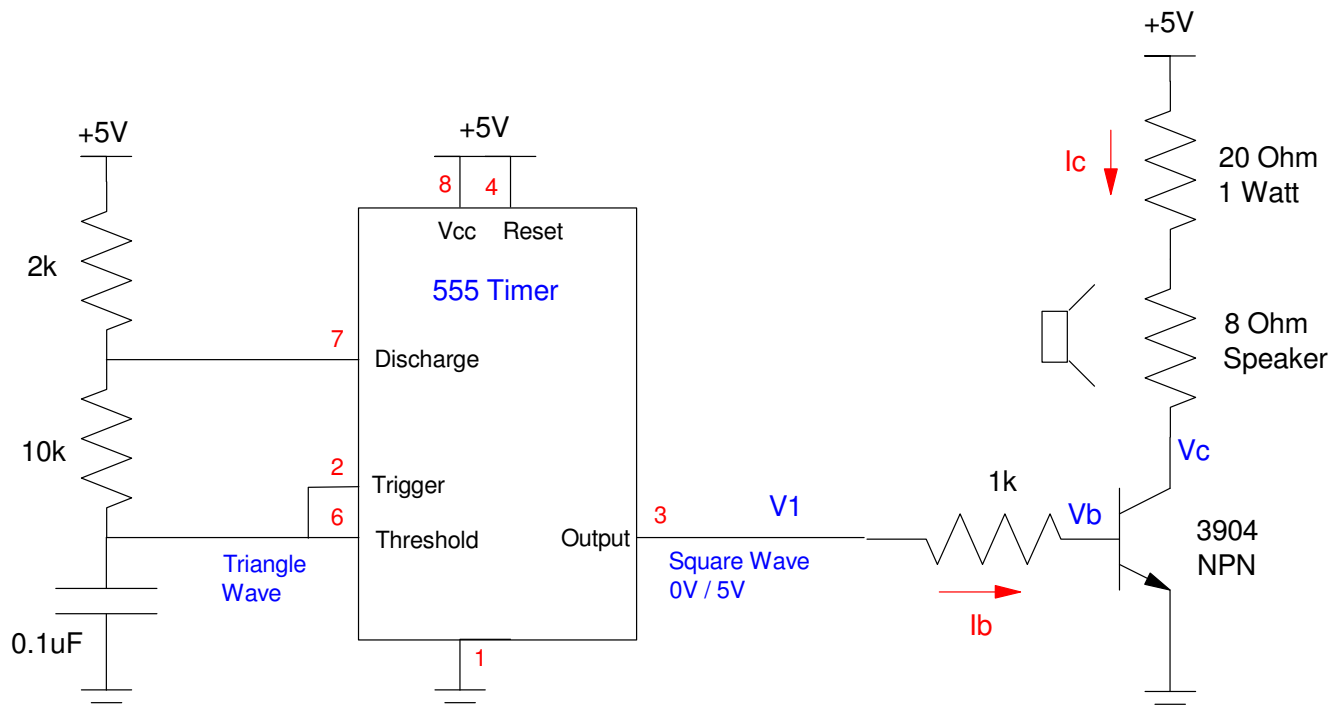4) Build this circuit with your lab kits and verify

- The frequency at V_1
- That the transistor is off when $V_1 = 0V$ (connect the 1k resistor to ground rather than the 555 timer)
- That the transistor is saturated when $V_1 = 5V$ (connect the 1k resistor to +5V)
- That the speaker is loud and annoying (the transistor acts as an amplifier)



Circuit for problem 1 - 4

Comparator

Add an electronic switch to turn the speaker on and off

5) Design a comparator (shown in blue - don't add the red resistors (they are for a Schmitt trigger)) to

- Turn on the speaker ($V_2 = 5V$) when $T > 30C$, and
- Turn off the speaker ($V_2 = 0V$) when $T < 30C$

6) Simulate the comparator in CircuitLab to verify the on / off temperature (or resistance or voltage)

7) Build this circuit and verify it's on and off temperature (or voltage or resistance. Replace R with a potentiometer for test purposes)

Schmitt Trigger

Add an electronic switch to turn the speaker on and off

8) Design a Schmitt Trigger (modify section in blue) to

- Turn on the speaker ($V_2 = 5V$) when $T > 35C$, and
- Turn off the speaker ($V_2 = 0V$) when $T < 30C$

9) Simulate the comparator in CircuitLab to verify the on / off temperature (or resistance or voltage)

10) Build this circuit and verify it's on and off temperature (or voltage or resistance. Replace R with a potentiometer for test purposes)

