


ECE 320 - Quiz #4 - Name _____

Max/Min, Clipper, Transistors. Fall 2021

1) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 * \text{Birth Month} + \text{Birth Day}$. May 14th for example gives $R = 1514$ Ohms


| R | V1 | V2 | V3 | I4 | I5 |
|-------------------------|----|----|----|----|----|
| $1000 + 100 * Mo + Day$ | | | | | |
| | | | | | |

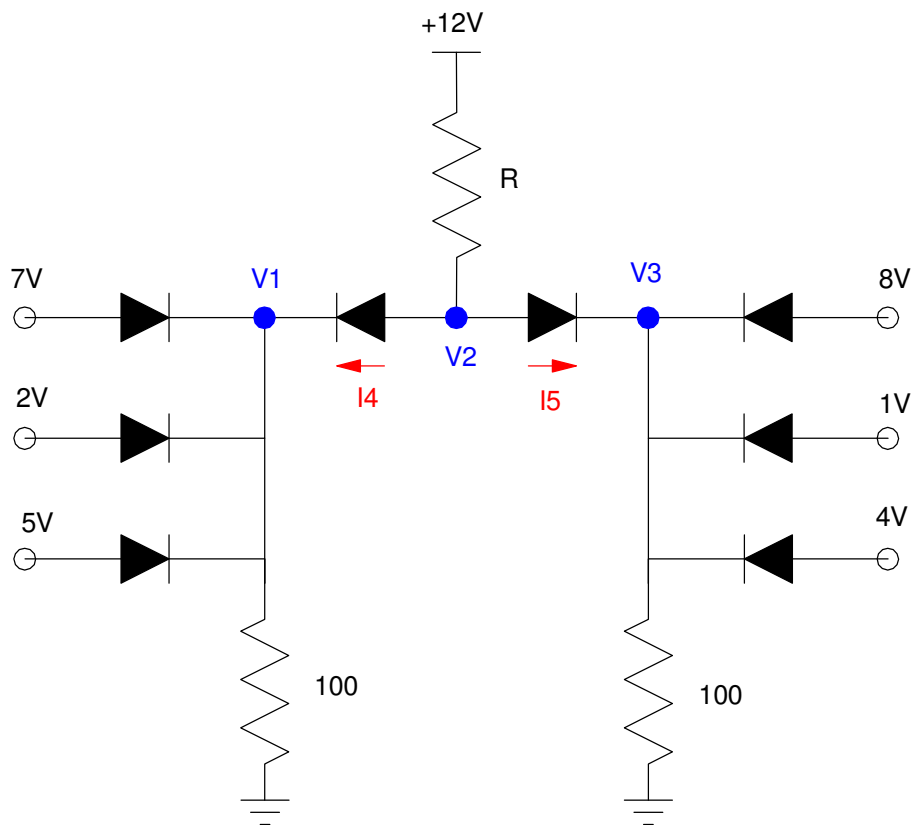

2) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 * \text{Birth Month} + \text{Birth Day}$. May 14th for example gives $R = 1514 \text{ Ohms}$



| R 1000 + 100*Mo + Day | V1 | V2 | V3 | I4 | I5 |
|--------------------------|----|----|----|----|----|
| | | | | | |

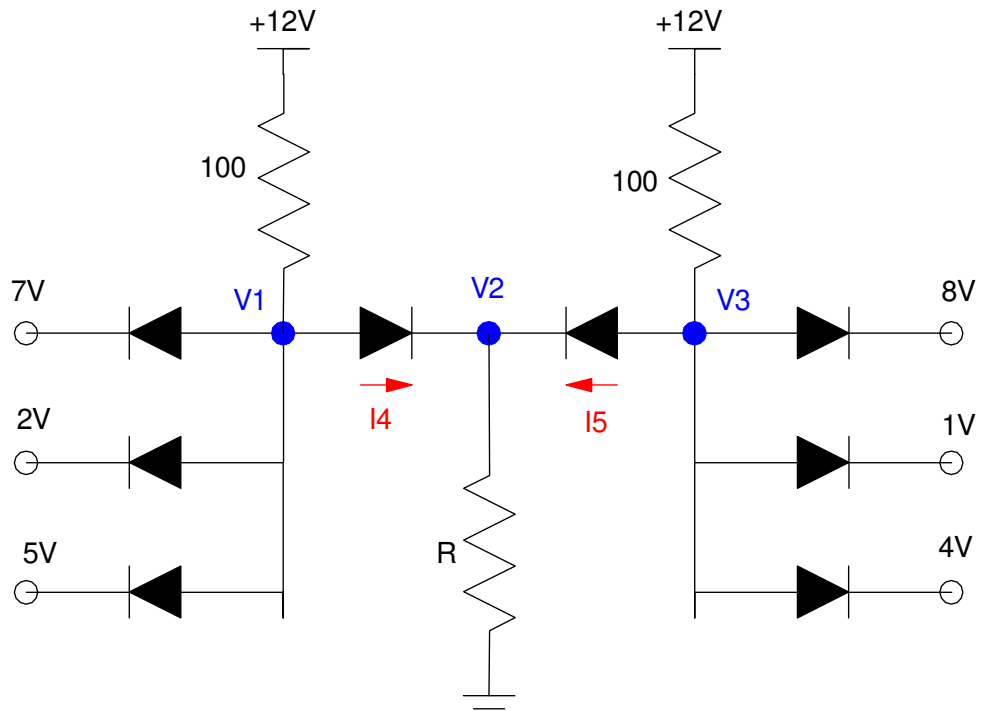

3) Clipper: Determine {R0, R1, R2, Vz1, Vz2} to implement the following function.

- Let R3 be 1000 + 100 * your birth month + your birth day. May 14th would give R = 1514 Ohms.

| R3 1000 + 100*Mo + Day | R0 | Vz1 | R1 | Vz2 | R2 |
|---------------------------|----|-----|----|-----|----|
| | | | | | |

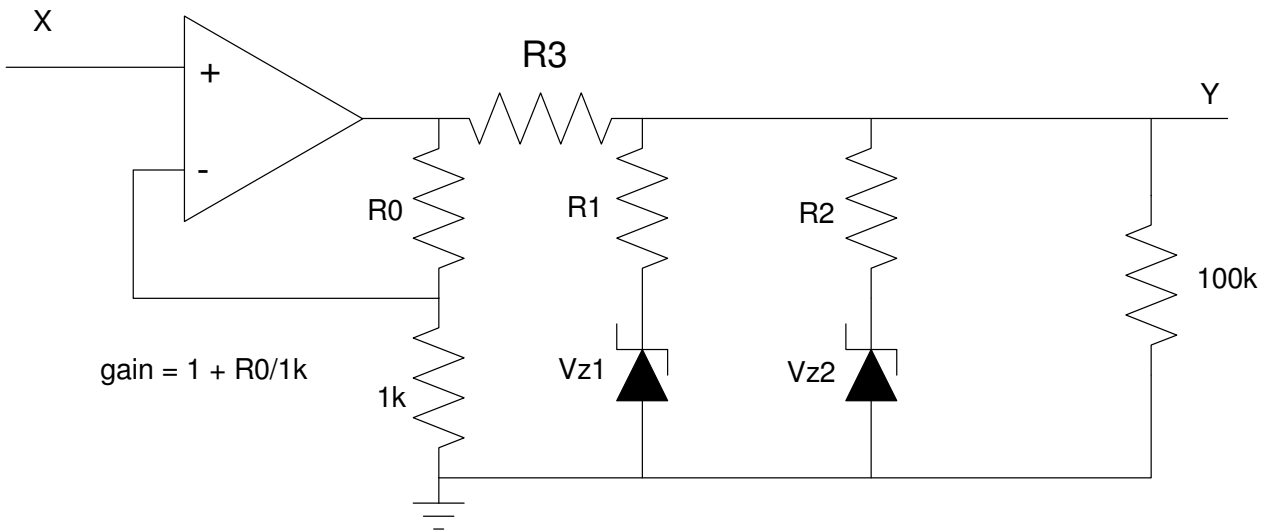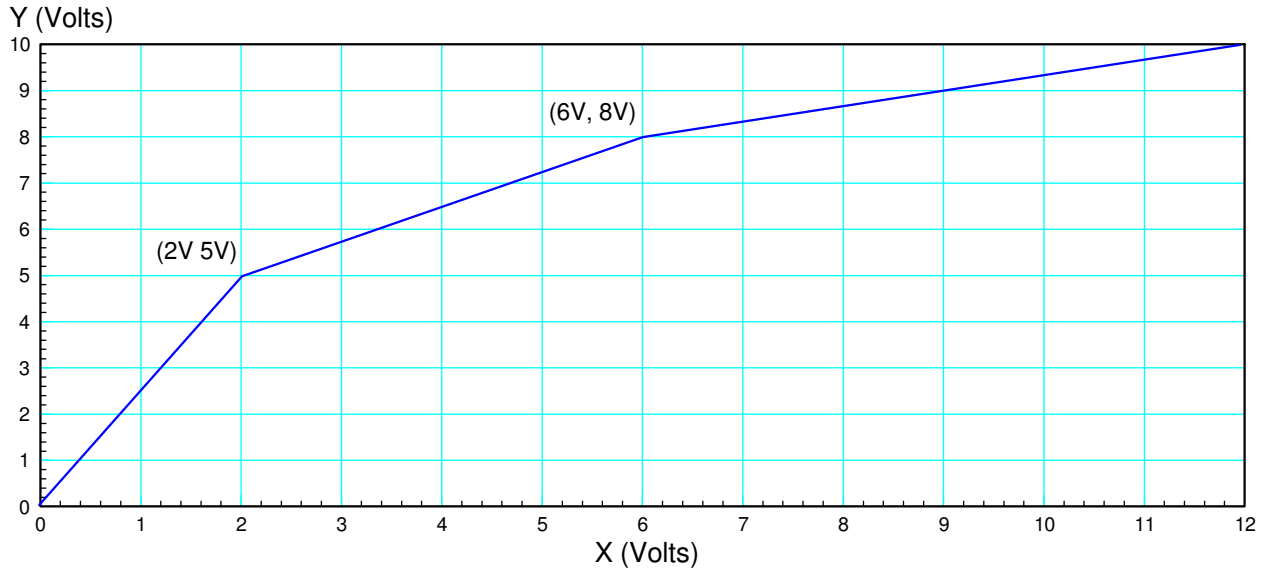

4) Clipper: Design a circuit to clip the voltage at +7V and -3V

$$y = \begin{cases} +3V & x > 3 \\ x & -6 < x < 3 \\ -6V & x < -6 \end{cases}$$


5) The VI characteristics for an NPN transistor are shown below

- Draw the load line for the following circuit
- Show on the load line the operating point (V_{ce} , I_c) when $V_{in} = 4V$ & $8V$.

Assume

- $V_{be} = 0.7V$
- $V_{ce} = 0.2V$ when saturated

| R 1000 + 100*Mo + Day | Load Line | $V_{in} = 4.0V$ | $V_{in} = 8.0V$ |
|--------------------------|--|---|---|
| | x and y intercept or show on graph | V_{ce} and I_c or show on graph | V_{ce} and I_c or show on graph |

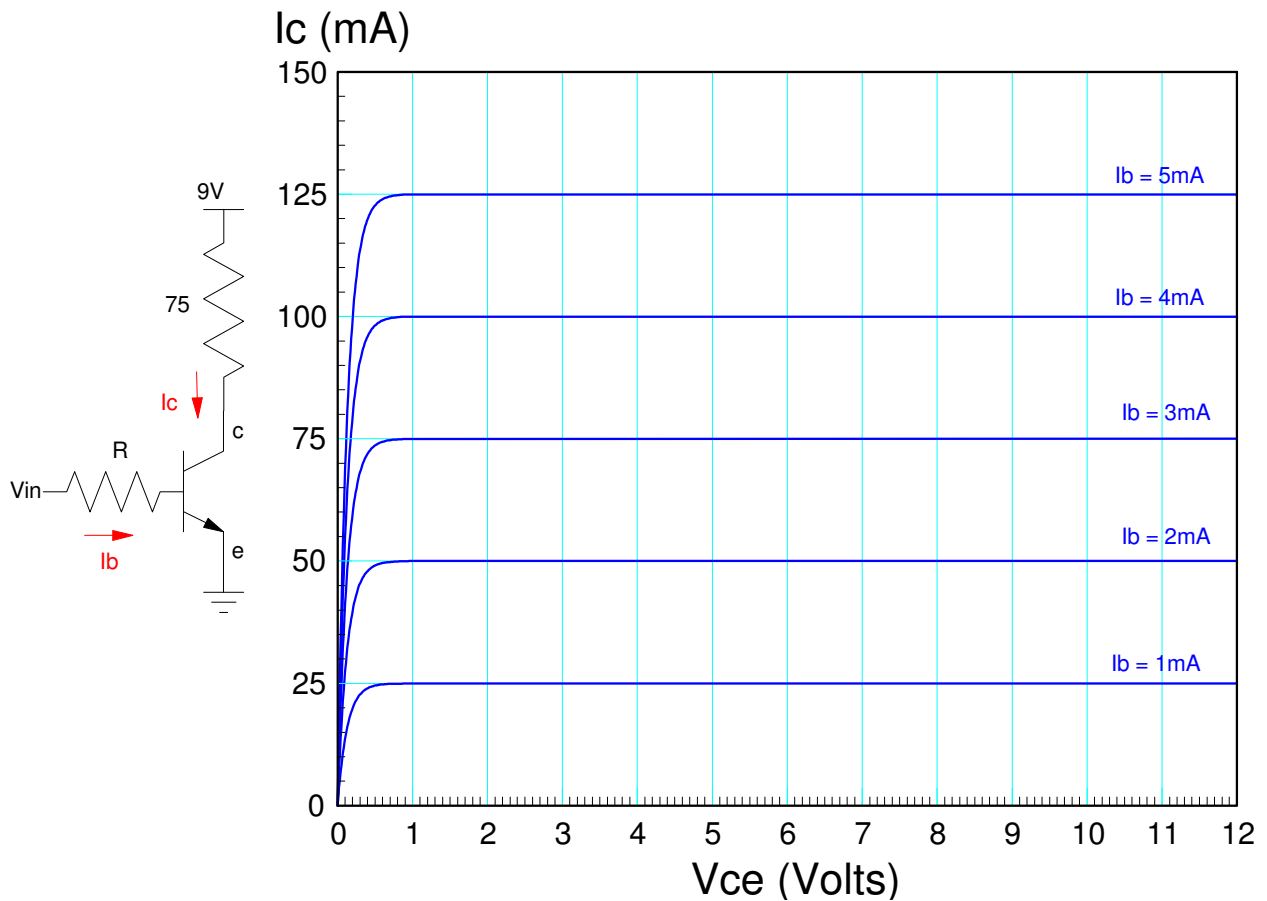

6) The voltages for the following circuit are measured (shown below). From these measurements, determine the following:

| R 1000 + 100*Mo + Day | I _b (mA) | I _c (mA) | Current Gain (beta) | Operating Region off / active / saturated |
|--------------------------|---------------------|---------------------|---------------------|--|
| | | | | |

