

ECE 320 - Quiz #7 - Name _____

DC to AC, SCR, Boolean Logic

DC to AC Converter

1) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)
- Energy = $\frac{1}{2}(a_n^2 + b_n^2)$ Watts (assuming a 1 Ohm resistor)

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	5 birth month	5	3	0	0
bn (sine)	0	14 Birth Date	0	0	2	0
$E = \frac{1}{2}(a^2 + b^2)$	0	110.5	12.5	4.5	2	0

Determine the following:

Total Energy in the signal	Energy in the 1st harmonic	Efficiency % of energy in the 1st harmonic
129.5W	110.5W	85.3%

DC to AC Converter: Differential equations for a Circuit

2) Determine the differential equations which describe the following circuit.

Assume

- $R_1 = 1..12$ Ohms (your birth month)
- $R_2 = 1..31$ Ohms (your birth date)

$$I_1 = C_1 \frac{dV_1}{dt} = 0.01 \cdot \frac{dV_1}{dt} = \left(\frac{V_0 - V_1}{20} \right) - I_3$$

$$I_2 = C_2 \frac{dV_2}{dt} = 0.02 \cdot \frac{dV_2}{dt} = I_3 - \frac{V_2}{14}$$


$$V_3 = L \frac{dI_3}{dt} = 0.1 \cdot \frac{dI_3}{dt} = V_1 - V_2 - 5I_3$$

solving

$$\frac{dV_1}{dt} = 5V_0 - 5V_1 - 100I_3$$

$$\frac{dV_2}{dt} = 50I_3 - 3.571V_2$$

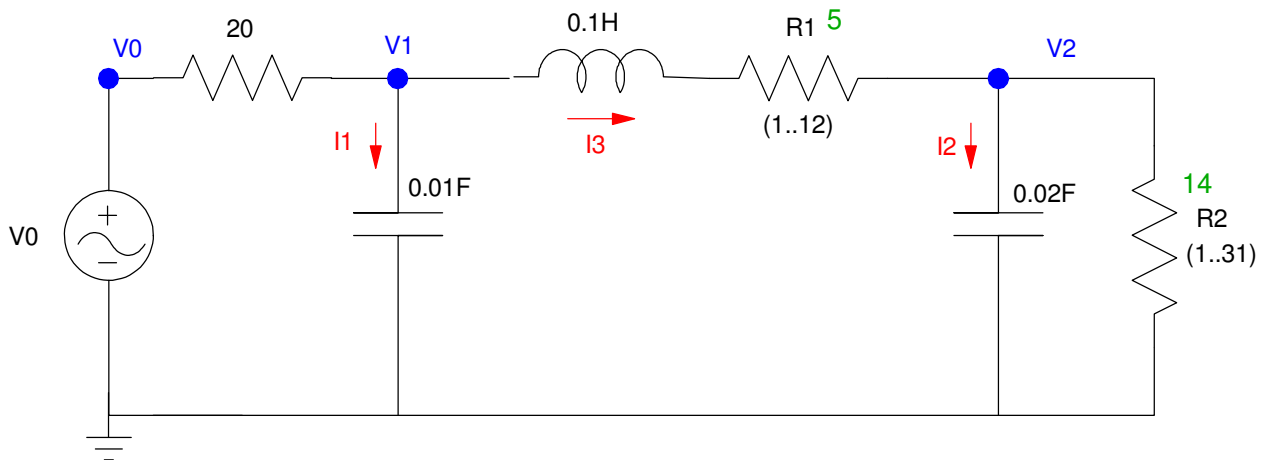
$$\frac{dI_3}{dt} = 10V_1 - 10V_2 - 50I_3$$



SCR (5 diode version)

3) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume a firing angle of 85 degrees.

R 1000 + 100*Mo + Day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)
1514	5.979V	19.3Vpp	5.281V	1.860Vpp

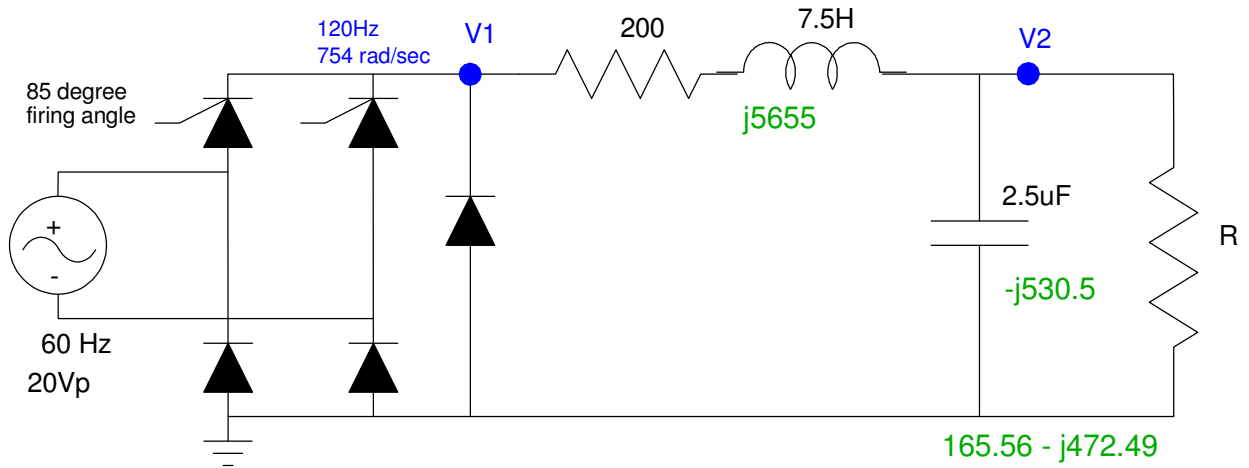

$$V_1(DC) = \left(\frac{18.6+0.7}{\pi} \right) \cdot (1 + \cos(85^\circ)) - 0.7 = 5.979V$$

$$V_2(DC) = \left(\frac{1514}{1514+200} \right) 5.979V = 5.281V$$

$$V_1(AC) = 19.3V_{pp}$$


$$V_2(AC) = \left(\frac{165.56-j472.49}{(165.56-j472.49)+(200+j5655)} \right) 19.3V_{pp}$$

$$V_2(AC) = 1.860V_{pp}$$

4) SCR Design. Determine the firing angle and C so that

- $V_2(\text{DC}) = 9.00\text{V}$
- $V_2(\text{AC}) = 1.00\text{V}_{pp}$
- $R = 1000 + 100 * (\text{Birth Month}) + (\text{Birth Day})$. May 14th would give $R = 1514\ \text{Ohms}$.

V1(DC)	Firing Angle	C	R 1000 + 100*Mo + Day
10.189V	39.42 deg	4.33uF	1514

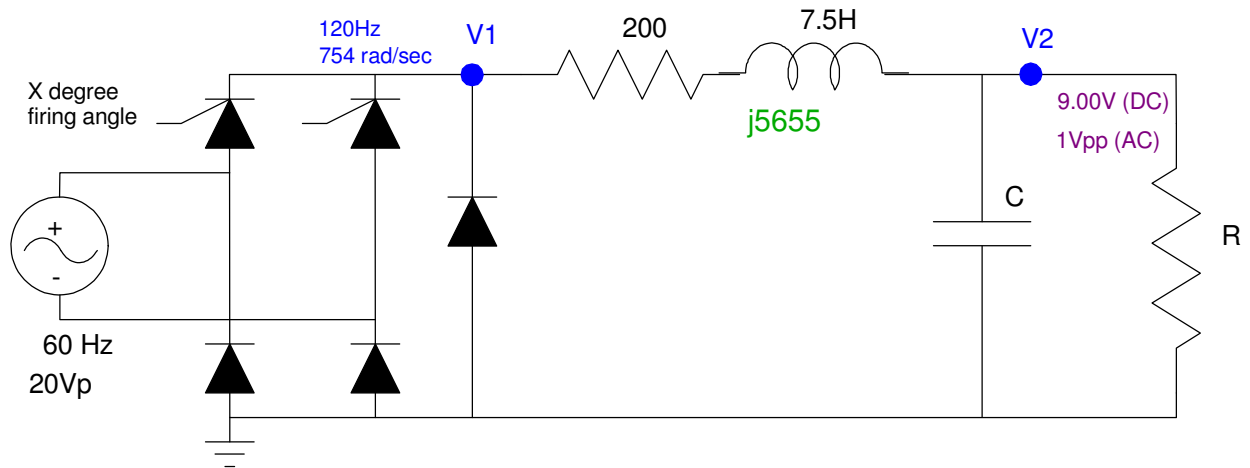

$$V_2 = 9.00\text{V}$$

$$V_1 = \left(\frac{1514+200}{1514} \right) 9.00\text{V} = 10.189\text{V}$$

$$10.189\text{V} \approx \left(\frac{18.6+0.7}{\pi} \right) \cdot (1 + \cos(\theta)) - 0.7$$

$$\theta = 39.425^\circ$$

If $C = 0$

$$V_2 = \left(\frac{1514}{(1514)+(200+j5655)} \right) 19.3\text{V}_{pp}$$

$$V_2 = 4.945\text{V}_{pp}$$

For $V_2 = 1\text{V}_{pp}$

$$\left| \frac{1}{j\omega C} \right| = \left(\frac{1\text{V}_{pp}}{4.945\text{V}_{pp}} \right) 1514\Omega = 306\Omega$$


$$C = 4.33\mu\text{F}$$

5) Design a circuit using NAND gates to implement the following logic

- hint: Circle the ones

f(A,B,C,D)		CD			
		00	01	11	10
AB	00	x	1	x	0
	01	1	x	0	0
	11	0	1	1	0
	10	1	x	x	x
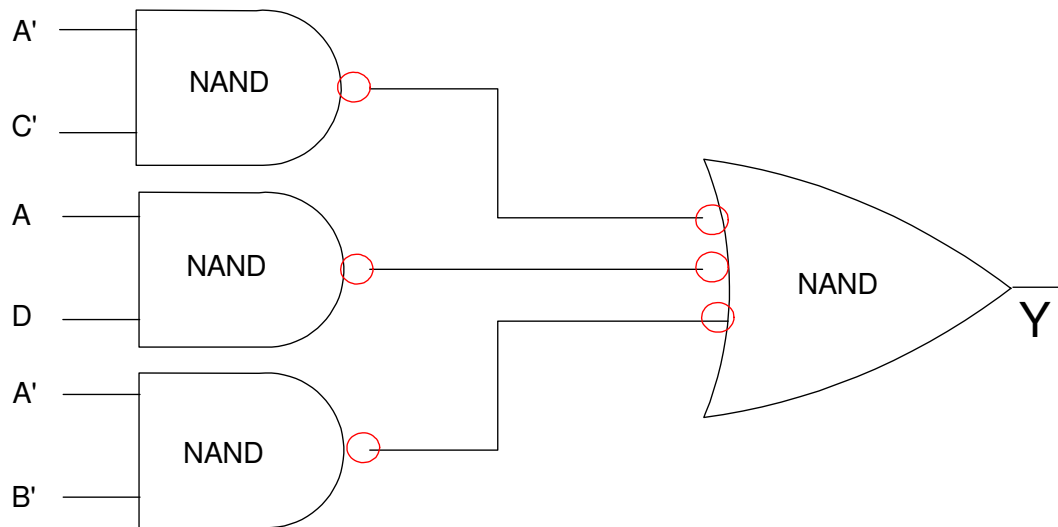
$$Y = \overline{A}C + AD + A\overline{B}$$



6) Design a circuit using NOR gates to implement the following logic

- hint: Circle the zeros

f(A,B,C,D)		CD			
		00	01	11	10
AB	00	x	1	x	0
	01	1	x	0	0
	11	0	1	1	0
	10	1	x	x	x

$$\bar{Y} = \bar{A}C + AB\bar{D}$$

$$Y = (A + \bar{C})(\bar{A} + \bar{B} + D)$$

