

# ECE 320 - Quiz #8 - Name \_\_\_\_\_


DTL, TTL Logic, MOSFETs.

## DTL Logic Gate:

Determine the voltges and currents for the following DTL gate. Assume

- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ , gain = 100)
- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

$R$ $1000 + 100*\text{mo} + \text{day}$	$V_1$	$I_2$	$V_3$	$I_4$	$V_5$
<b>1514</b>	<b>0</b>	<b>0</b>	<b>4.894V</b>	<b>69.86uA</b>	<b>0.2V</b>

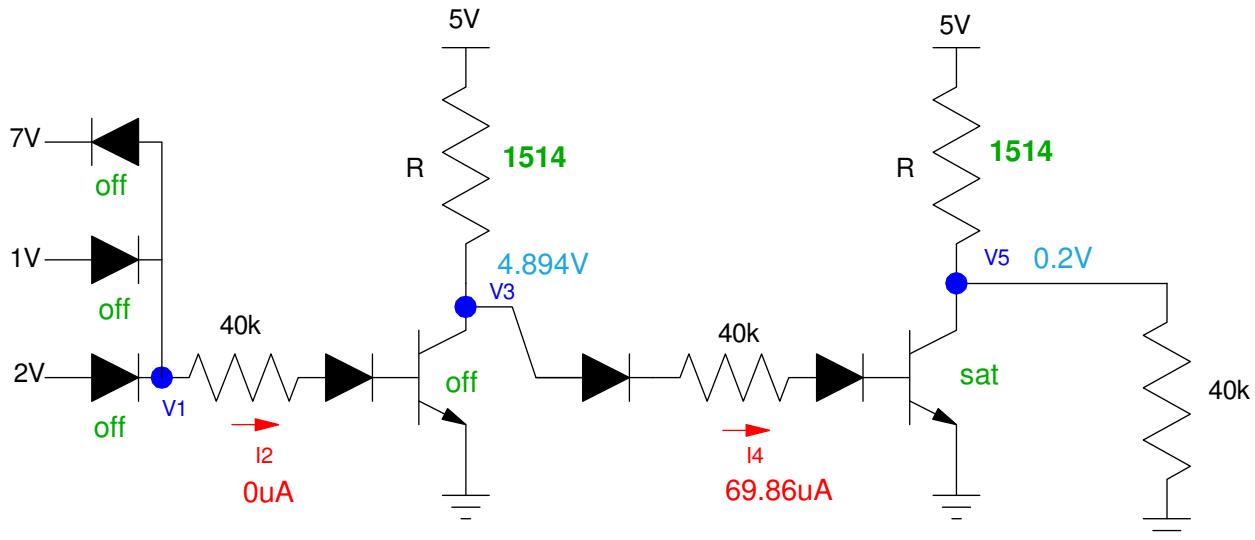

The diodes on the left are all off

- The diode to 7V is reversed, so it's off
- The other two diodes need 2.1V to overcome the three diodes to ground

This results in

- $V_1 = 0$
- $I_2 = 0$

To find  $I_4$  and  $V_3$ :

$$I_4 = \left( \frac{5V - 2.1V}{40k + 1514} \right) = 69.86\mu A$$

$$V_3 = 5V - 1514\Omega \cdot 69.86\mu A = 4.894V$$

$V_5$  is saturated:  $I_4$  allows 6.986mA to flow through the second transistor.  $R$  limits the current to 3.3mA


$$\beta I_b > I_c \quad \text{saturated}$$

## DTL Logic Gate:

Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ , gain = 100)
- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

$R$ $1000 + 100\text{mo} + \text{day}$	$V_1$	$I_2$	$V_3$	$I_4$	$V_5$
<b>1514</b>	<b>5.30V</b>	<b>97.50uA</b>	<b>0.2V</b>	<b>0uA</b>	<b>4.818V</b>

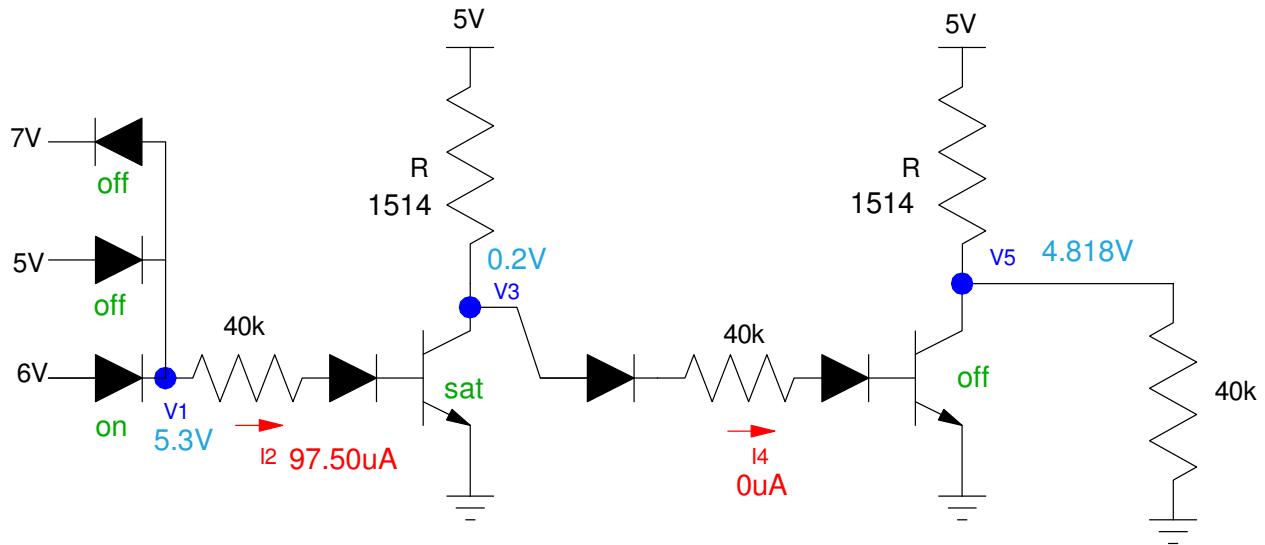


## Open Collector Logic

Determine the voltages and currents for the following circuit. Assume

- Ideal silicon diodes ( $V_f = 0.7V$ )
- $V_{be} = 0.7V$
- $\beta = 100$
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

$R$ $1000 + 100*\text{mo} + \text{day}$	$I_1$	$I_2$	$I_3$	$V_4$
<b>1514</b>	<b>0</b>	<b>90uA</b> allows 9mA	<b>90uA</b> allows 9mA	<b>0.2V</b> 9mA > 7.794mA

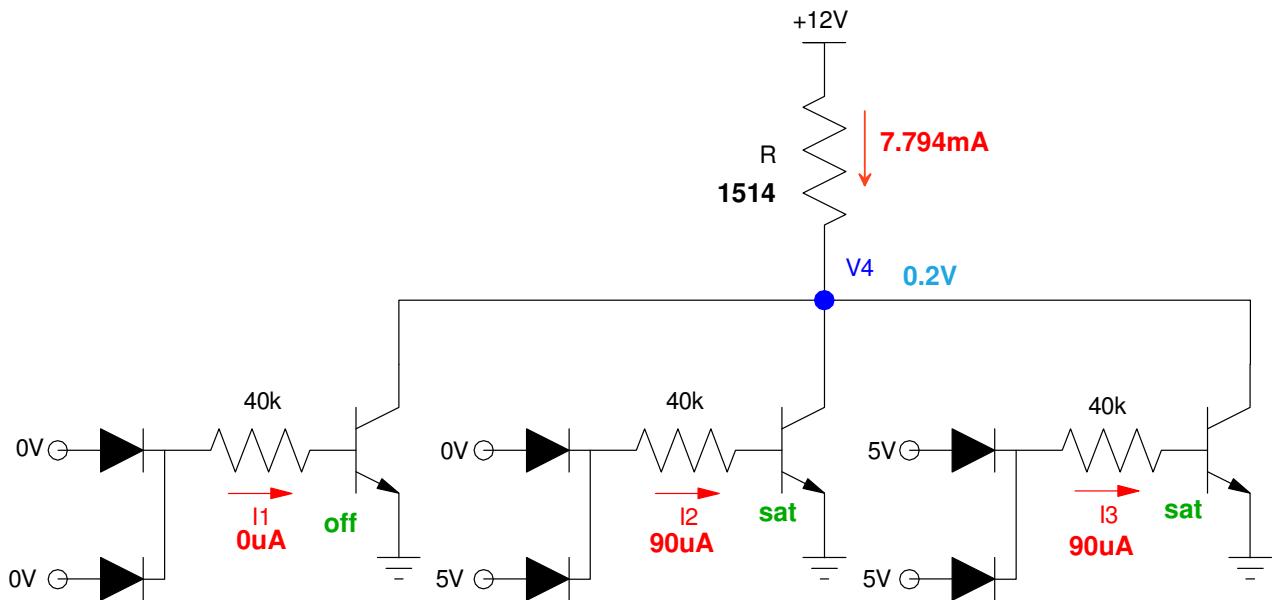


## TTL Logic

Determine the voltges and currents for the following DTL gate. Assume

- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ ,  $\beta = 2$  (left) or 100 (right) transistor)
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

$R$ $1000 + 100\text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$	$I_4$	$I_5$
<b>1514</b>	<b>1.4V</b>	<b>0.7V</b>	<b>0.2V</b>	<b>45uA</b> $I_c = 0.5 * I_b$	<b>135uA</b> $I_b + I_c$

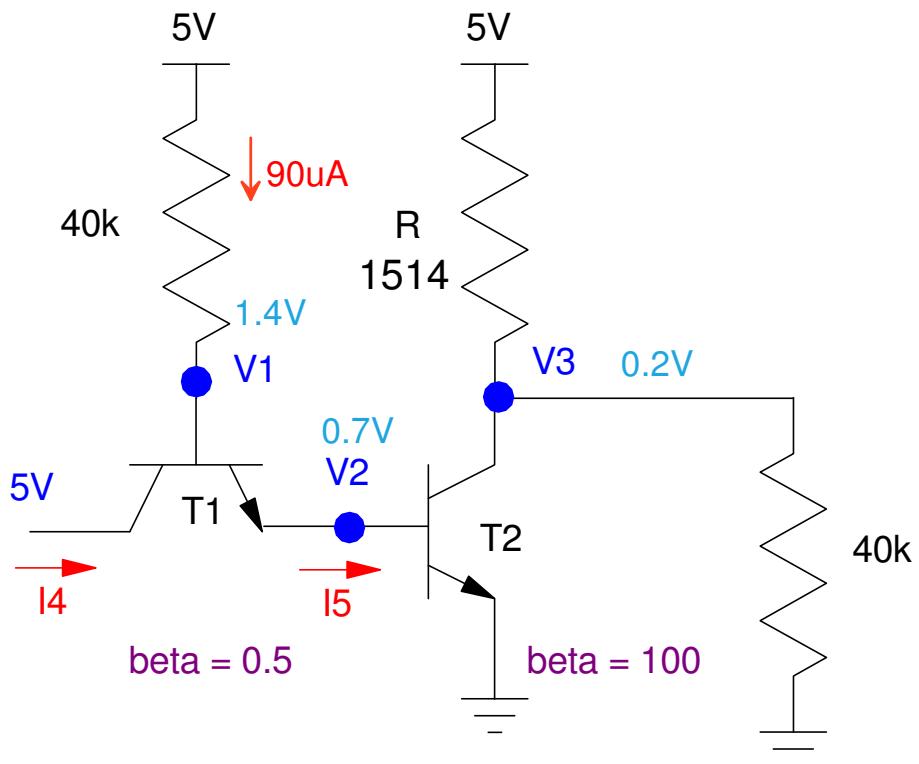


## MOSFET & Load Lines

For the following MOSFET

- Determine the transconductance gain,  $k_n$ ,
- Draw the load line for the following circuit.
- Mark the operating point for  $V_{gs} = 5V$

R 1000 + 100*mo + day	$k_n$ A / V <sup>2</sup>	Load Line show on graph	$V_{ds}$ $V_g = 5V$	$I_{ds}$ $V_g = 5V$
<b>1514</b>	<b>0.00075</b>	x-intercept = 10V y-intercept = 6.6mA	<b>3.6V</b> from graph	<b>4.2mA</b> from graph

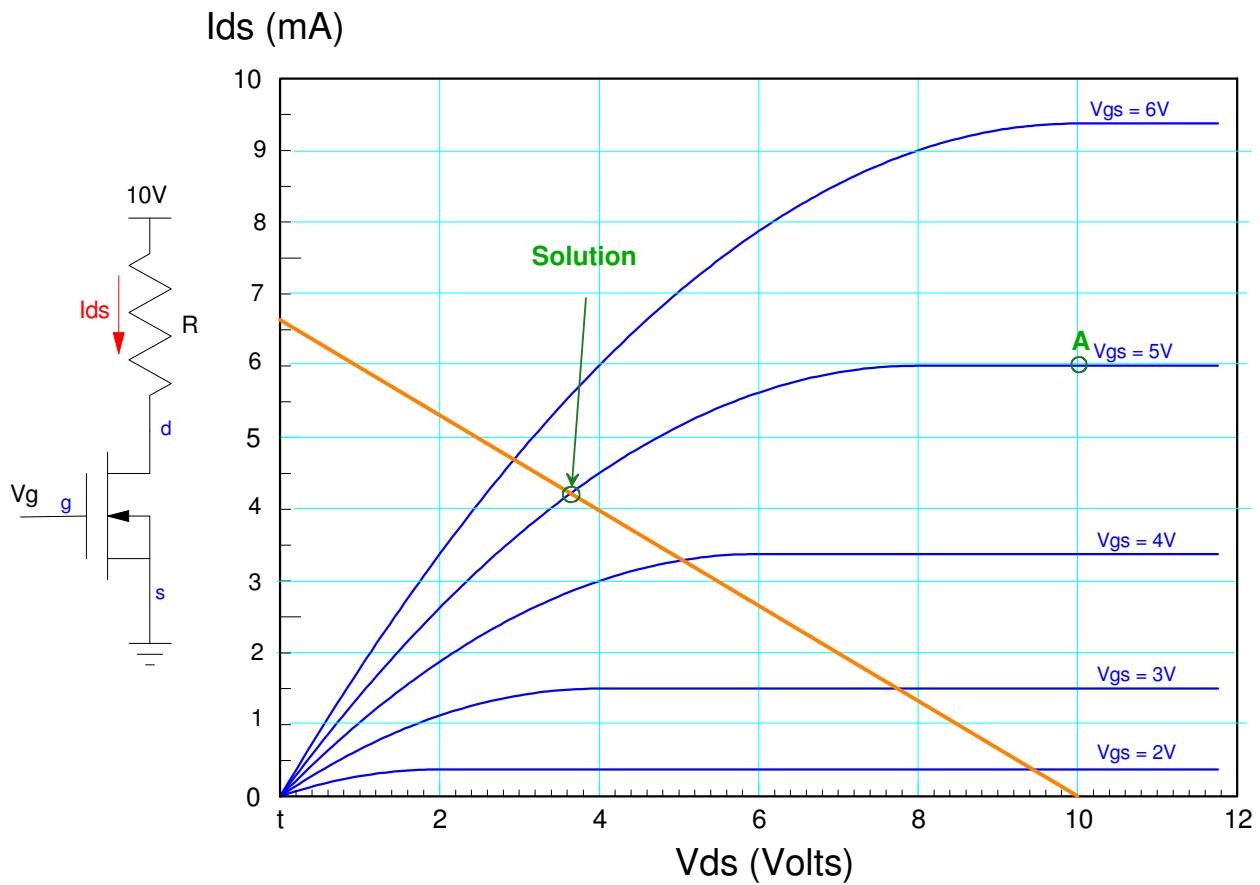

$k_n$ : Pick a point (A) in the saturated region

$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})^2$$

$$6mA = \frac{k_n}{2} (5V - 1V)^2$$

$$k_n = 0.75 \frac{mA}{V^2}$$

## MOSFETs

For the following MOSFET circuit, assume

- $k_n = 0.5 \text{ A/V}^2$
- $V_{th} = 2.00\text{V}$

Determine the operation point ( $V_{ds}$ ,  $I_{ds}$ ) for  $V_g = 10\text{V}$


$R$ $1000 + 100*\text{mo} + \text{day}$	$V_{ds}$ $V_g = 10\text{V}$	$I_{ds}$ $V_g = 10\text{V}$
<b>1514</b>	<b>0.0016 V</b>	<b>6.6039 mA</b>

Ohmic Region:  $V_{ds} < V_{gs} - V_{th}$

$$I_{ds} = k_n \left( V_{gs} - V_{th} - \frac{V_{ds}}{2} \right) V_{ds}$$

Saturated Region:  $V_{ds} > V_{gs} - V_{th}$
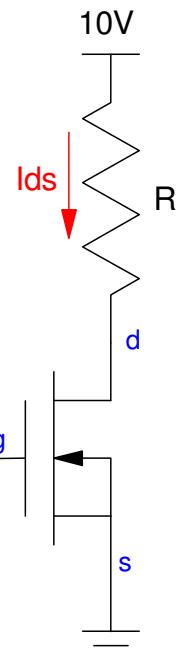
$$I_{ds} = \frac{k_n}{2} (V_{gs} - V_{th})_2$$



Assume ohmic, Write 2 equations for 2 unknowns

$$I_{ds} = 0.5 \left( 10 - 2 - \frac{V_{ds}}{2} \right) V_{ds}$$

$$V_{ds} + 1514I_{ds} = 10$$

Solving gives two solutions

$$I_{ds} = 6.6039\text{mA}$$

$$V_{ds} = 0.0016\text{V}$$

$$R_{ds} = V_{ds} / I_{ds} = 0.25 \text{ Ohms}$$

and

$$I_{ds} = -3.97\text{mA}$$

$$V_{ds} = 16.001\text{V}$$

The former is the correct solution