

# ECE 320 - Homework #2

Semiconductors, PN Junction, Ideal Diodes. Due Wednesday, September 8th

Please make the subject "ECE 320 HW#2" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Semiconductors

1) Why does the voltage drop across a pn junction decrease as temperature increases?

*As temperature increases, the number of thermal electrons / holes increases. This makes the n-type and p-type materials behave more and more like intrinsic (undoped) silicon. In the limit, when the doping no longer matters, the voltage drop will go to zero.*

2) What doping of Boron (p-type) do you need to make an 1206 resistor have a resistance of 2200 Ohms? The dimensions of an 1206 resistor are

$$L = 3.20\text{mm}, W = 1.60\text{mm}, H = 0.95\text{mm}$$

$$R = \frac{\rho L}{A}$$

$$2200\Omega = \frac{\rho \cdot 0.32\text{cm}}{0.16\text{cm} \cdot 0.095\text{cm}}$$

$$\rho = 104.5 \Omega \cdot \text{cm}$$

$$\sigma = \frac{1}{\rho} = 0.009596 = n_p \cdot q \cdot \mu_p$$

$$0.009596 = n_p \cdot (1.6 \cdot 10^{-19}) \cdot (500)$$

$$n_p = 1.196 \cdot 10^{14} \text{ atoms / cc}$$

3) A thermistor has the following resistance - voltage relationship

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees C. What is the resistance at

-48F Coldest day in Fargo (Jan 8, 1887)

- T = -44.44C
- R = 53,599 Ohms

0F Recommended temperature of a freezer

- T = -17.78C
- R = 8922.3 Ohms

+40F Recommended temperature of a refrigerator

- T = 4.44C
- R = 2640.2 Ohms

+114F Hottest day in Fargo (Jul 6, 1936)

- T = 45.56C
- R = 429.3 Ohms

## Diode VI Characteristics


Assume the VI characteristics for a diode are

$$V_d = 0.052 \cdot \ln\left(\frac{I_d}{10^{-8}} + 1\right) \quad I_d = 10^{-8} \left(\exp\left(\frac{V_d}{0.052}\right) - 1\right)$$

4) For the 1-diode circuit (next page - 200 Ohms is red - black - brown )

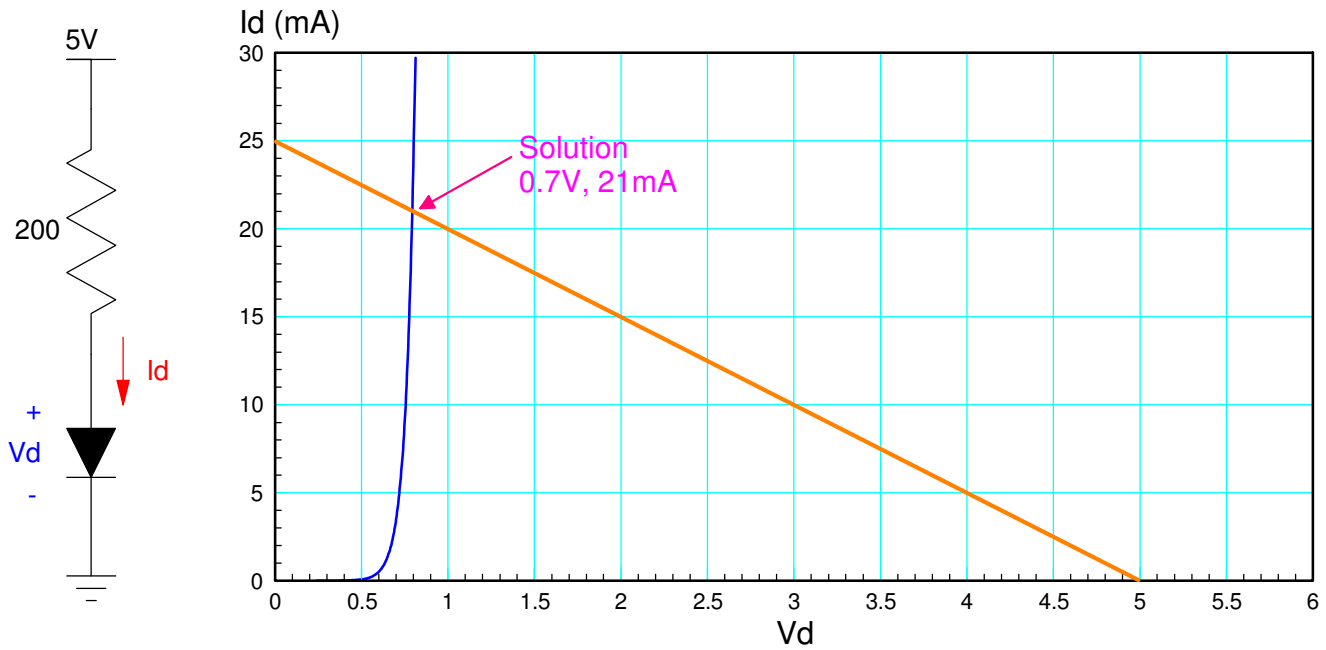a) Draw the load-line for the following circuit (next page). Determine  $V_d$  and  $I_d$  from the graph.

- When  $I_d = 0$ ,  $V_d = 5V$
- When  $V_d = 0$ ,  $I_d = 5V / 200 \text{ Ohms} = 25\text{mA}$



b) Write the voltage node equations and solve for  $V_d$  and  $I_d$  assuming the VI equations above

There are 2 unknowns ( $V_d$ ,  $I_d$ ). We need 2 equations for 2 unknowns. One is the diode equation

$$V_d = 0.052 \cdot \ln\left(\frac{I_d}{10^{-8}} + 1\right)$$

The second is a current loop equation (voltage nodes also works)

$$V_d + 200I_d = 5$$

Solving using `fminsearch` in Matlab. First, create a function where you

- Guess  $V_d$
- From  $V_d$ , compute the  $I_d$  using the blue and orange line
- Return the square of the distance between the two

```
function [ J ] = Diode1( z )  
  
Vd = z(1);  
Idss = 1e-8;  
nVt = 0.052;  
Id1 = Idss* exp( Vd/nVt - 1 );  
Id2 = (10 - Vd) / 200;  
e1 = (Id1 - Id2)*1000; % mA  
J = (e1)^2;  
disp([z, log10(J)])  
pause(0.1);  
end
```

Solving using `fminsearch()` in Matlab:

```
>> [V, e] = fminsearch('Diode1',2)  
2.0000    22.5387  
2.1000    24.2090  
1.9000    20.8683  
1.8000    19.1980  
1.6000    15.8572  
1.4000    12.5165  
:  
:  
0.8496    -1.8885  
0.8495    -3.5884  
0.8494    -2.4549  
0.8495    -4.5133  
0.8495    -3.1325  
0.8495    -4.5574  
  
V =    0.8495  
e = 2.7705e-005
```

**ans:  $V_2 = 0.8495V$**

5) Determine  $V_d$  and  $I_d$  assuming an ideal silicon diode ( $V_f = 0.7V$ )

$$V_d = 0.7V$$

$$I_d = \frac{5V - 0.7V}{200\Omega} = 21.5mA$$

6) Build this circuit in CircuitLab and solve for  $V_d$  and  $I_d$ . (Use a 1N4004 diode)



	Vd	Id
4a) Graphical solution	0.7V	21mA
4b) Numeric Solution	0.8495 V	20.75mA
5) Ideal Diode	0.7V	21mA
6) Simulation (CircuitLab)	0.7252V	21.37mA
7) Lab (experimental)	0.729 V	21.36mA

Problem 4 to 7

Problem 8 - 10: Note: If you don't have four 100 Ohm resistors (10 - black - brown), replace the resistors with the ones you \*do\* have - ideally all the same and close to 100 Ohms. Do problems 8 - 11 using the resistors you use for the experimental results (problem #10).

8) Write the voltage node equations assuming ideal diodes. Solve for {V1, V2, and V3} using Matlab

$$I_{d1} = 10^{-8} \exp \frac{V_1 - V_2}{0.052} - 1$$


$$I_{d2} = 10^{-8} \exp \frac{V_2 - V_3}{0.052} - 1$$

$$I_{d3} = 10^{-8} \exp \frac{V_3}{0.052} - 1$$

$$\frac{V_1 - 5}{100} + I_{d1} + \frac{V_1 - V_2}{100} + \frac{V_1 - V_3}{100} + \frac{V_1}{100} = 0$$

$$-I_{d1} + I_{d2} + \frac{V_2 - V_1}{100} = 0$$
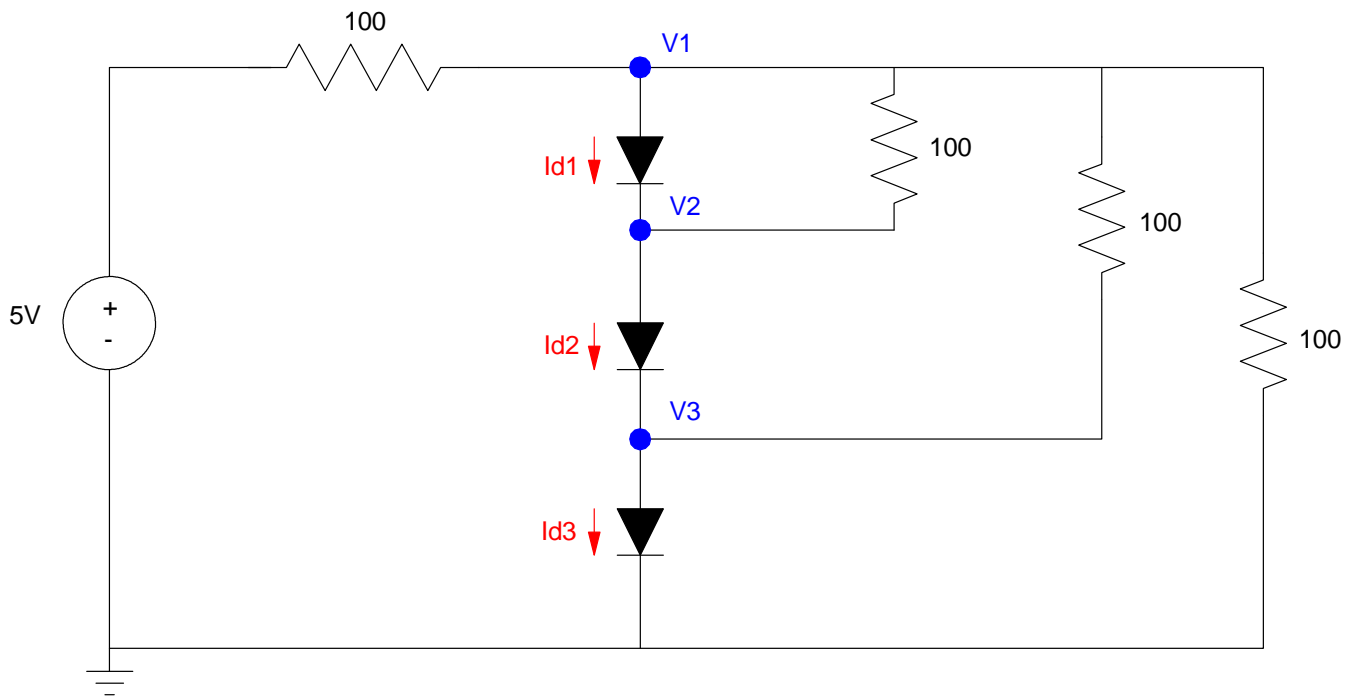
$$-I_{d2} + I_{d3} + \frac{V_3 - V_1}{100} = 0$$



Solve using Matlab. First, create a function

```
function [ J ] = Diode3( z )
V1 = z(1);
V2 = z(2);
V3 = z(3);

Idss = 1e-8;
nVt = 0.052;

Id1 = Idss* exp( (V1 - V2)/nVt - 1 );
Id2 = Idss* exp( (V2 - V3)/nVt - 1 );
Id3 = Idss* exp( (V3 - 0)/nVt - 1 );

e1 = (V1 - 5)/100 + Id1 + (V1-V2)/100 + (V1-V3)/100 + (V1/100);
e2 = (V2-V1)/100 - Id1 + Id2;
e3 = (V3-V1)/100 - Id2 + Id3;

J = (e1)^2 + (e2)^2 + (e3)^2;

disp([V1, V2, V3, log10(J)])
pause(0.1)

end
```

Solve for {V1, V2, V3} using fminsearch() in Matlab

```
>> [V,e] = fminsearch('Diode3',[3,2,1])

    V1      V2      V3      log10(error)
    3.0000    2.0000    1.0000    -0.2200
    3.1500    2.0000    1.0000     2.6161
    3.0000    2.1000    1.0000     1.7326
    :
    :
    2.5962    1.7348    0.8697    -8.8025
    2.5962    1.7349    0.8697    -9.4757

    V1      V2      V3
V =  2.5962  1.7349  0.8697


e =  3.3442e-010
```

9) Assume ideal silicon diodes. ( $V_f = 0.7V$ ). Define {V1, V2, and V3}.

Assume all diodes are on. Then

- $V_3 = 0.7V$
- $V_2 = 1.4V$
- $V_1 = 2.1V$

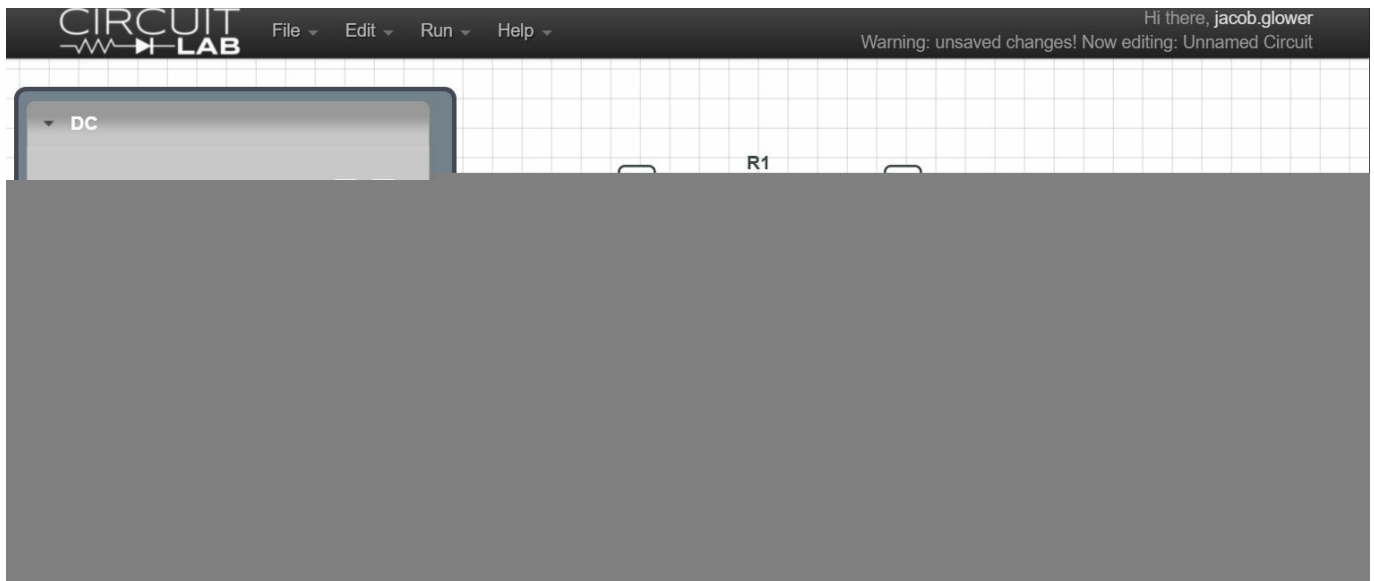10) Simulate this circuit in CircuitLab to determine {V1, V2, and V3}



11) Build this circuit with your breadboard and measure {V1, V2, V3}

- Include a photo to receive credit for problem #11



	V1	V2	V3
8) Numeric Solution	<b>2.5962 V</b>	<b>1.7349 V</b>	<b>0.8697 V</b>
9) Ideal Diode	<b>2.1 V</b>	<b>1.4 V</b>	<b>0.7 V</b>
10) Simulation (CircuitLab)	<b>1.771 V</b>	<b>1.373 V</b>	<b>0.710 V</b>
11) Lab (experimental)	<b>1.73V</b>	<b>1.359V</b>	<b>0.707V</b>