

ECE 320 - Homework #7


DC to AC, SCR, Boolean Logic. Due Monday, October 11th

DC to AC

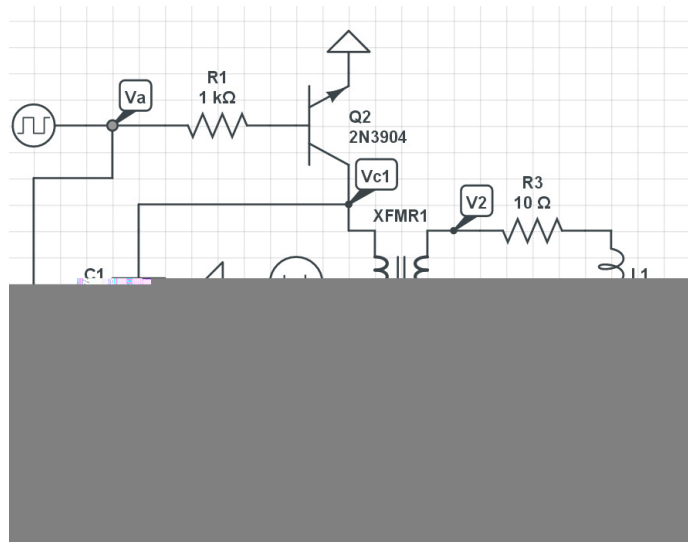1) Let

- $A = 0V / 5V$ square wave, 60Hz, 0 degree time delay
- $B = 0V / 5V$ square wave, 60Hz, 180 degree time delay
- $C1 = 10\mu F$

Determine using CircuitLab the voltage $V2$ (i.e. the voltage across a DC motor, modeled as a 10 Ohm & 100mH load)



2) Adjust C1 so that the voltage across the motor is as close to a sine wave as possible (trial and error)

In theory, resonance is

$$\omega = \frac{1}{\sqrt{LC}}$$

For 377 rad/sec (60Hz), L = 0.1H, C = 70uF. Adjusting to get a sine wave, C = 120uF

Simulation Results (problem 5)

```
>> DC = mean(V2)
      8.7647
```