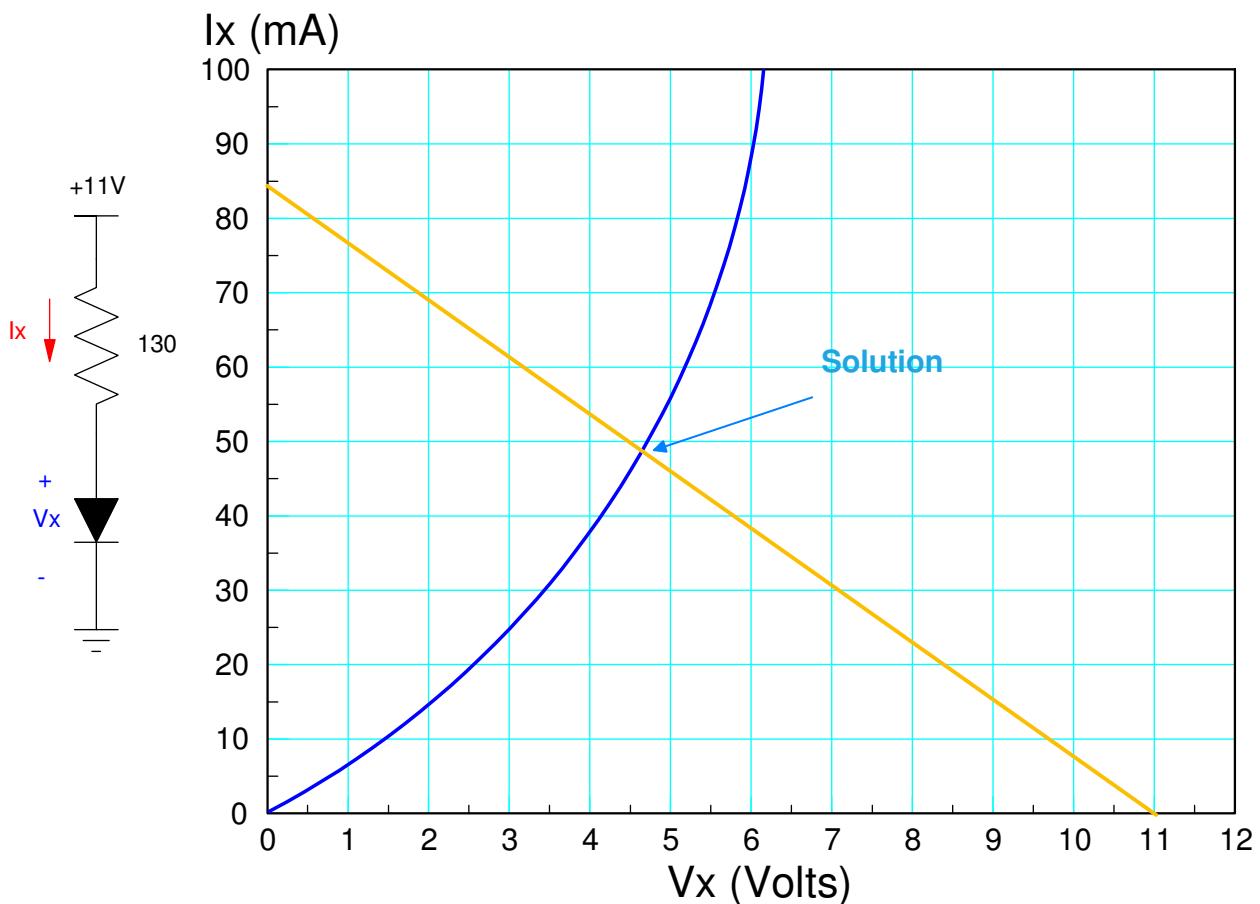


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

- 1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_x and V_x .

Load Line	V_x	I_x
show on graph	4.6V	48mA




2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.052 \ln(10^8 \cdot I_d + 1) \quad I_d = 10^{-8} \cdot \left(\exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

Write N equations to solve for N unknowns: {V1, V2, V3, V4, Id1, Id2, Id3}.

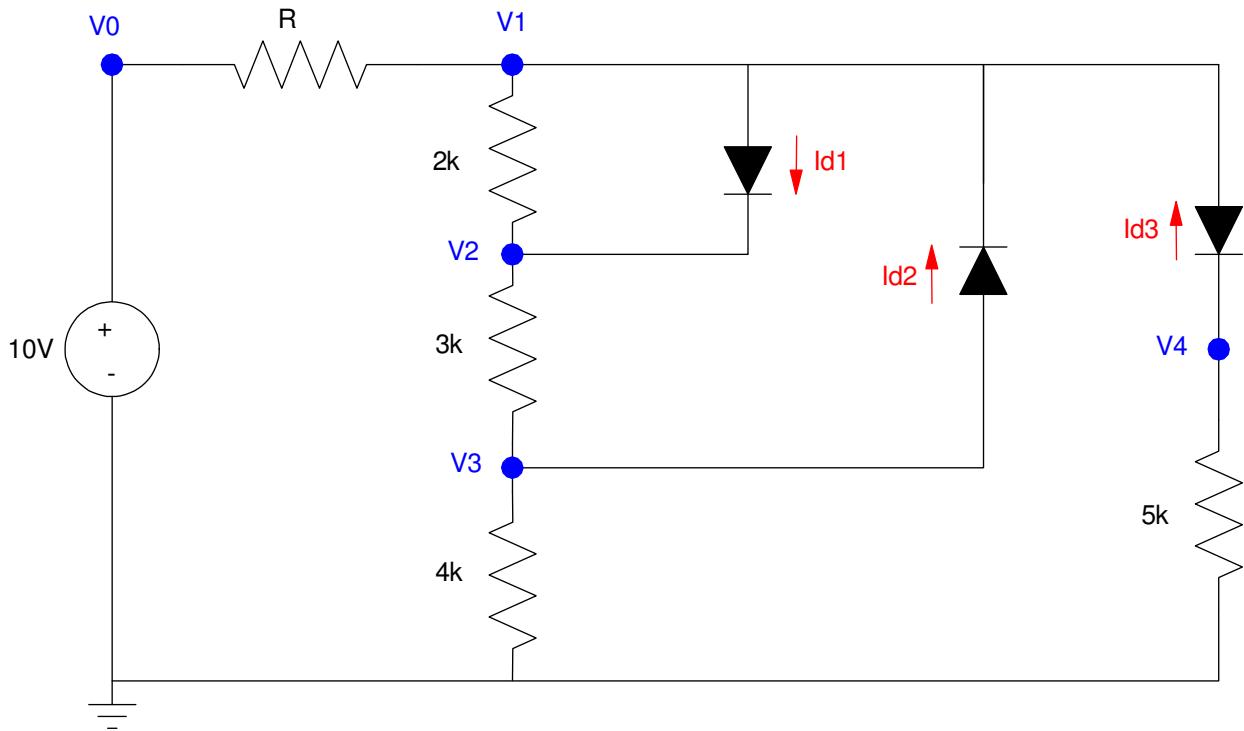- Note: you do not need to solve.
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.



$$I_{d1} = 10^{-8} \cdot \left(\exp\left(\frac{V_1 - V_2}{0.052}\right) - 1 \right)$$

$$I_{d2} = 10^{-8} \cdot \left(\exp\left(\frac{V_3 - V_1}{0.052}\right) - 1 \right)$$

$$-I_{d3} = 10^{-8} \cdot \left(\exp\left(\frac{V_1 - V_4}{0.052}\right) - 1 \right)$$

$$\left(\frac{V_1 - V_0}{R}\right) + \left(\frac{V_1 - V_2}{2k}\right) + I_{d1} - I_{d2} - I_{d3} = 0$$

$$\left(\frac{V_2 - V_1}{2k}\right) + \left(\frac{V_2 - V_3}{3k}\right) - I_{d1} = 0$$


$$\left(\frac{V_3 - V_2}{3k}\right) + \left(\frac{V_3}{4k}\right) + I_{d2} = 0$$

$$I_{d3} + \left(\frac{V_4}{5k}\right) = 0$$

3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 1000 + 100*(\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.

R $1000 + 100*\text{mo} + \text{day}$	V_1	V_2	V_3
1514	6.8221V	6.1221V	3.4983V

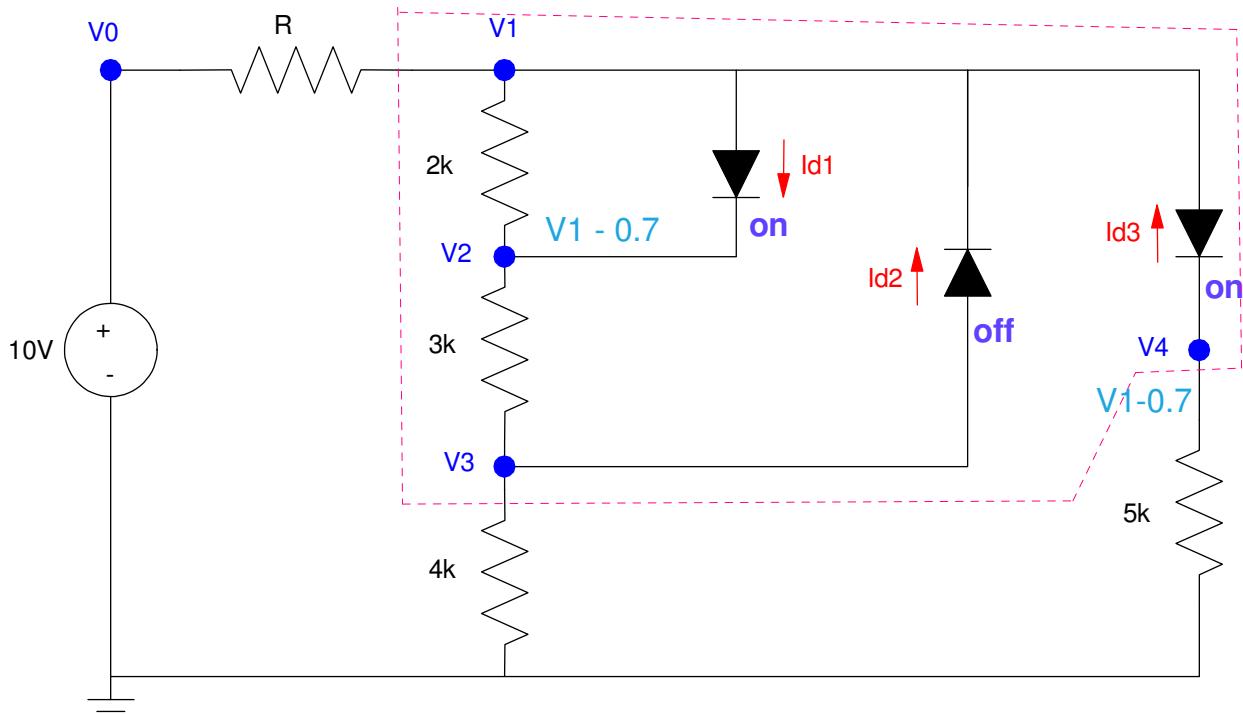

SuperNode

$$\left(\frac{V_1-10}{1514}\right) + \left(\frac{V_3}{4k}\right) + \left(\frac{V_1-0.7}{5k}\right) = 0$$

Node V_3

$$\left(\frac{V_3-(V_1-0.7)}{3k}\right) + \left(\frac{V_3}{4k}\right) = 0$$

Solving

$$V_3 = \left(\frac{4}{7}\right)(V_1 - 0.7)$$


$$V_1 = 6.8221V$$

$$V_2 = V_1 - 0.7 = 6.1221V$$

$$V_3 = 3.4983V$$

4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter

R	V1		V2	
	DC	AC	DC	AC
1514	12.91V	2.781V _{pp}	11.40V	1.077V _{pp}

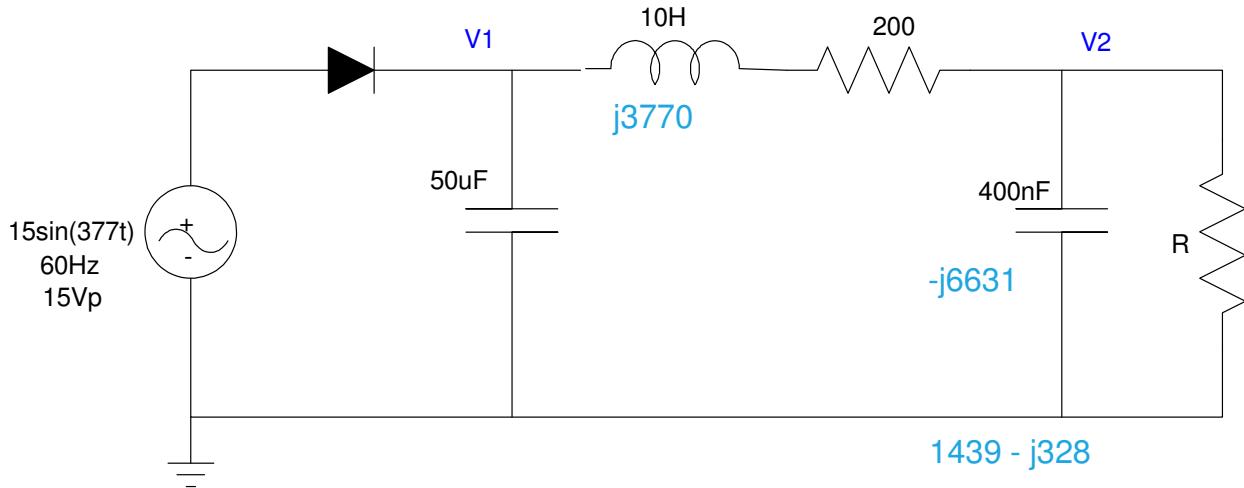

$$\max(V1) = 14.3V$$

$$I \approx \left(\frac{14.3V}{R+200} \right) = 8.34mA$$

$$I = C \cdot \frac{dV}{dt}$$

$$8.34mA = 50\mu F \cdot \frac{dV}{1/60s}$$

$$dV = 2.781V = V_{1pp}$$

$$V_1(DC) = 14.3V - \frac{1}{2} \cdot 2.781V_{pp} = 12.91V$$


$$V_2(DC) = \left(\frac{1514}{1514+200} \right) V_1(DC) = 11.40V$$

$$V_2(AC) = \left(\frac{1439-j328}{(1439-j328)+(200+j3770)} \right) V_1(AC) = 1.077V_{pp}$$

5) Max/Min: Analysis: Determine currents I1..I6. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100*(\text{your birth month}) + (\text{birth date})$



R	I1	I2	I3	I4	I5	I6
1514	0	9.29mA	3.303mA	0	20.6mA	0

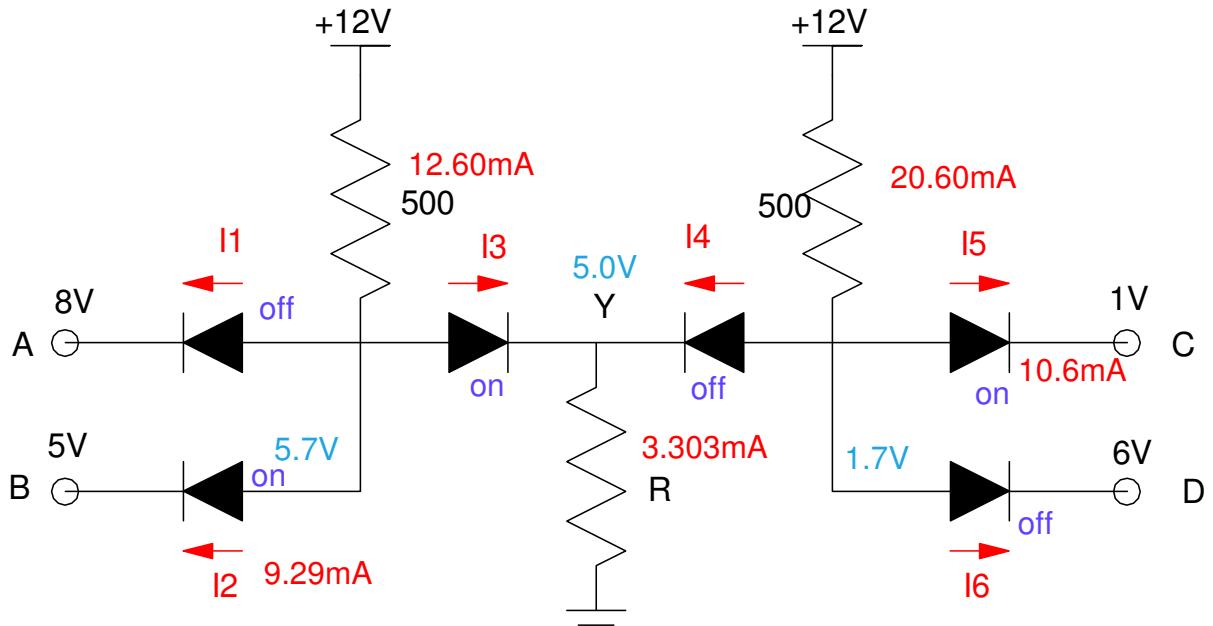

6) Clipper Design: Determine the resistor and zerner voltages to implement the following function

R0	Vz1	R1	Vz2	R2

Y (Volts)

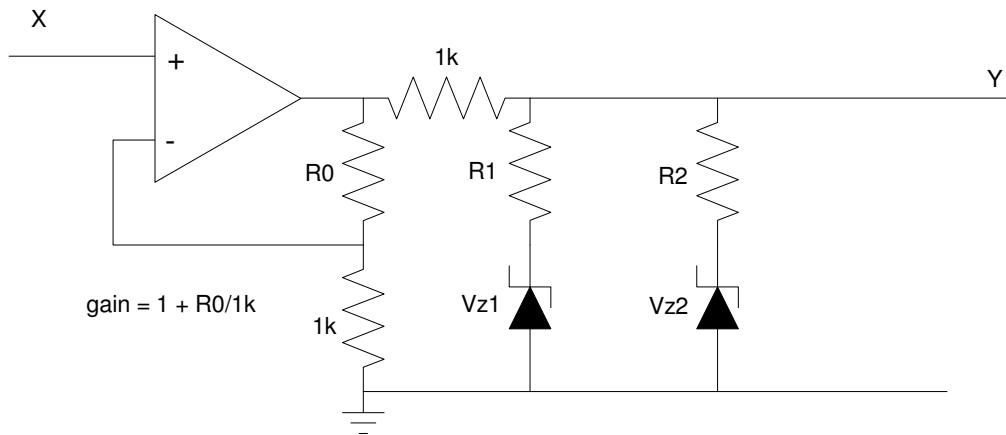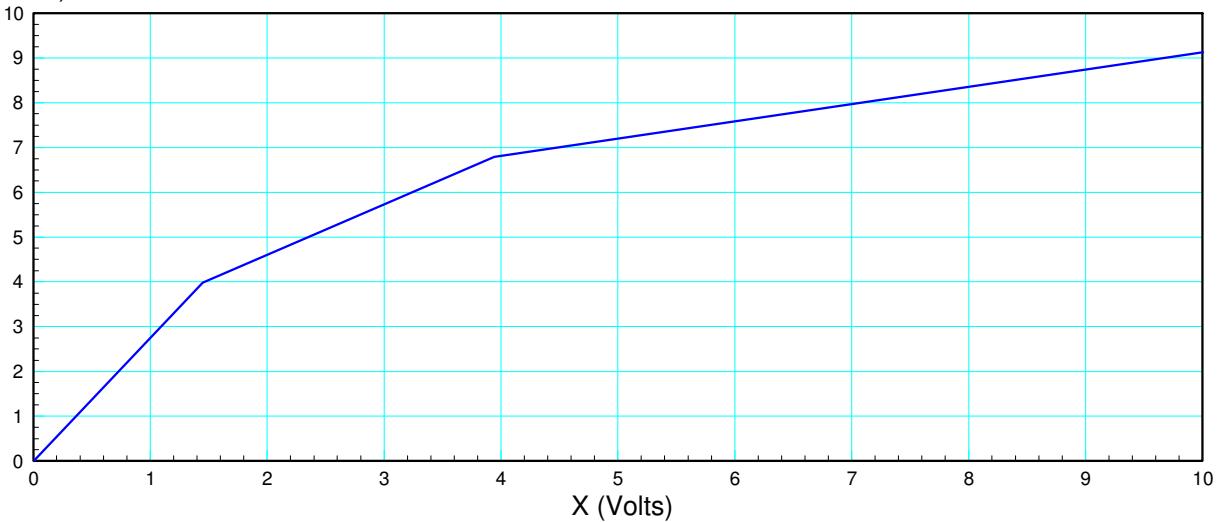


ECE 320 - Final (pt 2) - Name _____

Transistors and Mosfets

- 6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 5V$

R 1000 + 100*Mo + Day	Current Gain $hfe = \beta$	Load Line	V_{ce}	I_c
1514	10	show on graph	4.2V	28mA

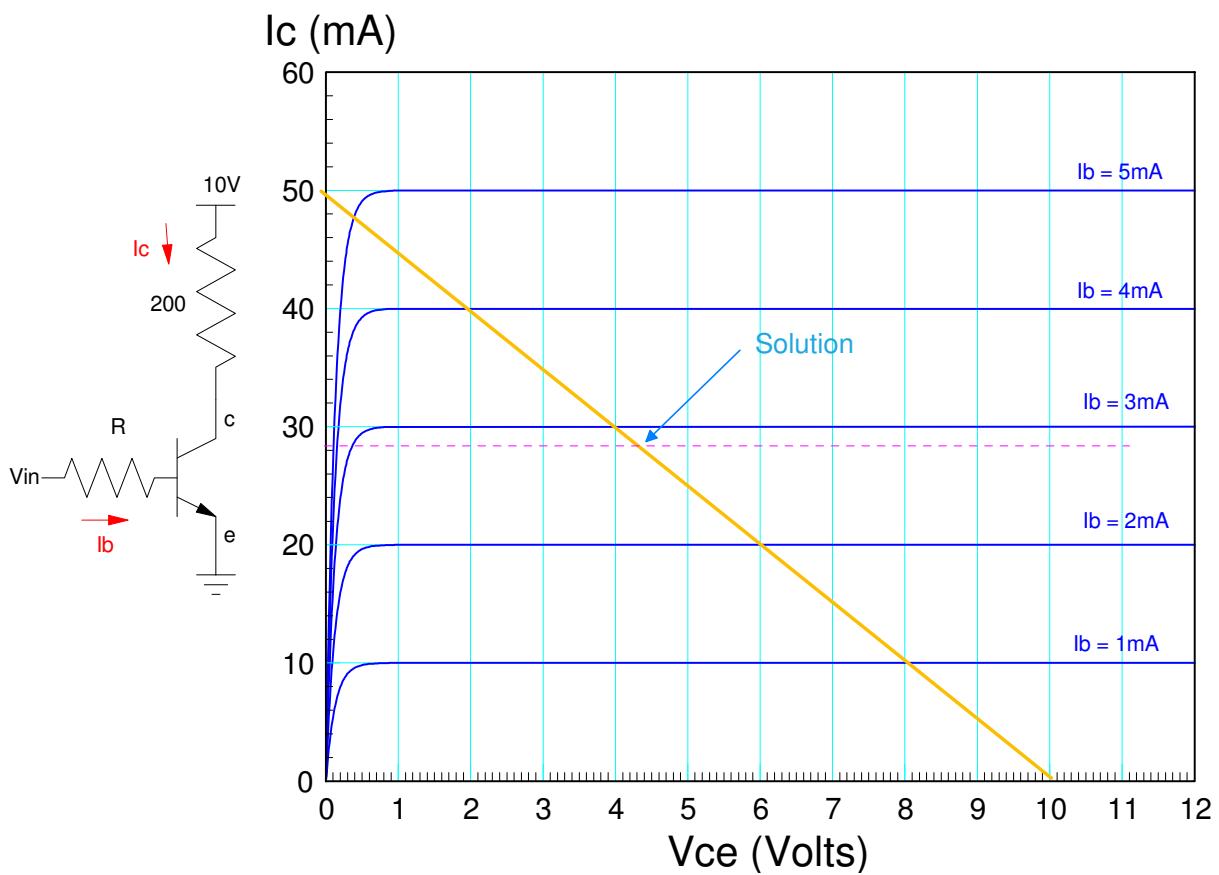


7) H-Bridge: Assume

- $R = 1000 + 100*(\text{birth month}) + (\text{birth day})$. May 14th would give 1514 Ohms
- Ideal silicon transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)

Determine the currents for voltages for the following H bridge.

R $1000 + 100*\text{Mo} + \text{Day}$	I1	I2	I3	V4	V5
1514	6.143mA	192mA	6.143mA	9.8V	0.2V

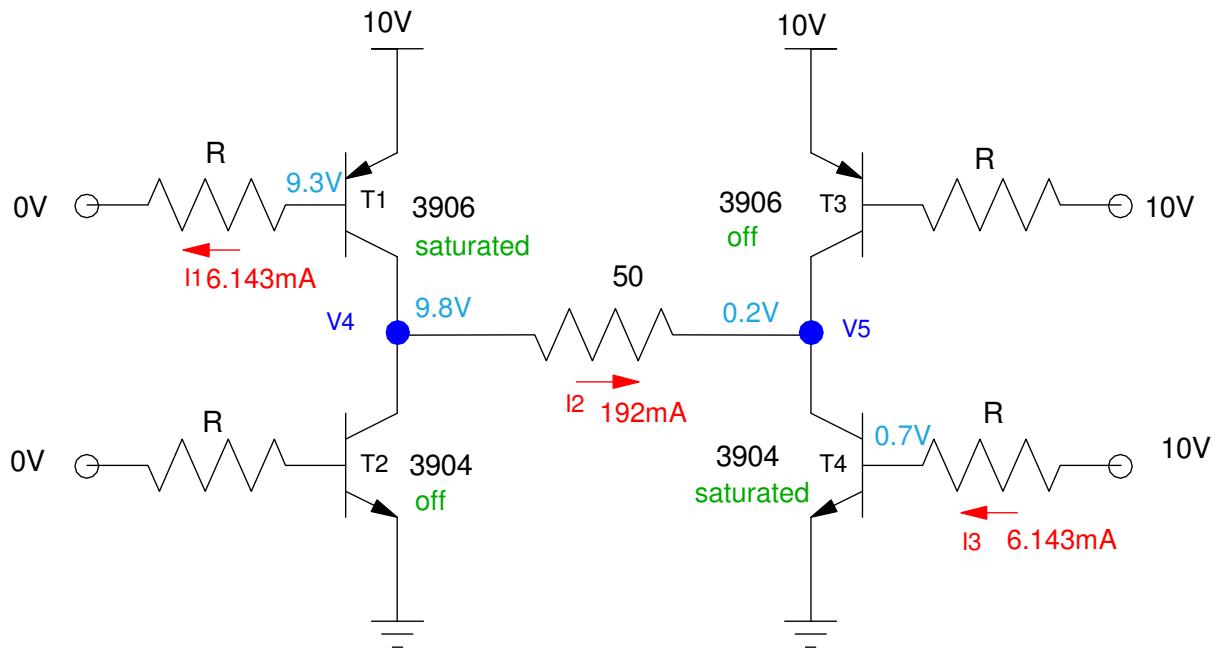


8) Schmitt Trigger: For the following Schmitt trigger, determine

- The voltage at V1 where V2 goes high,
- The voltage at V1 where V2 goes low, and
- R_b so that the transistor is saturated when V2 = +5V

Let R = 1000 + 100*(birth month) + (birth day)


R 1000 + 100*Mo + Day	V1(on) Voltage at V1 where V2 goes high	V1(off) Voltage at V1 where V2 goes low	R _b Pick R _b so that the transistor saturates
1514	2.3V	2.96V	172 < R_b < 2150 25mA < I _b < 1.96mA

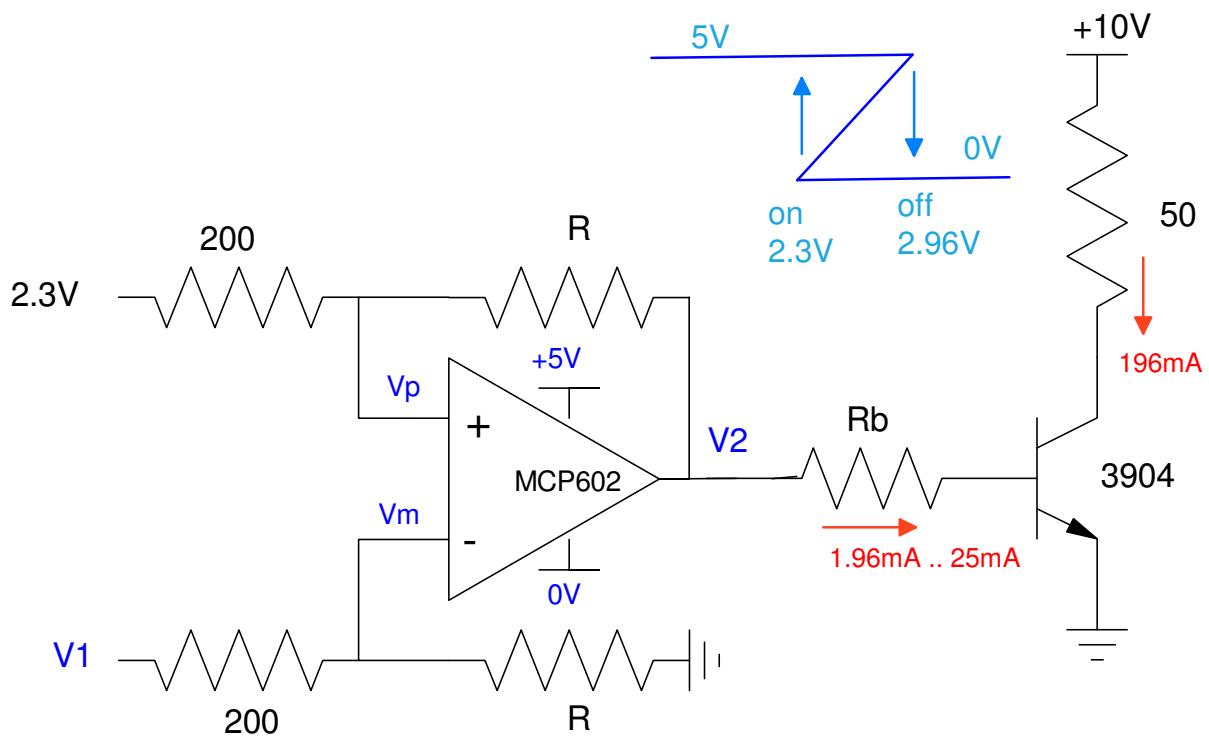

9) DTL Logic: Determine the voltages and currents for the following DTL logic gate. Assume

- $R = 1000 + 100*(\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(\text{sat})} = 0.2V$, $\beta=100$)


R	V1	I2	V3	I4	V5
1514	4.3V	180uA	0.2V	0mA	4.648V

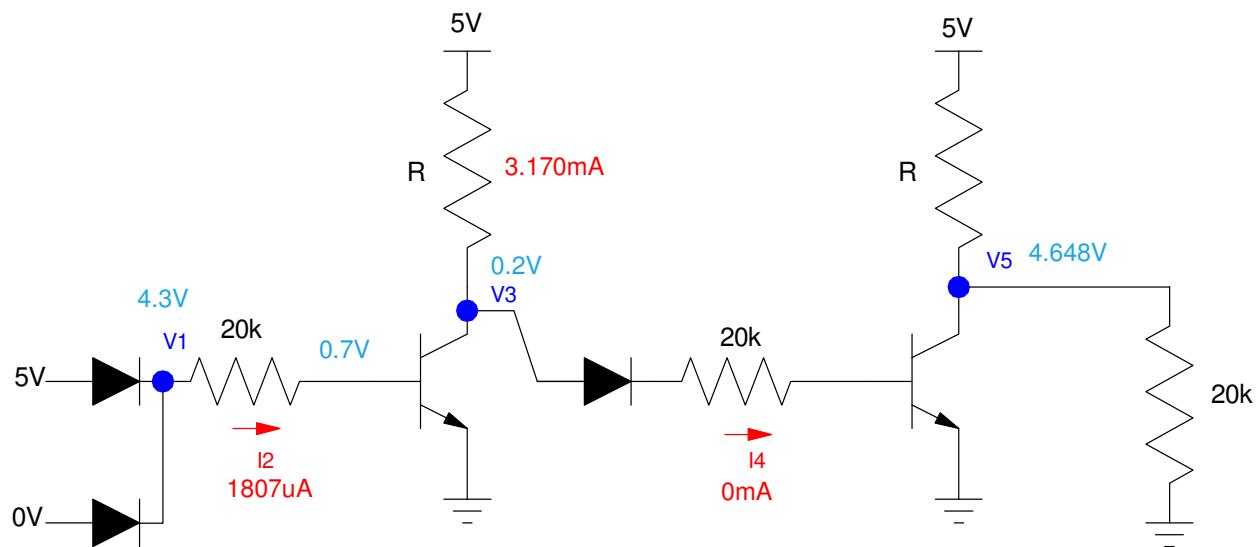

10) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line, and
- Determine $\{V_{ds}, I_{ds}\}$ when $V_g = 5V$

k_n transconductance gain	Load Line	I_{ds}	V_{ds}	Operating Region off / active / ohmic
30.4 $\mu A/V^2$ or 30.4 mA/V ²	show on graph	240 μA or 190mA	4.95V or 2.2V	saturated or ohmic

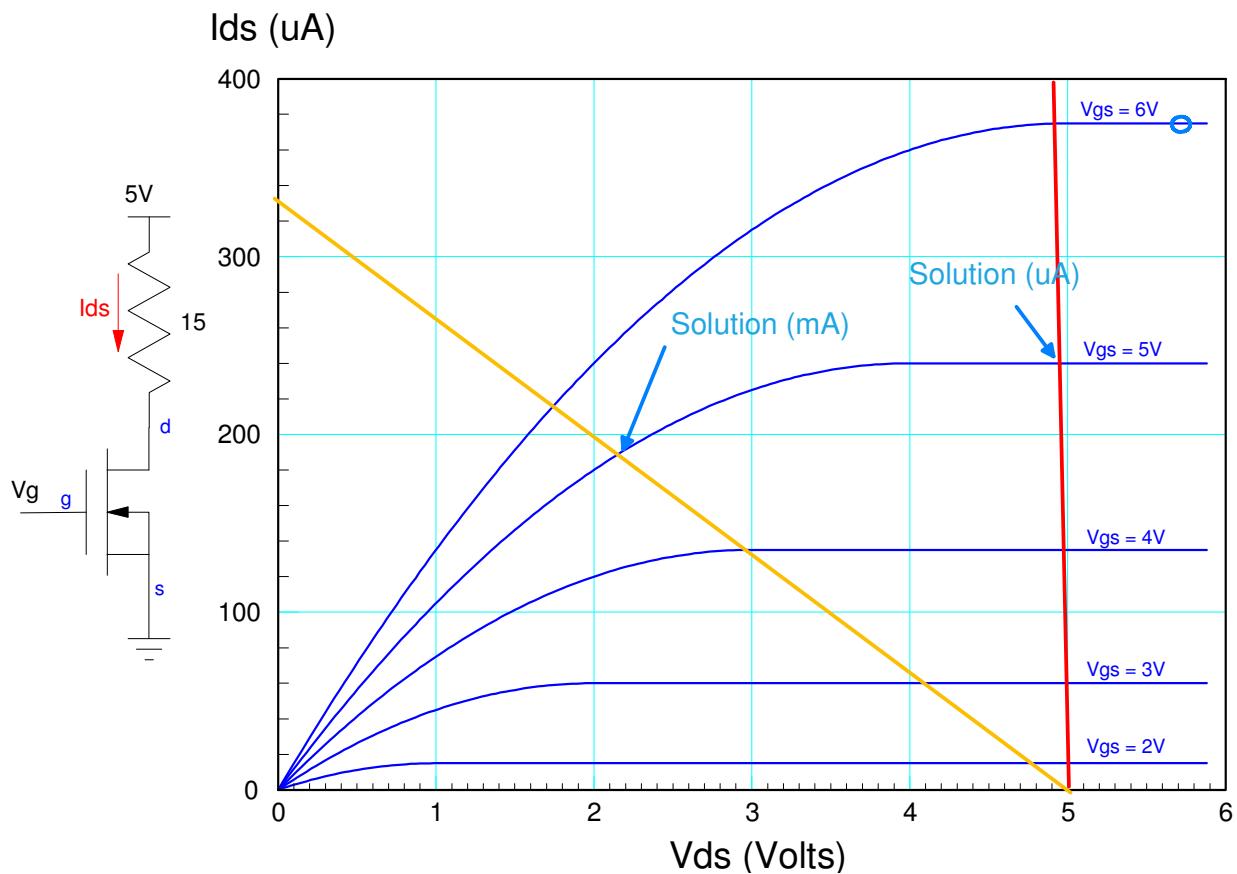

Pick a point A (saturated region)

$$I_{ds} = \frac{k_n}{2}(V_{gs} - V_{th})^2$$

$$380 \mu A = \frac{k_n}{2}(6 - 1)^2$$

$$k_n = 30.4 \frac{\mu A}{V^2}$$