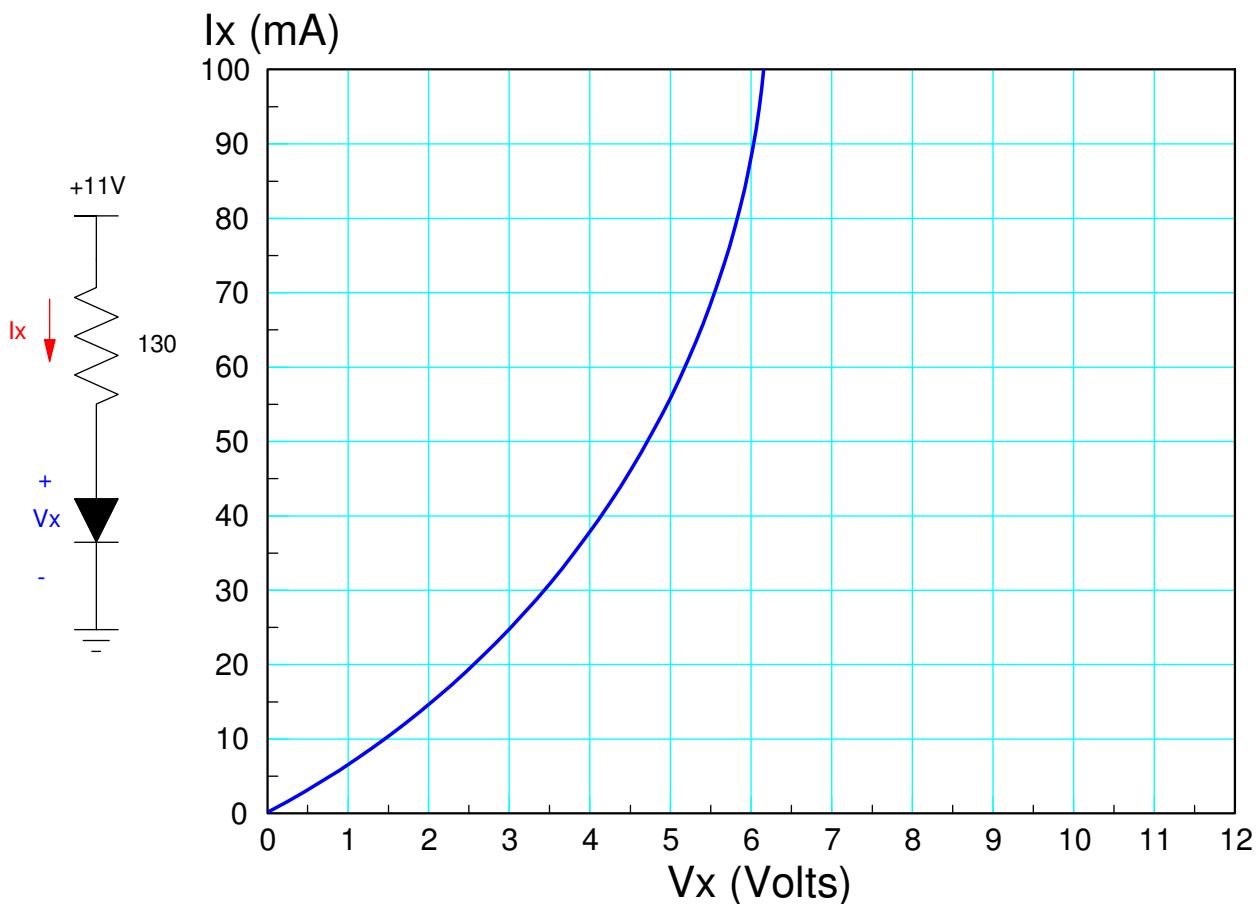


# ECE 320 - Final (pt 1) - Name \_\_\_\_\_

## Semiconductors & Diodes

- 1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine  $I_x$  and  $V_x$ .

Load Line	$V_x$	$I_x$
show on graph		




2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.052 \ln(10^8 \cdot I_d + 1) \quad I_d = 10^{-8} \cdot \left( \exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

Write N equations to solve for N unknonws: {V1, V2, V3, V4, Id1, Id2, Id3}.

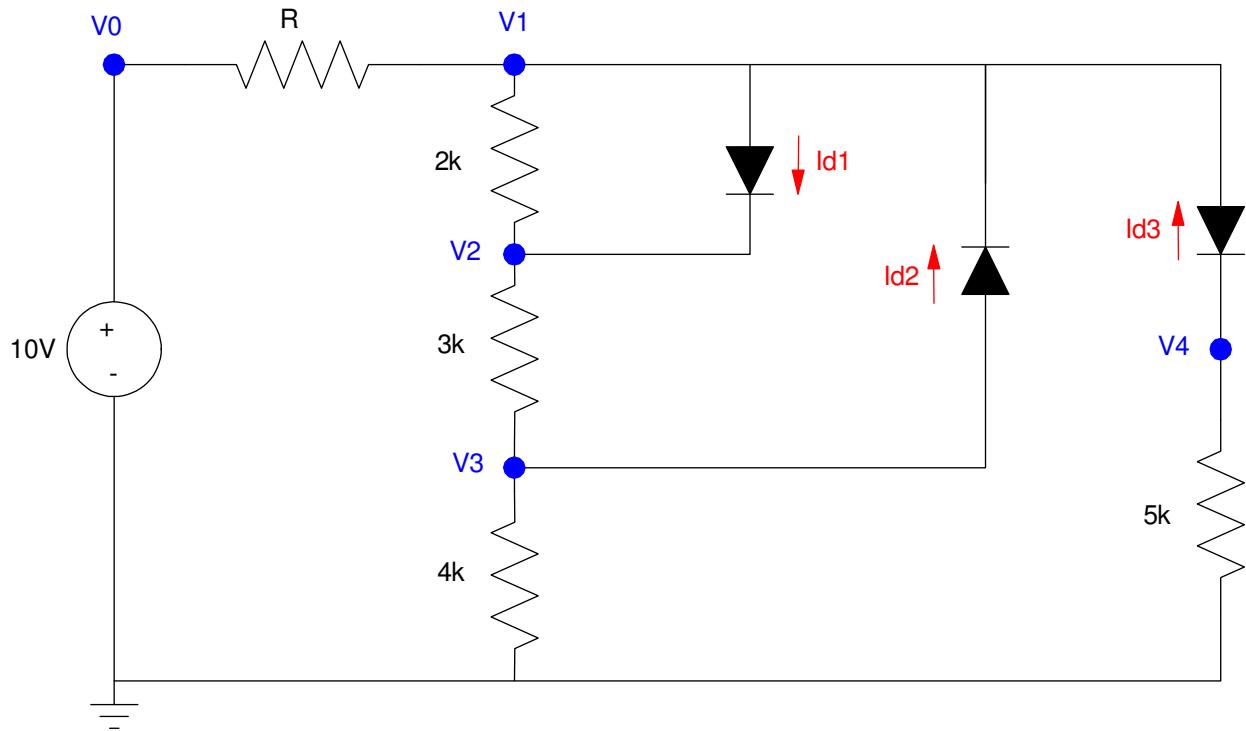
- Note: you do not need to solve.
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$ . For example, May 14th gives 1514 Ohms.



3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:


- $V_d = 0.7V$        $I_d > 0$
- $I_d = 0$                $V_d < 0.7V$
- $R = 1000 + 100*(\text{your birth month}) + (\text{birth date})$ . For example, May 14th gives 1514 Ohms.

$R$ $1000 + 100*\text{mo} + \text{day}$	$V_1$	$V_2$	$V_3$

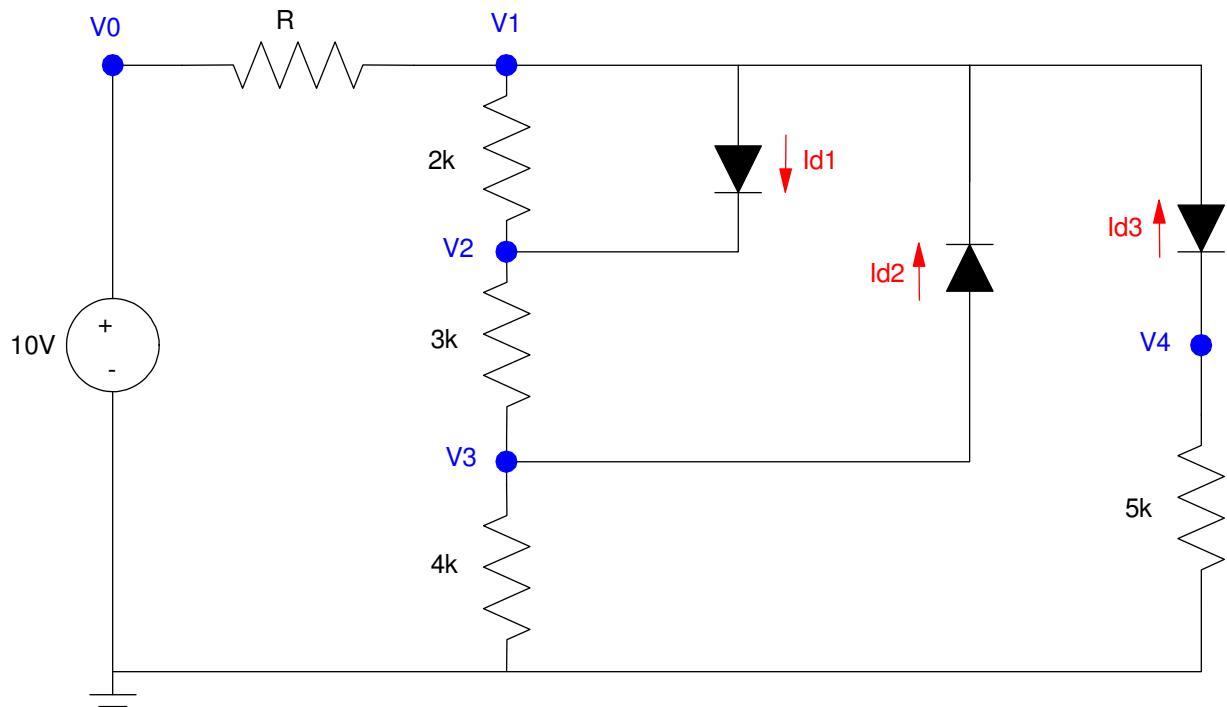

4) AC to DC: Analysis: Determine V<sub>1</sub> and V<sub>2</sub> (both DC and AC) for the following AC to DC converter


R	V <sub>1</sub>		V <sub>2</sub>	
	DC	AC	DC	AC

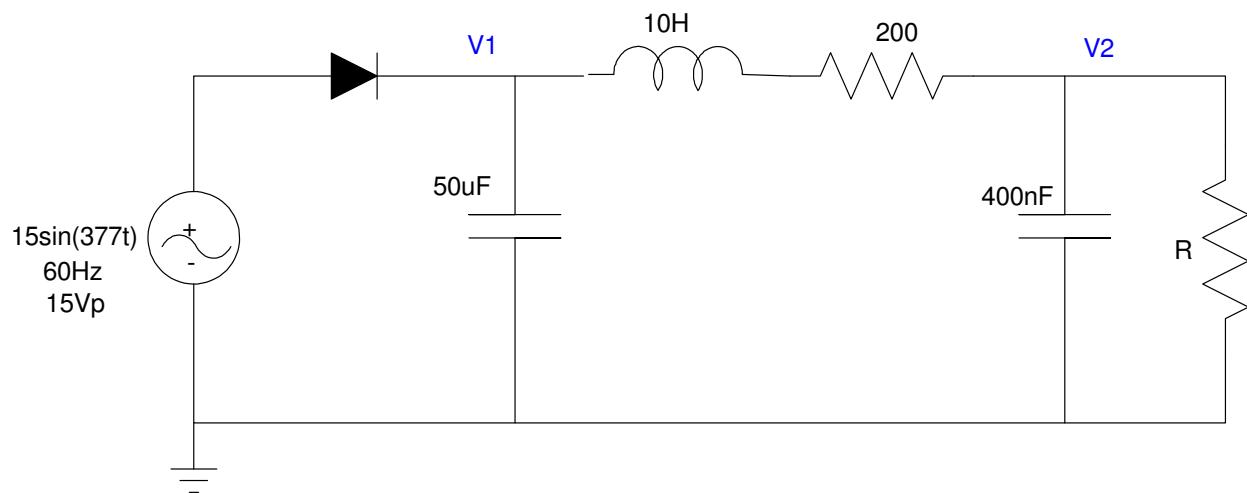

5) Max/Min: Analysis: Determine currents I1..I6. Assume

- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$

R	I1	I2	I3	I4	I5	I6

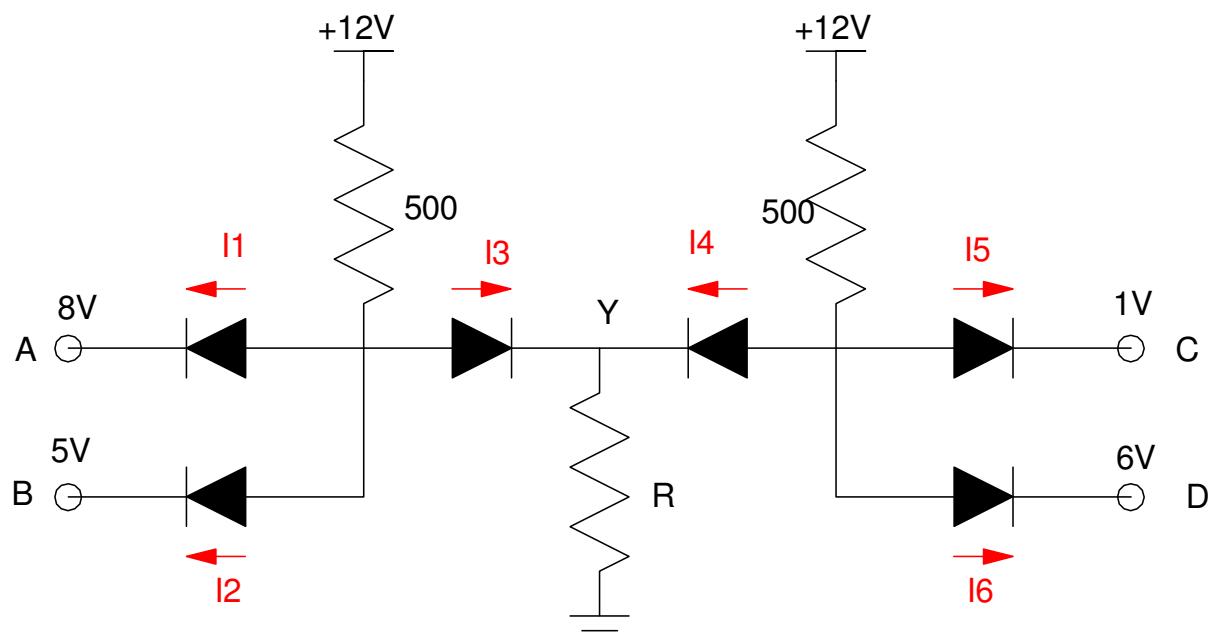


# ECE 320 - Final (pt 2) - Name \_\_\_\_\_

Transistors and Mosfets

- 6) Determine the current gain,  $\beta$ . Also draw the load line and determine the operating point when  $V_{in} = 5V$

$R$ 1000 + 100*Mo + Day	Current Gain $hfe = \beta$	Load Line	$V_{ce}$	$I_c$
		show on graph		

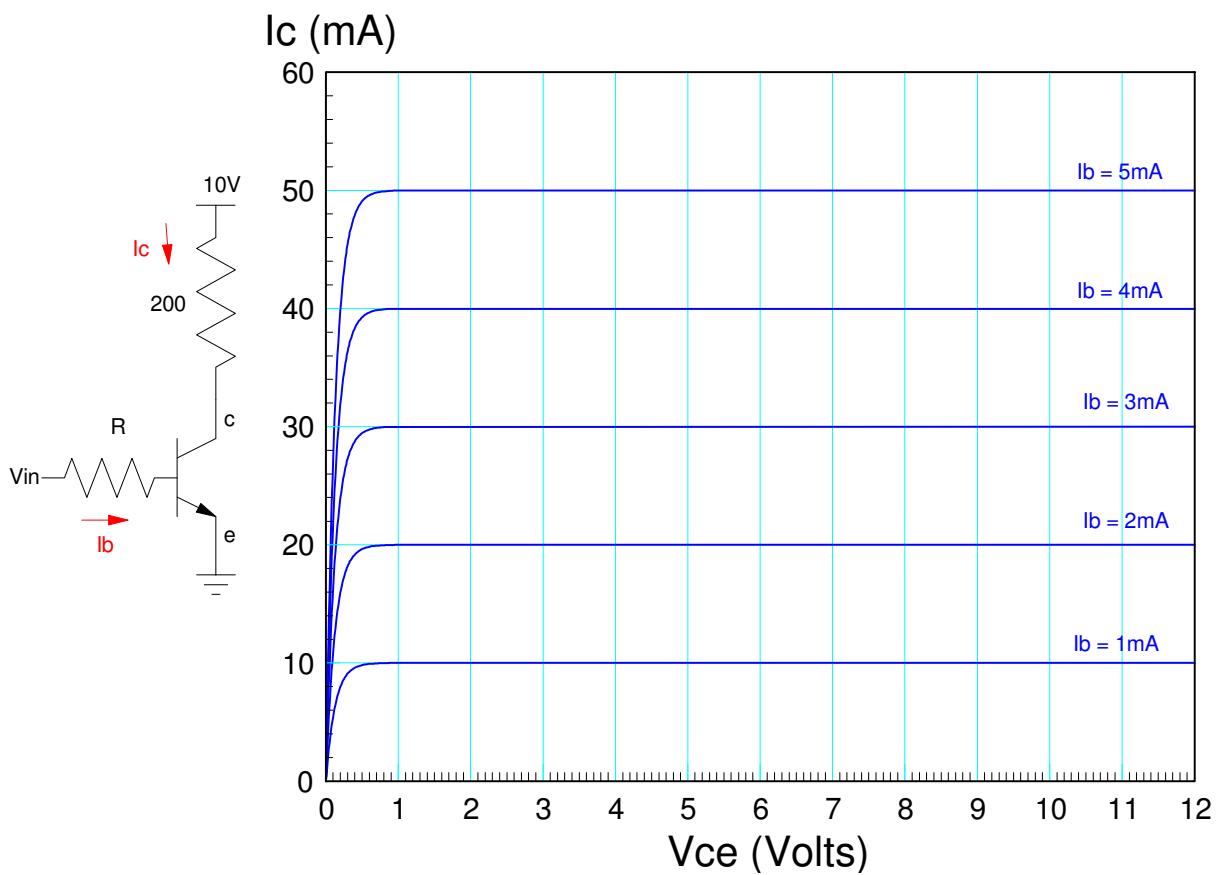


7) H-Bridge: Assume

- $R = 1000 + 100*(\text{birth month}) + (\text{birth day})$ . May 14th would give 1514 Ohms
- Ideal silicon transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ ,  $\beta = 100$ )

Determine the currents for voltages for the following H bridge.

$R$ $1000 + 100*\text{Mo} + \text{Day}$	$I_1$	$I_2$	$I_3$	$V_4$	$V_5$

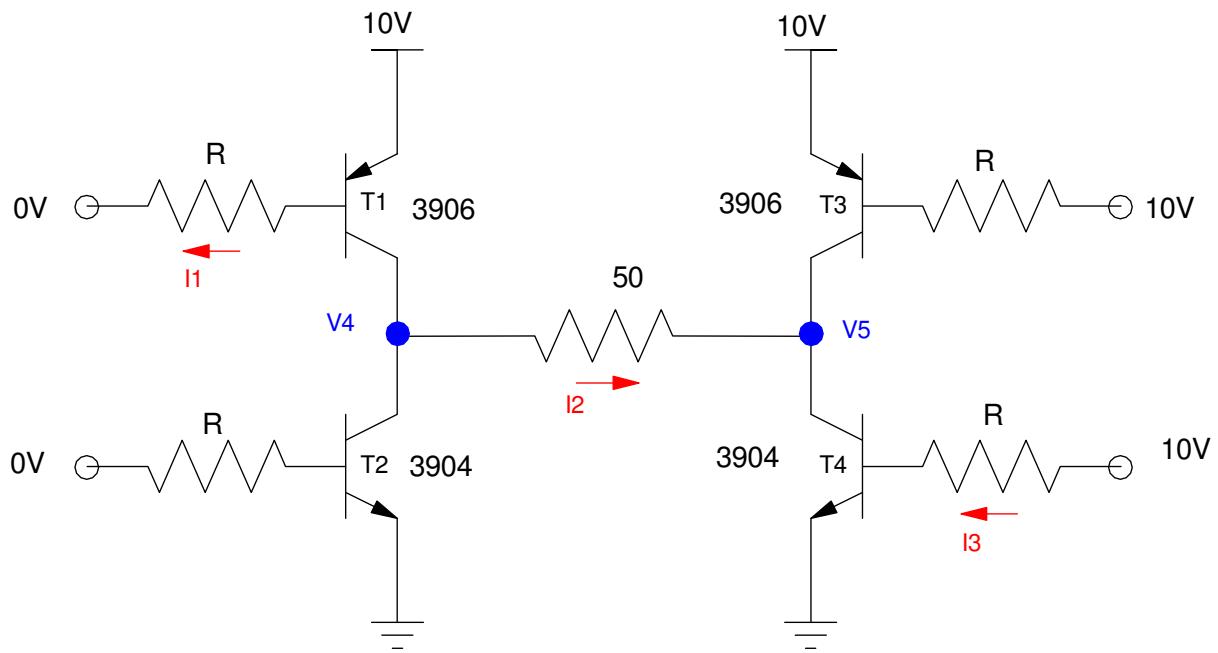


8) Schmitt Trigger: For the following Schmitt trigger, determine

- The voltage at V1 where V2 goes high,
- The voltage at V1 where V2 goes low, and
- R<sub>b</sub> so that the transistor is saturated when V2 = +5V

Let R = 1000 + 100\*(birth month) + (birth day)


R 1000 + 100*Mo + Day	V1(on) Voltage at V1 where V2 goes high	V1(off) Voltage at V1 where V2 goes low	R <sub>b</sub> Pick R <sub>b</sub> so that the transistor saturates

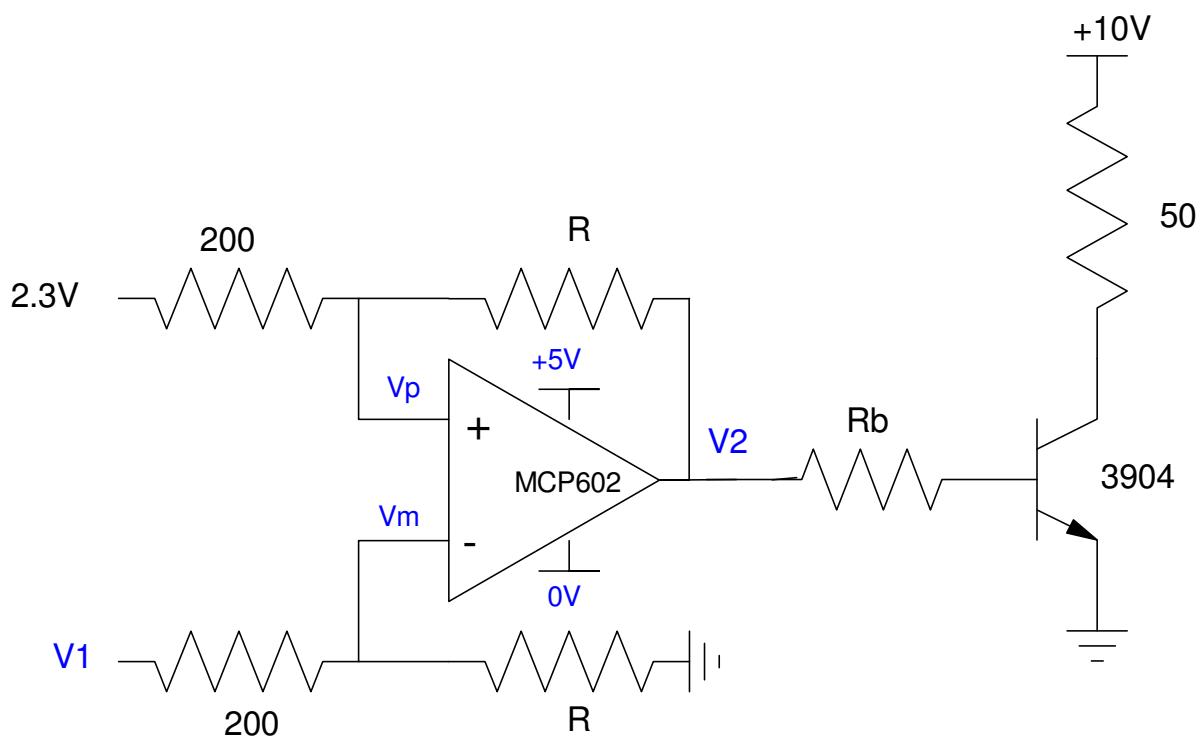

9) DTL Logic: Determine the voltages and currents for the following DTL logic gage. Assume

- $R = 1000 + 100*(\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ( $V_f = 0.7V$ ), and
- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(\text{sat})} = 0.2V$ ,  $\beta=100$ )

R	V1	I2	V3	I4	V5

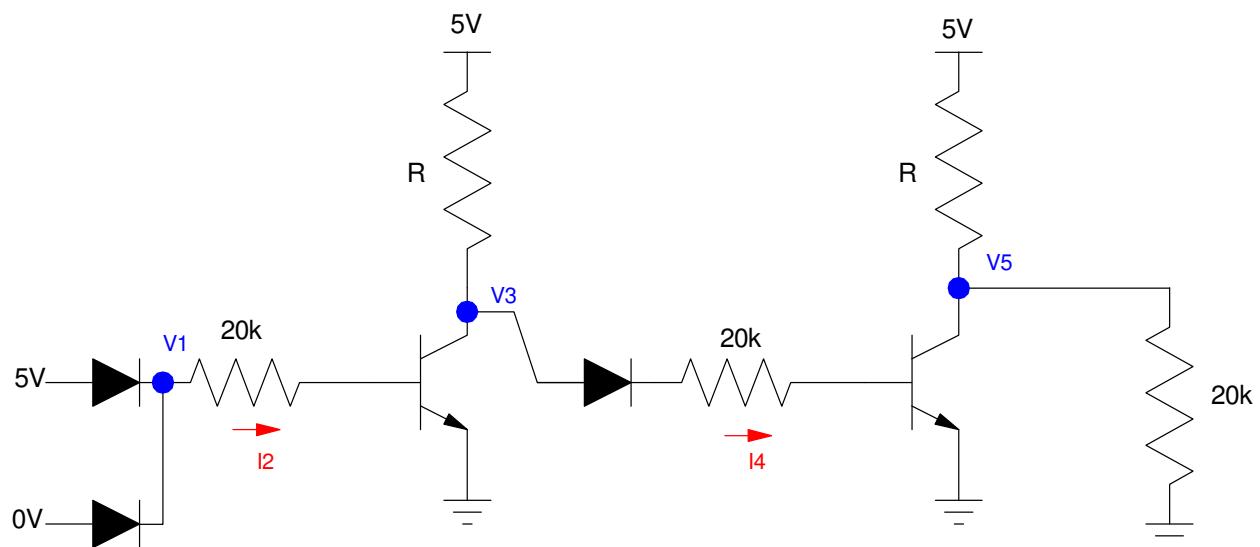

10) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain,  $k_n$ ,
- Draw the load line, and
- Determine  $\{V_{ds}, I_{ds}\}$  when  $V_g = 5V$

$k_n$ transconductance gain	Load Line	$I_{ds}$	$V_{ds}$	Operating Region off / active / ohmic
	show on graph			

