


# ECE 320 - Quiz #3 - Name \_\_\_\_\_

Ideal Diodes, LEDs, AC to DC Converters - Spring 2019

1) Determine the voltages and currents for the circuit. Assume

- Ideal silicon diodes ( $V_f = 0.7V$ ).
- $R$  is  $1000 + 100 \times (\text{your birth month}) + (\text{you}).\text{b}$  (For example, May 14 = 1514 Ohms)


V1	V2	V3	Id1	Id2	Id3

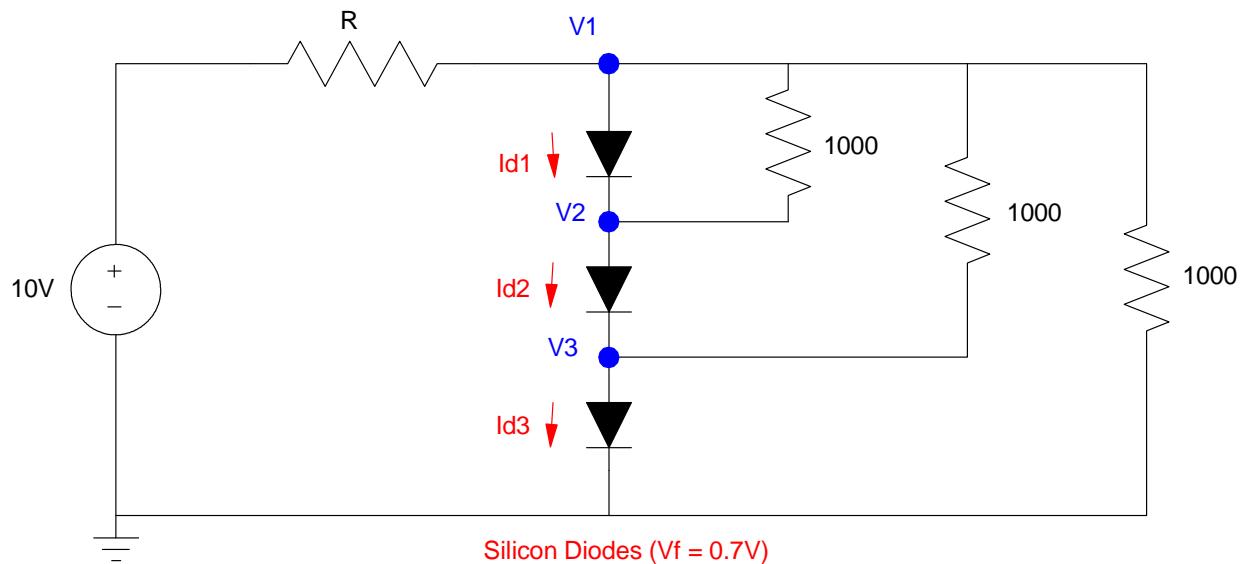

2) Determine the voltages and currents for the circuit. Assume

- Ideal red diodes ( $V_f = 1.9V$ ).
- $R$  is  $1000 + 100^*(\text{your birth month}) + (\text{you}).b$  Friday example, May 14 = 1514 Ohms)


V1	V2	V3	Id1	Id2	Id3

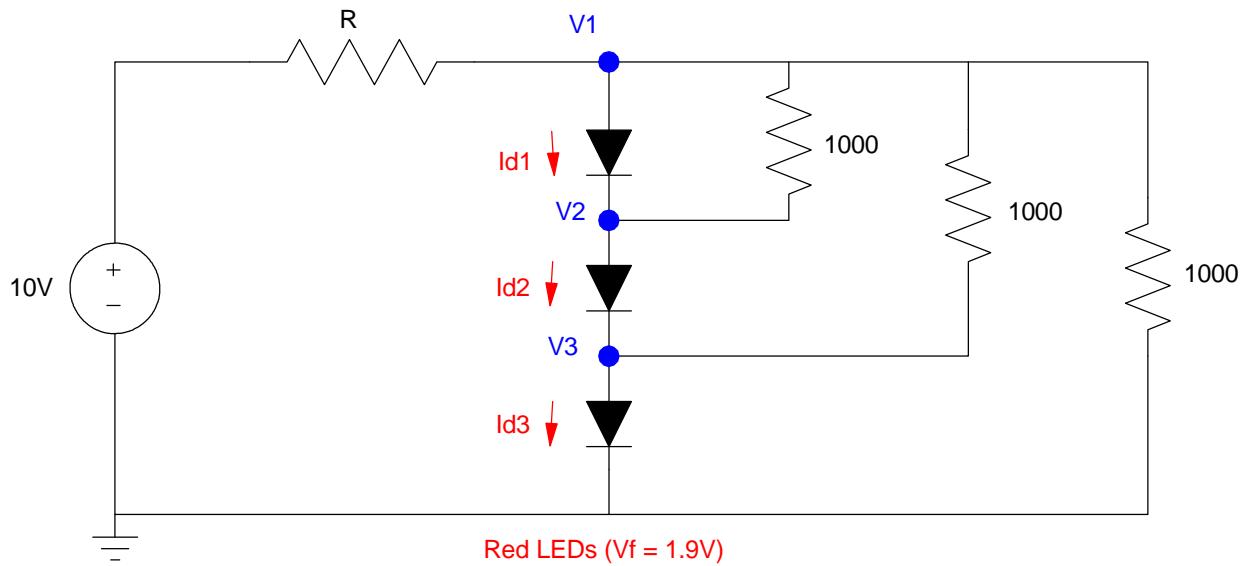

3) A red and green LED are connected to a 10V battery. Determine the current and brightness of each LED.  
Assume


- R is  $1000 + 100 \times (\text{your birth month}) + (\text{you})$ . For example, May 14 = 1514 Ohms
- Red LED:  $V_f = 1.9V @ 20mA, 3,000\text{mcd} @ 20mA$
- Green LED:  $V_f = 3.0V @ 20mA, 3,000\text{mcd} @ 20mA$

R	Red LED		Green LED	
	Ir	mcd(red)	Ig	mcd(green)

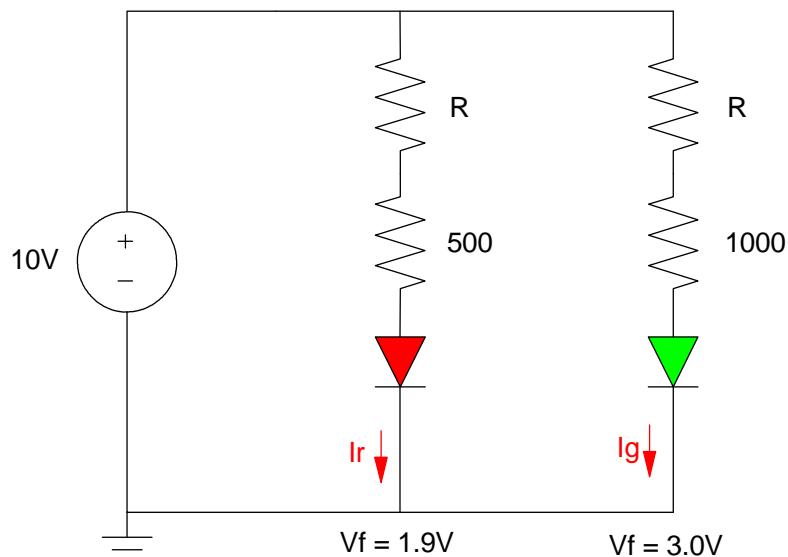

- 4) The following waveforms are found using **CircuitLab** for V1 for an AC to DC converter. Determine the following


Frequency (Hz)	V1 (blue waveform)	
	DC (average)	AC (Vpp)

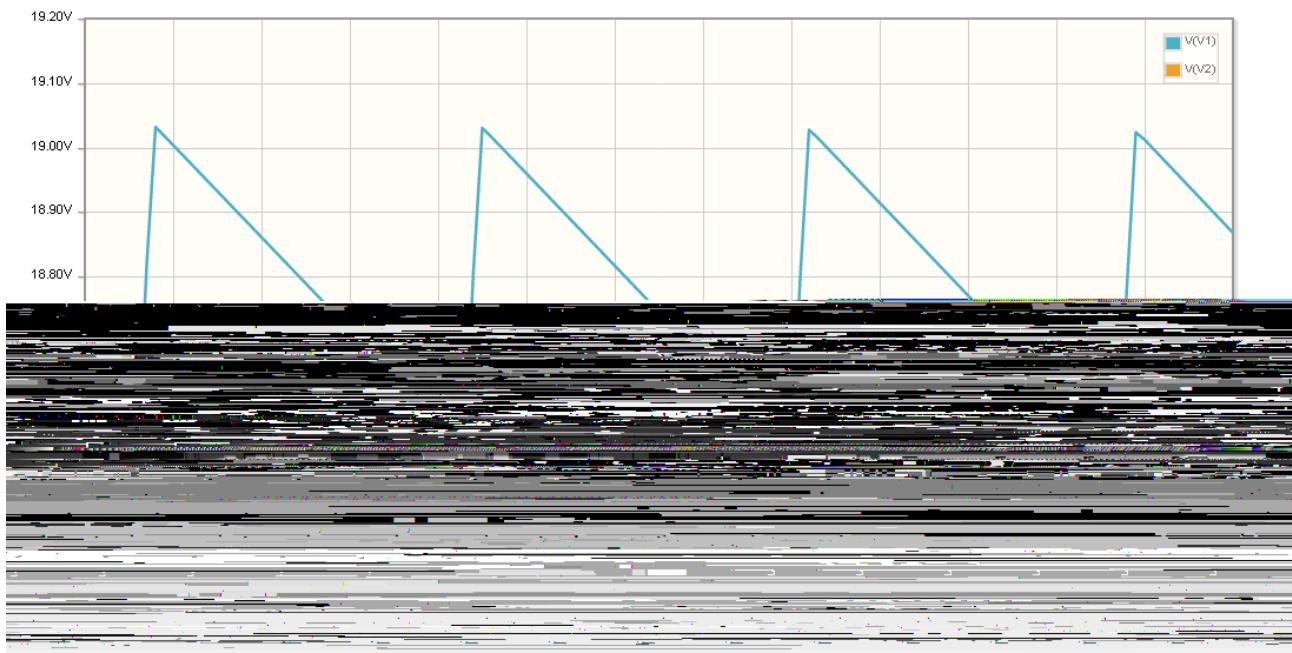

5) Determine the voltages V1 and V2 (both DC and AC). Assume

- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R$  is  $1000 + 100^*(\text{your birth month}) + (\text{your birthday})$  For example, May 14 = 1514 Ohms

V1		V2	
DC (mean(V1))	AC (V1pp)	DC (mean(V2))	AC (V2pp)

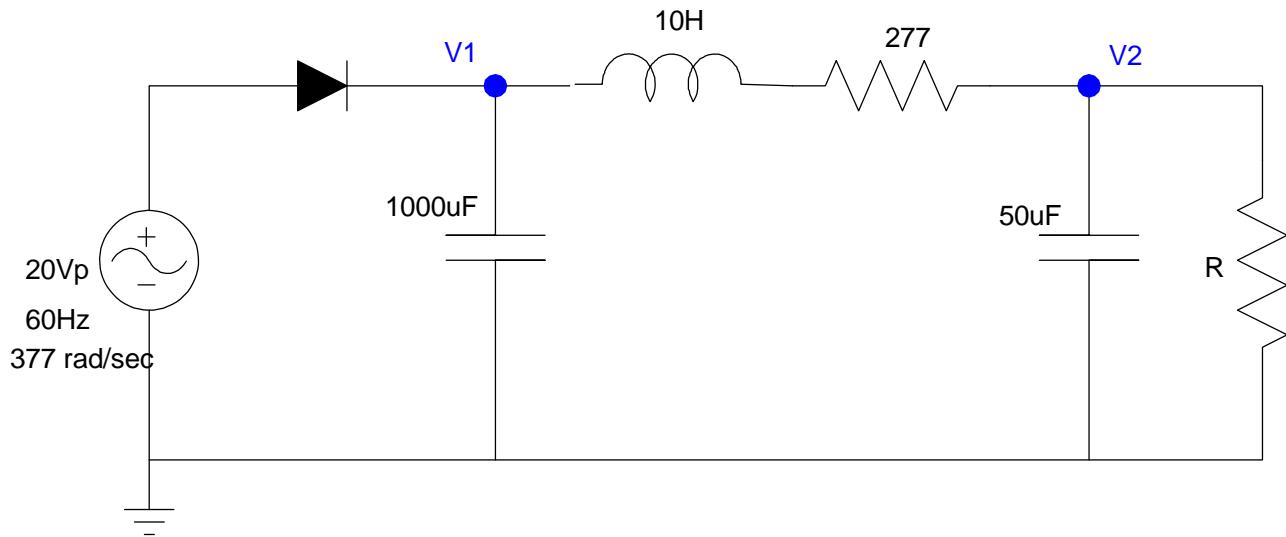

6) Determine C<sub>1</sub>, and C<sub>2</sub> so that

- The ripple at V<sub>1</sub> is 4Vpp and
- The ripple at V<sub>2</sub> = 200mVpp

Let R be  $1000 + 100 \times (\text{your birth month}) + (\text{your birth day})$ . For example, May 14 = 1514 Ohms

R	C <sub>1</sub>	C <sub>2</sub>

