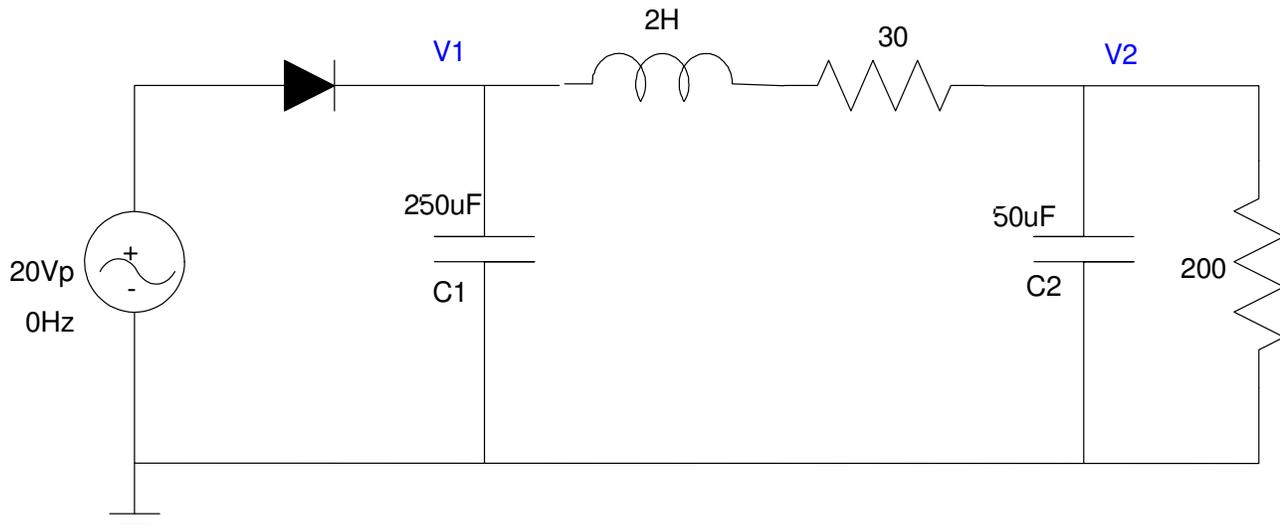


AC to DC Converters

5) Determine the voltages at V1 and V2 (DC and AC)



$$\max(V_1) = 19.3V$$

$$I \approx \left(\frac{19.3V}{230\Omega} \right) = 83.91mA \quad \text{worst case}$$

$$I = C \frac{dV}{dt}$$

$$83.91mA = 250\mu F \frac{dV}{1/60s}$$

V1 Analysis

$$V_1(AC) = dV = 5.594V_{pp}$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_1(AC)$$

$$V_1(DC) = 16.50V$$

V2 Analysis

$$V_2(DC) = \left(\frac{200}{200+30} \right) V_1(DC) = 14.35V$$


$$200 \text{ Ohms} \parallel 50\mu F = 200 \parallel -j53.05 = 13.147 - j49.563$$

$$2H \gg j754 \text{ Ohms}$$

$$V_2(AC) = \left(\frac{(13.147-j49.563)}{(13.147-j49.563)+(30+j754)} \right) 5.594V_{pp}$$

$$V_2(AC) = 406mV_{pp}$$

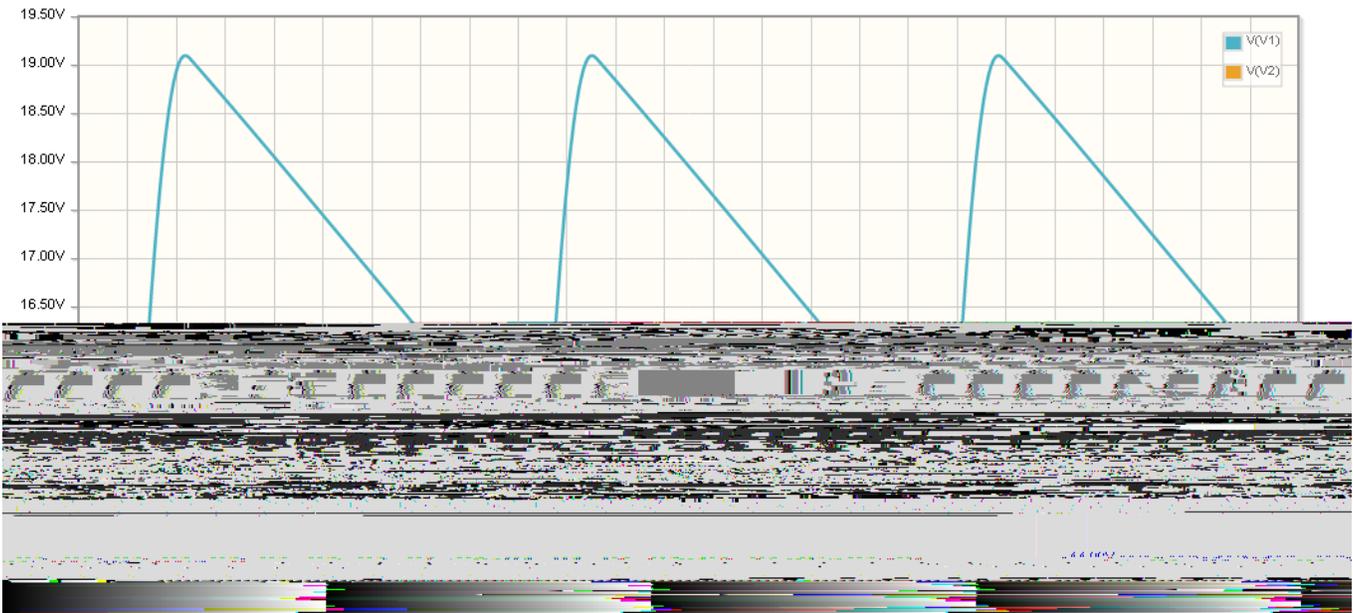6) Build the circuit in CircuitLab (or similar program) and verify your calculations for problem #5



V1 (Blue)

- Max = 19.09V
- Min = 14.78V
- DC = $(\text{Max} + \text{Min})/2 = 16.93\text{V}$ (16.50V computed)
- AC = $(\text{Max} - \text{Min}) = 4.310\text{Vpp}$ (5.594V computed)

V2 (orange)

- Max = 14.89V
- Min = 14.66V
- DC = 14.77V (14.35V computed)
- AC = 230mVpp (406mVpp computed)

7) Determine C1 and C2 so that AC voltages are: $V_1 = 2V_{pp}$ and $V_2 = 250mV_{pp}$.

$$V_1(AC) = 2V_{pp} \quad \text{given}$$

$$V_1(DC) = 19.3V - \frac{1}{2}2V_{pp} = 18.3V$$

$$V_2(DC) = \left(\frac{200}{200+30}\right) V_1(DC) = 15.913V$$

Finding C1:

$$I = \left(\frac{18.3V}{230\Omega}\right) = 79.57mA$$

$$I = C_1 \frac{dV}{dt}$$

$$79.57mA = C_1 \frac{2V_{pp}}{1/60s}$$

$$C_1 = 663\mu F$$

Finding C2: Assume $C_2 = 0$.


$$V_2(AC) = \left(\frac{200}{(200)+(5+j754)}\right) 2V_{pp} = 512mV_{pp}$$

For $V_2(AC)$ to be $250mV_{pp}$

$$\left|\frac{1}{j\omega C}\right| = \left(\frac{250mV}{512mV}\right) 200\Omega = 97.65\Omega$$


$$C_2 = 27.16\mu F$$

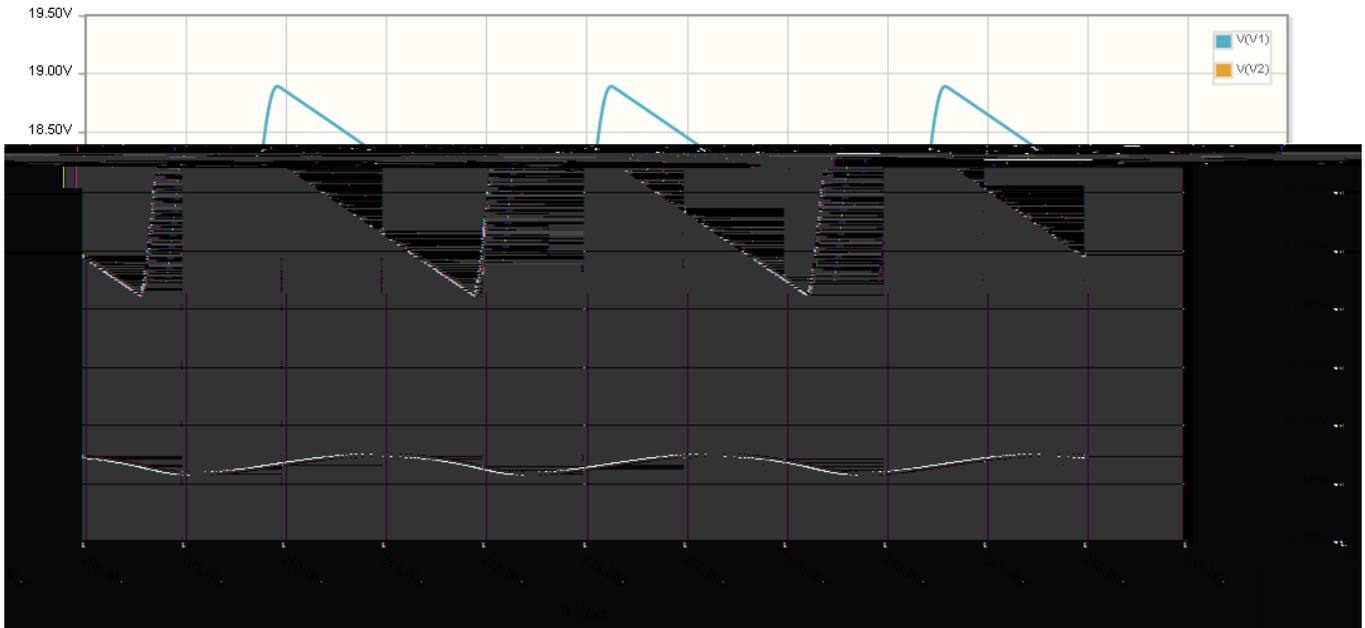8) Build this circuit in CircuitLab (or similar program) and verify your calculations for problem #7



V1: (blue)

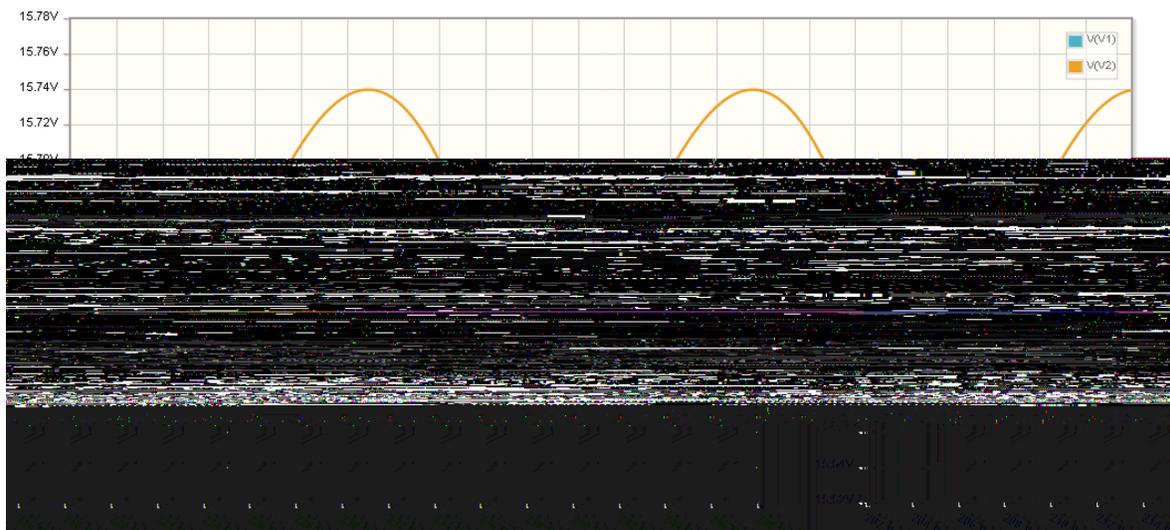- $\max(V1) = 18.89V$
- $\min(V1) = 17.13V$
- $V1(DC) = 18.01V$ (vs. $18.30V$ computed)
- $V1(AC) = 1.76V_{pp}$ (vs. $2.00V_{pp}$ computed)



V2 (orange)

- $\max(V2) = 15.74V$
- $\min(V2) = 15.58V$
- $V2(DC) = 15.66V$ (vs. $15.913V$ computed)
- $V2(AC) = 160mV_{pp}$ (vs. $250mV_{pp}$ computed)