

ECE 320 - Homework #7


Fourier Transform, DC to AC, SCR. Due March 1~~6~~22

Fourier Transform

The voltage V_1 is a 60% duty cycle square wave

$$V_1(t) = V_1(t + 1\text{ms})$$
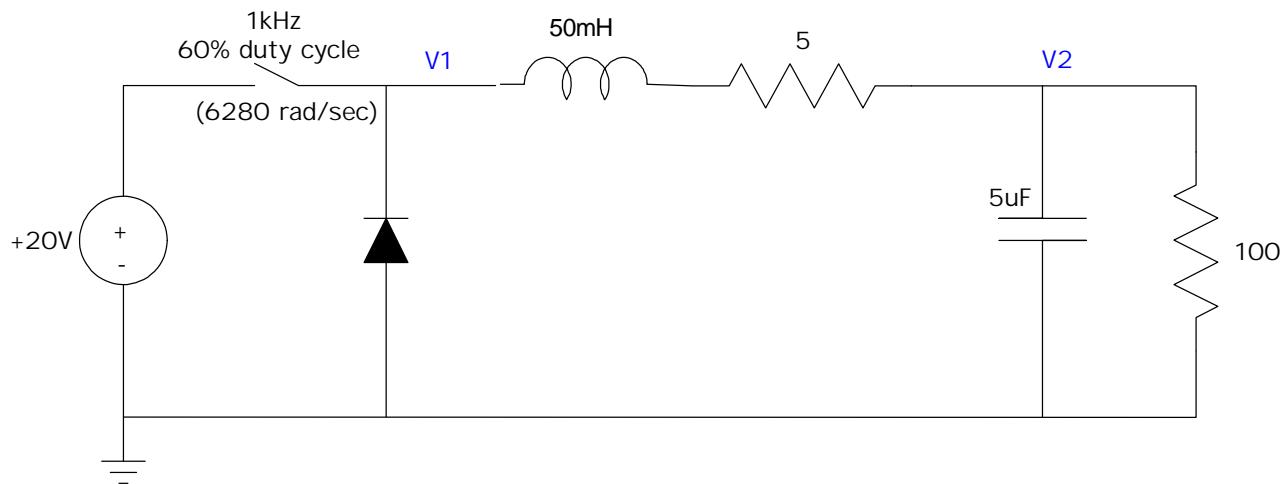
$$V_1(t) = \begin{cases} +20V & 0 < t < 600\text{ms} \\ -0.7V & 600\text{ms} < t < 1000\text{ms} \end{cases}$$



- 1) Determine the first five terms for the Fourier transform for $V_1(t)$

- DC
- 1kHz, sine and cosine
- 2kHz, sine and cosine

$$V_1(t) = a_0 + a_1 \cos(w_0 t) + b_1 \sin(w_0 t) + a_2 \cos(2w_0 t) + b_2 \sin(2w_0 t)$$

Option 1: Slow Fourier Transform (my preference)

```
>> a0 = mean(V1)
a0 = 11.7188
```

```
>> a1 = 2*mean(V1 .* cos(2*pi*t))
a1 = -3.8689
```

```
>> b1 = 2*mean(V1 .* sin(2*pi*t))
b1 = 11.9197
```

```
>> a2 = 2*mean(V1 .* cos(2*pi*2*t))
a2 = 3.1342
```

```
>> b2 = 2*mean(V1 .* sin(2*pi*2*t))
b2 = 2.2743
```

Option #2: Complex Fourier Transform (same result)

```
>> c0 = mean(V1)  
c0 = 11.7188  
  
>> c1 = 2*mean(V1 .* exp(-j*2*pi*t))  
c1 = -3.8689 -11.9197i  
  
>> c2 = 2*mean(V1 .* exp(-j*2*pi*2*t))  
c2 = 3.1342 - 2.2743i
```

meaning

$$v_1(t) = 11.7188$$


$$- 3.8689 \cos(w_0 t) + 11.9197 \sin(w_0 t)$$

$$+ 3.1342 \cos(2w_0 t) + 2.2743 \sin(2w_0 t)$$

:

Checking in Matlab
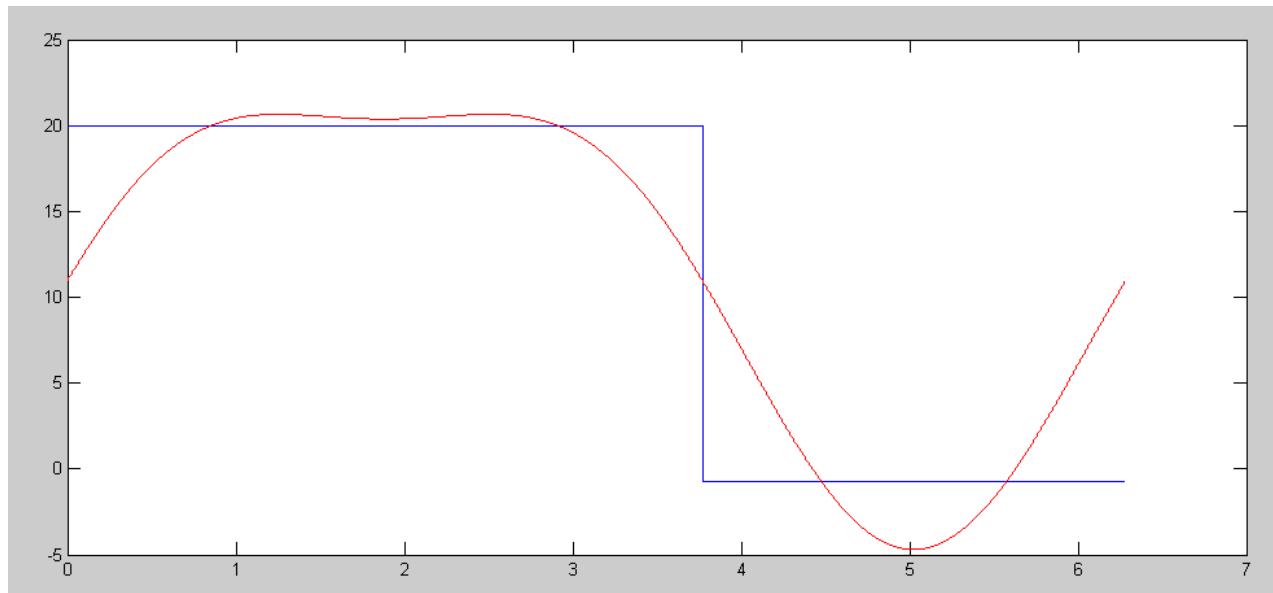
```
t = t * 2*pi;  
V1f = a0 + a1*cos(t) + b1*sin(t) + a2*cos(2*t) + b2*sin(2*t);  
plot(t,V1,'b',t,V1f, 'r');
```



2) Determine $V_2(t)$ at each frequency

- DC
- 1kHz
- 2kHz

Treat this as three separate problems...

DC:


$$w = 0$$

$$V_1 = 11.7188$$

$$L \circledR jwL = 0$$

$$C \circledR \frac{1}{jwC} = \infty$$
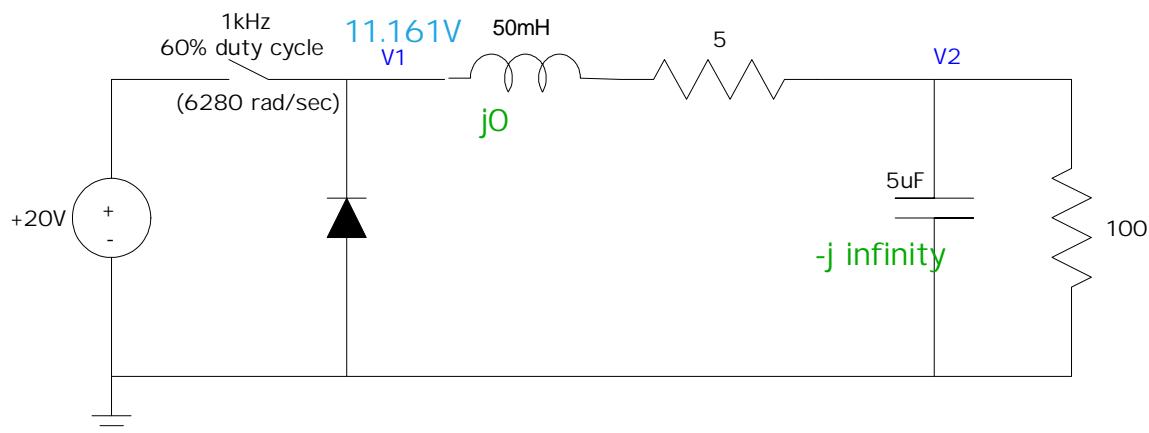
$$V_2 = \frac{100}{100+5} (11.7188) = 11.161$$



1kHz:

$$v_1(t) = -3.8689 \cos(\omega_0 t) + 11.9197 \sin(\omega_0 t)$$

$$\omega_0 = 2\pi f = 6280$$

$$V_1 = -3.8689 - j11.9197$$

$$L \circledR j\omega L = j314 \text{W}$$


$$C \circledR \frac{1}{j\omega C} = -j31.84 \text{W}$$

$$100 \text{W} \parallel -j31.84 \text{W} = 9.209 - j28.915$$

$$V_2 = \frac{(9.209 j28.915)}{(9.209 j28.915 + (5+j314))} (-3.8689 - j11.9197)$$

$$V_2 = -0.013 + j1.211$$
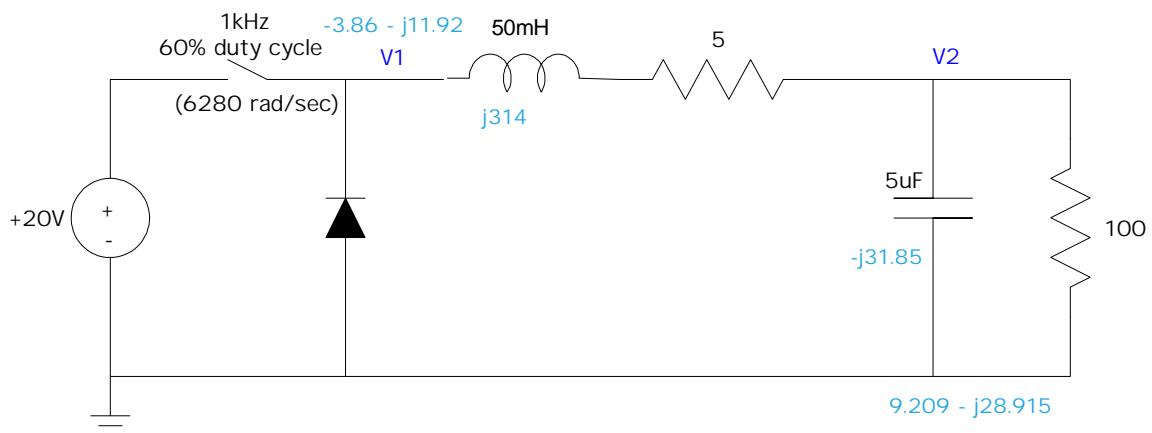
$$v_2(t) = -0.013 \cos(\omega_0 t) - 1.211 \sin(\omega_0 t)$$



2kHz:

$$2\omega_0 = 2 \times 6280 = 12,560$$

$$v_1(t) = +3.1342 \cos(2\omega_0 t) + 2.2743 \sin(2\omega_0 t)$$

$$V_1 = 3.1342 - j2.2743$$

$$L \otimes j\omega L = j628\text{N}$$


$$C \otimes \frac{1}{j\omega C} = -j15.924\text{N}$$

$$100\text{N} \parallel -j15.924\text{N} = 2.473 - j15.530\text{N}$$

$$V_2 = \frac{(2.473 j15.530)}{(2.473 j15.530 + (5+j628))} (3.1342 - j2.2743)$$

$$V_2 = -0.089 + j0.044$$
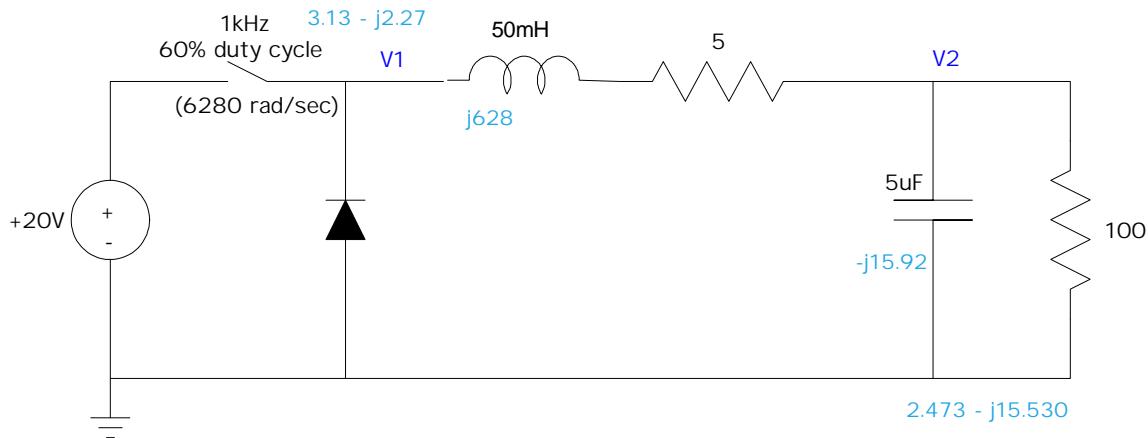
$$v_2(t) = -0.089 \cos(2\omega_0 t) - 0.044 \sin(2\omega_0 t)$$



So, the total answer is DC + 1kHz + 2kHz:

$$v_2(t) = 11.161$$

$$-0.013 \cos(\omega_0 t) - 1.211 \sin(\omega_0 t)$$

$$-0.089 \cos(2\omega_0 t) - 0.044 \sin(2\omega_0 t)$$

3) Compare the results from this homework set #6, problem #4 and #5.

- Does using the Fourier transform for $V_1(t)$ give accurate results in predicting $V_2(t)$?

 1

 2



| | V2 | | |
|---|----------|-----------|-----------|
| | DC | AC: 1kHz | AC (2KHz) |
| Calculated HW #6 | 11.16 V | 2.200 Vpp | 0 Vpp |
| Simulated HW #6 | 11.026 V | 2.588 Vpp | ? |
| Calculated Using Fourier Transforms HW #7 | 11.161 V | 2.422 Vpp | 0.199 Vpp |

DC to AC

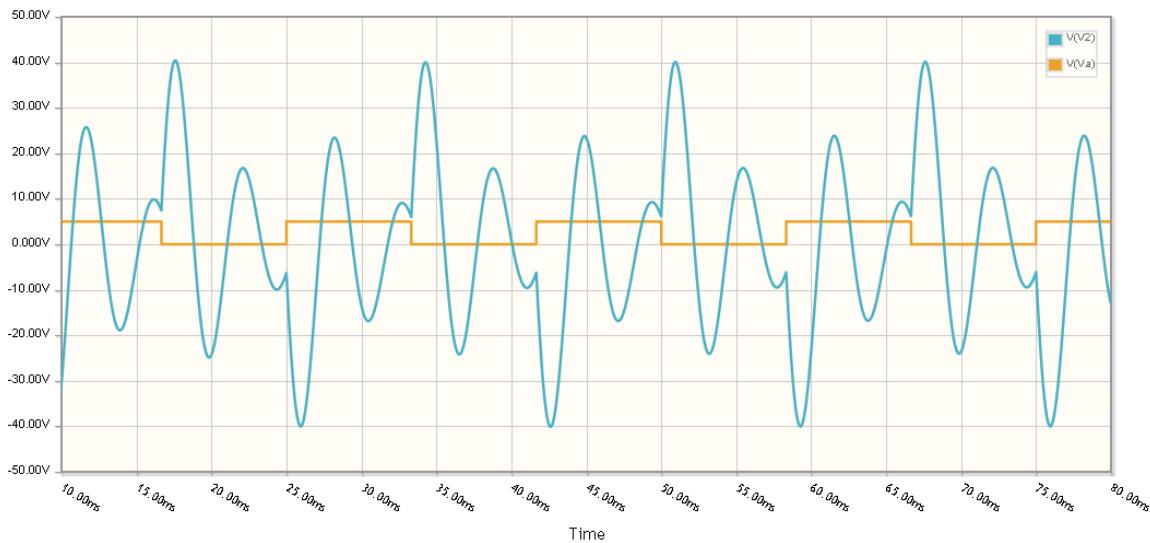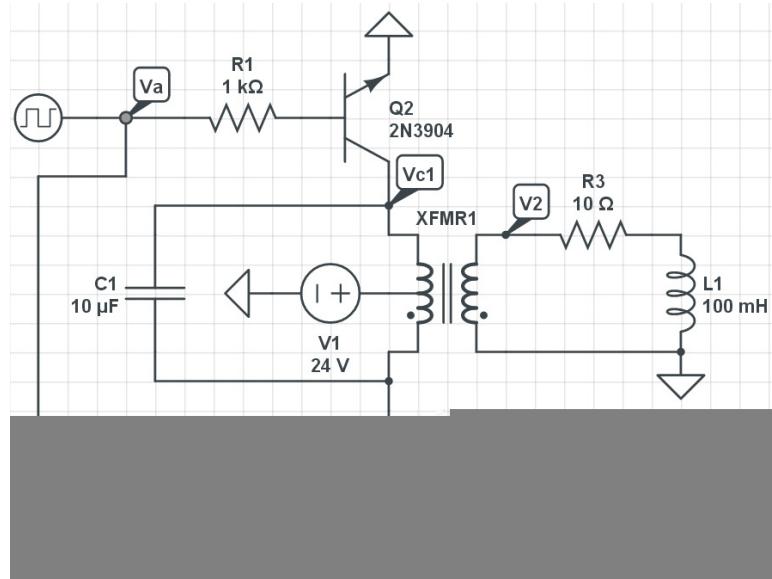4) Let

- A = 0V / 5V square wave, 60Hz, 0 degree time delay
- B = 0V / 5V square wave, 60Hz, 180 degree time delay
- C1 = 10μF

Determine using CircuitLab the voltage V2 (i.e. the voltage across a DC motor, modeled as a 10 Ohm 200mH load)




5) Adjust C so that the voltage across the motor is close to a sine wave as possible (trial and error)

Part of the problem is the LC isn't resonant at 60Hz do this, let the LC tank resonate at 60Hz (rad/sec)

$$Ls + \frac{1}{C} = s^2 + \frac{1}{C} L^2$$


$$\frac{1}{LC} = 377^2$$
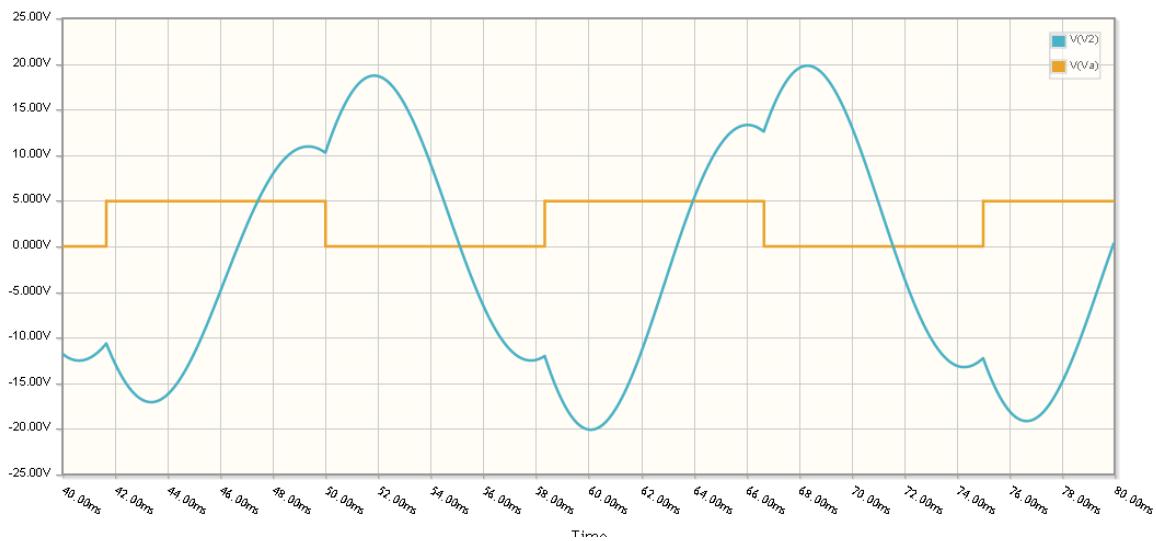
$$L = 100\text{mH}, C = 70.36\mu\text{F}$$




$v_2(t)$ with $C = 70.36\mu\text{F}$

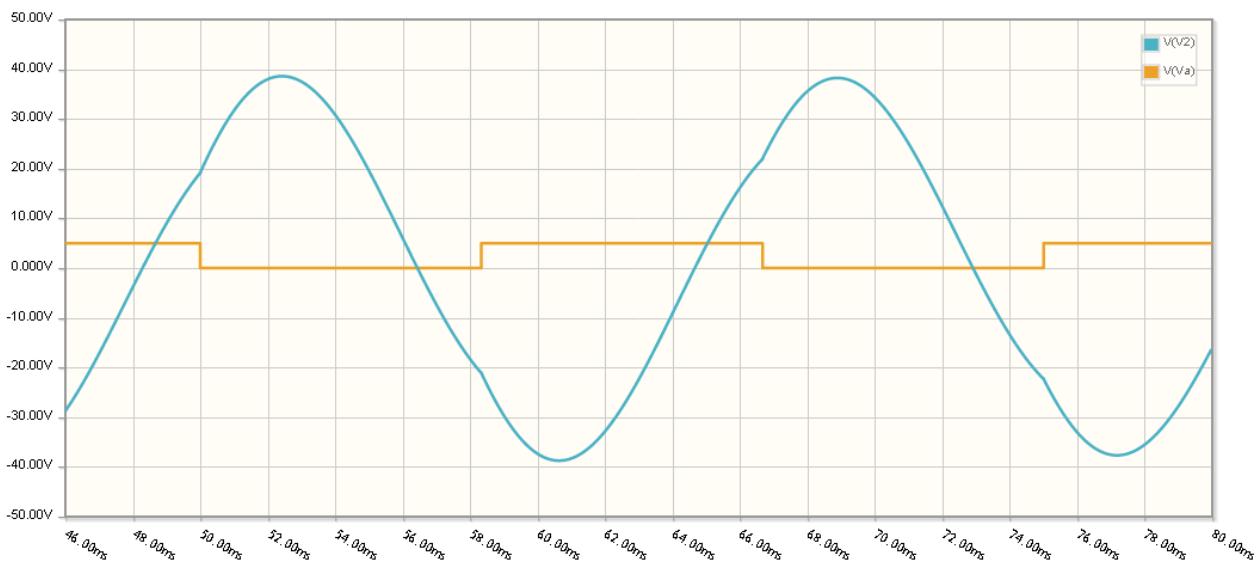Increasing C to 110 μF works slightly better (closer to a 60Hz sine wave at V2)



SCR

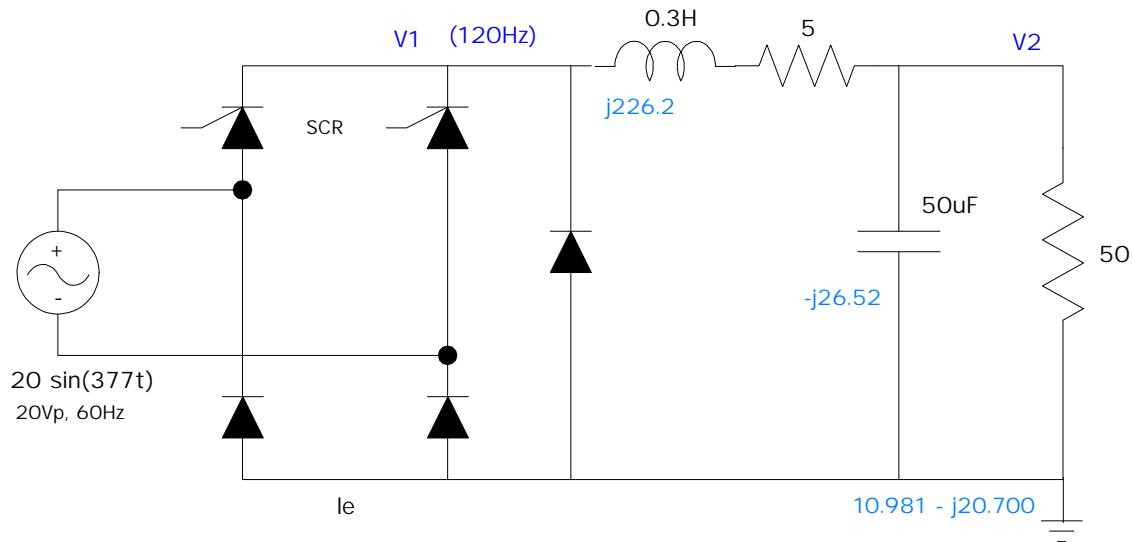6) Assume a firing angle of 25 degrees. Determine the voltage at V1 and V2 (both DC and AC).



$$V_1(D_C) = \frac{V_p + 0.7}{p} (1 + \cos q) - 0.7$$

$$V_1(D_C) = \frac{18.6 + 0.7}{p} (1 + \cos(25^\circ)) - 0.7$$

$$V_1(D_C) = 11.011V$$

$$V_2(D_C) = \frac{50}{50+5} 11.011V = 10.010V$$

$$V_1(A_C) = 18.6V - (-0.7V) = 19.3V_{pp}$$

$$V_2(A_C) = \frac{(10.981 + j20.700)}{(10.981 + j20.700 + (5 + j226.2))} \times 19.3V_p$$

$$V_2(A_C) = 2.194V_{pp}$$

7) Change this circuit so that

- The voltage at V2 is 8.00V (DC)
- With a ripple of 500mVpp

DC Analysis

$$V_1(D_C) = \frac{50+5}{50} \cdot 8.00V = 8.80V$$

$$V_1(D_C) = \frac{V_p + 0.7}{p} (1 + \cos q) - 0.7$$

$$8.80V = \frac{18.6 + 0.7}{p} (1 + \cos q) - 0.7$$

$$q = 56.88^\circ$$

AC Analysis

$$V_1(A_C) \approx 19.3V_{pp}$$


When C = 50μF, V2(AC) = 2.194Vpp

If C is 2x larger, the ripple is 2x smaller

$$C \otimes \frac{2.194/p}{0.5V_p} \cdot 50\text{mF} = 219.4\text{mF}$$

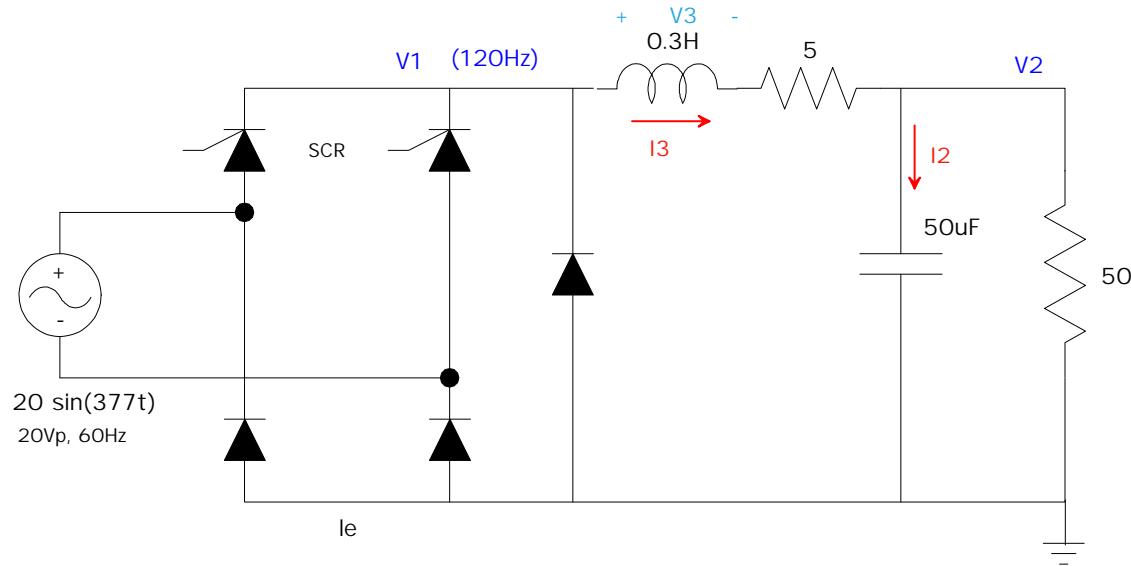8) Simulate this circuit in Matlab by

- Writing the differential equations which describe this circuit (state variables: I_L and V_C)
- Specify $V_1(t)$ as a full-wave rectified sine wave tipped at X degrees (from problem #4)
- Use numerical integration to find $V_2(t)$



$$V_3 = 0.3 \frac{dI_3}{dt} = V_1 - 5I_3 - V_2$$

$$I_2 = 219.4 \text{ mF} \quad \frac{dV_2}{dt} = I_3 - \frac{V_2}{50}$$

The coupled differential equations that describe this circuit is thus

$$\frac{dV_2}{dt} = 4557.9 I_3 - 91.158 I_2$$

$$\frac{dI_3}{dt} = 3.333 V_1 - 16.667 I_3 - 3.3333 I_2$$

Solving in Matlab using numerical integration

Matlab Script:

```
t = 0;
dt = 1e-6;
I3 = 0;
V2 = 0;
V = [];

while(t < 10/120)

    phase = mod(377*t,pi);

    if(phase < 56.88*pi/180)
        V1 = -0.7;
    else
        V1 = 20*sin(phase) - 1.4;
    end
    V1 = max(V1, -0.7);

    dV2 = 4557.9*I3 - 91.158*V2;
    dI3 = 3.333*V1 - 16.667*I3 - 3.3333*V2;

    V2 = V2 + dV2*dt;
    I3 = I3 + dI3*dt;
    t = t + dt;


    if(t > 8/120)
        V = [V ; V1, V2];
    end
end

t = [1:length(V)]' * dt;
plot(t,V(:,1),'b',t,V(:,2), 'r');
```

Result:

```
ans =
V1(DC)   V2(DC)
8         2
>> max(V) - min(V)
ans =
V1pp      V2pp
0         0
```

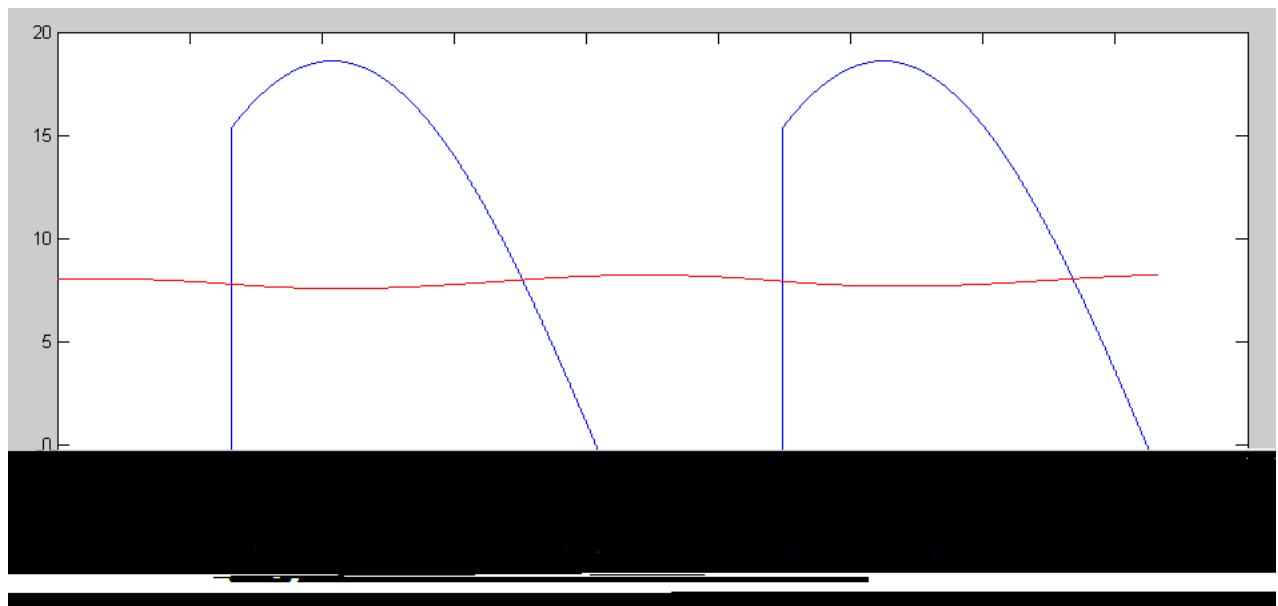The AC term is slightly off due to approximating the first harmonic as max-min rather than the 1st term in the Fourier series expansion.



Resulting Signals at V1 (blue) and V2 (red)