

ECE 320 - Homework #8


Boolean Logic, DTL, TTL Logic. Due Monday, March 8th

Boolean Logic

- Implement the following function using NAND gates (i.e. circle the ones)

f(A,B,C,D)		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$Y = A + C'D' + BC' + BD'$$

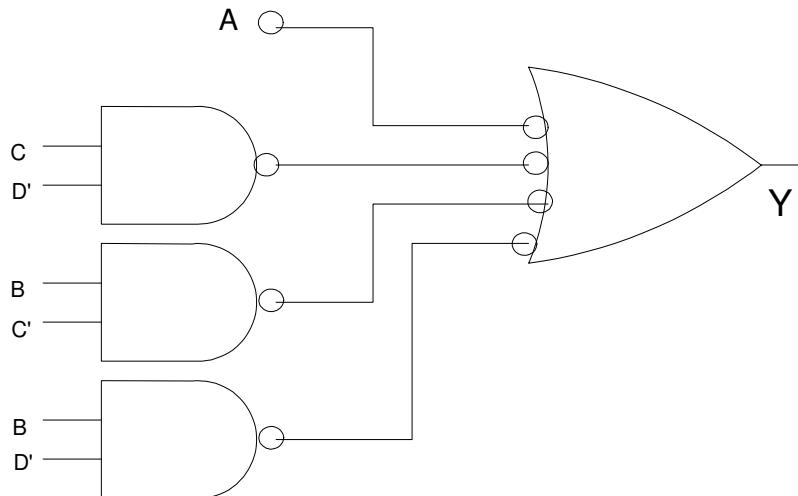


2) Implement the following function using NOR gates (i.e. circle the zeros)

f(A,B,C,D)		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x


$$Y' = CD + A'B'D + A'B'C$$
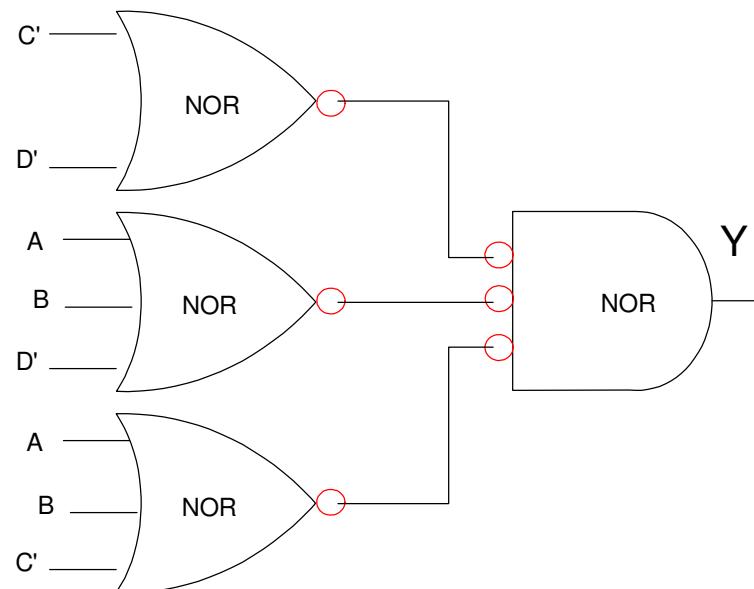
$$Y = (C' + D')(A + B + D')(A + B + C')$$



DTL Logic

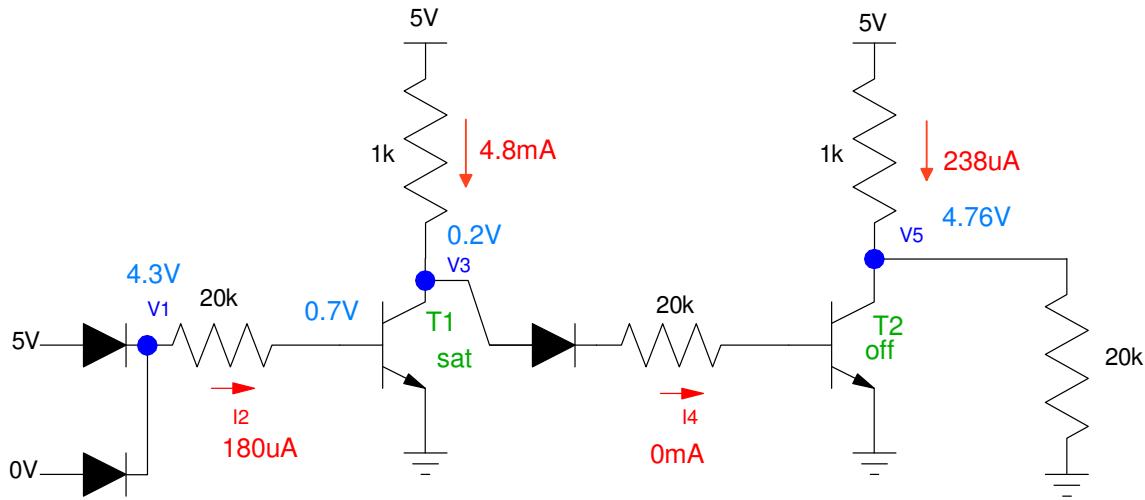3) Determine the voltages and currents for the following DTL OR gate



The 5V source turns on transistor T1 (saturated)



$$I_2 = \left(\frac{5V - 0.7V - 0.7V}{20k} \right) = 180\mu A$$

$$\beta I_2 = 18mA > 4.8mA \quad T1 \text{ is saturated}$$

0.2V at V3 isn't enough to turn on T2 (off)

$$V_5 = \left(\frac{20k}{20k+1k} \right) 5V = 4.76V$$

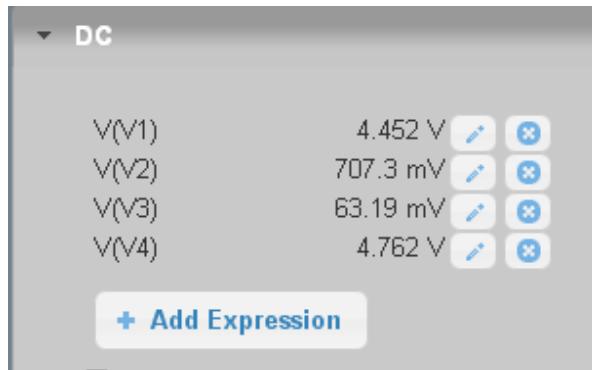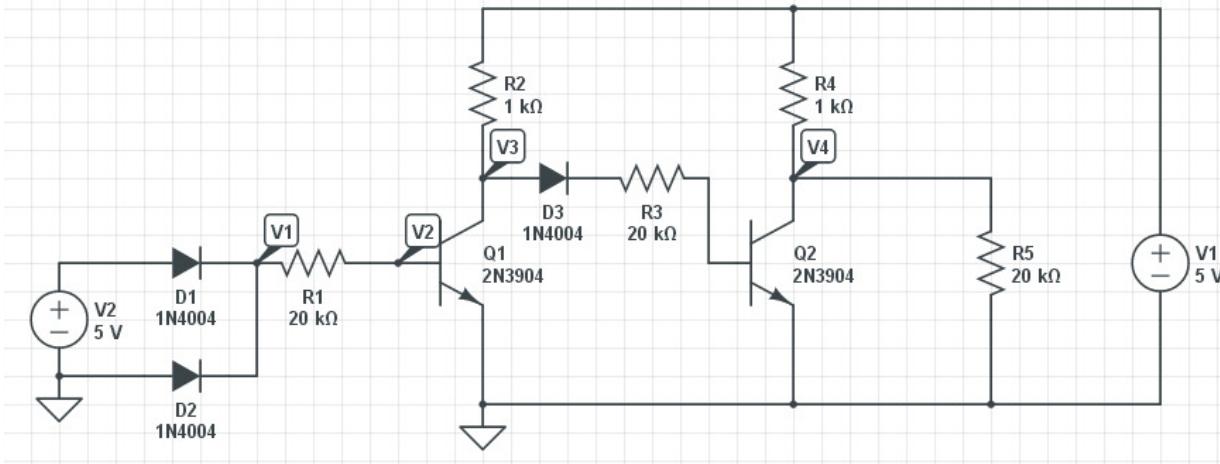- 4) Simulate this circuit in CircuitLab to verify your answers for problem #3




	V1	V2	V3	V4
Calculated	4.3V	0.7V	0.2V	4.76V
Simulated	4.452V	0.707V	0.063V	4.762V


The circuit below uses a DTL NAND gate to drive the speaker when

- The 555 timer outputs 5V, and
- The comparitor outputs 5V.,


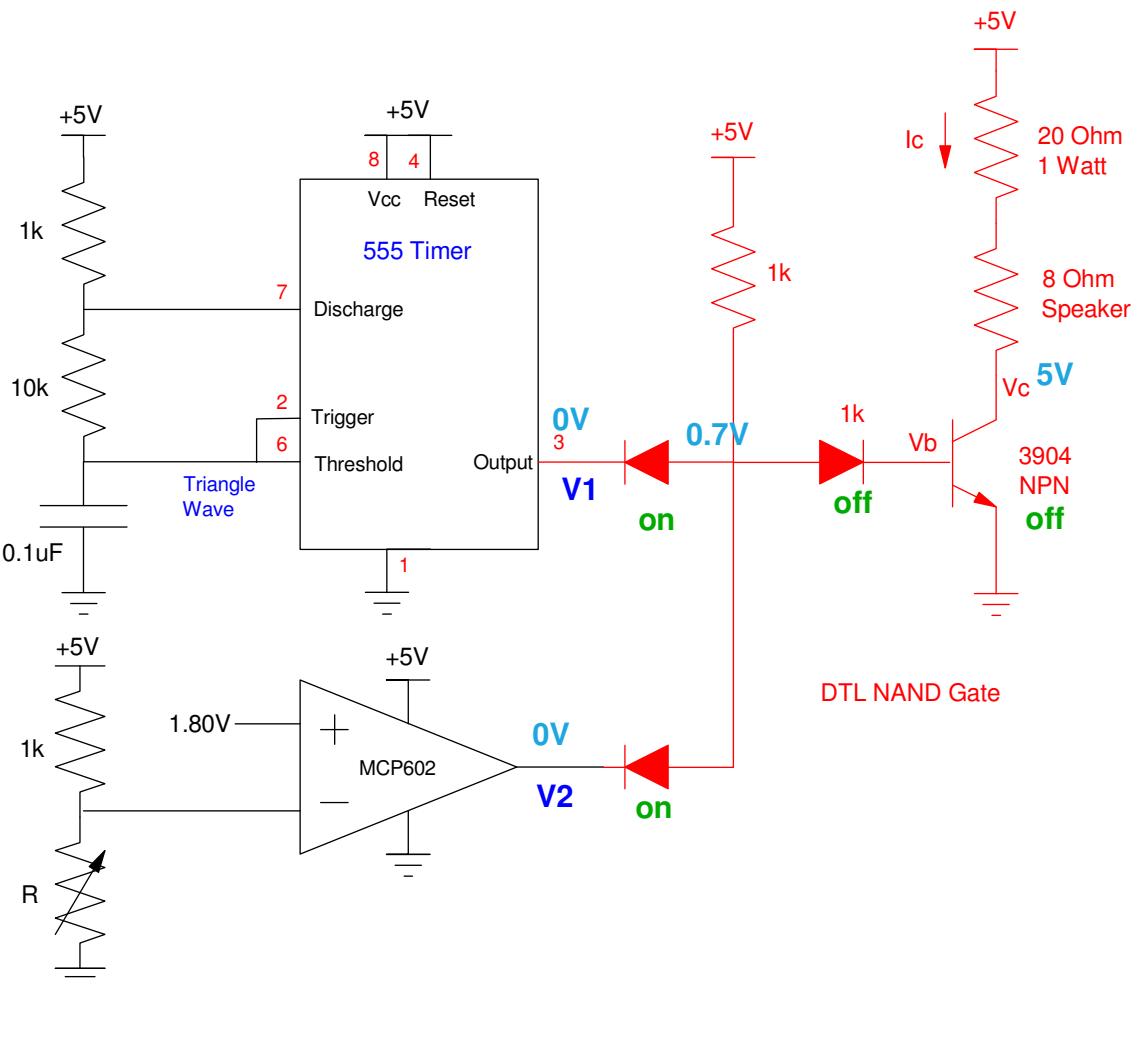
5) Determine the voltages when

- $V_1 = V_2 = 0V$ (red)
- $V_1 = V_2 = 5V$
- $V_1 = 0V, V_2 = 5V$ (blue)



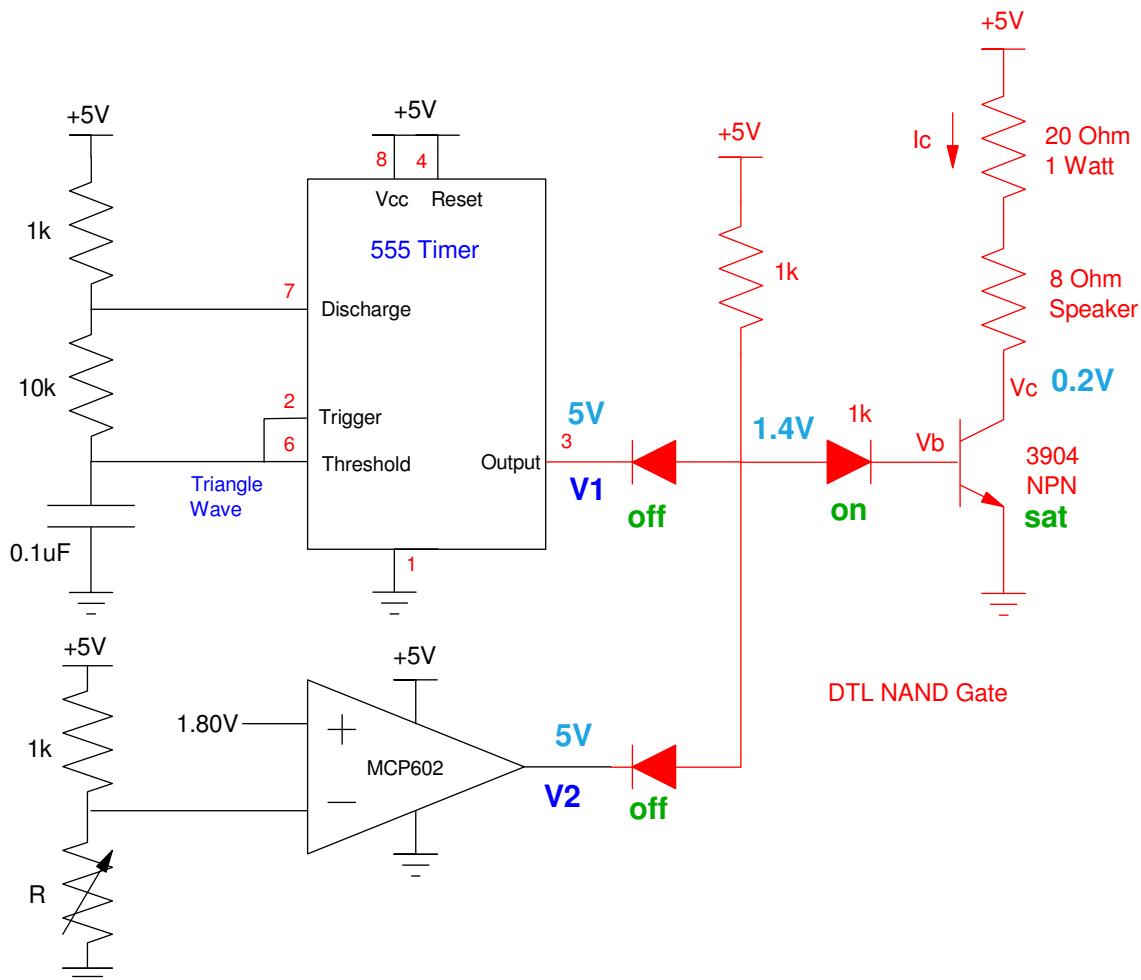

6) Verify your design using CircuitLab.

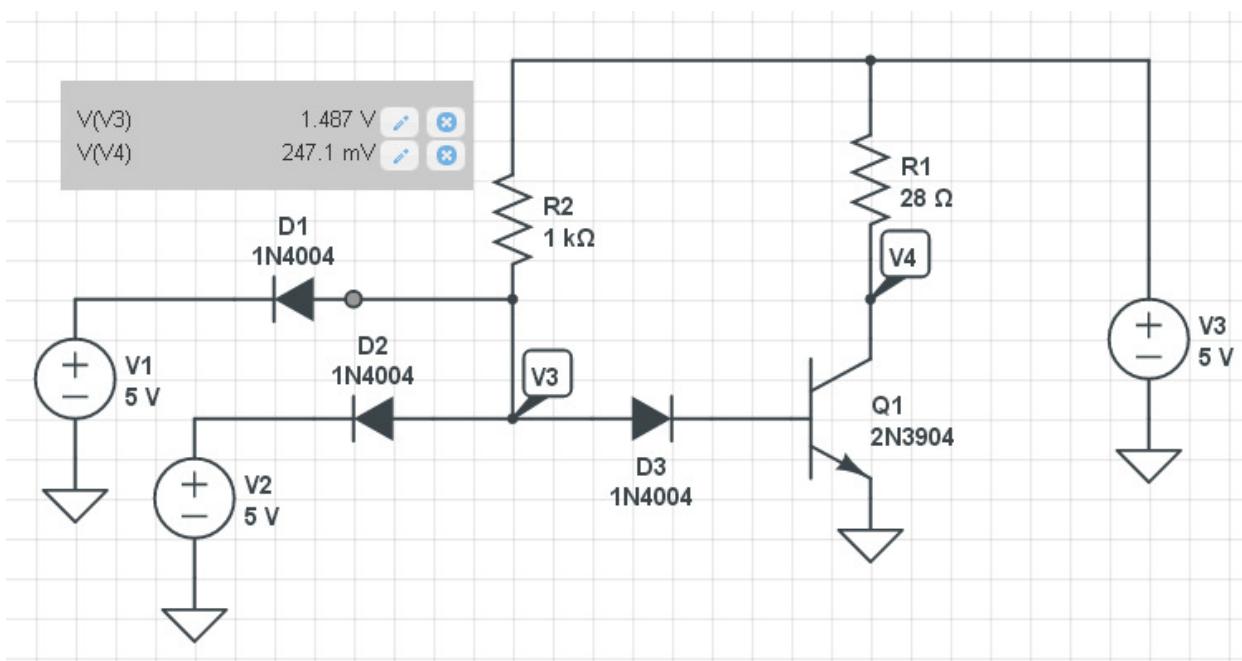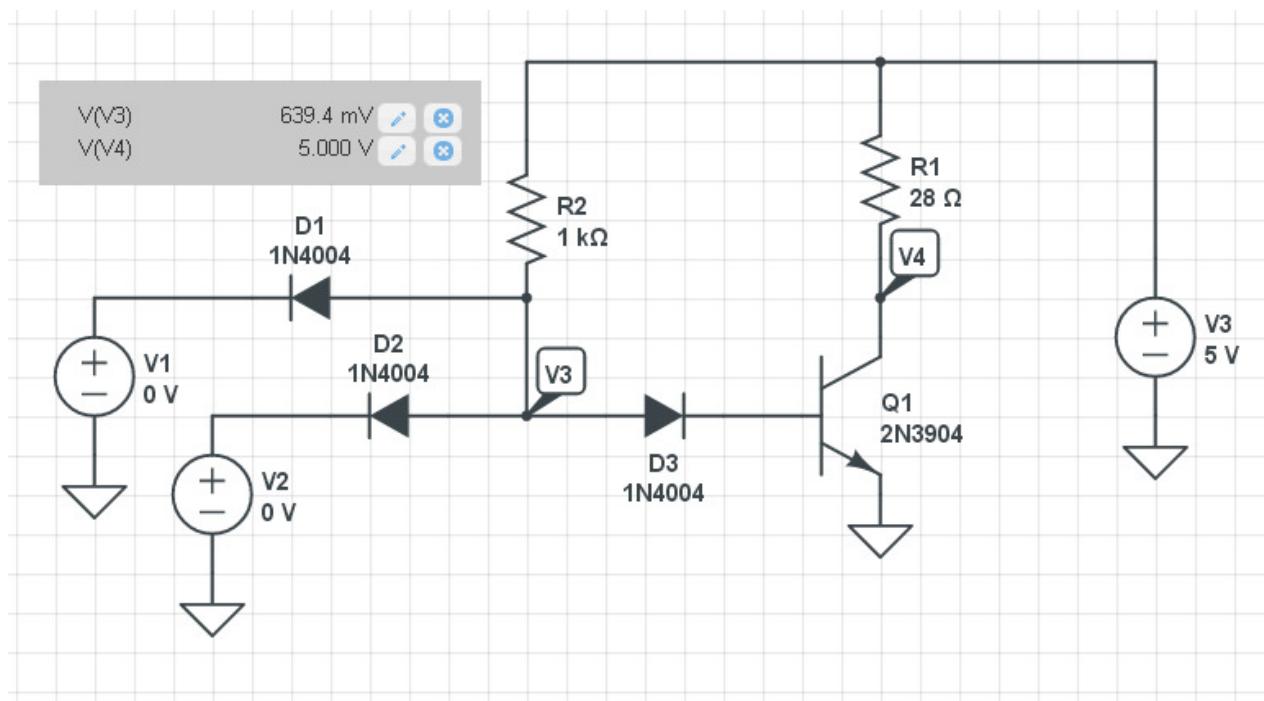

Lab: 7) (20pt): Verify your design in hardware (build and test the circuit with your lab kit).




- The 555 timer from homework set #5 for V1, and
- Connecting theThe comparitor from homework set #5 for V2

Verify that

- The speaker turns on when $T > T_{on}$ and
- The speaker turns off when $T < T_{on}$



Setting the comparitor to turn on at 1.80V

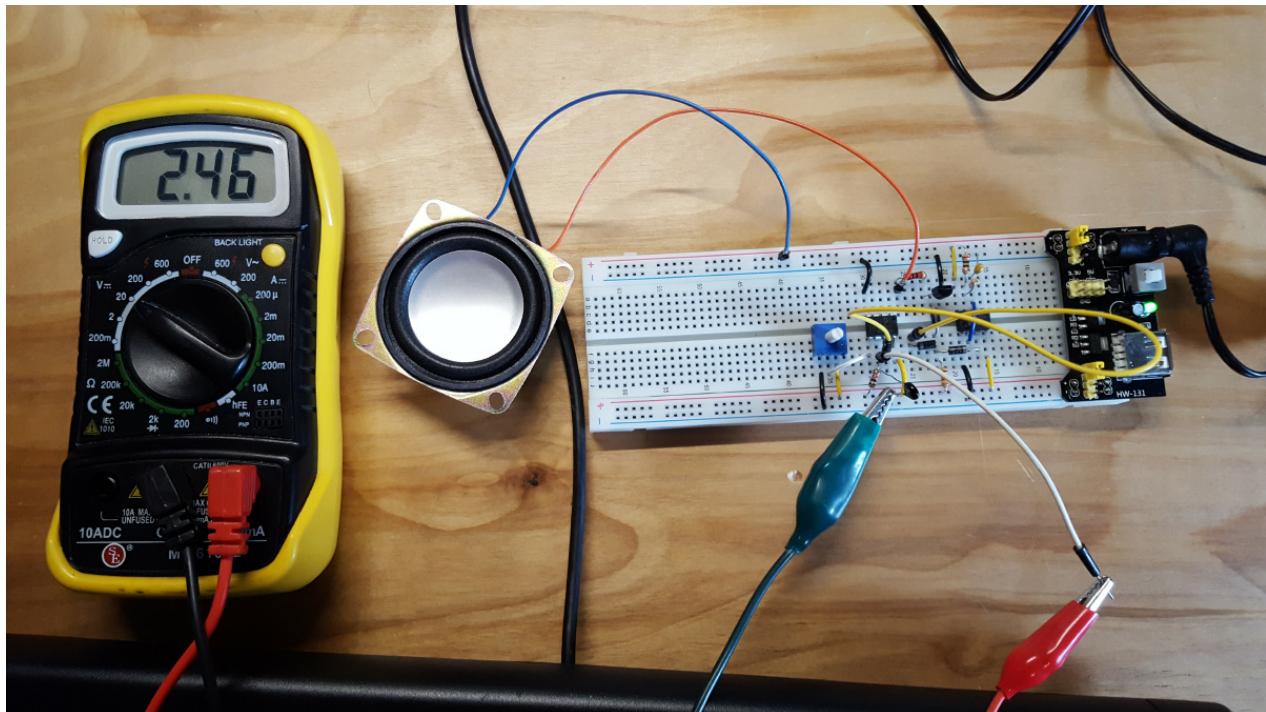- Speaker turns on when $V_r < 1.80V$
- Speaker turns off when $V_r > 1.83V$



TTL Logic

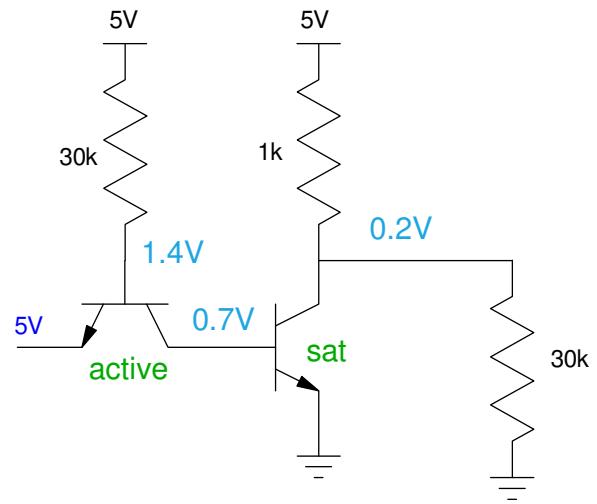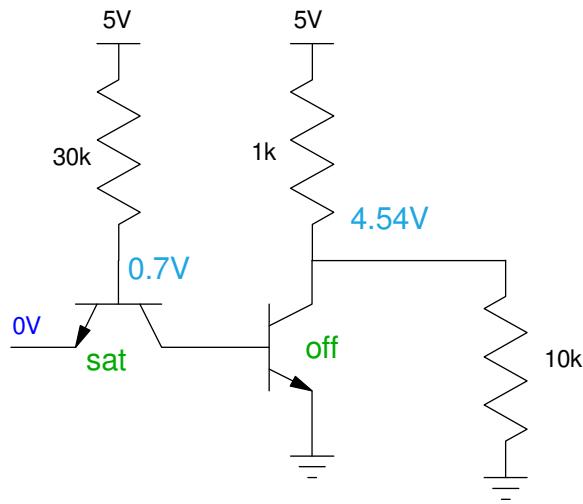- 8) Determine the voltages for the following TTL inverter. Assume 3904 transistors.



9) Simulate these circuits in CircuitLab and determine the voltage and currents

