
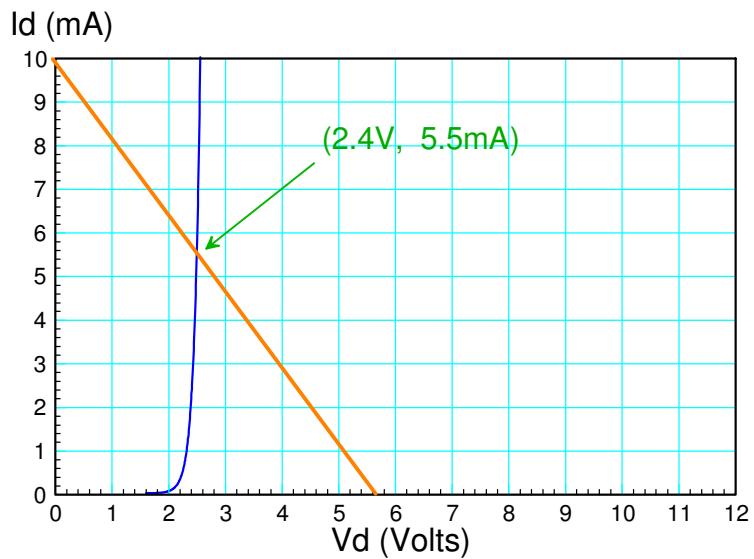


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

- 1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

R $900 + 100 \cdot \text{mo} + \text{day}$	Load Line x-intercept (volts)	Load Line y-intercept (mA)	V_d Volts	I_d mA
1414	5.857V	10.0mA	2.4V	5.5mA

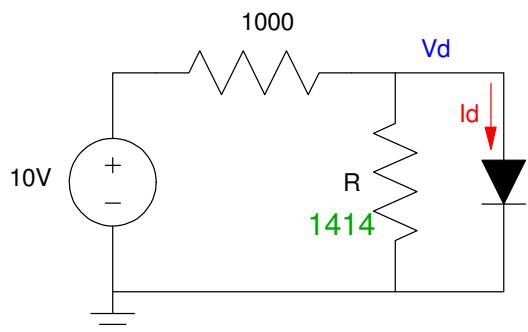

x-intercept ($I_d = 0$)

$$V_d = \left(\frac{1414}{1414+1000} \right) 10V = 5.857V$$

y-intercept ($V_d = 0$)

$$I_d = \left(\frac{10V}{1000\Omega} \right) = 10mA$$

2) Nonlinear equations: Diode circuit


Assume the VI characteristics for the diodes shown below are

$$V_d = 0.038 \ln(10^{11} \cdot I_d + 1) \quad I_d = 10^{-11} \cdot$$

3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 900 + 100*(\text{your birth month}) + (\text{birth date}).$

R $900 + 100*\text{mo} + \text{day}$	I_{d1}	I_{d2}	I_{d3}
1414	0	1.578mA	0
V1	V2	V3	V4
7.571V	7.291V	6.871V	0V

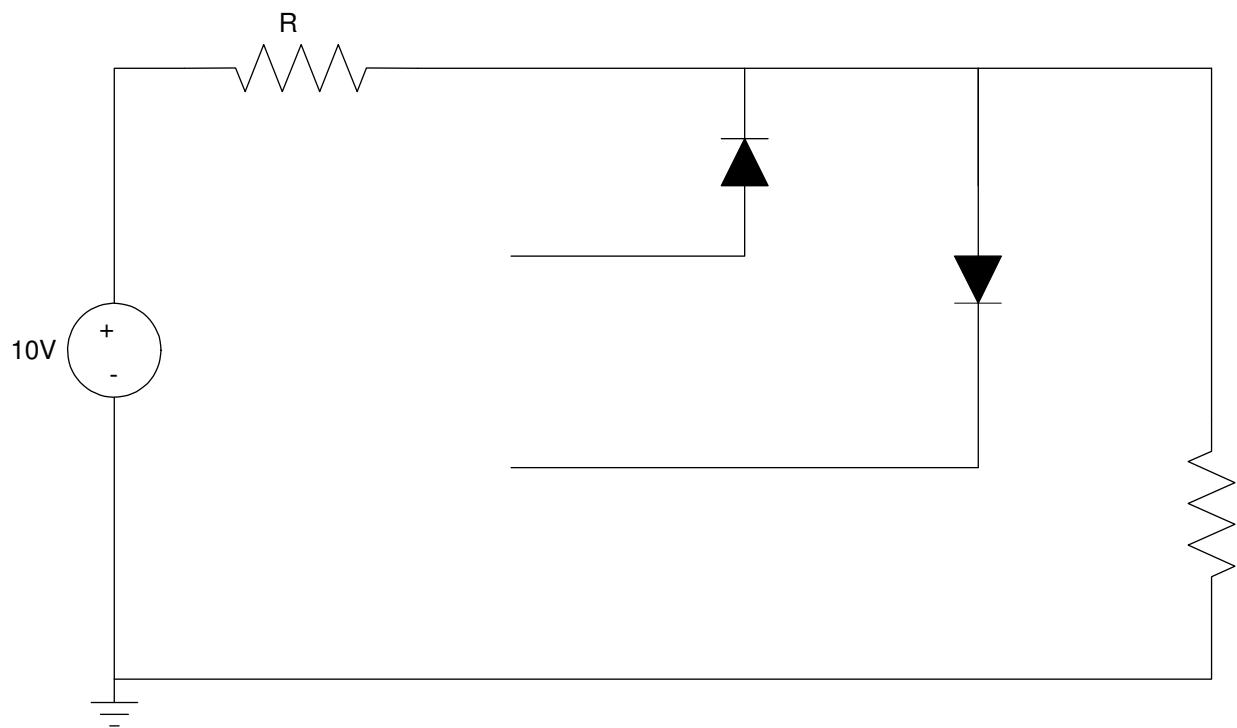


ECE 320 - Final (pt 2) - Name _____

Transistors and Mosfets

- 6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 5V$

R 900 + 100*Mo + Day	Current Gain $h_{fe} = \beta$	Load Line x-intercept (Volts)	Load Line y-intercept (mA)	V_{ce} $V_{in} = 5V$	I_c $V_{in} = 5V$
1414	25	20V	133.3mA	8.596V	76.025mA

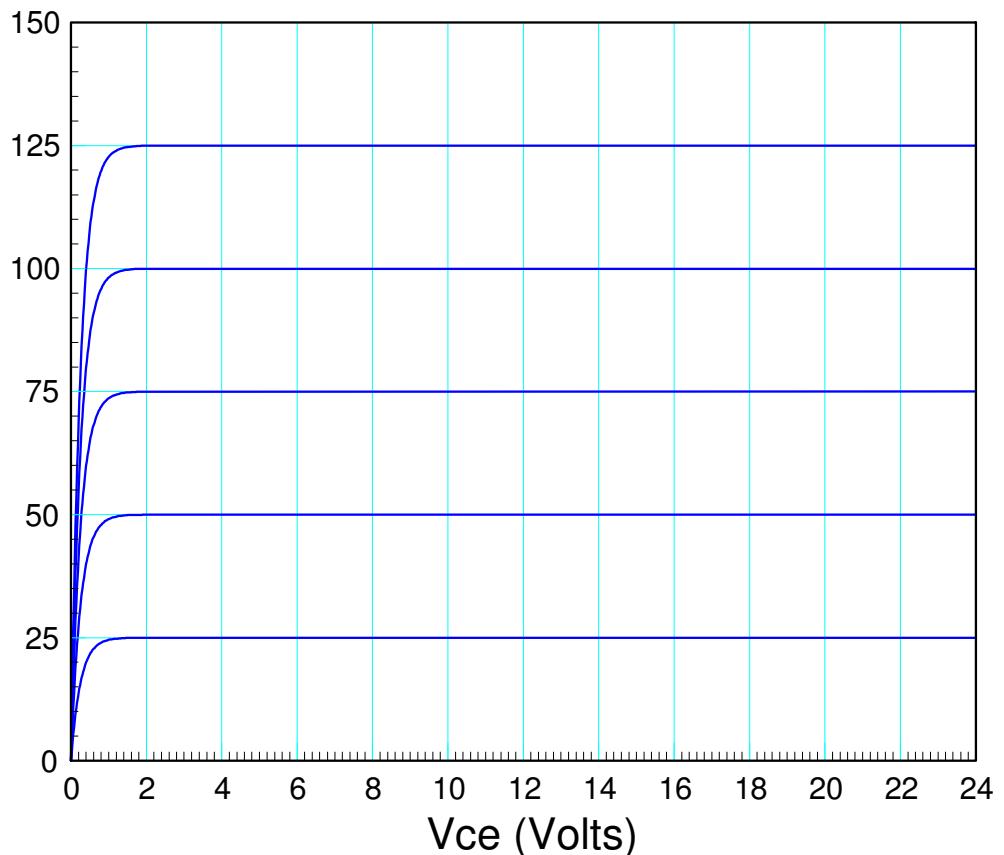


7) Design a Schmitt Trigger & transistor switch

- Turns on the LED at $R_t < 2000$ Ohms
- Turns off the LED when $R_t > 2200$ Ohms

Assume

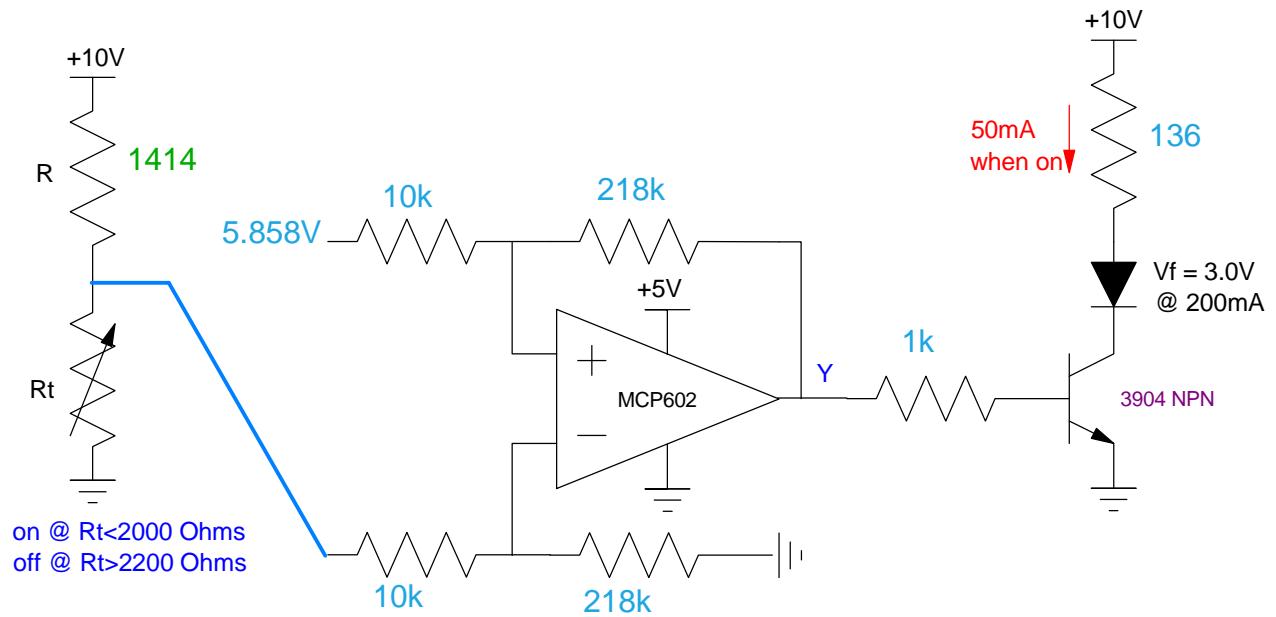- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $V_{ce(\text{sat})} = 0.2V$
- Current gain $b^- = 100$




$$R_t = 2000:$$

•

8) DTL Logic: Determine the voltages and currents for the following DTL logic gage. Assume

- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta=100$)


R $900 + 100 \cdot \text{mo} + \text{da}$	V1	V2	V3	I4	I5	I6
1414	0.2V saturated	9.021V off	0.2V saturated	2.051mA	0 off	4.895mA

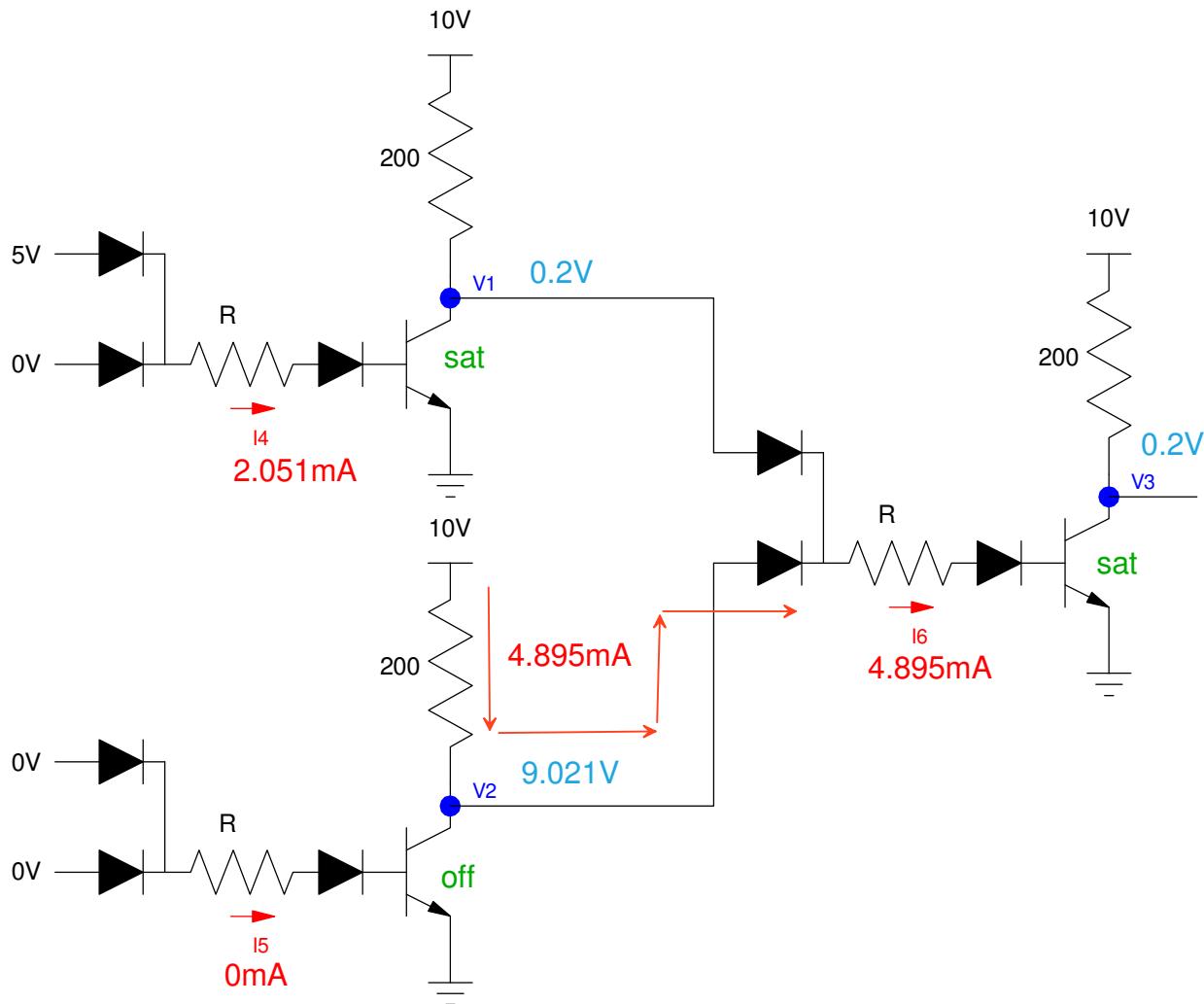

9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine { V_{ds} , I_{ds} } when $V_g = 7V$

k_n transconductance gain	Load Line $x=$ intercept	Load Line y intercept	V_{ds} $V_g = 7V$	I_{ds} $V_g = 7V$	Operating Region off / active / ohmic
0.015 A/V²	10V	222.2 mA	4.6V	120mA	saturated

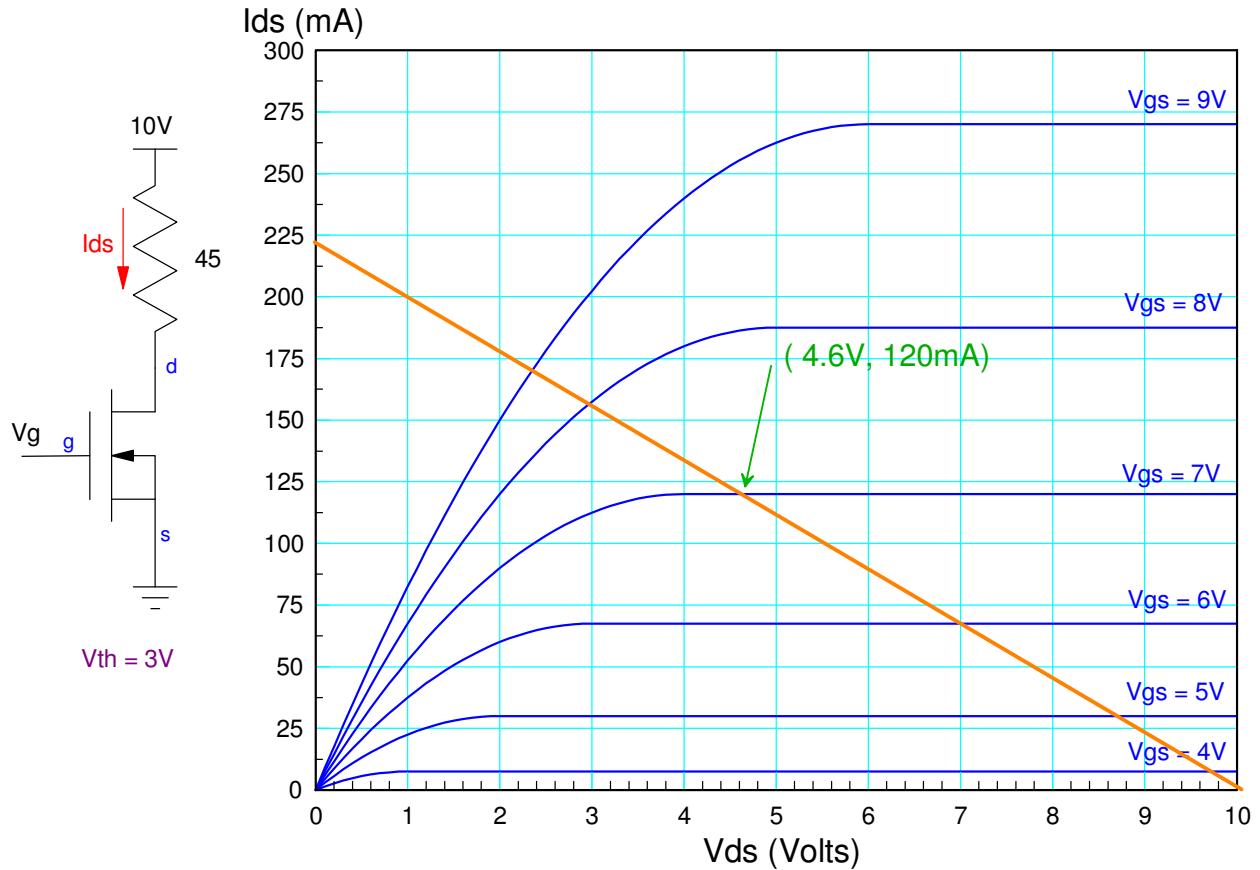

$$270mA = \frac{k_n}{2}(9V - 3V)^2$$

$$k_n = 0.015 \frac{A}{V^2}$$

10) CMOS Logic

a) Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD				
		00	01	11	10	
AB		00	0	0	1	1
01		x	0	x	0	
11		0	x	x	0	
10		1	1	0	0	

$$\bar{Y} = B + \bar{A}\bar{C} + AC$$

