

# ECE 320 - Homework #7

DC to AC, SCR. Due Monday, February 28th


## DC to AC

1) Let  $L1 = 200\text{mH}$

- $V_a = 0\text{V} / 5\text{V}$  square wave, 60Hz, 0 degree time delay
- $V_b = 0\text{V} / 5\text{V}$  square wave, 60Hz, 180 degree time delay
- $C1 = 10\mu\text{F}$

Determine using CircuitLab the voltage  $V2$  (i.e. the voltage across a DC motor, modeled as a 10 Ohm & 100mH load)

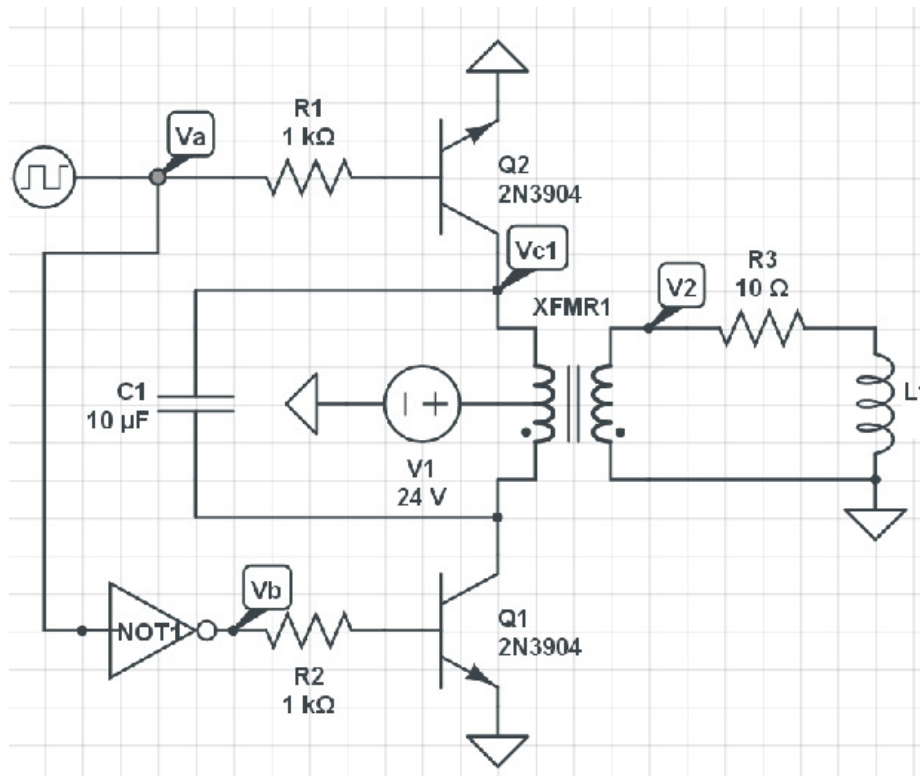
2) Adjust  $C1$  so that the voltage across the motor is as close to a sine wave as possible (trial and error)



DC to AC Converter (problem 1 & 2)

## Circuits and Differential Equations

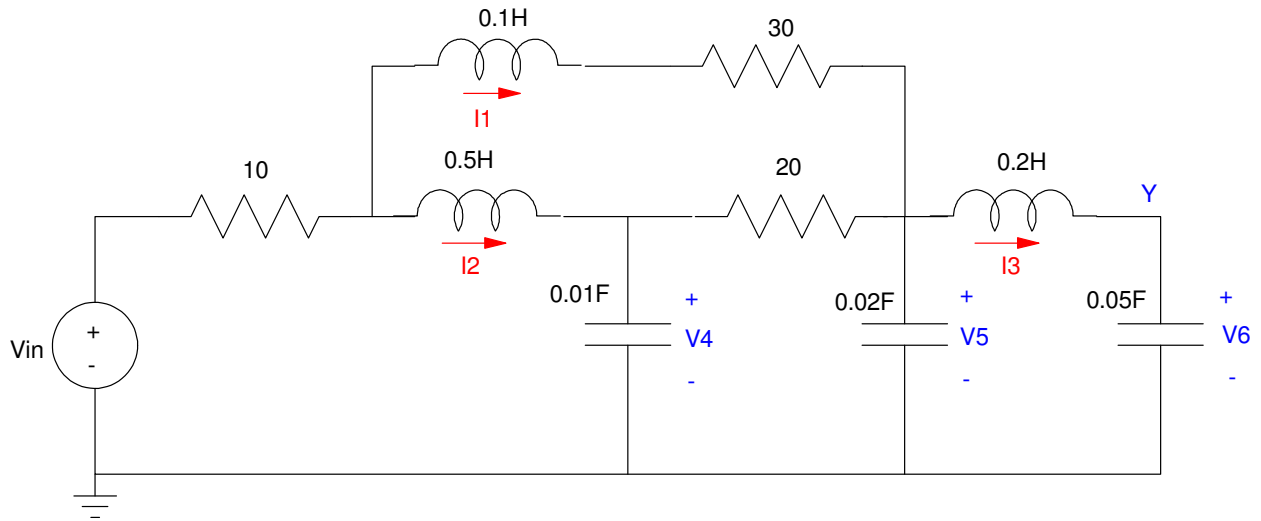3) Write the differential equations that describe the following circuit



## SCR

4) Assume a firing angle of 45 degrees. Determine the voltage at V1 and V2 (both DC and AC).

5) Change this circuit so that

- The voltage at V2 is 9.00V (DC)
- With a ripple of 1.00Vpp

6) Simulate this circuit in Matlab by

- Writing the differential equations which describe this circuit ( state variables:  $I_L$  and  $V_C$  )
- Specify  $V_1(t)$  as a full-wave rectified sine wave going from  $\theta$  to  $\pi + \theta$
- Use numerical integration to find  $V_2(t)$

