

# ECE 320 - Quiz #2 - Name \_\_\_\_\_

Semiconductors, pn Junction, ideal diodes - Spring 2022

1a) What are holes and electrons?

**Electrons:** negatively charged particles that form covalent bonds and move around to carry current.

**Holes:** A missing electron in a covalent bond. A missing negative charge behaves like a positive charge.

1b) The voltage drop across a silicon diode is about 0.7V.

- Does this voltage go up or down as temperature goes up?
- Why does this happen?

**Voltage goes down.**

The voltage across a pn junction is a function of the doping level / the intrinsic carrier concentration level

$$V_d = V_T \cdot \ln\left(\frac{N_A N_D}{n_i^2}\right)$$

As temperature goes up, the number of thermal holes and electrons ( $n_i$ ) goes up. This makes the doping level less significant, making the diode pn-junction less distinct, reducing the voltage.

2) An 0603 resistor has the following dimensions

- $L = 0.06\text{cm}$
- $W = 0.03\text{cm}$
- $H = 0.02\text{cm}$

Determine the doping required to make a resistance of R ohms where

- $R = 1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ .
- For example, May 14th would give  $R = 1714$  Ohms

R $1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$	Required Doping of Boron atoms / cc
<b>1714</b>	<b>7.29e14</b>

$$R = \left( \frac{\rho L}{A} \right)$$

$$1714\Omega = \left( \frac{\rho \cdot 0.06\text{cm}}{(0.03\text{cm})(0.02\text{cm})} \right)$$

$$\rho = 17.14 \Omega \cdot \text{cm}$$

$$\sigma = \frac{1}{\rho} = 0.0583 = n_n \cdot q \cdot \mu_n$$

$$0.0583 = n_n \cdot (1.6 \cdot 10^{-19}) \cdot (500)$$

$$n_n = 7.29 \cdot 10^{14} \frac{\text{atoms}}{\text{cc}}$$


3) Thermistors: Assume the VI characteristics of a thermistor are

$$R_T = 2000 \exp\left(\frac{4350}{T+273} - \frac{4350}{298}\right) \Omega$$

where T is the temperature in degrees C. Determine  $R_T$  and the temperature if  $V_1 = 7.3V$

- Let R be  $1200 + (\text{your birth month}) * 100 + \text{your birthday}$ . ( March 14th would give  $R = 1714 \text{ Ohms}$  )

R 1200 + 100*Month + Day	$R_T$ (Ohms) Thermistor	Temperature (C)
<b>1714 Ohms</b>	<b>2662 Ohms</b>	<b>19.27 C</b>

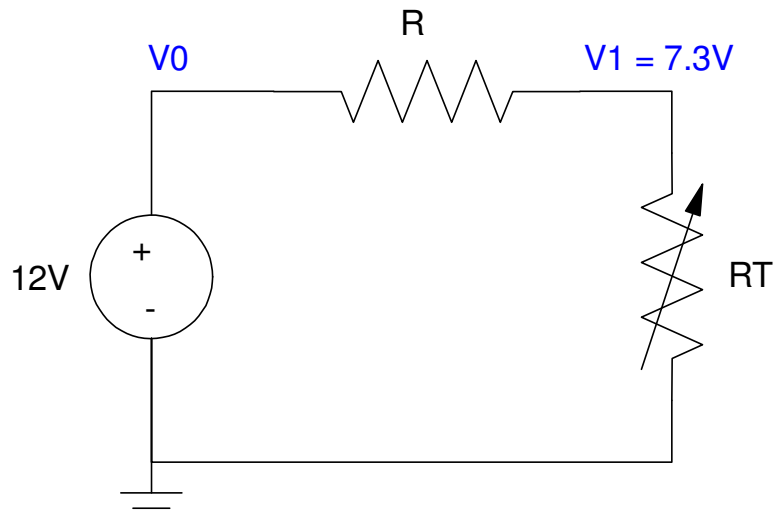

$$V_1 = 7.3V = \left(\frac{R_T}{R_T + 1714}\right) 12V$$

$$R_T = \left(\frac{7.3V}{12V - 7.3V}\right) 1714\Omega$$


$$R_T = 2662.17\Omega$$

$$T = 19.27^\circ C$$

4) Load Lines: The VI characteristic for a diode is show on the graph below. Draw the load line for the following circuit and from the graph, determine  $V_d$  and  $I_d$

- Let R be  $1200 + 100 * (\text{Birth Month}) + (\text{Birthday})$

R $1200 + 100 * \text{Month} + \text{Day}$	Load Line x-intercept	Load Line y-intercept	$V_d$	$I_d$
<b>1714</b>	<b>10V</b>	<b>5.83mA</b>	<b>3.3V</b>	<b>3.8mA</b>

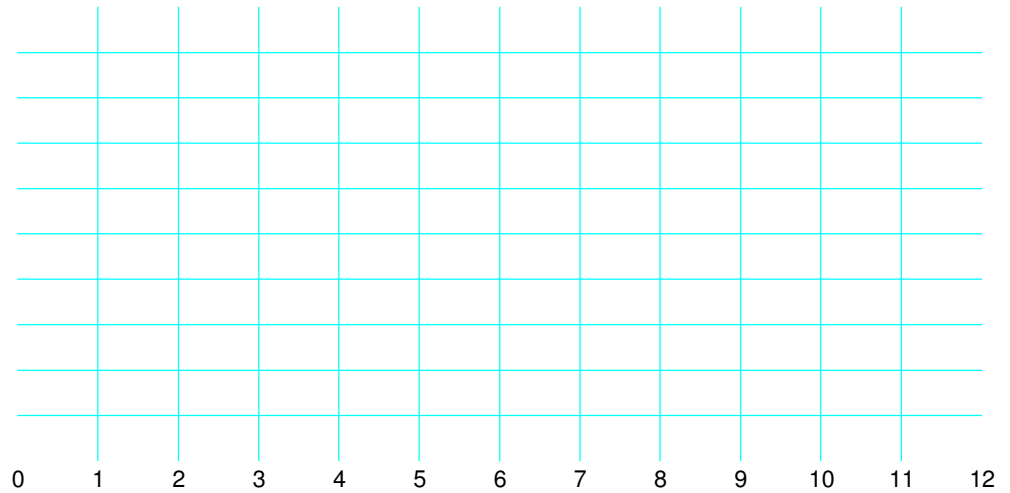

5) Diodes (nonlinear equations): Assume

- The VI characteristics of a diode are

$$I_d = 10^{-11} \cdot \left( \exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

- $R = 1200 + 100 * (\text{your birth month}) + (\text{your birth date})$ .

Write 7 equations so solve for 7 unknowns:  $V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}$

- note: don't solve.

