

# ECE 320 - Quiz #2 - Name \_\_\_\_\_

Semiconductors, pn Junction, ideal diodes - Spring 2022

- 1a) What are holes and electrons?
- 1b) The voltage drop across a silicon diode is about 0.7V.
  - Does this voltage go up or down as temperature goes up?
  - Why does this happen?

2) An 0603 resistor has the following dimensions

- $L = 0.06\text{cm}$
- $W = 0.03\text{cm}$
- $H = 0.02\text{cm}$

Determine the doping required to make a resistance of R ohms where

- $R = 1200 + 100 * (\text{your birth month}) + (\text{your birth date})$ .
- For example, May 14th would give  $R = 1714$  Ohms

<b>R</b> $1200 + 100 * (\text{your birth month}) + (\text{your birth date})$	<b>Required Doping of Boron</b> atoms / cc


3) Thermistors: Assume the VI characteristics of a thermistor are

$$R_T = 2000 \exp\left(\frac{4350}{T+273} - \frac{4350}{298}\right) \Omega$$

where T is the temperature in degrees C. Determine  $R_T$  and the temperature if  $V_1 = 7.3V$

- Let R be  $1200 + (\text{your birth month}) * 100 + \text{your birthday}$ . ( March 14th would give  $R = 1714$  Ohms )


R 1200 + 100*Month + Day	RT (Ohms) Thermistor	Temperature (C)

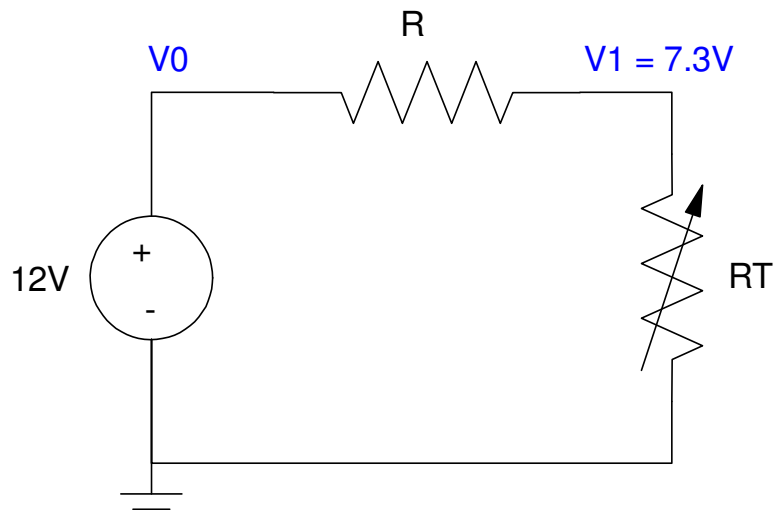

4) Load Lines: The VI characteristic for a diode is show on the graph below. Draw the load line for the following circuit and from the graph, determine  $V_d$  and  $I_d$

- Let  $R$  be  $1200 + 100 * (\text{Birth Month}) + (\text{Birthday})$

$R$ $1200 + 100 * \text{Month} + \text{Day}$	Load Line x-intercept	Load Line y-intercept	$V_d$	$I_d$

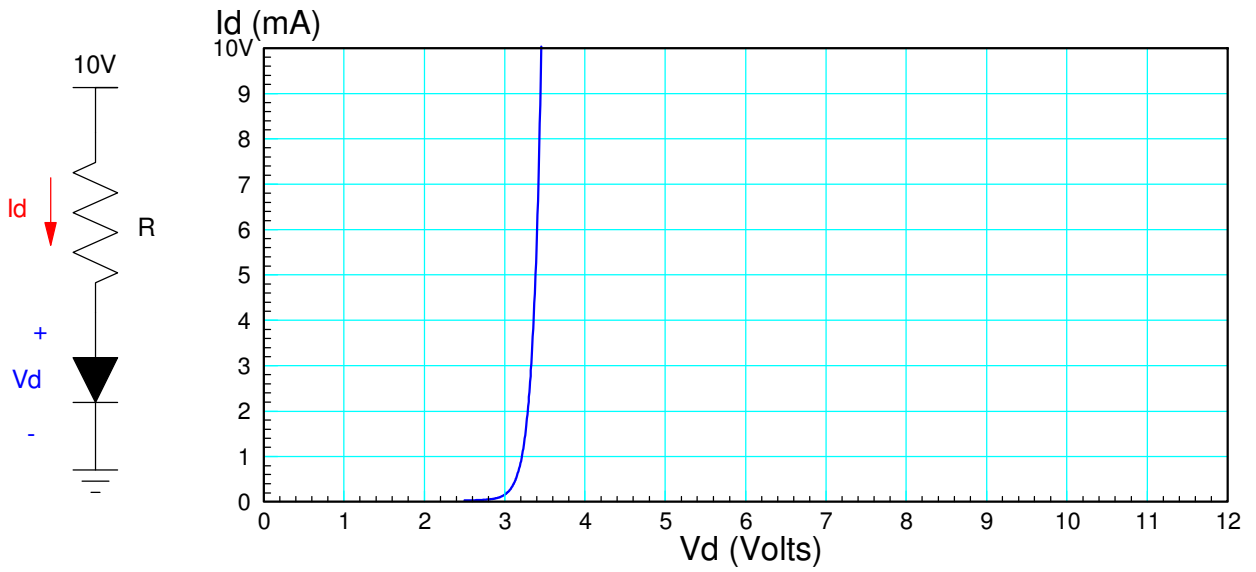

5) Diodes (nonlinear equations): Assume


- The VI characteristics of a diode are

$$I_d = 10^{-11} \cdot \left( \exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

- $R = 1200 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$ .

Write 7 equations so solve for 7 unknowns:  $V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}$

- note: don't solve.

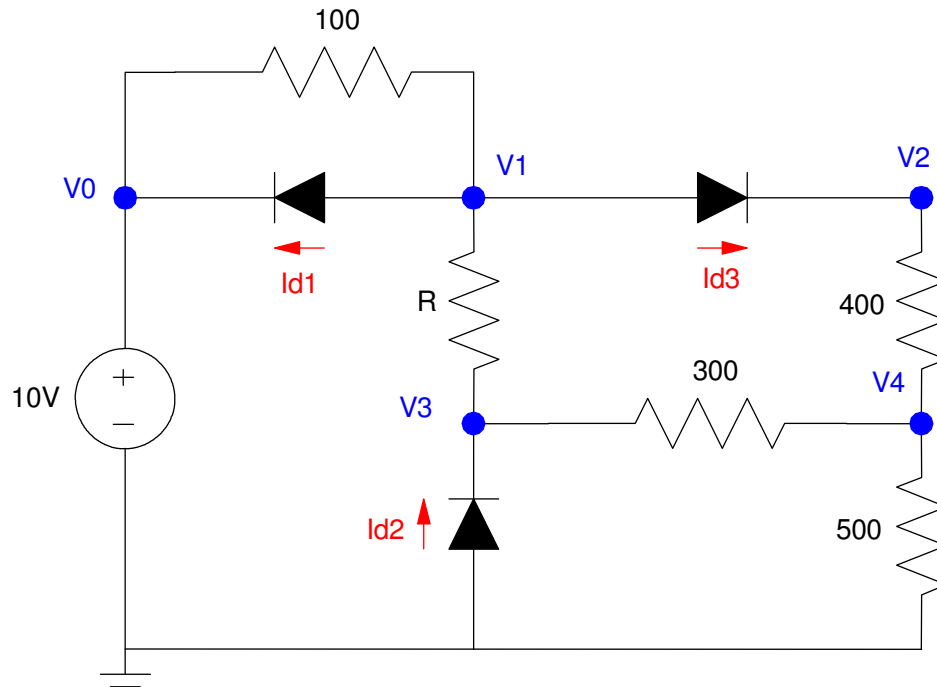

6) Diodes (nonlinear equations): Assume

- The VI characteristics of a diode are

$$I_d = 10^{-11} \cdot \left( \exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

- $R = 1200 + 100 * (\text{your birth month}) + (\text{your birth date})$ .

Write 7 equations so solve for 7 unknowns:  $V_1$ ,  $V_2$ ,  $V_3$ ,  $I_{d1}$ ,  $I_{d2}$ ,  $I_{d3}$ ,  $I_{d4}$

- note: don't solve.

