


ECE 320 - Quiz #3 - Name _____

Ideal Diodes, LEDs, AC to DC Converters - Spring 2022

1) Determine the voltages and currents for the following circuit. Assume

- R is $900 + 100 * (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1414 Ohms)


R	V1	I2	I3	I4	I5
$900 + 100 * \text{mo} + \text{day}$					

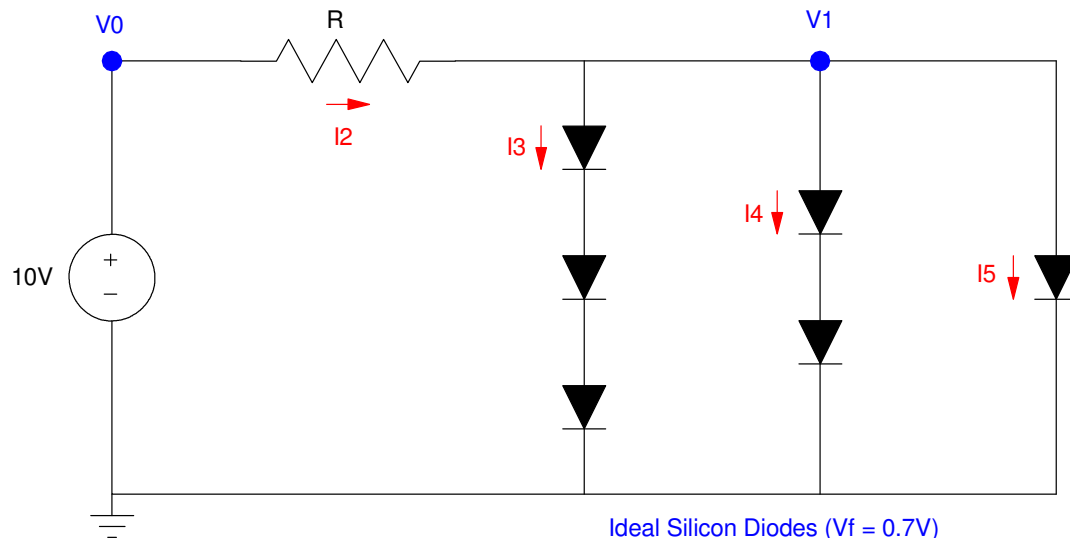

2) Determine the voltages and currents for the following circuit. Assume

- Ideal green LEDs ($V_f = 3.0V$).
- R is $900 + 100 * (\text{your birth month}) + (\text{your birthday})$.

V1	V2	V3	Id1	Id2	Id3

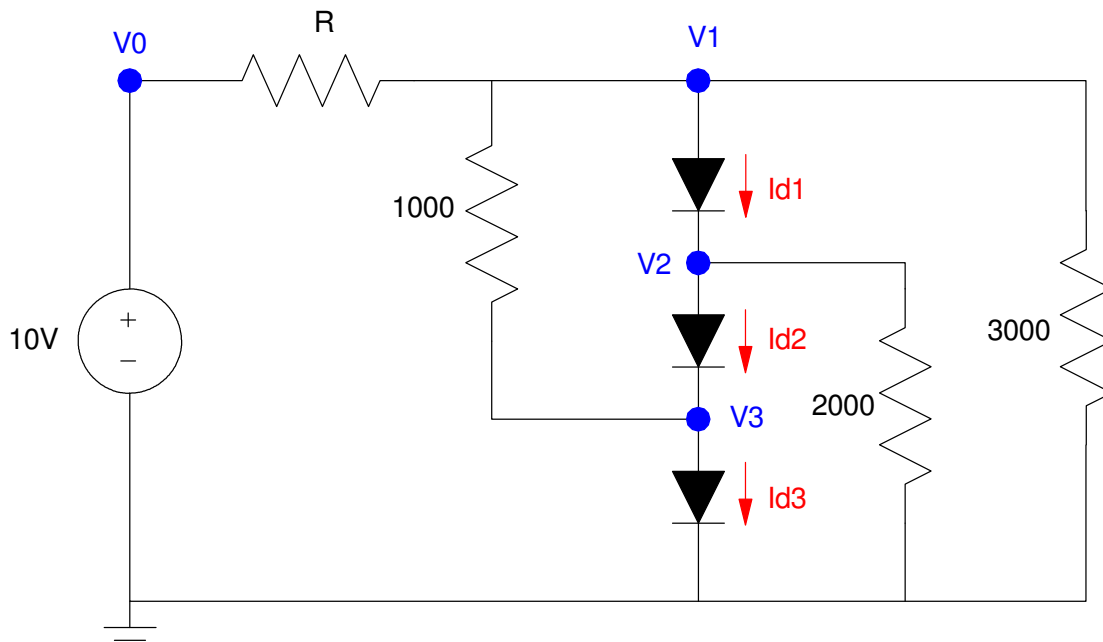


3) A green and white LED are connected to a 10V source. Determine the current and brightness of each LED.

Assume


- R is $900 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$.
- 3W LED: $V_f = 3.6\text{V}$ @ 750mA 180 Lumens @ 750mA
- 10W LED: $V_f = 11.0\text{V}$ @ 1000mA 650 Lumens @ 1000mA

R $900 + 100 \cdot \text{mo} + \text{day}$	3W LED		10W LED	
	Ia	Lumens	Ib	Lumens

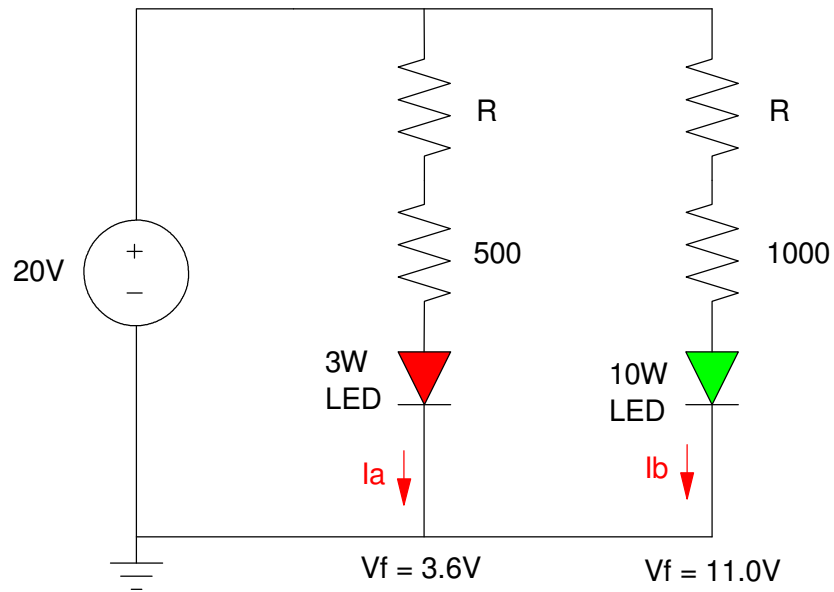

4) The following waveforms are found using CircuitLab for V2 for an AC to DC converter. Determine the following


Frequency (Hz)	V2	
	DC (average)	AC (Vpp)

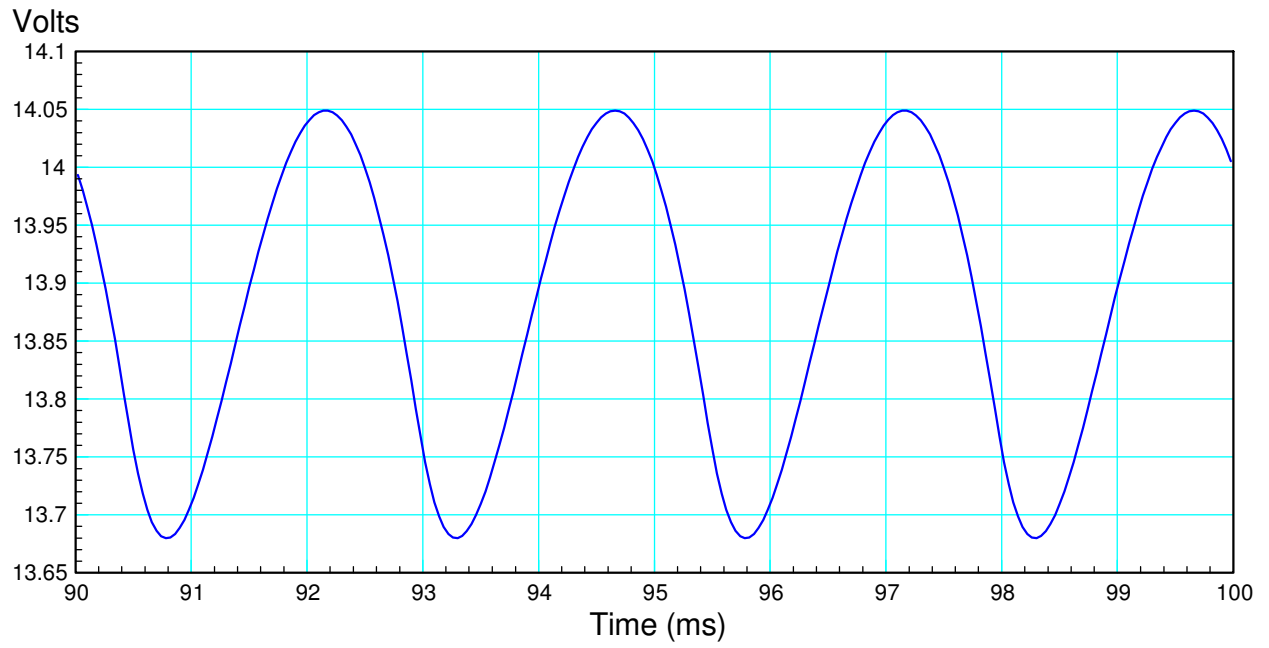

5) Determine the voltages V1 and V2 (both DC and AC). Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $C1 = (900 + 100 \cdot (\text{your birth month}) + (\text{your birthday})) \mu F$.

C1 (μF) 900 + 100*mo + day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)

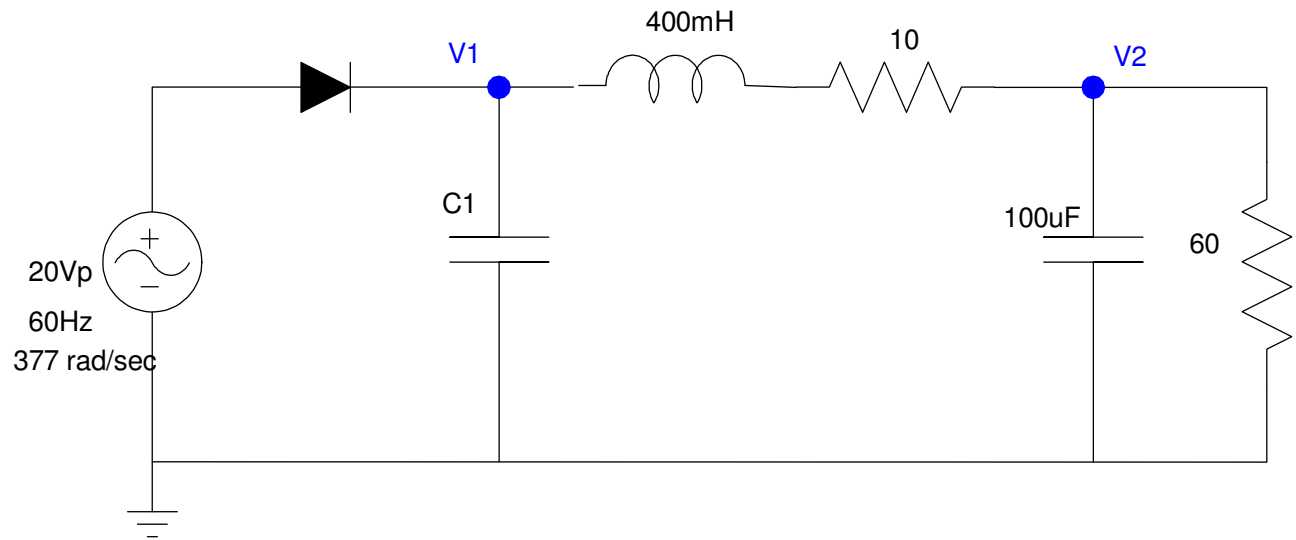

6) Determine C1, and C2 so that

- The ripple at V1 is 4Vpp and
- The ripple at V2 = 500mVpp

C1	C2

