


# ECE 320 - Quiz #4 - Name \_\_\_\_\_

Max/Min, Clipper, Transistors. Spring 2022

1) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 900 + 100 * \text{Birth Month} + \text{Birth Day}$ . May 14th for example gives  $R = 1414$  Ohms


| $R$<br>$900 + 100 * \text{Mo} + \text{Day}$ | $V_1$  | $V_2$ | $V_3$ | $I_4$ | $I_5$ |
|---|--------|-------|-------|-------|-------|
| 1414  | 8.30 V | 6.00V | 5.30V | 0     | 0.6mA |

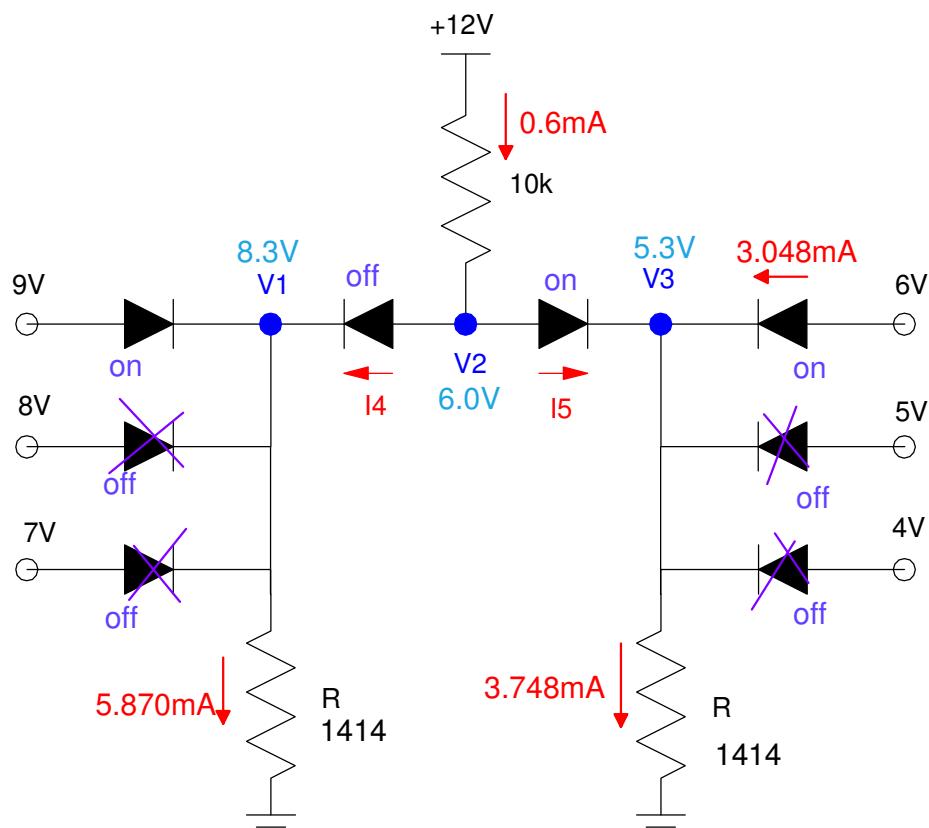

2) Max/Min: Determine the voltages and currents for the following min/max circuit.

- Assume ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 900 + 100 * \text{Birth Month} + \text{Birth Day}$



| $R$<br>$900 + 100*\text{Mo} + \text{Day}$ | $V_1$  | $V_2$  | $V_3$  | $I_4$  | $I_5$ |
|---|--------|--------|--------|--------|-------|
| 1414                                      | 7.70 V | 7.00 V | 4.70 V | 0.7 mA | 0     |

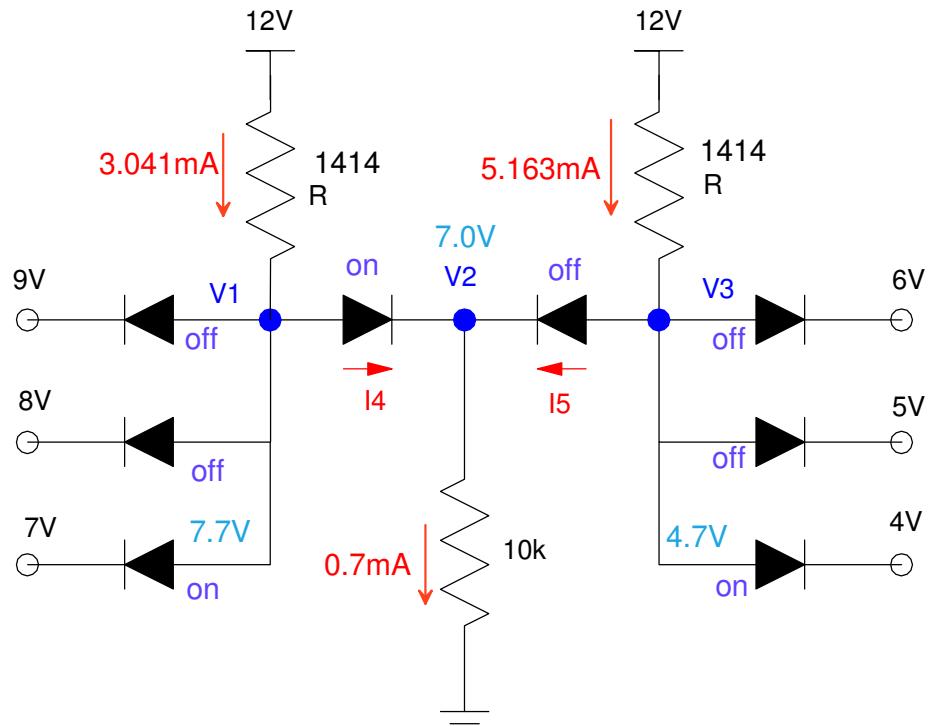

3) Clipper: Determine {R0, R1, R2, Vz1, Vz2} to implement the following function.

- Let R3 be  $900 + 100 * \text{Mo} + \text{Day}$ .

| R3<br>$900 + 100 * \text{Mo} + \text{Day}$ | R0    | Vz1  | R1  | Vz2  | R2  |
|--|-------|------|-----|------|-----|
| 1414                                       | 2.33k | 5.0V | 490 | 8.0V | 181 |

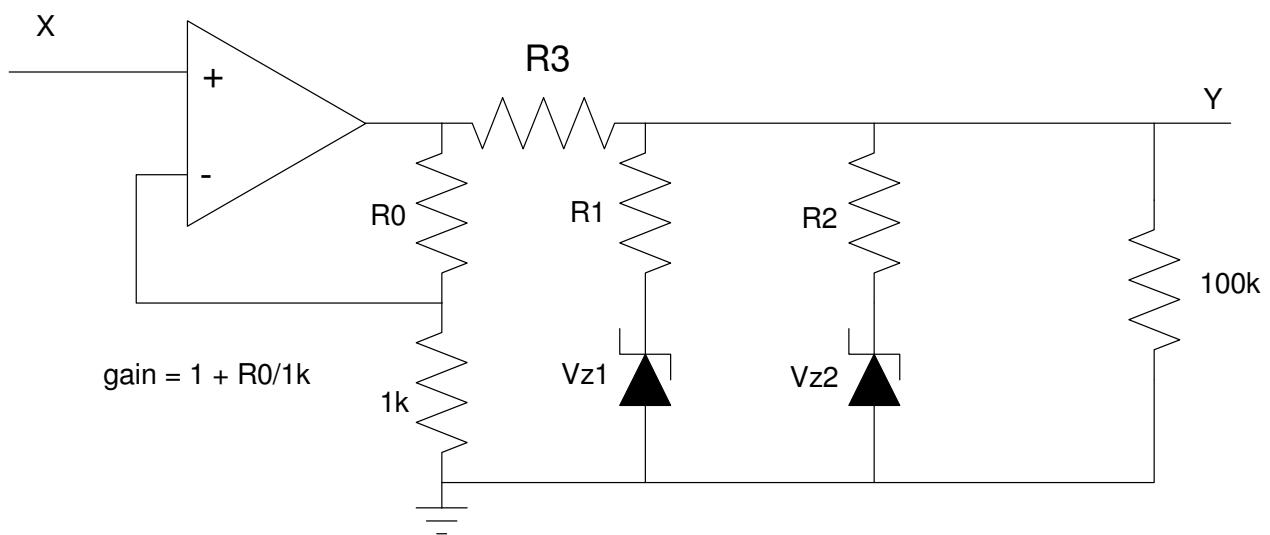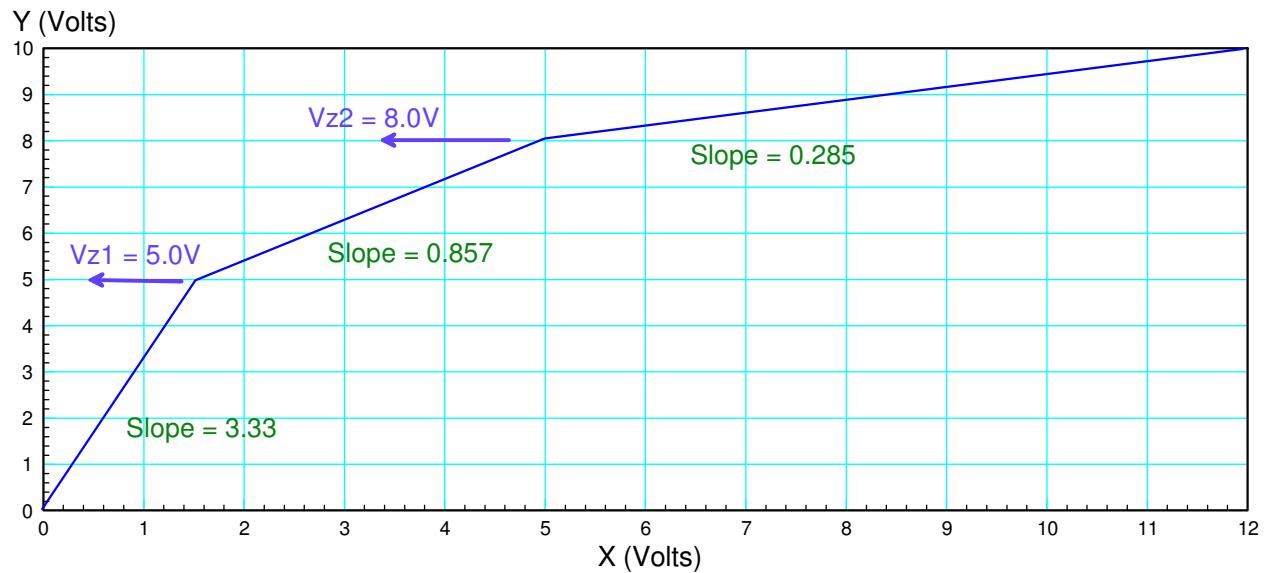


$$0.857 = \left( \frac{R_1}{R_1+R_3} \right) 3.333 \Rightarrow R_1 = 490\Omega$$

$$0.285 = \left( \frac{R_{12}}{R_{12}+R_3} \right) 3.33 \Rightarrow R_{12} = R_1 || R_2 = 132.3\Omega$$

$$\Rightarrow R_2 = 181\Omega$$

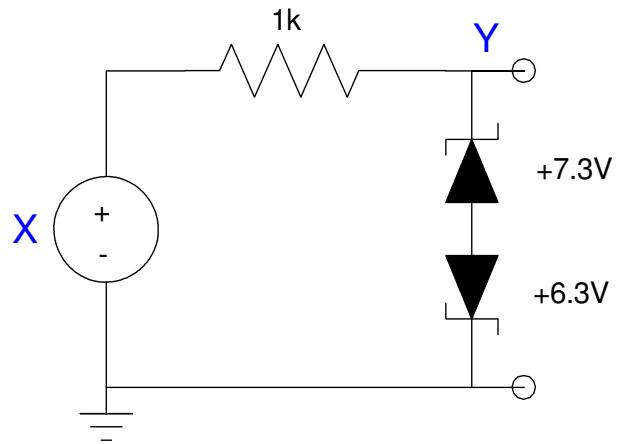4) Clipper: Design a circuit to clip the voltage at +8V and -7V

$$y = \begin{cases} +8V & x > 8V \\ x & -7V < x < 8V \\ -7V & x < -7V \end{cases}$$




5) The VI characteristics for an NPN transistor are shown below

- Draw the load line for the following circuit
- Show on the load line the operating point ( $V_{ce}$ ,  $I_c$ ) when  $V_{in} = 2V$  &  $6V$ .

Assume

- $V_{be} = 0.7V$
- $V_{ce} = 0.2V$  when saturated

| $R$<br>900 + 100*Mo + Day | Load Line                  | $V_{in} = 2.0V$                             | $V_{in} = 6.0V$                                |
|---------------------------|----------------------------|---|--|
| 1414                      | $x = 20V$<br>$y = 14.14mA$ | $V_{ce} = 10.8V$<br>$I_c = 6.5mA$<br>Active | $V_{ce} = 0.2V$<br>$I_c = 14.0mA$<br>Saturated |

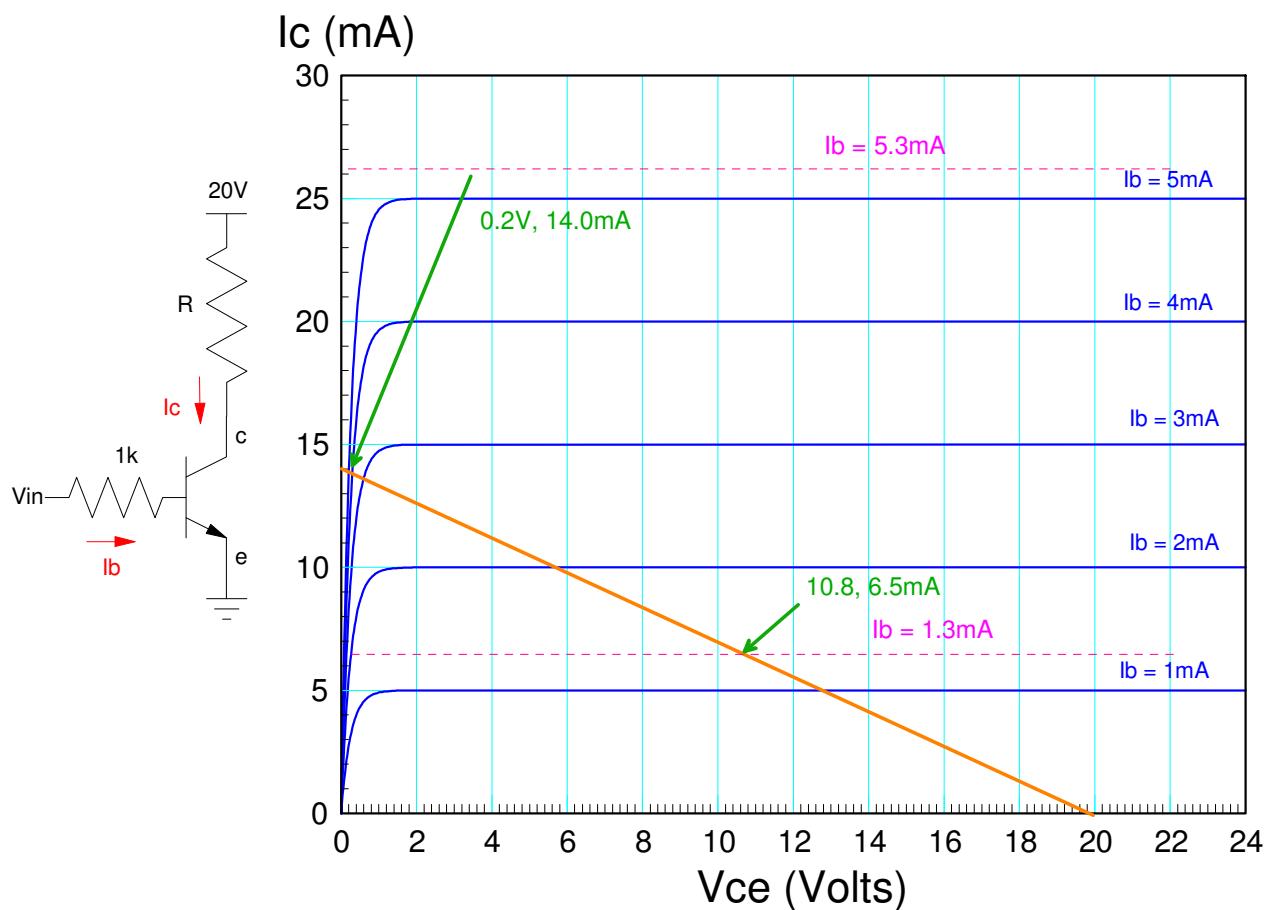

6) The voltages for the following circuit are measured (shown below). From these measurements, determine the following:

| R<br>900 + 100*Mo + Day | Ib (mA) | Ic (mA) | Current Gain (beta) | Operating Region<br>off / active / saturated |
|-------------------------|---------|---------|---------------------|--|
| 1414                    | 3.055mA | 918.0mA | 300.5               | Active<br>$V_{ce} > 0.2V$                    |

