

# ECE 320 - Quiz #5 - Name \_\_\_\_\_

555 Timers, Transistor Switch, Comparitors, Schmitt Triggers - Spring 2022


1) 555 Timers. Determine R<sub>1</sub>, R<sub>2</sub>, and C so that the 555 timer outputs a 60% duty cycle 220Hz square wave:

$$t_{on} = (R_1 + R_2) \cdot C \cdot \ln(2) = 2.727ms$$

$$t_{off} = R_2 \cdot C \cdot \ln(2) = 1.818ms$$

Let R<sub>1</sub> be your birthday day (900 + 100\*Month + Day)

R1 900 + 100*Month + Day	R2	C
<b>1414</b>	<b>2828</b>	<b>927nF</b>

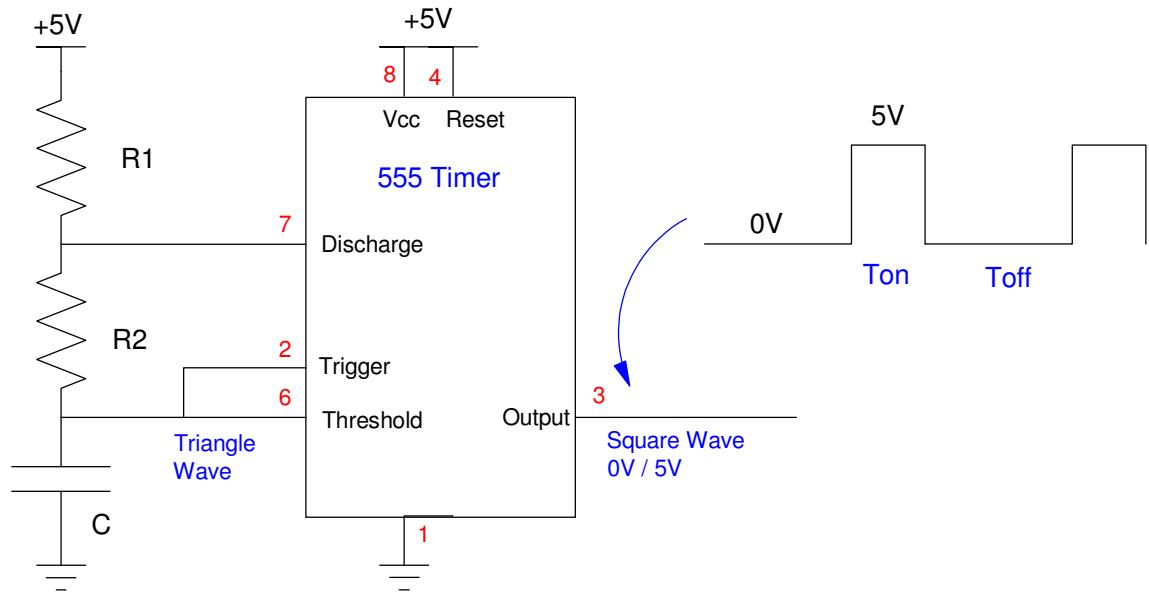

$$\frac{(R_1+R_2) \cdot C \cdot \ln(2)}{R_2 \cdot C \cdot \ln(2)} = \frac{2.727ms}{1.818ms}$$

$$\frac{R_1+R_2}{R_2} = \frac{2.727ms}{1.818ms}$$

$$R_2 = \left( \frac{1.818ms}{2.727ms - 1.818ms} \right) R_1 = 2R_1 = 2828\Omega$$

$$R_2 \cdot C \cdot \ln(2) = 1.818ms$$

$$C = 927nF$$

2) Transistor Switch: Design. Specify R<sub>1</sub> and R<sub>2</sub> so that when V<sub>in</sub> = 5.00V,

- I<sub>c</sub> = (100\*Birth Month + Birth Day ) mA.
- The transistor is saturated, and
- I<sub>b</sub> < 25mA (the maximum output of a 555 timer)

Assume 6144 transistors

- | V<sub>be</sub> | = 0.7V
- | V<sub>ce</sub> | = 0.2V when saturated
- $\beta = 60$

I <sub>c</sub> (mA) 100*(Mo) + (Day)	R <sub>c</sub>	min value of R <sub>b</sub>	max value of R <sub>b</sub>
<b>514 mA</b>	<b>9.34 Ohms</b>	<b>172 Ohms</b>	<b>501.9 Ohms</b>


$$R_c = \left( \frac{5V - 0.2V}{514mA} \right) = 9.34\Omega$$

$$\left( \frac{I_c}{\beta} \right) < I_b < 25mA$$

$$\left( \frac{514mA}{60} \right) = 8.57mA < I_b < 25mA$$

$$\left( \frac{5V - 0.7V}{8.57mA} \right) < R_b < \left( \frac{5V - 0.7V}{25mA} \right)$$

$$501.9\Omega < R_b < 172\Omega$$

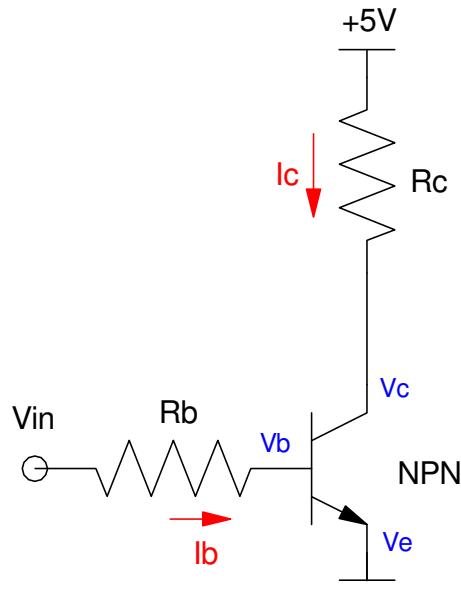

3) Darlington Pair (analysis). Assume two 6144 NPN transistors are connected as a Darlington pair.

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- $\beta = 60$

Let  $R_b$  be  $900 + 100(\text{Birth Month}) + \text{Birth Day}$ . Find the currents and voltages.


$R_b$ $900 + 100\text{Mo} + \text{Day}$	$I_1$	$I_2$	$I_3$
<b>1414</b>	<b>2.546mA</b> $(5 - V_1) / R_b$	<b>28.94mA</b>	<b>1736mA</b> $60 * I_2$
	$V_1$	$V_2$	$V_3$
	<b>1.4V</b>	<b>0.7V</b>	<b>0.9V</b>

$$I_1 = \left( \frac{5V - 1.4V}{1414\Omega} \right) = 2.546mA$$

$$I_4 = \left( \frac{15V - 0.9V}{8\Omega} \right) = 1763mA = I_3 + I_5$$

$$I_3 = 60I_2$$


$$I_2 = I_5 + I_1$$

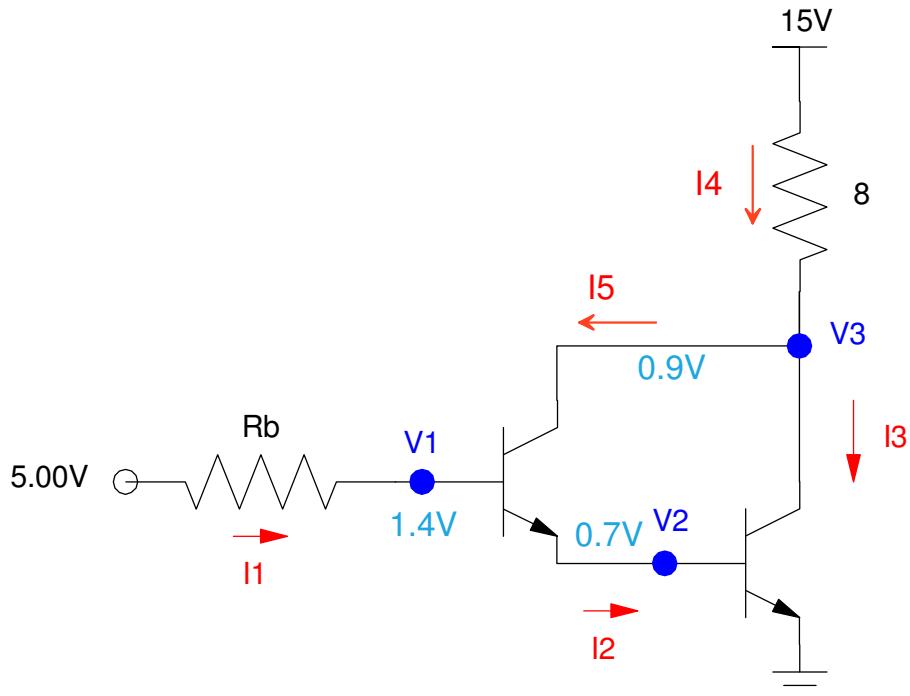

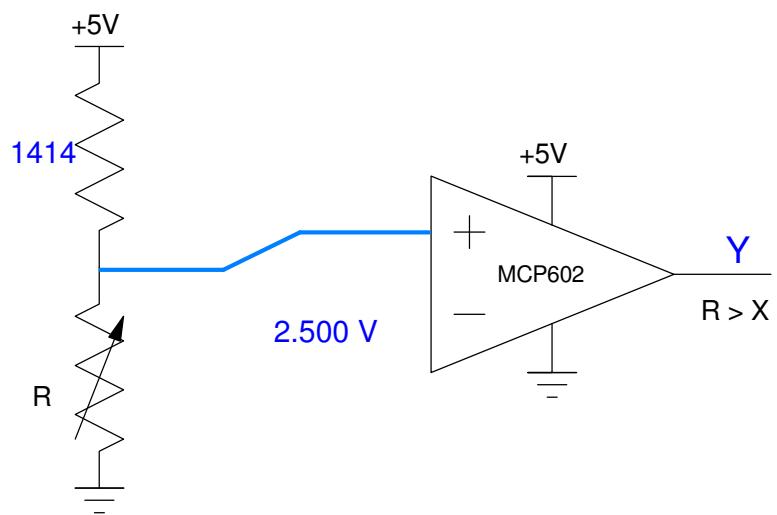4) Comparitor: Design a circuit which output

- 0V when  $R < 1414$  Ohms
- 5V when  $R > 1414$  Ohms

where  $X$  is  $900 + 100*(\text{Birth Month}) + (\text{Birth Day})$ .



5) Schmitt Trigger: Design a circuit which output

- 0V when  $R < 1414$  Ohms
- 5V when  $R > 1914$  Ohms
- No change for  $1414 < R < 1914$  Ohms

Let  $X$  be  $900 + 100(\text{Birth Month}) + (\text{Birth Date})$ .

At 1414 Ohms


$$X = 2.500V$$

At 1914 Ohms

$$X = 2.876V$$

Gain
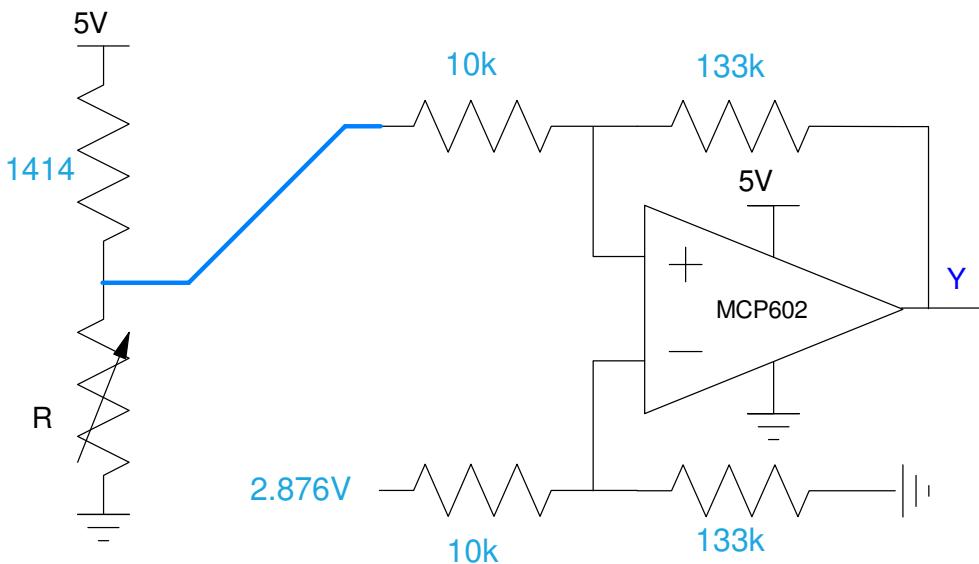
$$\text{gain} = \left( \frac{5V - 0V}{2.876V - 2.500V} \right) = 13.31$$



6) Schmitt Trigger: Analysis. Determine the voltages and resistance where the following Schmitt trigger turns on and off. Assume Rx is  $900 + 10^*(\text{Birth Month}) + (\text{Birth Day})$ .

Rx $900 + 100^*\text{Mo} + \text{Day}$	On ( $V_2 = +5V$ )		Off ( $V_2 = 0V$ )	
1414	V1	R	V1	R
	<b>3.00V</b>	<b>2121 Ohms</b>	<b>1.89V</b>	<b>859 Ohms</b>

Output goes high at 3.00V (offset voltage)

Gain = 4.50 (ratio of resistors)

$$gain = \left( \frac{5V - 0V}{3.33V - V_{off}} \right)$$

$$V_{off} = 1.89V$$

