

# ECE 320 - Quiz #6 - Name \_\_\_\_\_

H Bridges, DC to DC Converters, Fourier Transforms

## H-Bridge Analysis:

1) Determine the voltages and currents for the following H-bridge. Assume ideal 3904 & 3906 transistors:

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- Current gain =  $\beta = 100$

Let  $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$

R	I1	I2	-I3	V4	V5
900 + 100*mo + day					
1414	28.25uA	1.883mA	18.83uA	11.8V T1 is saturated	9.137V T4 is active


$$I_1 = \left( \frac{12V - 0.7V}{400k} \right) = 28.25\mu A \quad \text{allows } 2.825mA$$

$$I_3 = \left( \frac{12V - 0.7V}{600k} \right) = 18.83\mu A \quad \text{allows } 1.883mA \quad \lll \text{ winner!}$$

$$\max(I_2) = \left( \frac{12V - 0.2V - 0.2V}{1414\Omega} \right) = 8.204mA$$

$$V_4 = 12V - 0.2V$$

$$V_5 = V_4 - 1.883mA \cdot 1414\Omega$$

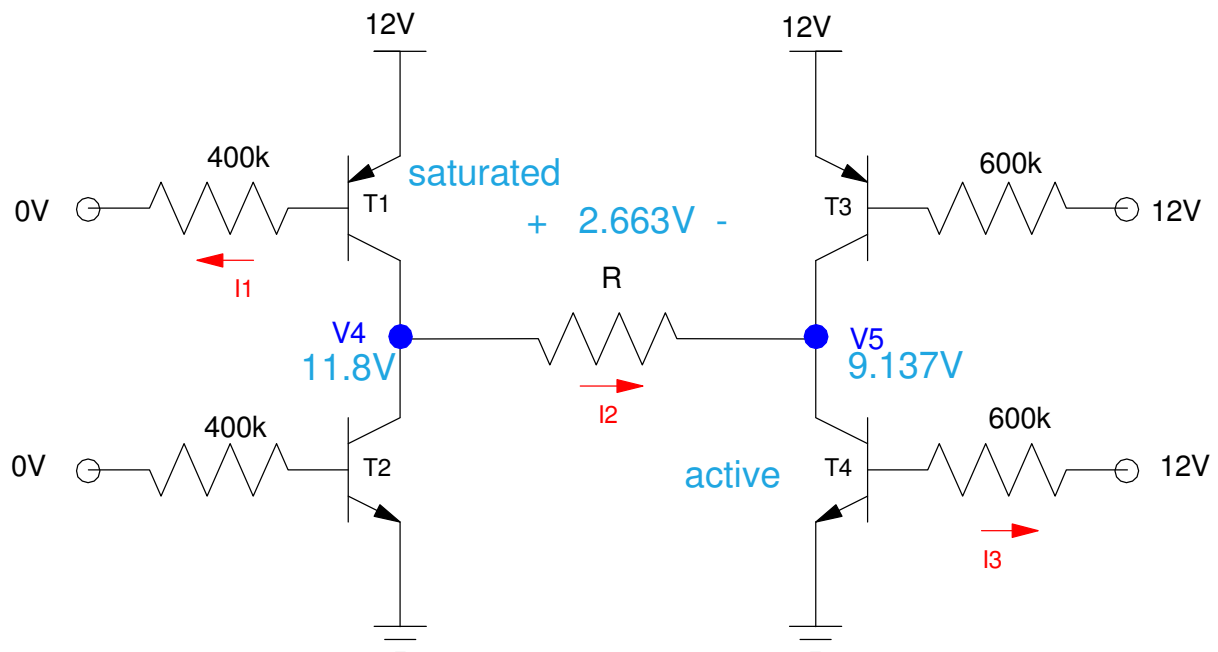

## H-Bridge Analysis:

2) Determine the voltages and currents for the following H-bridge. Assume ideal 3904 & 3906 transistors:


- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- Current gain = beta = 100

R	I1	I2	-I3	V4	V5
900 + 100*mo + day					
1414	282.5uA	8.204mA	188.3uA	11.8V T1 is saturated	0.2V T4 is saturated

$$I_1 = \left( \frac{12V - 0.7V}{40k\Omega} \right) = 282.5\mu A \quad \text{allows } 28.25mA$$

$$I_3 = \left( \frac{12V - 0.7V}{60k\Omega} \right) = 188.3\mu A \quad \text{allows } 18.83mA$$

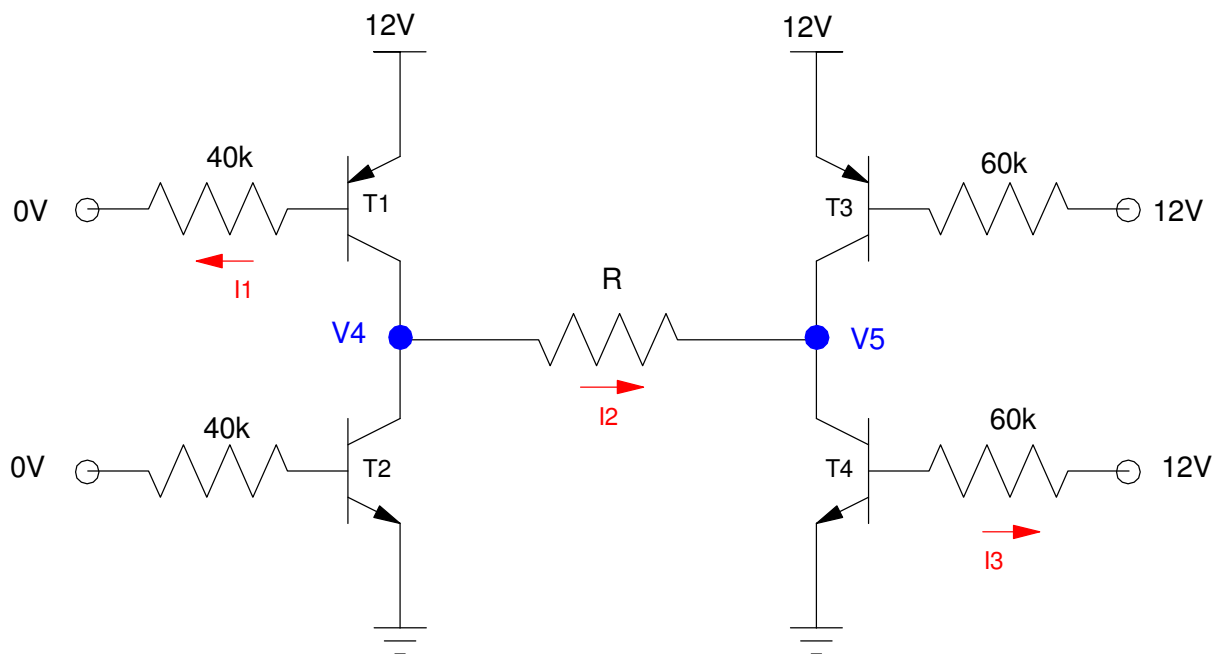
$$\max(I_2) = \left( \frac{12V - 0.2V - 0.2V}{1414\Omega} \right) = 8.204mA \quad \lll \text{ Winner!}$$



## DC to DC Converter: Analysis (note: 24V DC power supply)

3) Determine the voltages at V1 and V2 (both DC and AC)

R 900 + 100*mo + day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)
1414	20.295V	24.7Vpp	17.780V	2.6834Vpp

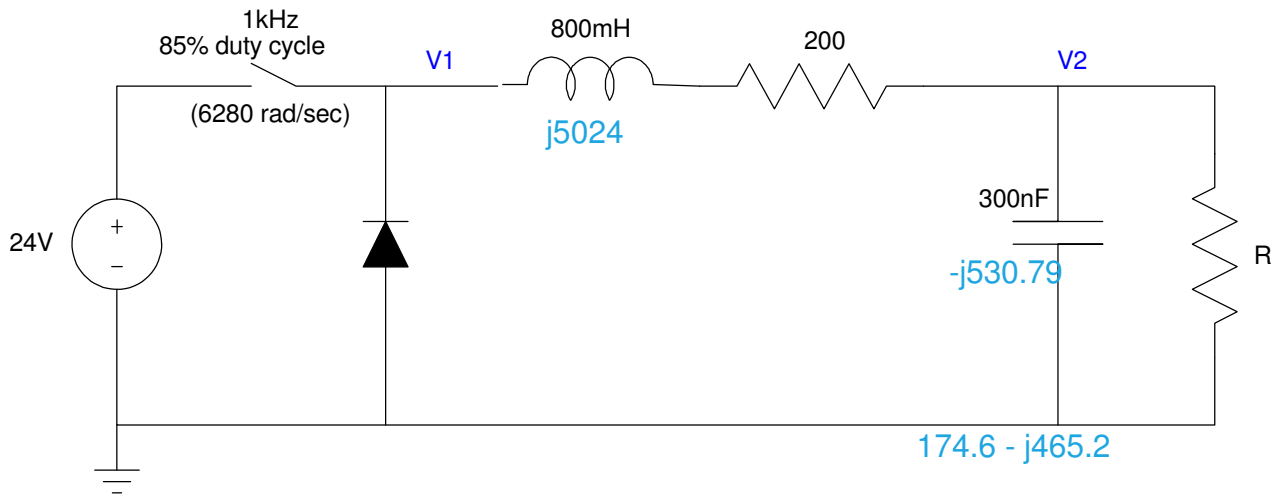

$$V_1(DC) = 0.85 \cdot 24V + 0.15 \cdot (-0.7V) = 20.295V$$

$$V_2(DC) = \left( \frac{1414}{1414+200} \right) \cdot V_1(DC) = 17.780V$$

$$V_1(AC) \approx 24.7V_{pp}$$

$$V_2(AC) \approx \left( \frac{(174.6-j465.2)}{(174.6-j465.2)+(200+j5024)} \right) \cdot V_1(AC)$$


$$V_2(AC) \approx 2.6834V_{pp}$$

## DC to DC Converter: Design (note: +24V DC power supply)

4) Determine the duty cycle and C so that

- $V_2(\text{DC})$  is 7.50V and
- $V_2(\text{AC}) = 350\text{mV}_{\text{pp}}$

R 900 + 100*mo + day	Duty Cycle (X) %	C
1414	37.5%	1.78uF

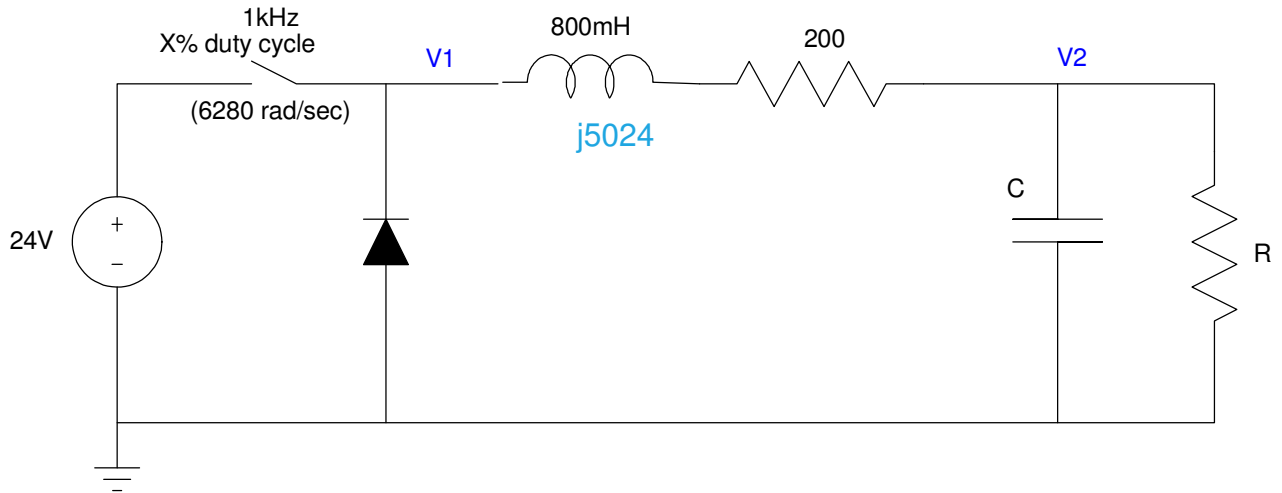

$$V_1(\text{DC}) = \left( \frac{1414+200}{1414} \right) \cdot 7.50\text{V} = 8.561\text{V}$$

$$\text{duty cycle} = \left( \frac{8.561\text{V} + 0.7\text{V}}{24\text{V} + 0.7\text{V}} \right) = 37.5\%$$

If C = 0

$$V_2(\text{AC}) = \left( \frac{1414}{1414 + (200 + j5024)} \right) \cdot 20.7\text{V}_{\text{pp}}$$

$$V_2(\text{AC}) = 5.547\text{V}_{\text{pp}}$$

For  $V_2(\text{AC}) = 350\text{mV}_{\text{pp}}$

$$\left| \frac{1}{j\omega C} \right| = \left( \frac{350\text{mV}_{\text{pp}}}{5.547\text{V}_{\text{pp}}} \right) \cdot 1414\Omega = 89.223\Omega$$

$$C = 1.78\mu\text{F}$$

## DC to DC Converter

5) Determine the voltages and currents for the following DC to DC converter. Assume ideal 3904 & 3906 transistors:


- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$  when saturated
- Current gain =  $\beta = 100$

R	V1	V2	I3	I4	I5
$900 + 100 \cdot m\Omega + \text{day}$	0.2V NPN is saturated	23.8V PNP is saturated	430uA	16.34mA	476mA

Checking if saturated:

$$100I_3 = 43mA > 16.34mA \quad \text{NPN is saturated}$$
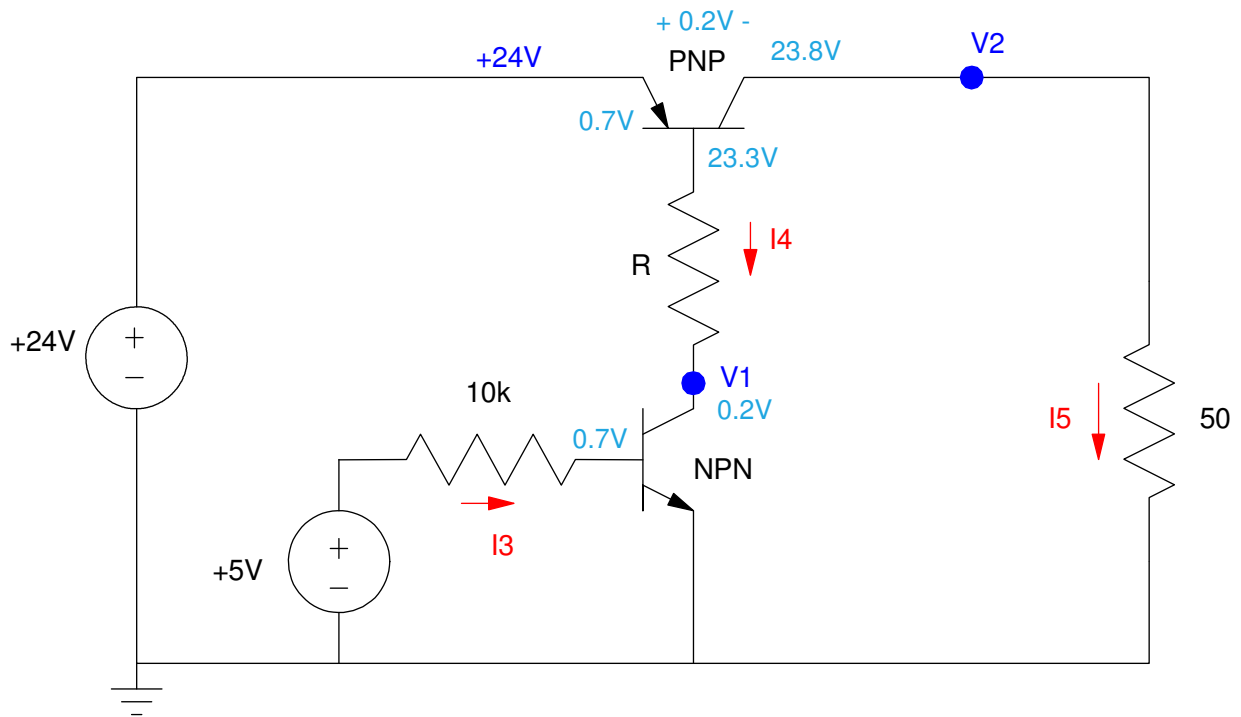
$$100I_4 = 1634mA > 476mA \quad \text{PNP is saturated}$$



## Fourier Transform

6) Determine  $y(t)$  given that

$$x(t) = 24 + m \sin(40t) + d \cos(80t)$$

where

- $m$  is your birth month (1..12) and
- $d$  is your birth date (1..31)

m birth month (1..12)	d birth date (1..31)	y(t)
5	14	20.57 - 2.118 cos(40t) + 2.471 sin(40t) + 3.047 cos(80t) + 5.223 sin(80t)

DC

$$Y = \left( \frac{60}{60+10} \right) \cdot 24 = 20.57$$

40 rad/sec

$$Y = \left( \frac{60}{60+(10+j60)} \right) (0 - j5) = -2.118 - j2.471$$

80 rad/sec

$$Y = \left( \frac{60}{60+(10+j1200)} \right) (14 + j0) = 3.047 - j5.223$$

