

ECE 320 - Quiz #7 - Name _____

DC to AC, SCR

DC to AC Converter

1) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)
- $Energy = \frac{1}{2}(a_n^2 + b_n^2)$ *Watts: assumes a 1 Ohm resistive load*

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	5 <small>Birth Month (1..12)</small>	0	0	0	0
bn (sine)	0	14 <small>Birth Date (1..31)</small>	0	0	0	0
Energy (Watts)	0	110.5	0	0	0	0

Determine the following:

Total Energy in the signal Watts	Energy in the 1st harmonic Watts	Efficiency % of energy in the 1st harmonic
110.5	110.5	100%

DC to AC Converter

2) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)
- *Watts: assumes a 1 Ohm resistive load*
- $Energy = \frac{1}{2}(a_n^2 + b_n^2)$

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	60Vp	0	10Vp	14 Birth Date (1..31)	0
bn (sine)	0	0	5 Birth Month (1..12)	0	0	5Vp
Energy (Watts)	0	1800	12.5	50	98	12.5

Determine the following:

Total Energy in the signal Watts	Energy in the 1st harmonic Watts	Efficiency % of energy in the 1st harmonic
1973 W	1800 W	91.2%


Circuits & Differential Equations

3) Write the differential equation which describes the following circuit. Assume

- L = your birth month (1..12) mH
- R_2 = your birth date (1..31) Ohms

Note:

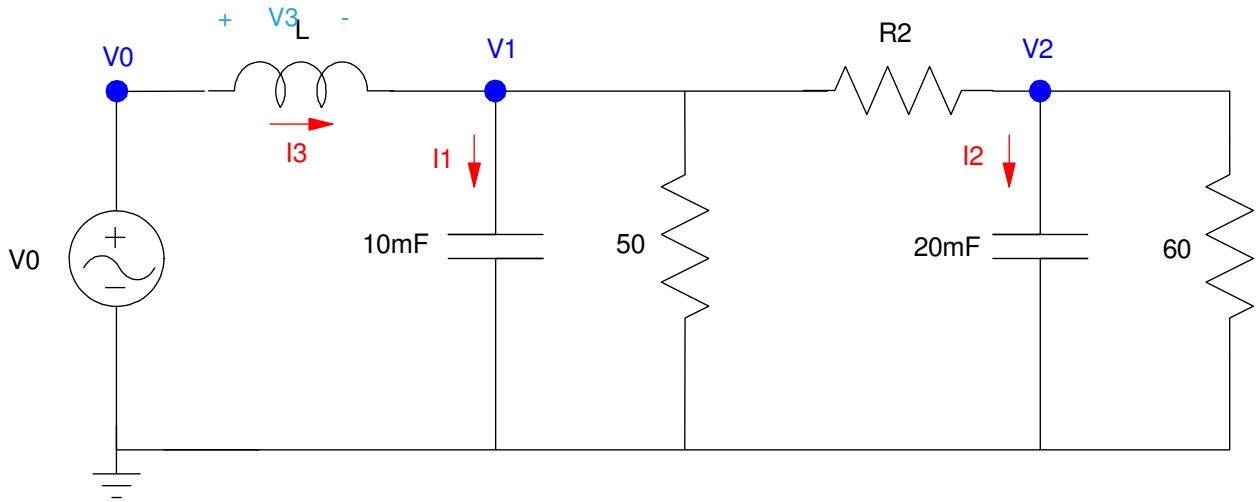- $I = C \frac{dV}{dt}$
- $V = L \frac{dI}{dt}$



$$V_3 = L \frac{dI_3}{dt} = V_0 - V_1$$

$$I_1 = 0.01 \frac{dV_1}{dt} = I_3 - \left(\frac{V_1}{50} \right) - \left(\frac{V_1 - V_2}{R_2} \right)$$


$$I_2 = 0.02 \frac{dV_2}{dt} = \left(\frac{V_1 - V_2}{R_2} \right) - \left(\frac{V_2}{60} \right)$$

SCR (4 diode version)

4) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume

- R1 = your birth month (1..12)
- X = 10 + your birth date (11..41 degree firing angle)

Firing Angle day + 10	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)
24 degrees	16.047 V	42.202 Vpp	13.755 V	4.902 Vpp

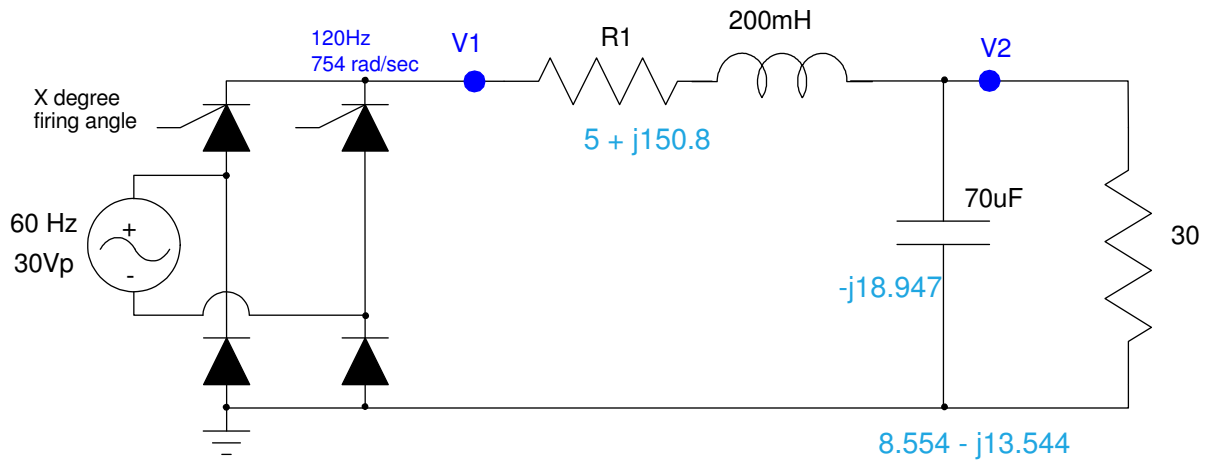

$$V_1(DC) = \left(\frac{2}{\pi}\right) \cdot 30V \cdot \cos(24^\circ) - 1.4$$

$$V_1(DC) = 16.047V$$

$$V_2(DC) = \left(\frac{30}{30+5}\right) V_1(DC)$$

$$V_2(DC) = 13.755V$$

$$V_1(AC) = 30(1 + \sin(24^\circ)) = 42.202V_{pp}$$

$$V_2(AC) = \left(\frac{(8.554-j13.544)}{(8.554-j13.544)+(5+j150.8)}\right) \cdot V_1(AC)$$


$$V_2(AC) = 4.902V_{pp}$$

SCR (5 diode version)

5) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume

- R1 = your birth month (1..12)
- X = 10 + your birth date (11..41 degree firing angle)

Firing Angle day + 10	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)
24 degrees	17.146 V	29.3 Vpp	14.697 V	3.403 Vpp

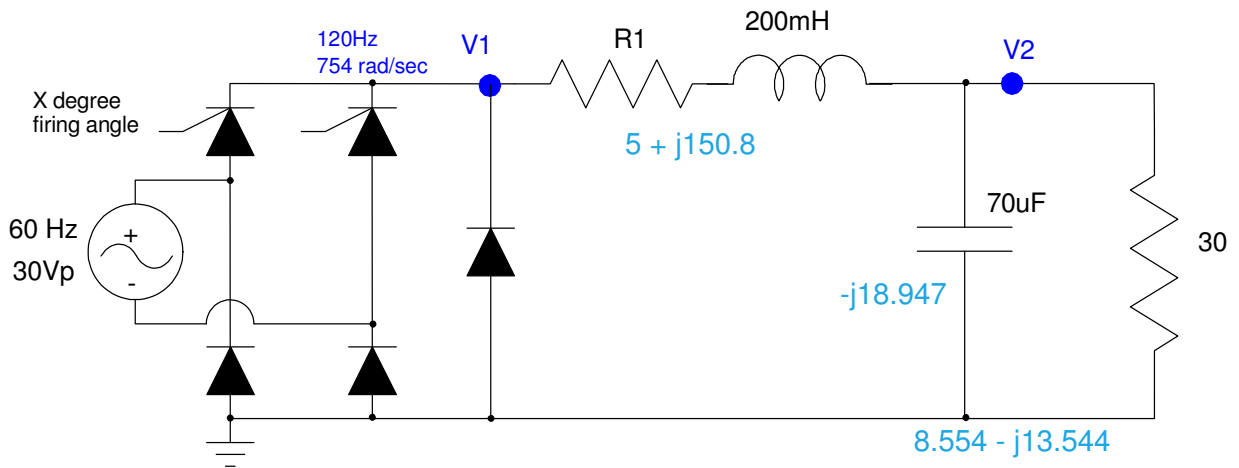

$$V_1(DC) = \left(\frac{29.3V}{\pi} \right) (1 + \cos(24^\circ)) - 0.7$$

$$V_1(DC) = 17.146V$$

$$V_2(DC) = \left(\frac{30}{30+5} \right) V_1(DC)$$

$$V_2(DC) = 14.697V$$

$$V_1(AC) = 29.3V_{pp}$$


$$V_2(AC) = \left(\frac{(8.554 - j13.544)}{(8.554 - j13.544) + (5 + j150.8)} \right) \cdot V_1(AC)$$

$$V_2(AC) = 3.403V_{pp}$$

6) SCR Design. Determine the firing angle and C so that

- $V_2(\text{DC}) = 10.00\text{V}$
- $V_2(\text{AC}) = 1.00\text{V}_{\text{pp}}$
- $R_1 = \text{Your Birth Month (1..12)}$

V1(DC)	Firing Angle	C	R1 Month (1..12)
11.667 V	46.828 degrees	444.5 uF	5 Ohms

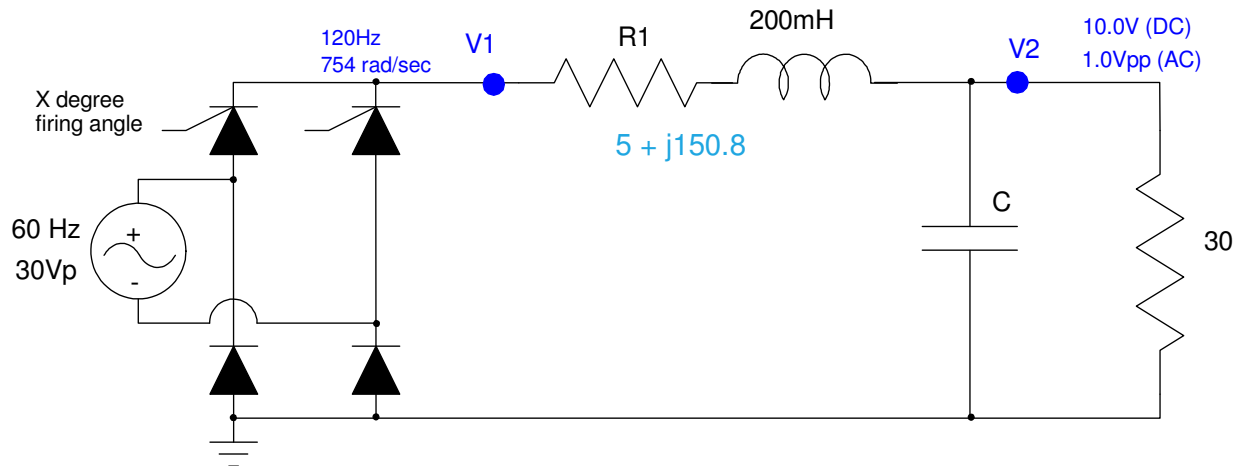

$$V_1(\text{DC}) = \left(\frac{30+5}{30} \right) 10.00\text{V} = 11.667\text{V}$$

$$V_1(\text{DC}) = \left(\frac{2}{\pi} \right) \cdot 30\text{V} \cdot \cos(\theta) - 1.4$$

$$\theta = 46.828^\circ$$

$$V_1(\text{AC}) = 30(1 + \sin(46.828^\circ)) = 51.879\text{V}_{\text{pp}}$$

If $C = 0$

$$V_2(\text{AC}) = \left(\frac{30}{30+(5+j150.8)} \right) \cdot 51.879\text{V}_{\text{pp}} = 10.054\text{V}_{\text{pp}}$$

To bring this down to 1.00V_{pp}

$$\left| \frac{1}{j\omega C} \right| = \left(\frac{1\text{V}_{\text{pp}}}{10.054\text{V}_{\text{pp}}} \right) 30\Omega = 2.984\Omega$$

$$C = 444.5\mu\text{F}$$

